

Last Lecture → BJT: Large Signal Analysis

9/16/2019


- 1) When applicable, simplify the circuit
- 2) Determine if BE/EB junction is forward (transistor = “on”)
 - If reverse, transistor → cut off
 - If forward, transistor → active / saturation
 - ∴ Make an educated guess of the region of operation
- 3) Substitute the appropriate model and or assumptions
- 4) Solve for the transistor operating point (I_C & V_{CE})
- 5) Verify proper operation @ the assumed region
 - If cut off → $V_{BE} < 0.5V$
 - If active → $V_{BE} \geq 0.5V, V_{CE} \geq 0.3V$
 - If saturation → $V_{BE} \geq 0.5V, I_C / I_B < \beta$

Example 6.12

9/16/2019

For the following circuit determine the voltages at all nodes and the current through all branches assuming:

- a) $V_{BE}=0.7V$, $\beta=100$, $V_{dd} = -V_{ss} = 5V$, and $V_B = 5V$
- b) $V_{BE}=0.7V$, $\beta=100$, $V_{dd} = -V_{ss} = 5V$, and $V_B = 0.3V$

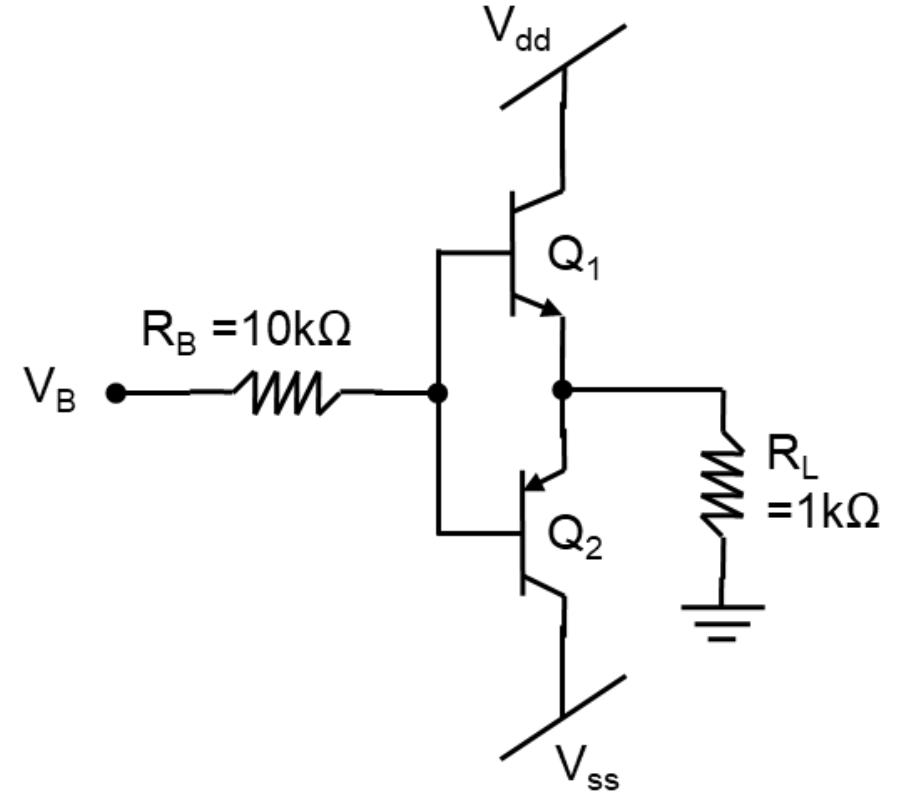

Example 6.11

9/16/2019

For the following circuit determine the voltages at every node and the bias currents of transistors Q_1 and Q_2 . Assume $V_{BE} = |V_{EB}| = 0.7$ and $\beta = 100$.

KVL V_{be} of Q_1 (with Thevenin equivalent circuit)

$$V_{th} = R_{th} \cdot I_1 + V_{BE1} + R_{E1} \cdot I_{E1}$$


$$\rightarrow I_{B1} = 12.8 \mu A$$

KVL V_{eb} of Q_2

$$R_{C1} \cdot [I_{C1} - I_{B2}] = V_{EB2} + R_{E2} \cdot I_{E2}$$

$$\rightarrow I_{B2} = 27.5 \mu A$$




Thevenin Eq.

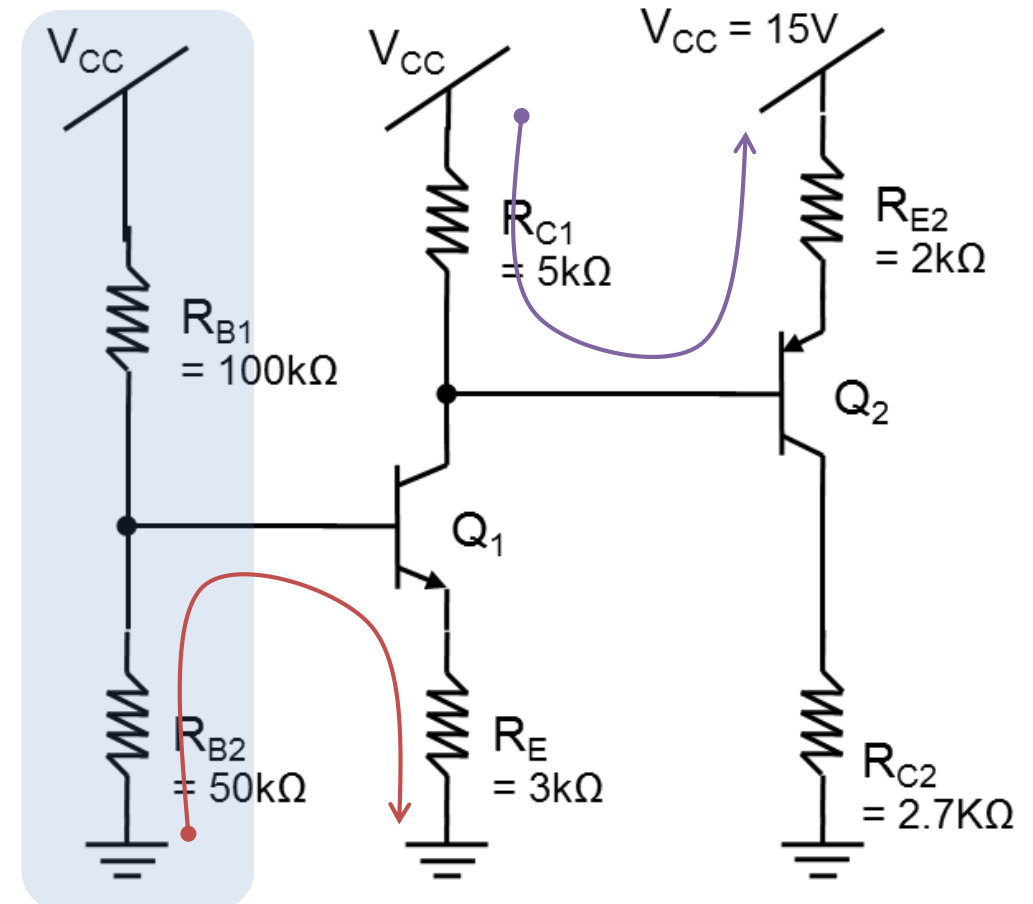

Large-Signal vs Small Signal Behavior

9/16/2019

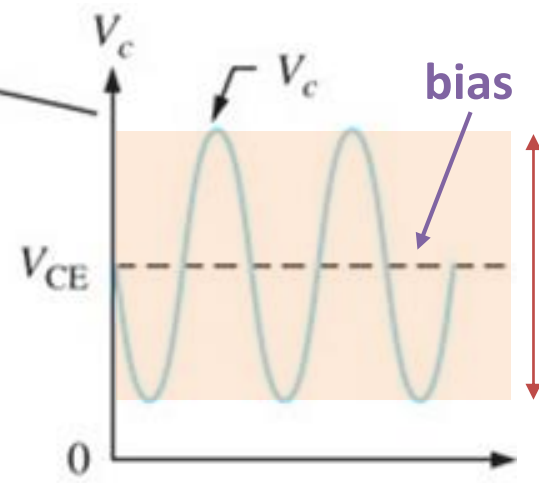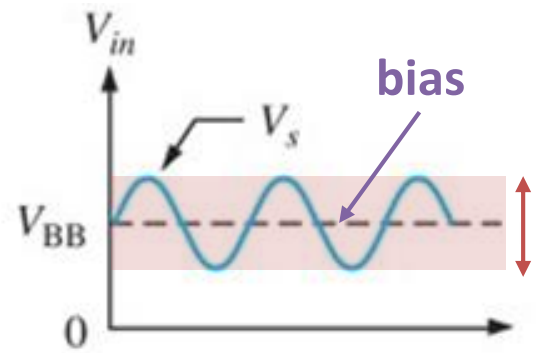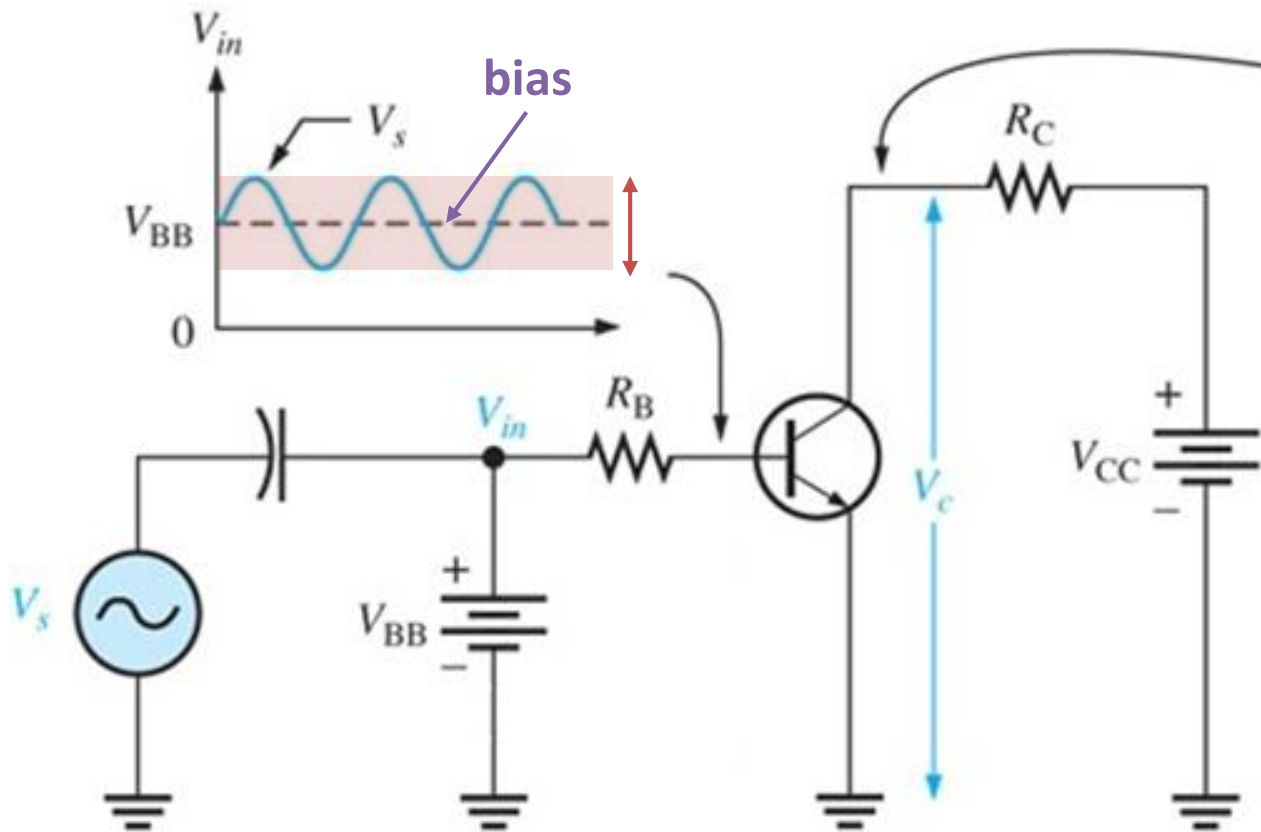- Bias current is established through V_{BB} and supplied by V_{CC}
- AC signal is coupled through the capacitor and superimposed to the DC signal




AC & DC analysis can be performed via superposition!



- Large-Signal (DC) – establishes the DC operating point of the circuit
- Small-Signal (AC) – determines de circuit behavior around the DC operating point

Small Signal Parameters

9/16/2019


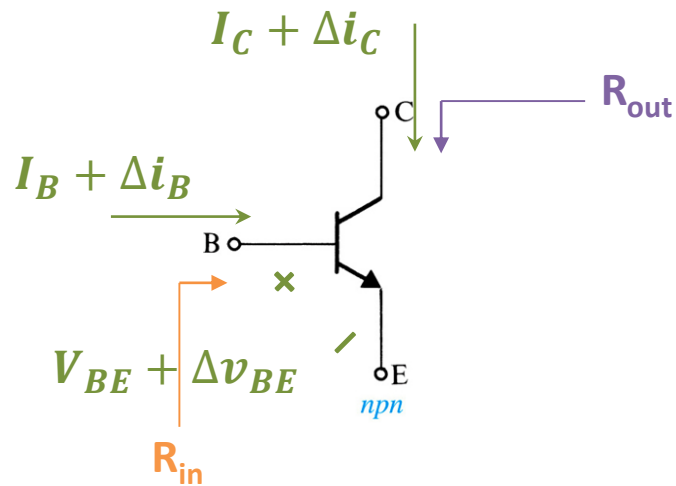


Output Impedance

$$R_{out} = \frac{\partial V_{out}}{\partial I_{out}} = \frac{\partial V_{CE}}{\partial I_C} = \frac{V_A}{I_C} = r_o$$

Trans-conductance
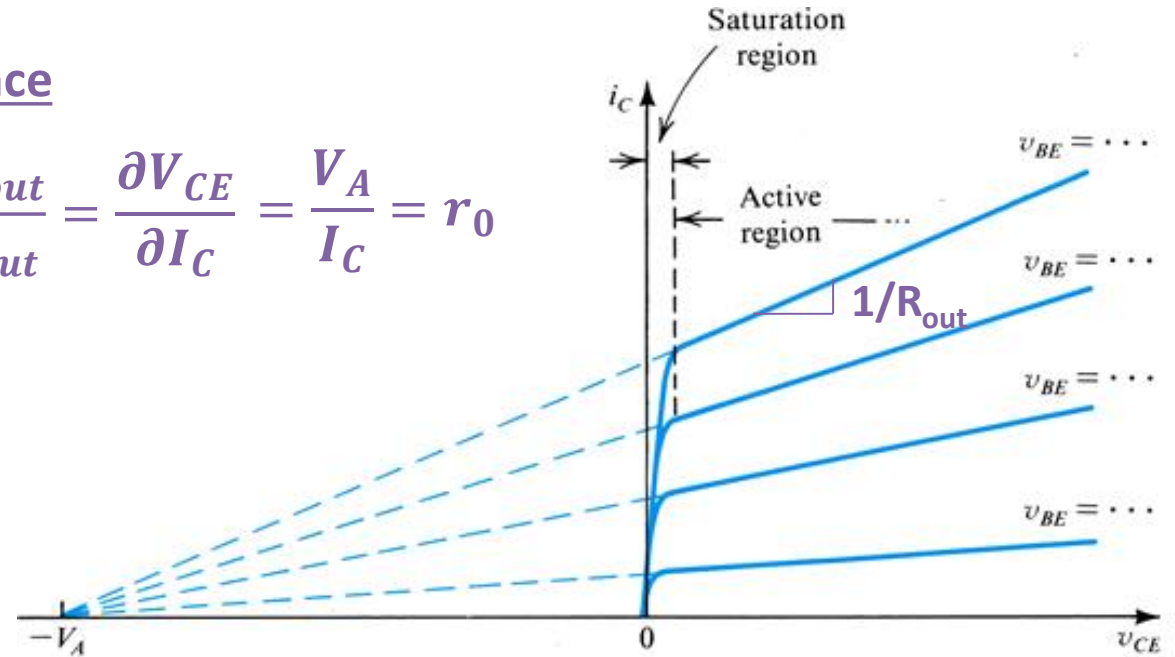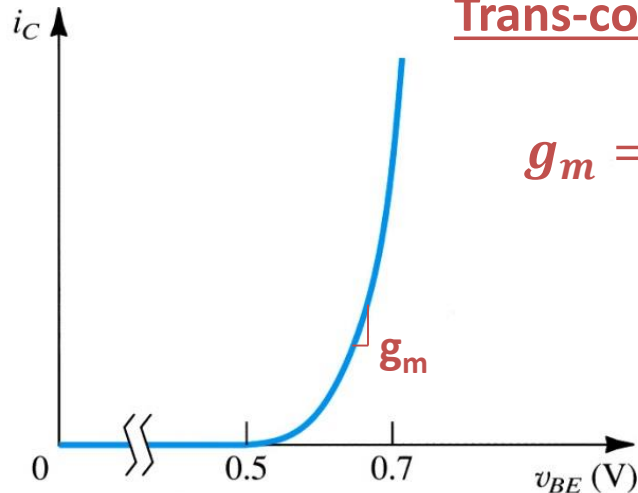
$$g_m = \frac{\partial I_{out}}{\partial V_{in}} = \frac{\partial I_C}{\partial V_{BE}} = \frac{I_C}{V_T}$$





Input Impedance

$$R_{in} = \frac{\partial V_{in}}{\partial I_{in}} = \frac{\partial V_{BE}}{\partial I_B} = \frac{\beta}{g_m} = r_{\pi}$$

Small Signal Equivalent Circuit

9/16/2019

- npn transistor

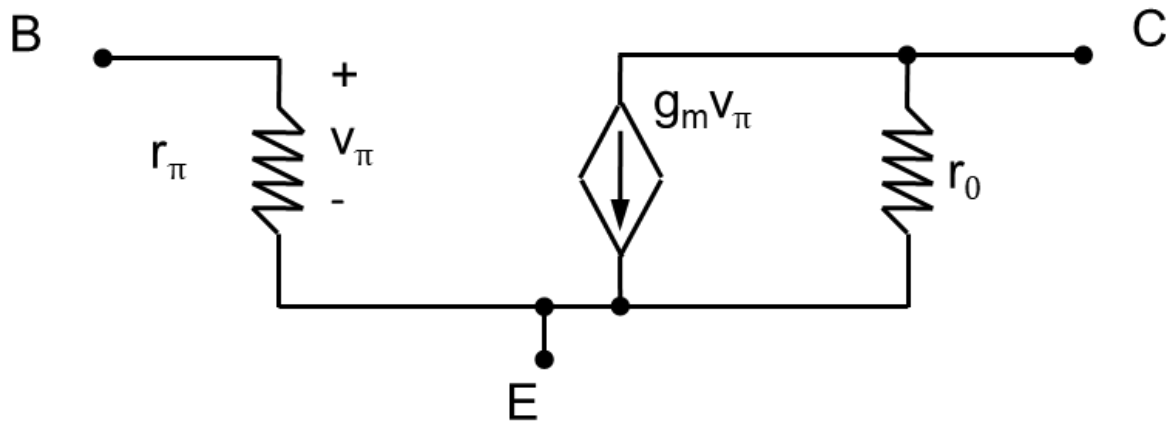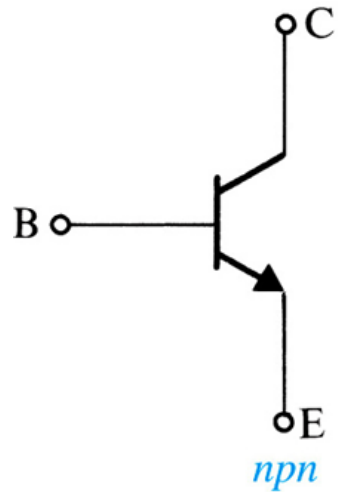

- pnp transistor

