
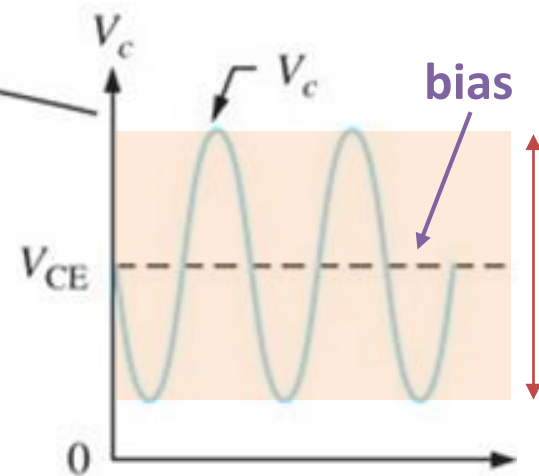


Large-Signal vs Small Signal Behavior

9/30/2019

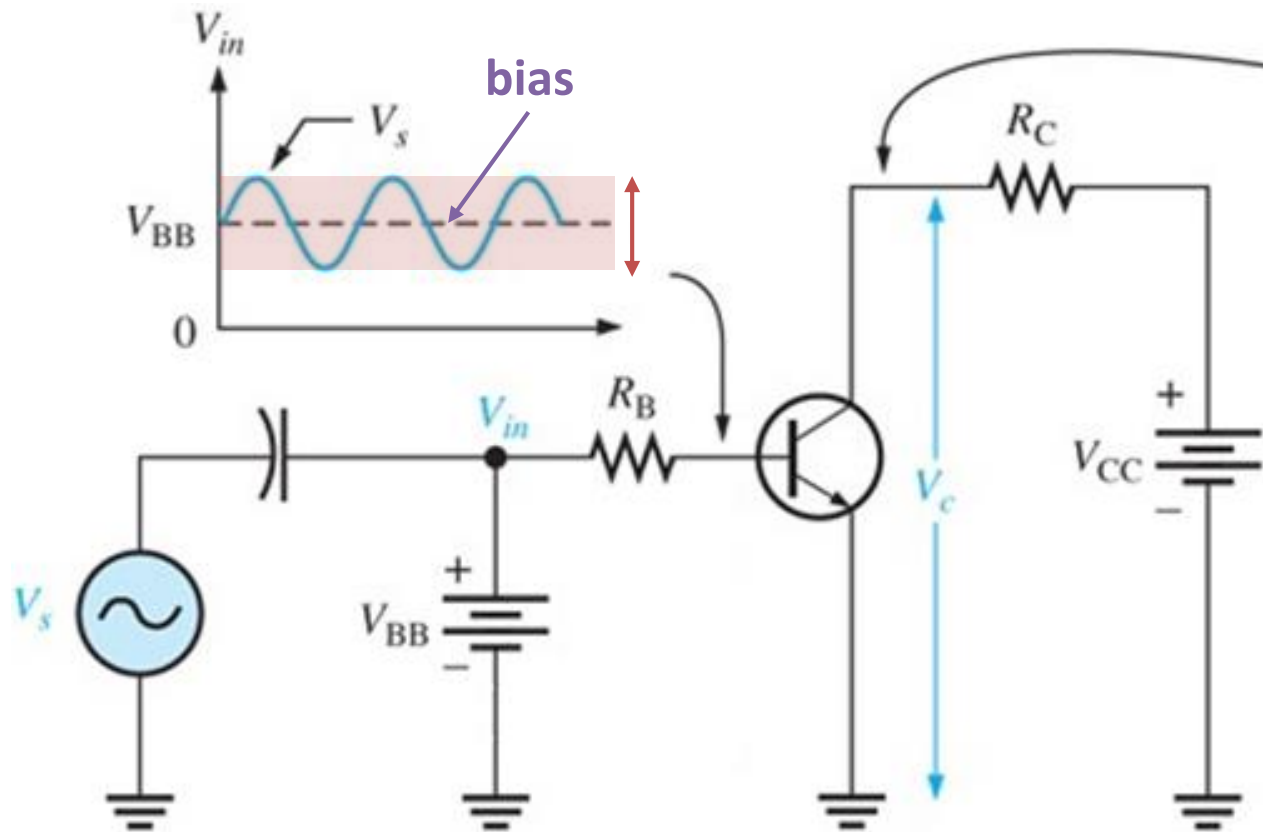- Bias current is established through V_{BB} and supplied by V_{CC}
- AC signal is coupled through the capacitor and superimposed to the DC signal




AC & DC analysis can be performed via superposition!



- Large-Signal (DC) – establishes the DC operating point of the circuit
- Small-Signal (AC) – determines de circuit behavior around the DC operating point


Small Signal Parameters

9/30/2019

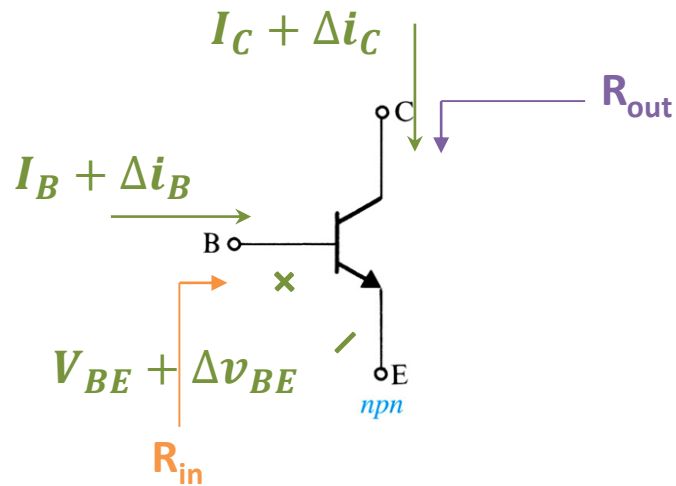


Output Impedance
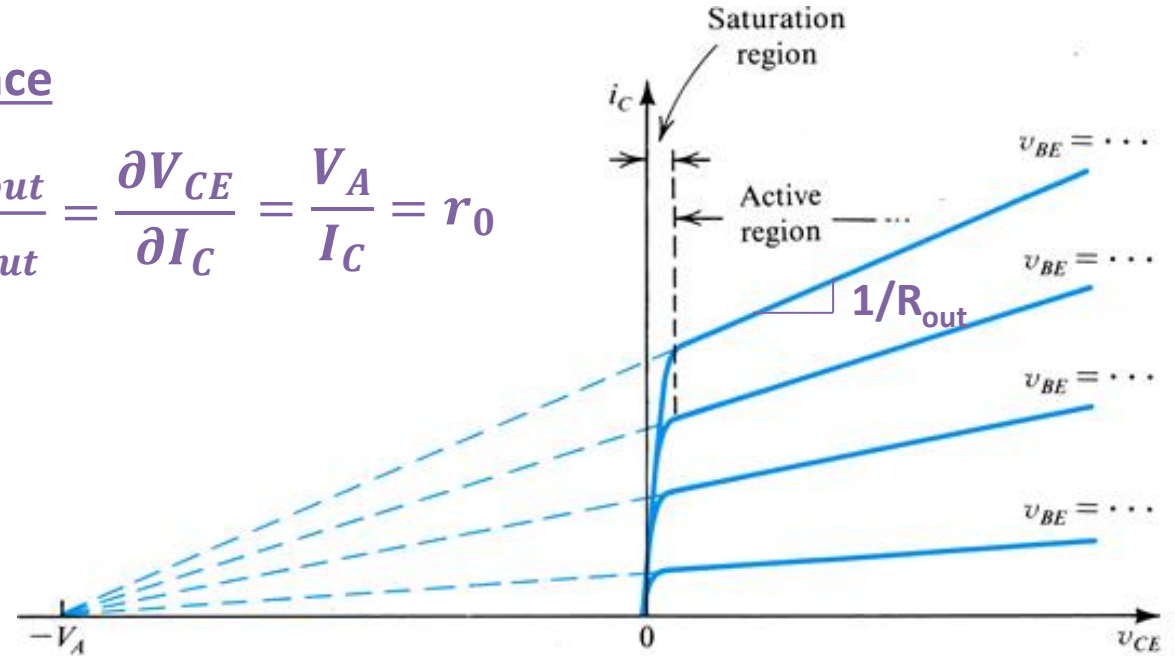
$$R_{out} = \frac{\partial V_{out}}{\partial I_{out}} = \frac{\partial V_{CE}}{\partial I_C} = \frac{V_A}{I_C} = r_o$$



Trans-conductance
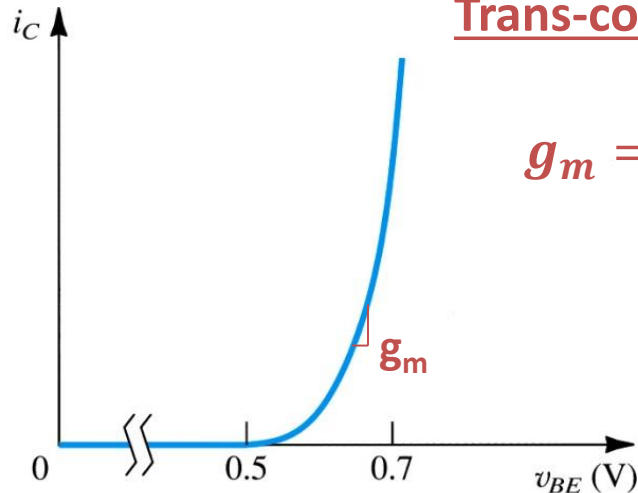
$$g_m = \frac{\partial I_{out}}{\partial V_{in}} = \frac{\partial I_C}{\partial V_{BE}} = \frac{I_C}{V_T}$$





Input Impedance

$$R_{in} = \frac{\partial V_{in}}{\partial I_{in}} = \frac{\partial V_{BE}}{\partial I_B} = \frac{\beta}{g_m} = r_{\pi}$$



Small Signal Equivalent Circuit

9/30/2019

- npn transistor

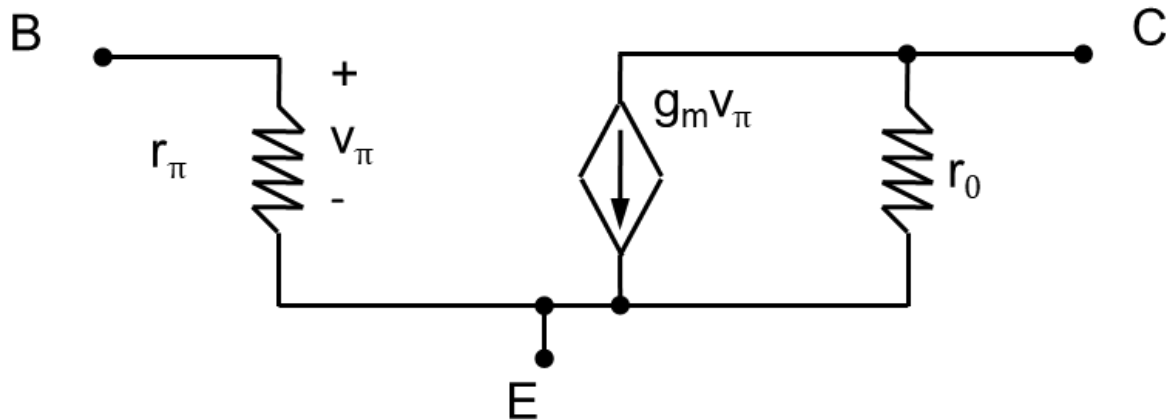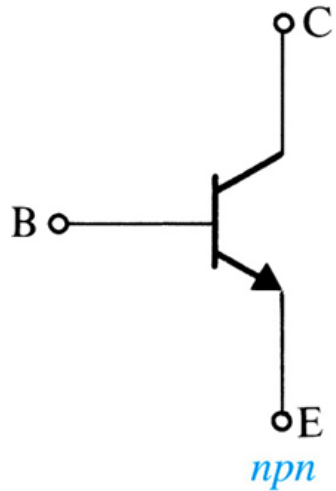

- pnp transistor

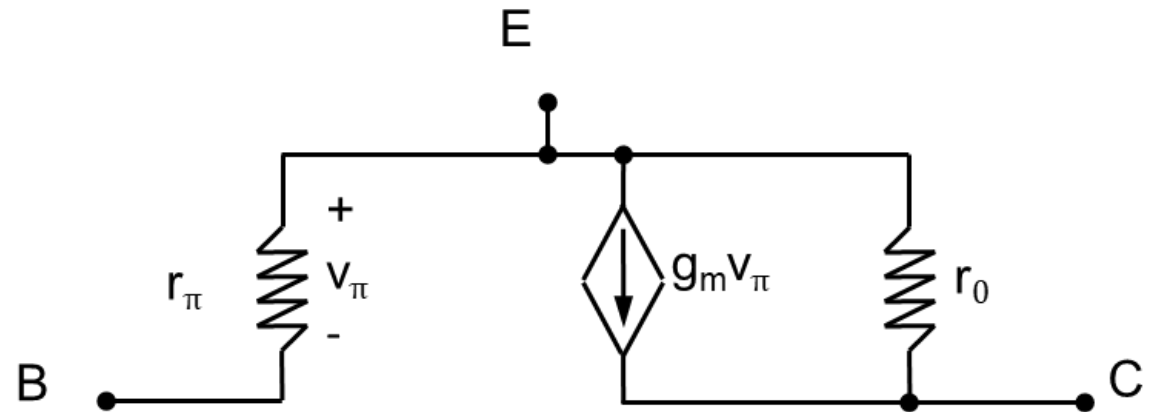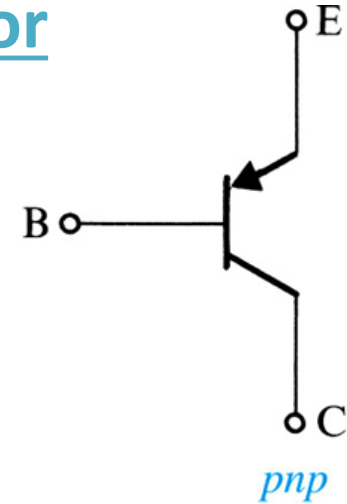


Small Signal Analysis

9/30/2019

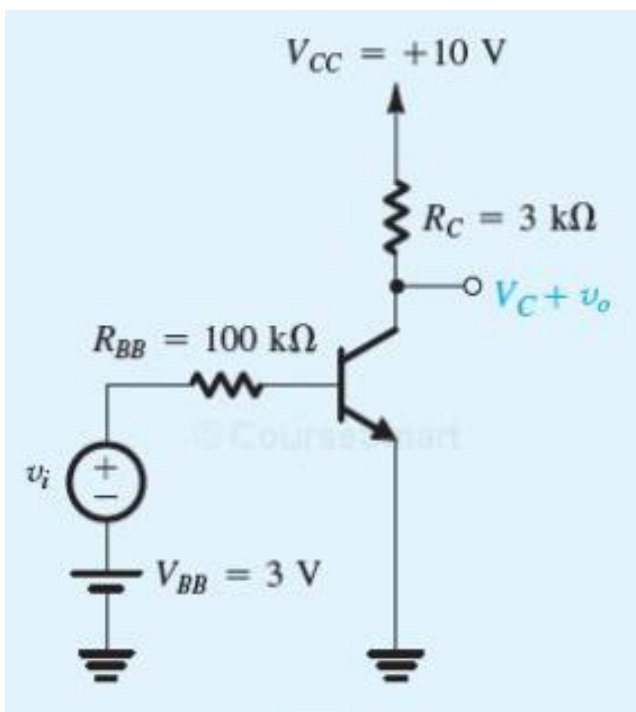- 1) Determine the transistor bias current (DC Analysis)
- 2) Determine the small-signal parameters
- 3) Draw the small-signal equivalent circuit
 - All DC sources off!
 - Low freq. cap shorted!
- 4) Replace transistor with small-signal circuit
- 5) Calculate the desired specifications


Common-Emitter Amplifier

Assuming $\beta=100$ and $V_{BE}=0.7V$ find the input resistance R_{in} (seen by v_s), the output resistance, and the overall voltage gain v_o/v_s .



Common-Emitter Amplifier

9/30/2019

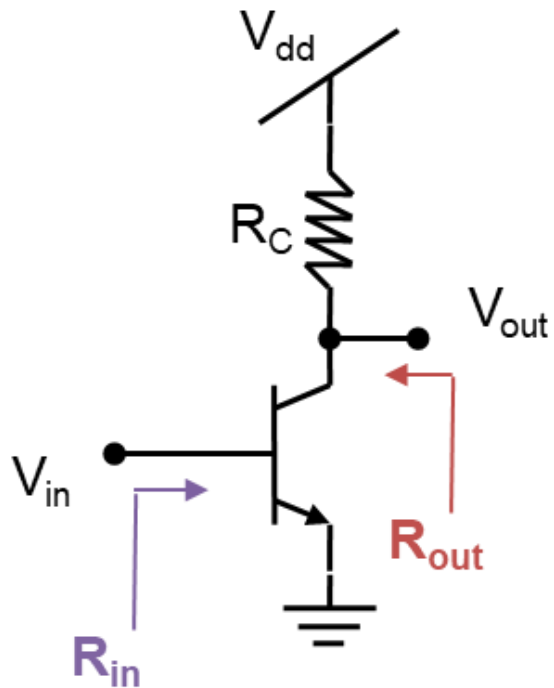


$$R_{in} = r_{\pi}$$

$$R_{out} = R_C // r_o$$

$$A_V = -g_m(R_C // r_o)$$

- High Gain!
- 180° Shift!

- Small Signal Characteristics

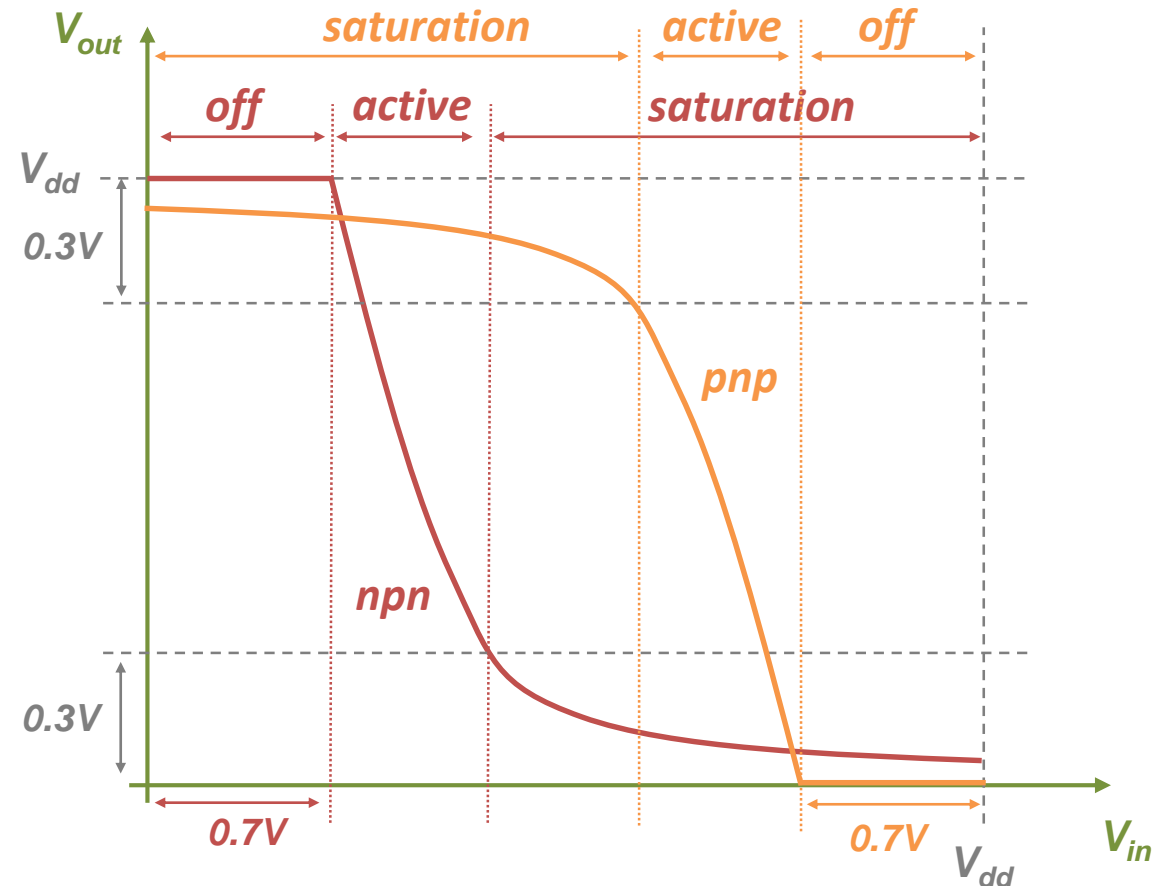

Common Emitter_{nnp} vs Commom Emitter_{pnp}? $A_{V_nnp} = A_{V_pnp}$