
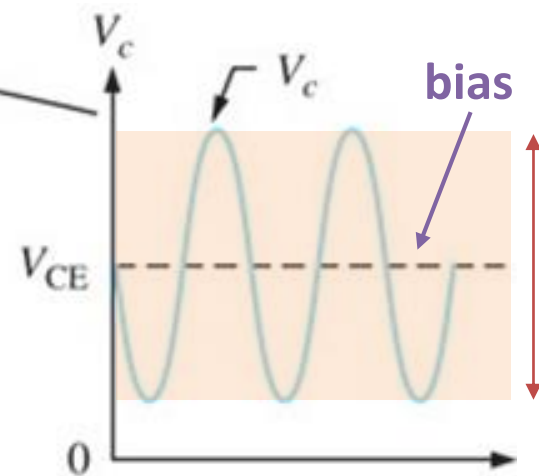


Last Lecture → AC / DC Behavior

10/4/2019

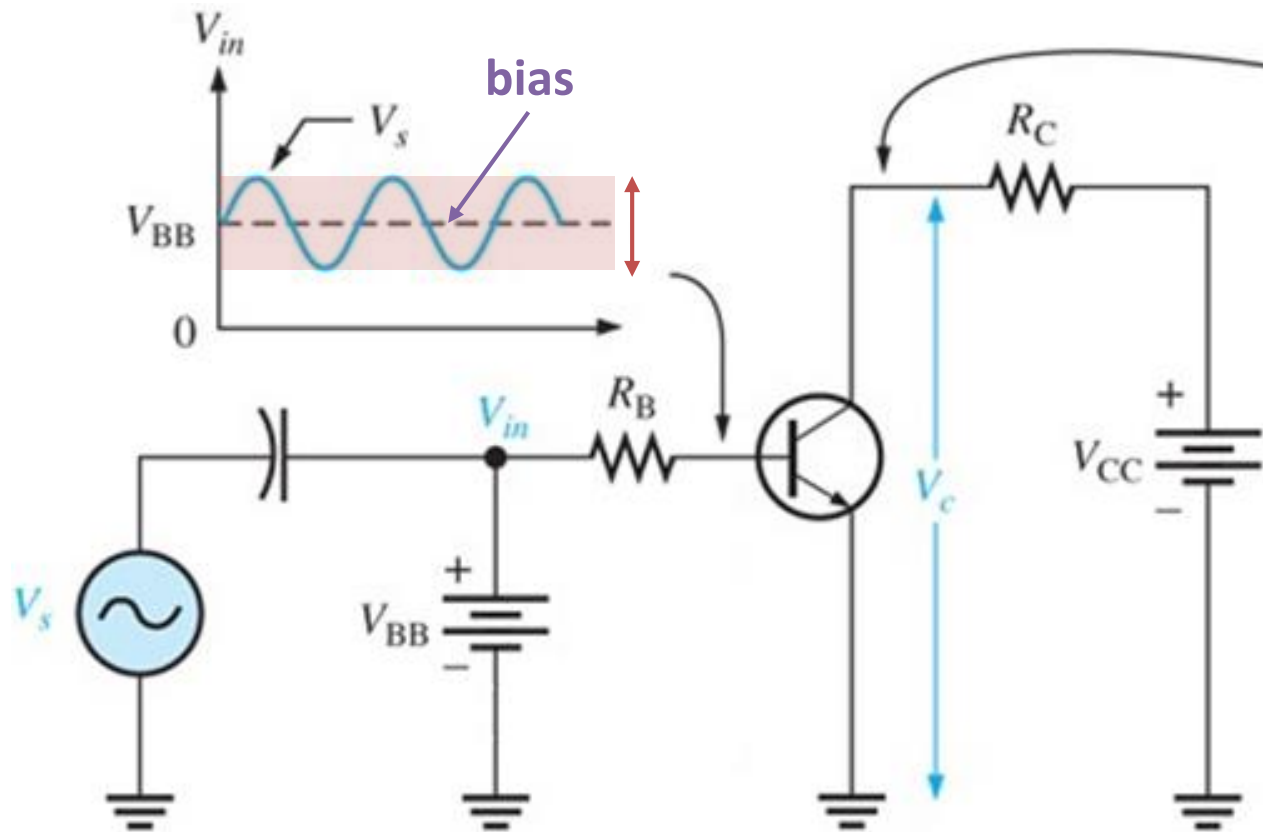- Bias current is established through V_{BB} and supplied by V_{CC}
- AC signal is coupled through the capacitor and superimposed to the DC signal



AC & DC analysis can be performed via superposition!




- Large-Signal (DC) – establishes the DC operating point of the circuit
- Small-Signal (AC) – determines de circuit behavior around the DC operating point


Last Lecture → Small Signal Circuit

10/4/2019

• npn transistor


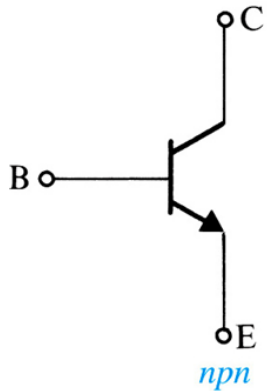


• npn transistor

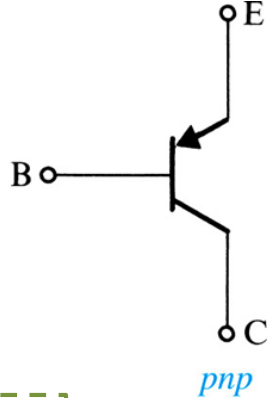

Analysis Procedure

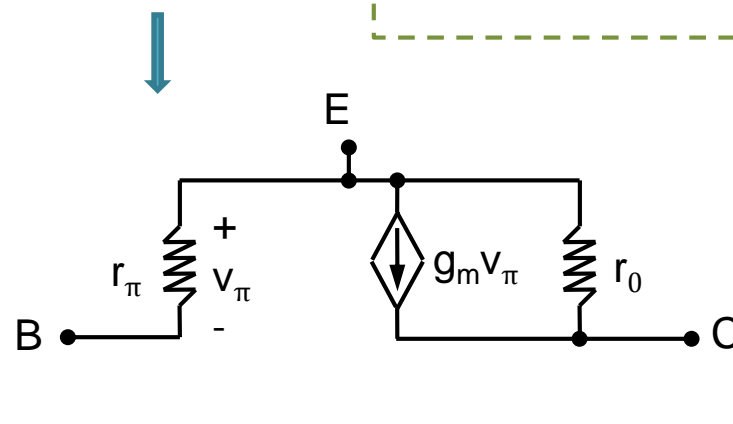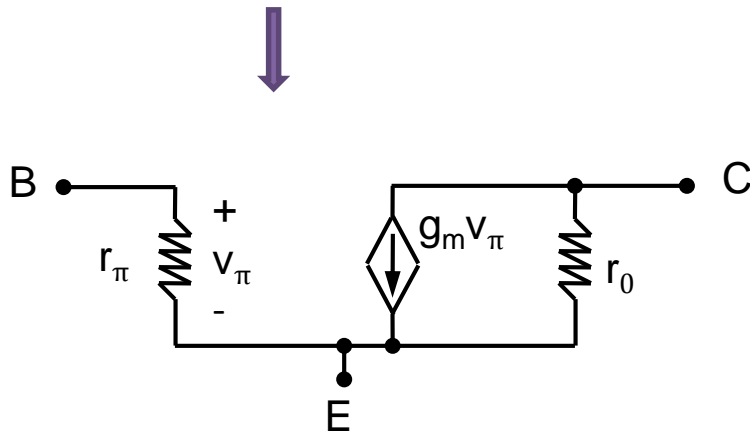- 1) Determine the transistor bias current (DC Analysis)
- 2) Determine the small-signal parameters
- 3) Draw the small-signal equivalent circuit
 - All DC sources off!
 - Low freq. cap shorted!
- 4) Replace transistor with small-signal circuit
- 5) Calculate the desired specifications



Small Signal Parameters


$$g_m = \frac{I_C}{V_T} \quad r_o = \frac{V_A}{I_C}$$

$$r_\pi = \frac{\beta}{g_m}$$


Last Lecture → Common-Emitter Amplifier

10/4/2019

• *npn*

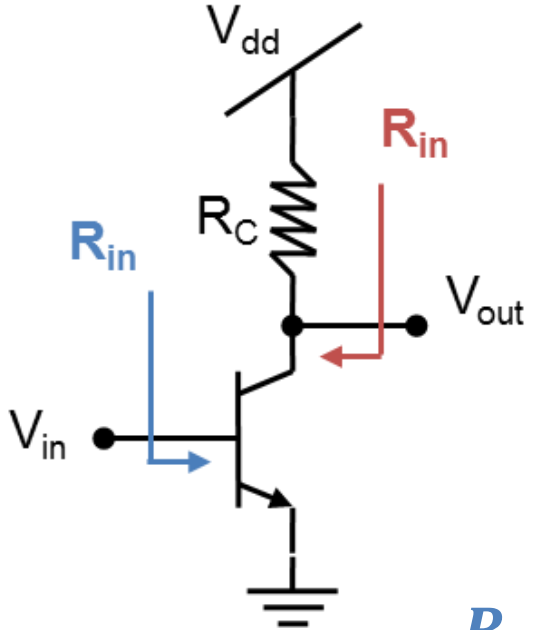


• *pnp*

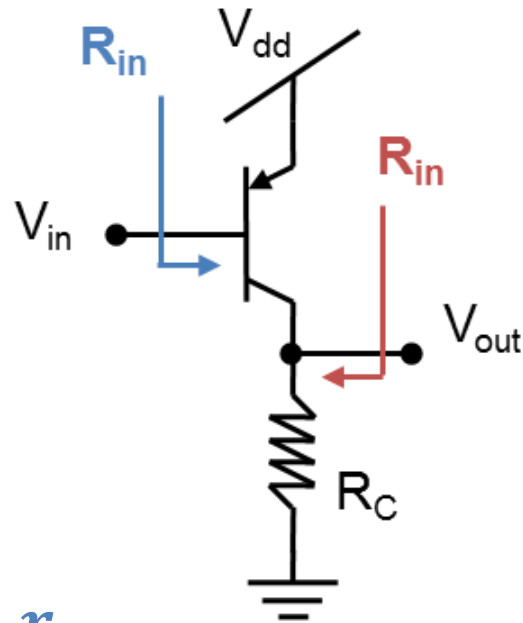

$$R_{in} = r_{\pi}$$

$$R_{out} = R_c // r_o$$


$$A_V = -g_m(R_c // r_o)$$

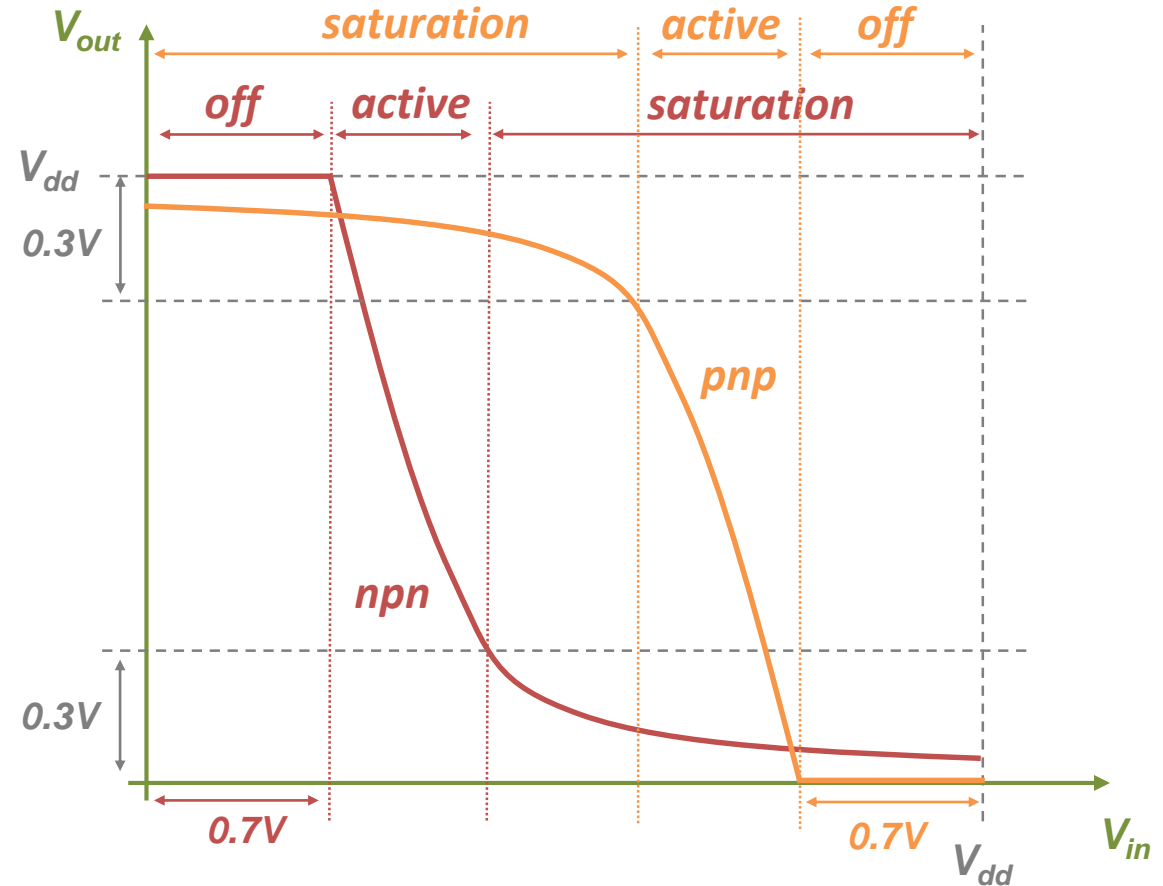

Problem 6.101

10/4/2019


Assuming $\beta = 200$, and $V_A = \infty$, find I_C and the dc voltage at the collector. Find the input resistances R_{ib} and R_{in} and the overall voltage gain v_o/v_{sig} .

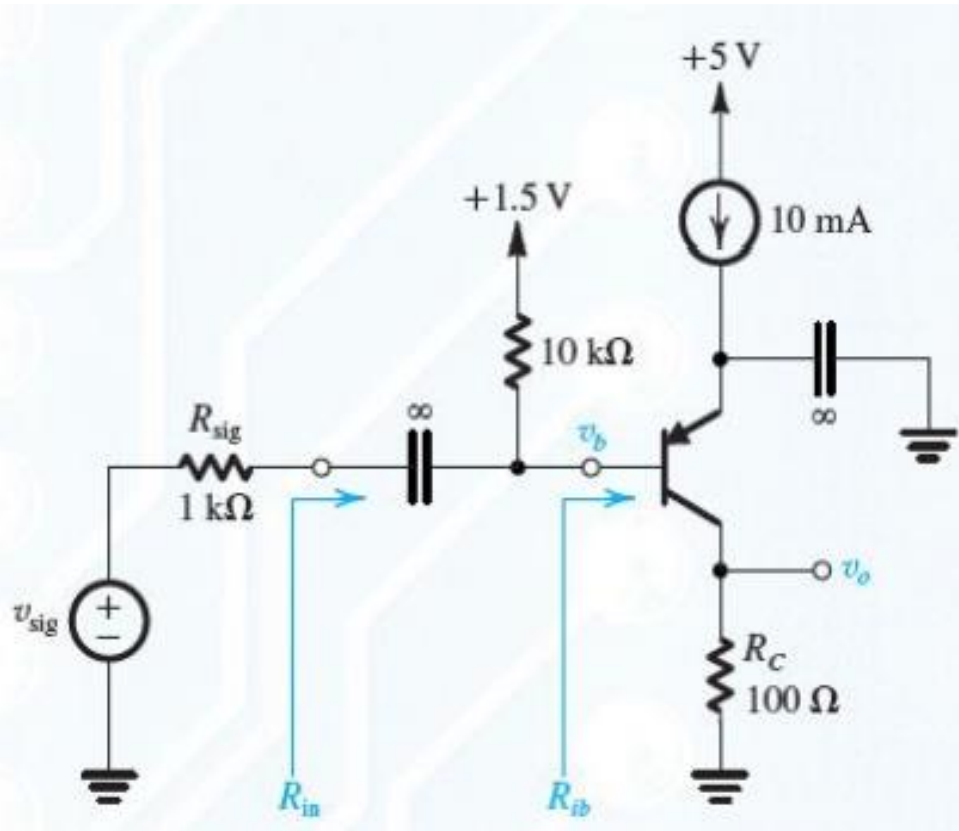

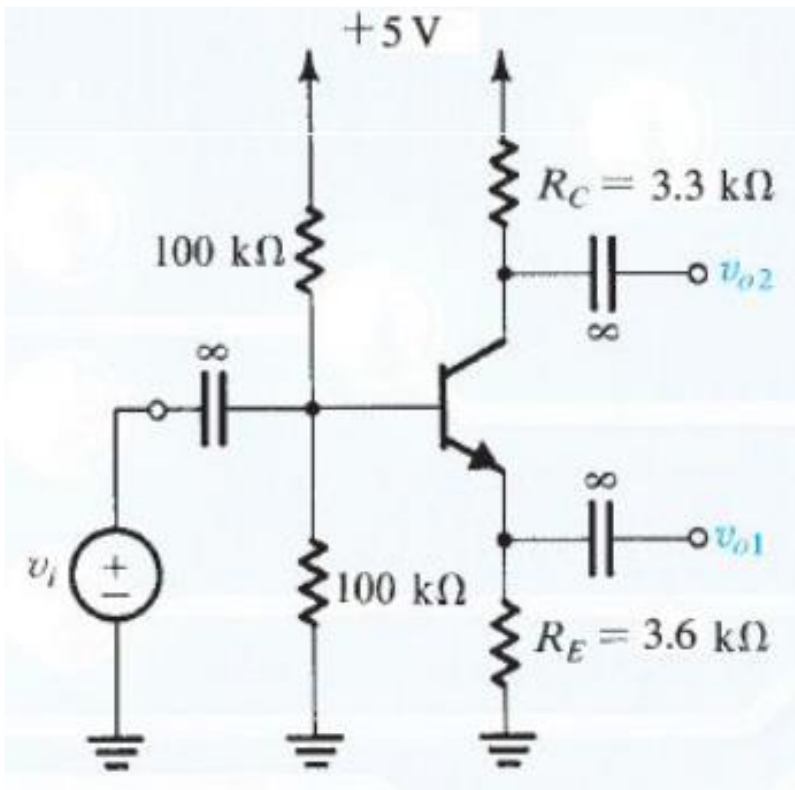Problem 6.107

10/4/2019

Assuming β is very large and the transistor is operating in active mode, find the collector bias current I_C . Using the small-signal model analyze the circuit to determine v_{o1}/v_i and v_{o2}/v_i . Determine the resistance seen by the input source ($V_A = \infty$) and the output resistances from v_{o1} and v_{o2} ($V_A = 100V$).



$$V_E = V_{CC}/2 - V_{BE} = 1.8V$$

$$V_C = V_{CC} - R_C \cdot I_C = 3.35V$$

$$I_C = I_E = \frac{V_E}{R_E} = 0.5mA$$