

Exam #2 → Wednesday, October 16

10/4/2019


BJTs - Chapter #6:

- 1) Semiconductor Physics
- 2) Regions of Operation
- 3) Large Signal Model
- 4) Large Signal Analysis
- 5) Small Signal Model
- 6) Small Signal Analysis


Last Lecture → Common-Emitter Amplifier

10/4/2019

• *npn*

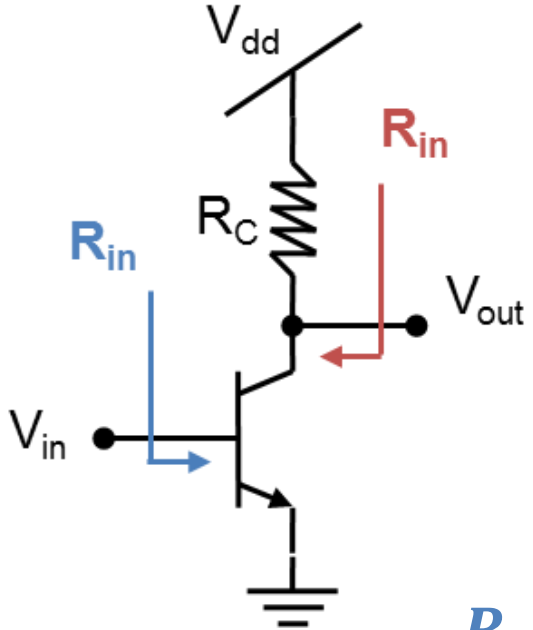


• *pnp*

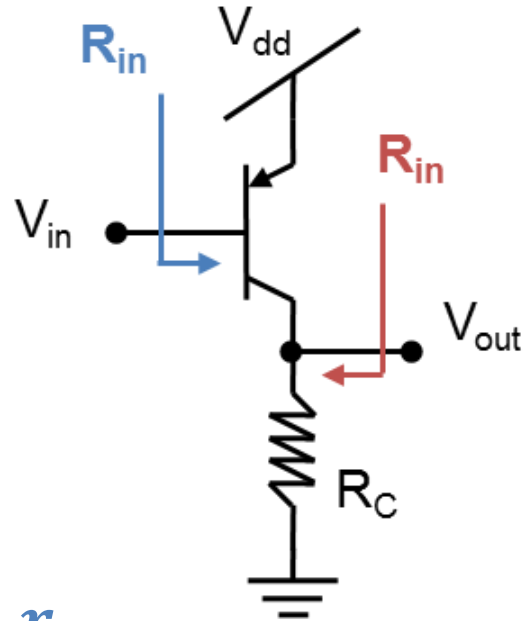

$$R_{in} = r_{\pi}$$

$$R_{out} = R_c // r_o$$


$$A_V = -g_m(R_c // r_o)$$

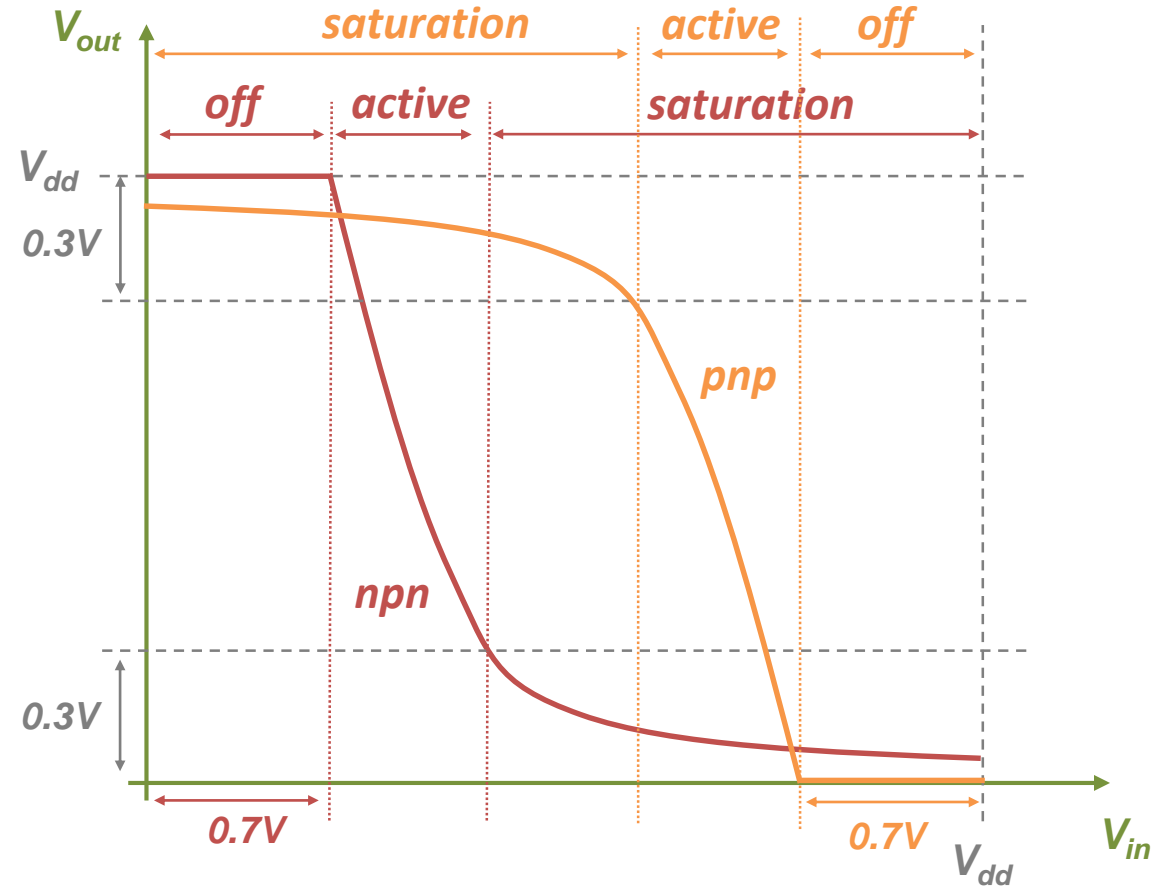

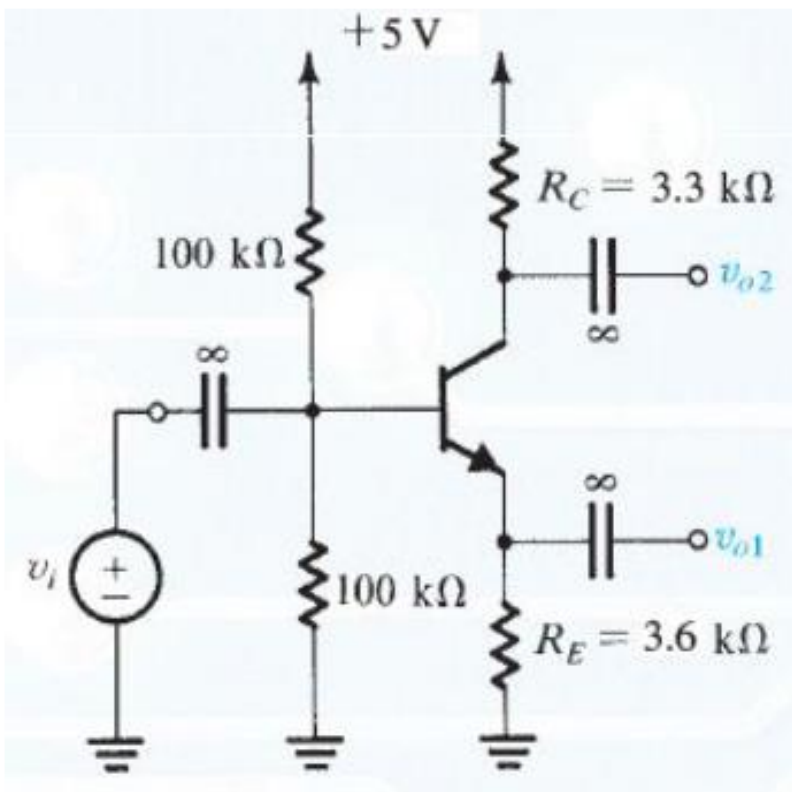Problem 6.107

10/4/2019

Assuming β is very large and the transistor is operating in active mode, find the collector bias current I_C . Using the small-signal model analyze the circuit to determine v_{o1}/v_i and v_{o2}/v_i . Determine the resistance seen by the input source ($V_A = \infty$) and the output resistances from v_{o1} and v_{o2} ($V_A = 100V$).



$$V_C = 3.35V$$

$$I_C = 0.5mA$$

$$g_m = 20mS$$


$$r_\pi = \infty$$

$$r_o = 200k\Omega$$


Common Collector Amplifier

10/4/2019

• *npn*

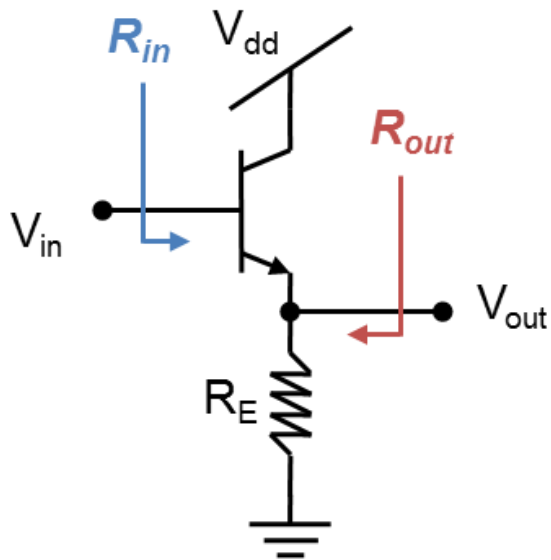


• *pnp*

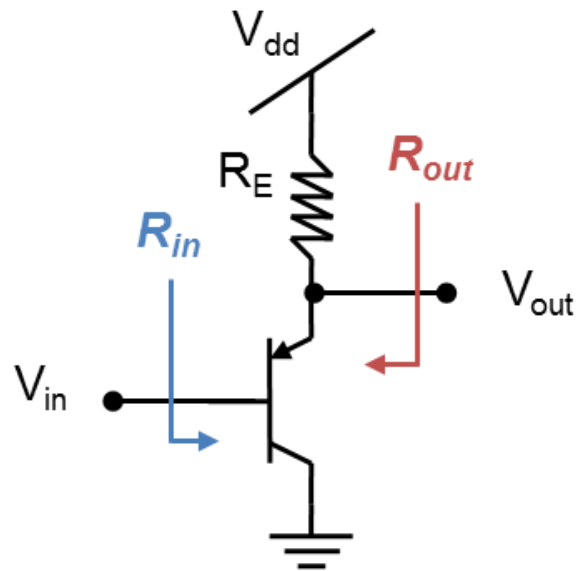

$$R_{in} = r_{\pi}(1 + g_m R_E)$$

$$R_{out} \approx 1/g_m$$

$$A_V = \frac{g_m R_E}{1 + g_m R_E} \approx 1$$

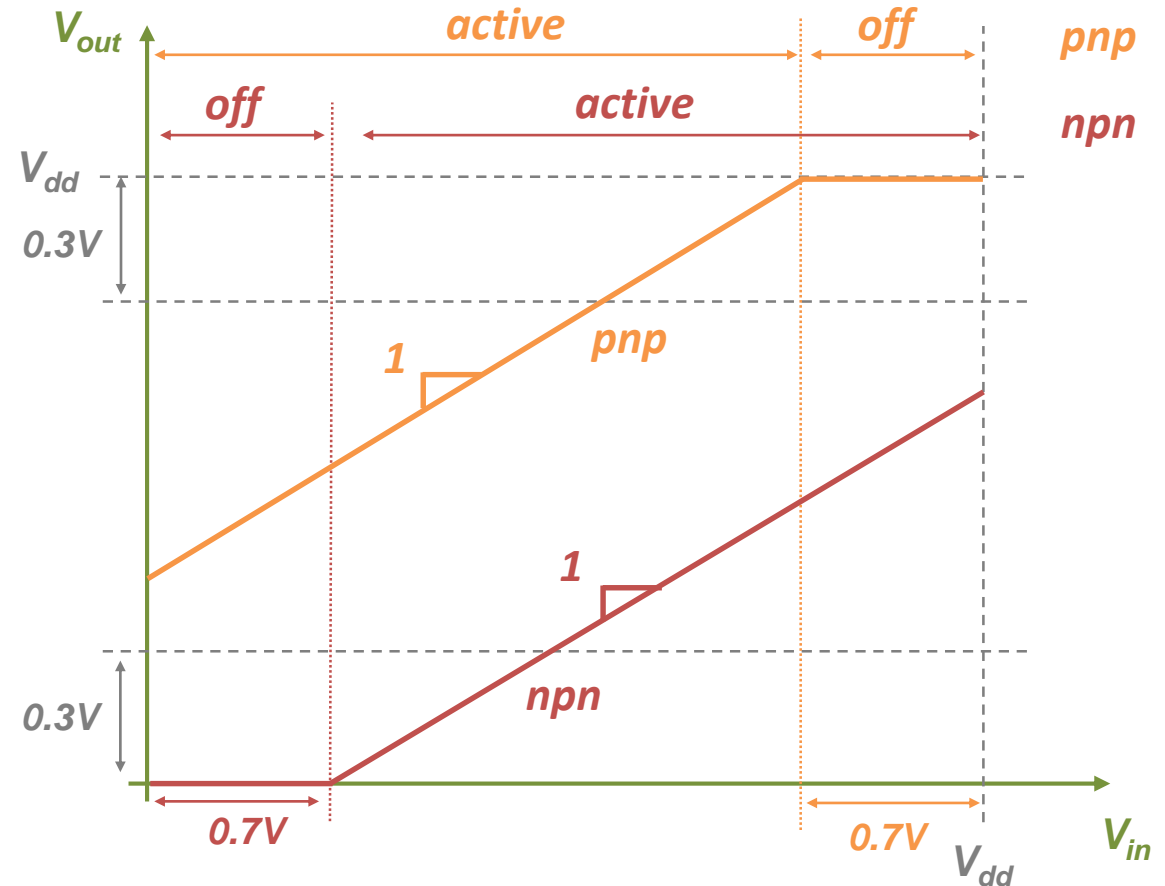


Exercise 6.44

10/4/2019


For the following circuit determine

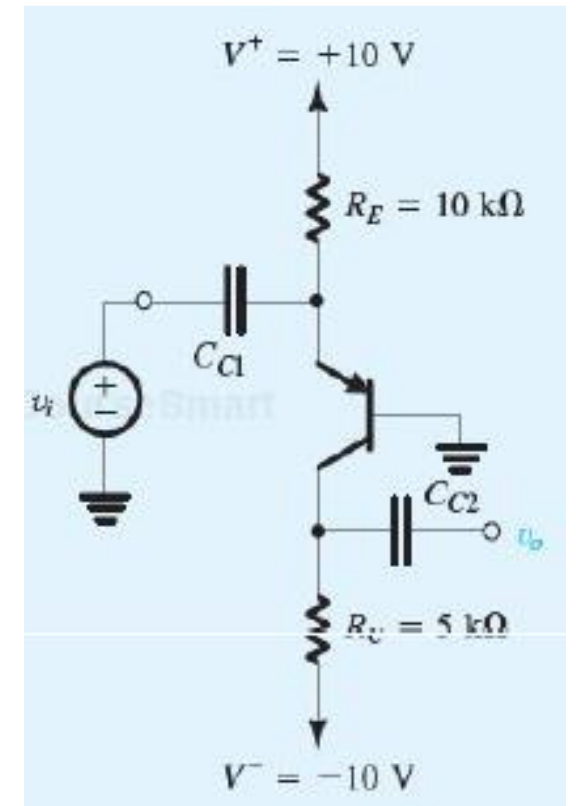1. the voltage gain v_o/v_i ($r_o = \infty$)
2. the impedance seen by the input source ($r_o = \infty$)
3. the output impedance




BJT – Single Stage Amplifiers


10/4/2019

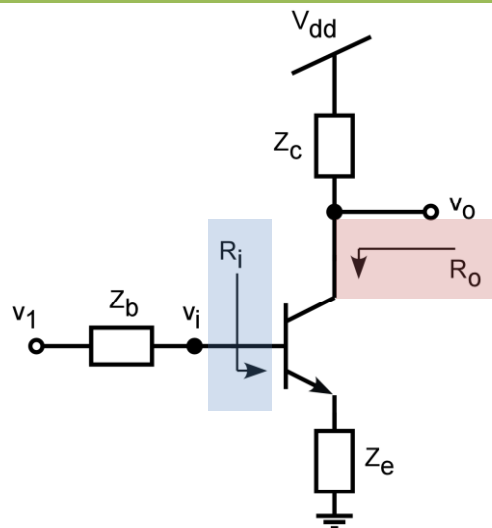

Common Emitter - CE

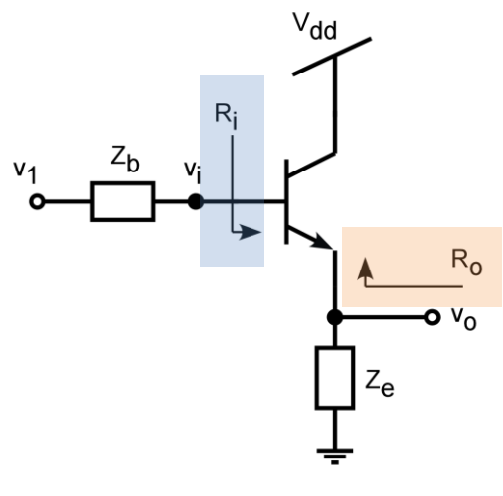

Common Collector - CC

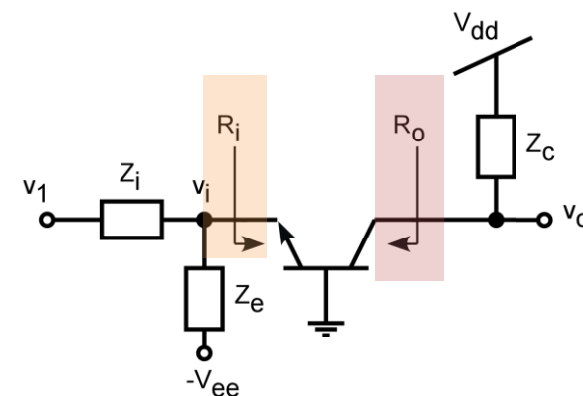

Common Base - CB


| Single Transistor Bipolar Amplifier | Common-Emmitter CE | Common-Collector CC | Common-Base CB |
|---|---|---|--------------------------------|
| Voltage Gain $A_v = \frac{v_o}{v_i}$ | $\cong -\frac{g_m}{1 + g_m Z_e} \cdot R_o // Z_c$ | $\cong +\frac{g_m}{1 + g_m Z_e} \cdot Z_e$ | $= +g_m \cdot R_o // Z_c$ |
| Input Resistance R_i | $= r_\pi (1 + g_m Z_e)$ | $= r_\pi (1 + g_m Z_e)$ | $\cong \frac{1}{g_m}$ |
| Output Resistance R_o | $= r_o (1 + g_m Z_e)$ | $\cong \frac{1}{g_m} + \frac{Z_b}{\beta_o + 1}$ | $= r_o [1 + g_m (Z_i // Z_e)]$ |

Problem 6.155

10/4/2019

For the given circuit, assuming $\beta_1=50$, $\beta_2=100$, $r_o=\infty$ and $V_{BE}=0.7V$,

- find the dc emitter currents of Q_1 and Q_2 along with the dc voltages V_{B1} and V_{B2} .
- Assuming a load resistance $R_L=1k\Omega$ is connected to the output terminal, determine the overall voltage gain v_o/v_{sig} and the input resistance R_{in} .

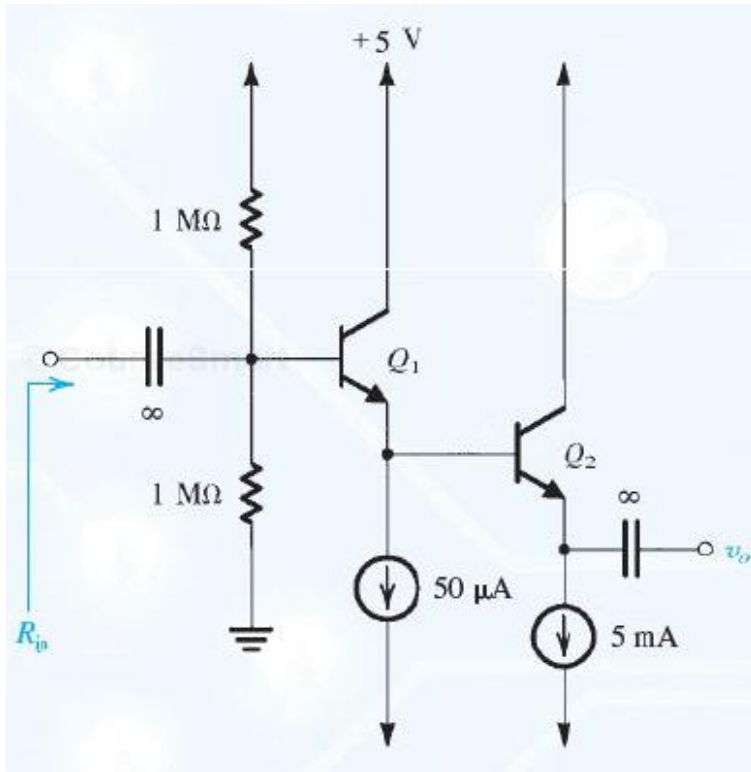


Problem 6.154

10/4/2019

For the given circuit, assume $\beta=100$ and $V_{BE}=0.7V$.

- Find the dc emitter currents and the small signal parameters.
- Determine the overall voltage gain v_o/v_{sig} and the input resistance R_{in} .
- Repeat b) for the case when capacitor C_B is open-circuited. Compare the results with those obtained in b).

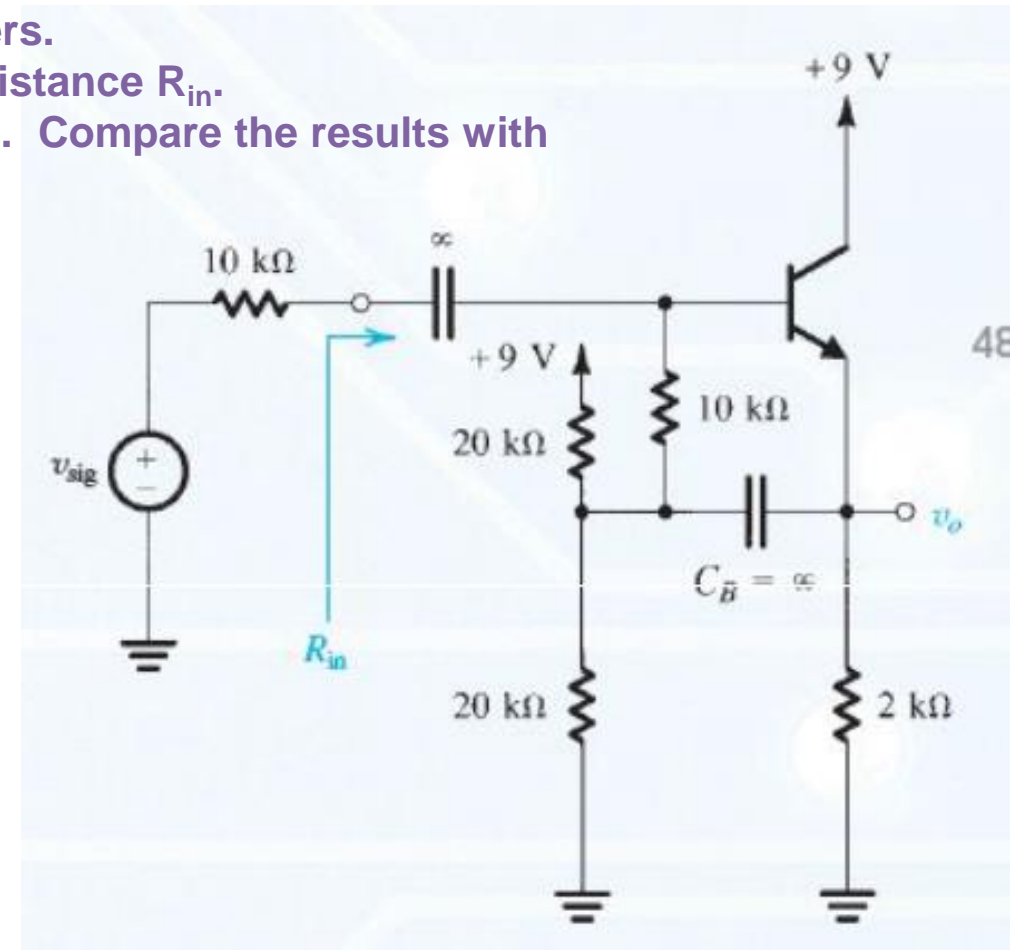


Problem 6.147

10/4/2019

***6.147** The amplifier of Fig. P6.147 consists of two identical common-emitter amplifiers connected in cascade. Observe that the input resistance of the second stage, R_{in2} , constitutes the load resistance of the first stage.

- (a) For $V_{CC} = 9\text{ V}$, $R_1 = 100\text{ k}\Omega$, $R_2 = 47\text{ k}\Omega$, $R_E = 3.9\text{ k}\Omega$, $R_C = 6.8\text{ k}\Omega$, and $\beta = 100$, determine the dc collector current and dc collector voltage of each transistor.
- (b) Draw the small-signal equivalent circuit of the entire amplifier and give the values of all its components.
- (c) Find R_{in1} and v_{b1}/v_{sig} for $R_{sig} = 5\text{ k}\Omega$
- (d) Find R_{in2} and v_{b2}/v_{b1} .
- (e) For $R_L = 2\text{ k}\Omega$, find v_o/v_{b2} .
- (f) Find the overall voltage gain v_o/v_{sig} .

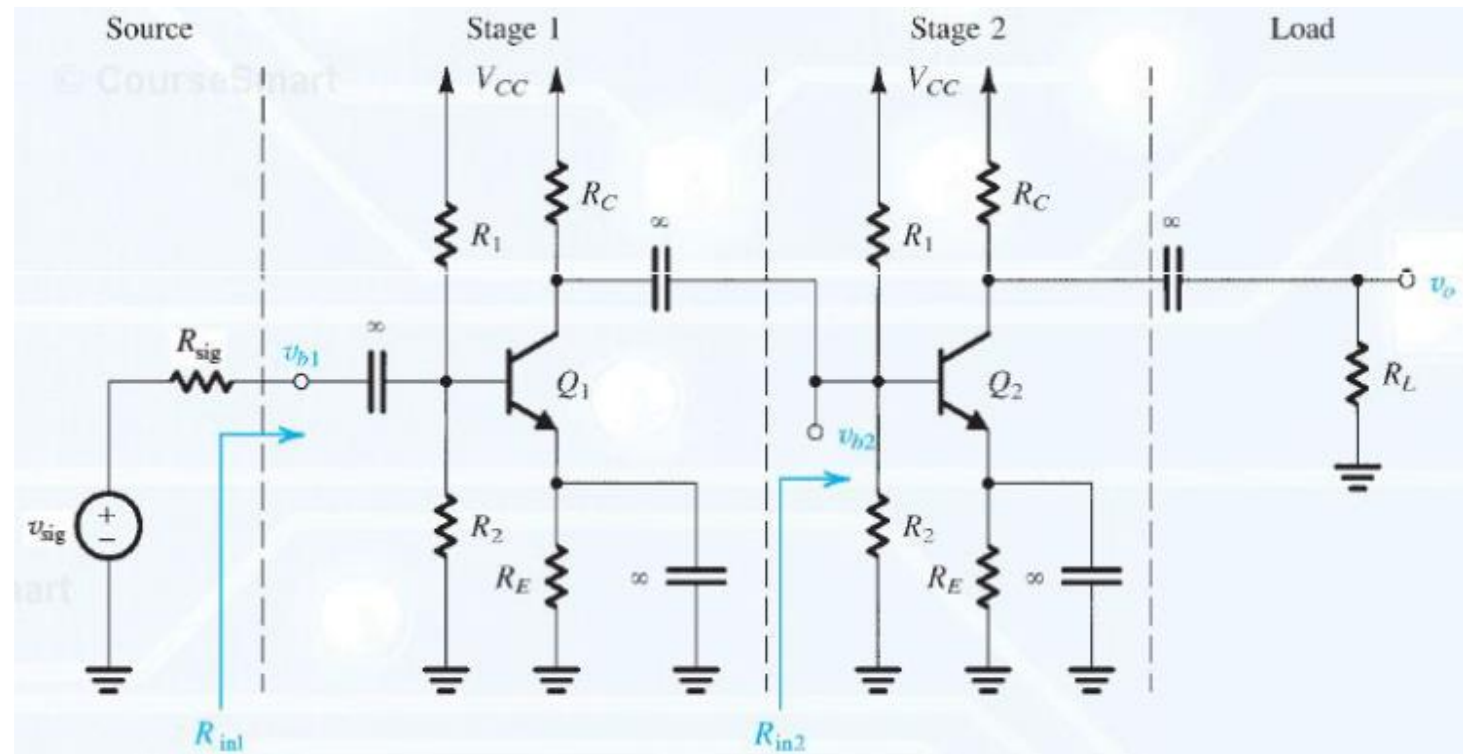


Problem 6.136

10/4/2019

For the given circuit, using a 3-V power supply,

- and assuming $R_{b2} = \infty$, design R_c and R_{b1} to provide $I_c = 3\text{mA}$ and $V_c = V_{cc}/2$ for $\beta = 90$.
- Find V_c and I_c for $\beta = \infty$.
- Re design R_c , R_{b1} and R_{b2} for $\beta = 90$ and using a current through R_{b2} equal to the base current.
- Find V_c and I_c for $\beta = \infty$.

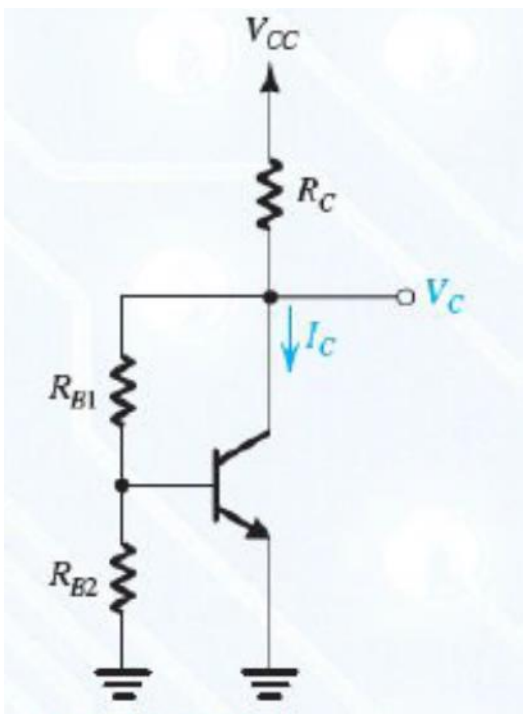


Problem 6.140

10/4/2019

For the given circuit, assuming all transistors to be identical with β infinite,

- derive an expression for the output current I_0 , and show that by selecting $R_1=R_2$ and keeping the current in each junction the same, the current I_0 will be $I_0=V_{CC}/(2R_E)$
- What must be the relationship of R_E to R_1 and R_2 be?
- For $V_{CC}=10V$ and $V_{BE}=0.7V$, design the circuit to obtain an output current of $0.5mA$.
- What is the lowest voltage that can be applied to the collector of Q_3 ?

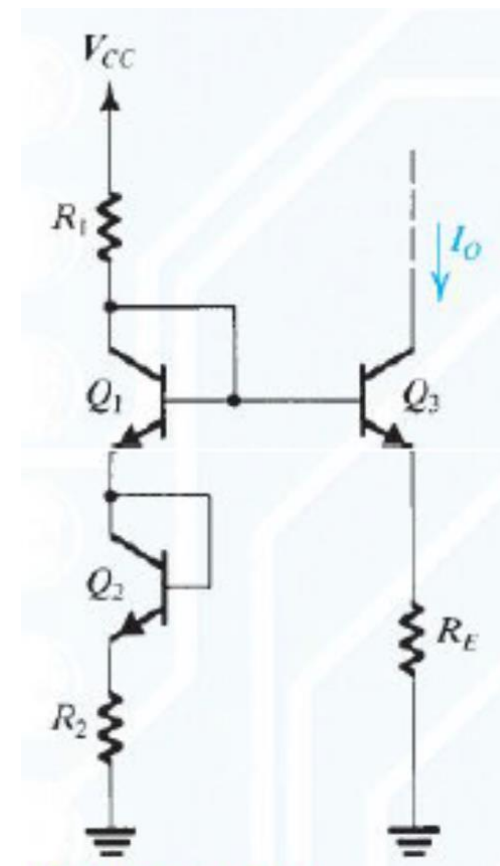

Problem 6.68

10/4/2019

Assuming $\beta = \infty$, design the given circuit so that the bias currents in Q_1 , Q_2 , and Q_3 are 1mA, 1mA, and 2mA, respectively, and $V_3 = 0$, $V_5 = -2V$, and $V_7 = 1V$.

