

Last Lecture → Large Signal Model

10/30/2019

- Strong Inversion – Ohmic

$$I_D = \mu C_{ox} \frac{W}{L} \left[(V_{GS} - V_{th}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

Condition

$$\begin{aligned} V_{GS} &> V_{th} \\ V_{DS} &< V_{OV} \end{aligned}$$

- Strong Inversion - Saturation

$$I_D = \frac{\mu C_{ox} W}{2 L} (V_{GS} - V_{th})^2 (1 + \lambda V_{DS})$$

$$\begin{aligned} V_{GS} &> V_{th} \\ V_{DS} &> V_{OV} \end{aligned}$$

- Weak Inversion - Saturation


$$I_D = I_0 \cdot e^{\frac{V_{GS} - V_{th}}{n U_T}}$$

$$V_{th} - 5 \cdot U_T < V_{GS} < V_{th} - 2 \cdot U_T$$

Example 5.7

10/30/2019

Assuming $\lambda=0$, design the circuit below, so that the transistor operates in saturation with $I_D=0.5\text{mA}$ and $V_D=3\text{V}$. The PMOS transistor has $V_{th}=-1\text{V}$, $K_p=1\text{mA/V}^2$. What is the largest value that R_D can have while maintaining saturation-region operation?

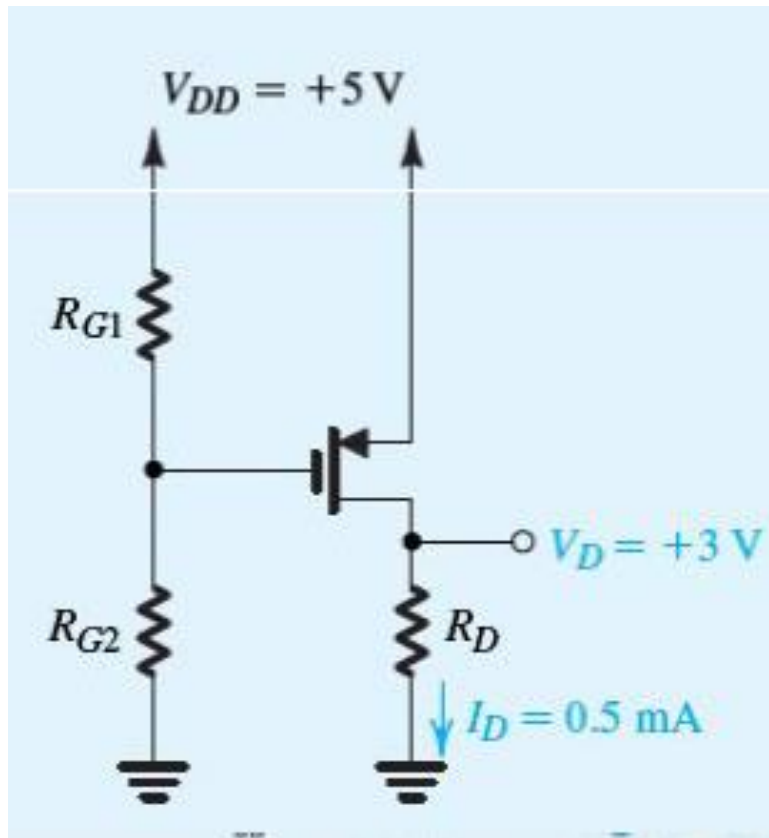

Example 5.5

10/30/2019

An n-channel MOSFET operating with $V_{ov}=0.5V$ exhibits a linear resistance $r_{DS}=1k\Omega$ when v_{DS} is very small.


- What is the value of the device trans-conductance parameter K_n ?
- Assuming $\lambda = 0$, what is the value of the current I_D obtained when v_{DS} is increased to 0.5V? And to 1V?
- Assuming an $\lambda = 0.1V^{-1}$, what is the value of the current I_D obtained when v_{DS} is increased to 0.5V? And to 1V?

MOS Behavior → Intuitively

10/30/2019

Choose the plot that best represents each circuit behavior!

Circuit (a) _____

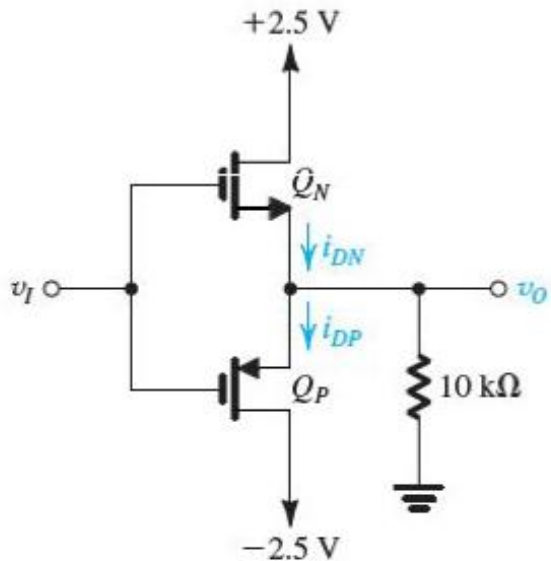

Circuit (b) _____

