

Last Lecture → Large Signal Model

11/4/2019

- Strong Inversion – Ohmic

$$I_D = \mu C_{ox} \frac{W}{L} \left[(V_{GS} - V_{th}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

Condition

$$\begin{aligned} V_{GS} &> V_{th} \\ V_{DS} &< V_{OV} \end{aligned}$$

- Strong Inversion - Saturation

$$I_D = \frac{\mu C_{ox} W}{2 L} (V_{GS} - V_{th})^2 (1 + \lambda V_{DS})$$

$$\begin{aligned} V_{GS} &> V_{th} \\ V_{DS} &> V_{OV} \end{aligned}$$

- Weak Inversion - Saturation


$$I_D = I_0 \cdot e^{\frac{V_{GS} - V_{th}}{n U_T}}$$

$$V_{th} - 5 \cdot U_T < V_{GS} < V_{th} - 2 \cdot U_T$$

Example 5.8

11/4/2019

Assuming matched NMOS and PMOS transistors with $V_{thn} = -V_{thp} = 1V$, $K_n = K_p = 1mA/V^2$ and $\lambda = 0$, find the drain currents I_{Dn} and I_{Dp} , as well as the voltage v_o , for $v_i = 0V$, $+2.5V$, and $-2.5V$.

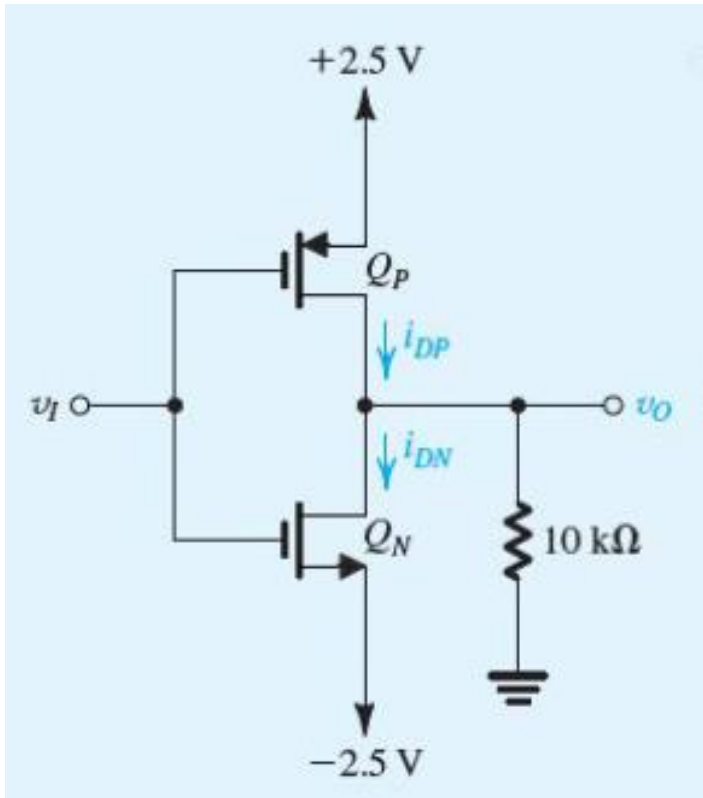

Exercise 5.15

11/4/2019

Assuming matched NMOS and PMOS transistors with $V_{thn} = -V_{thp} = 1V$, $K_n = K_p = 1mA/V^2$ and $\lambda = 0$, find the drain currents I_{Dn} and I_{Dp} , as well as the voltage v_o , for $v_i = 0V$, $+2.5V$, and $-2.5V$.

