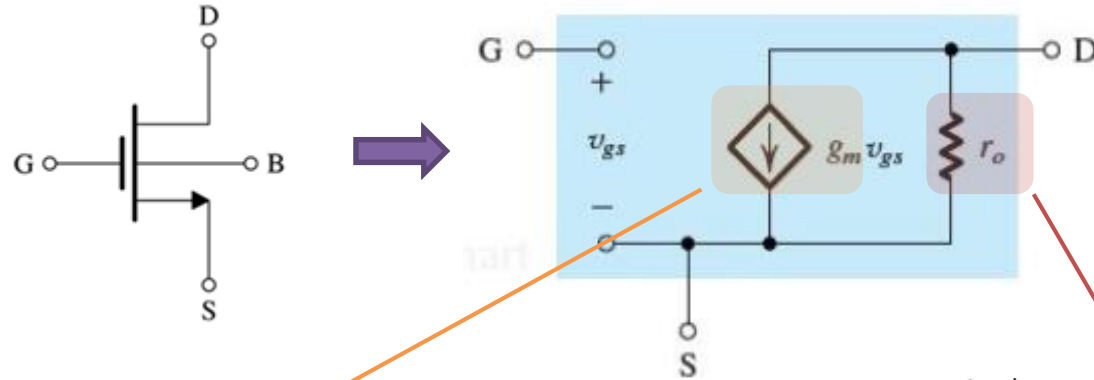


Last Lecture → Small Signal Parameters



11/12/2019

- Trans-conductance (g_m)
- Output Impedance (r_o)
- Input Impedance





$$r_o = \frac{1}{\lambda I_D}$$

$$g_m = \sqrt{2I_D K_n}$$

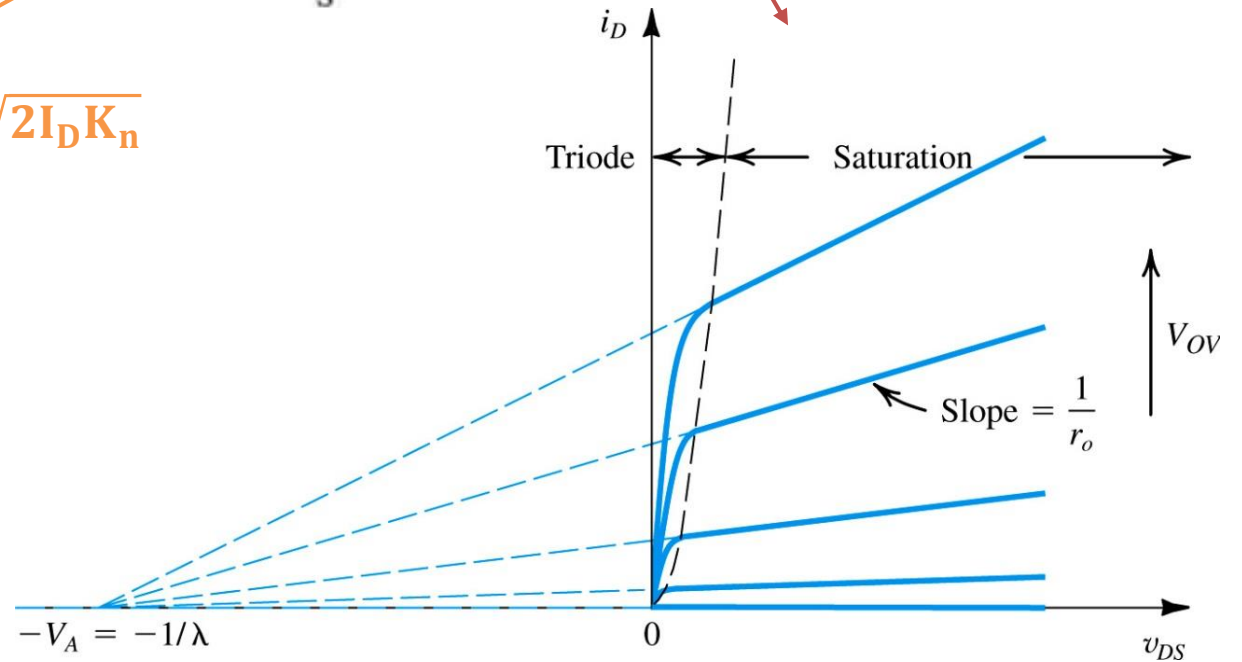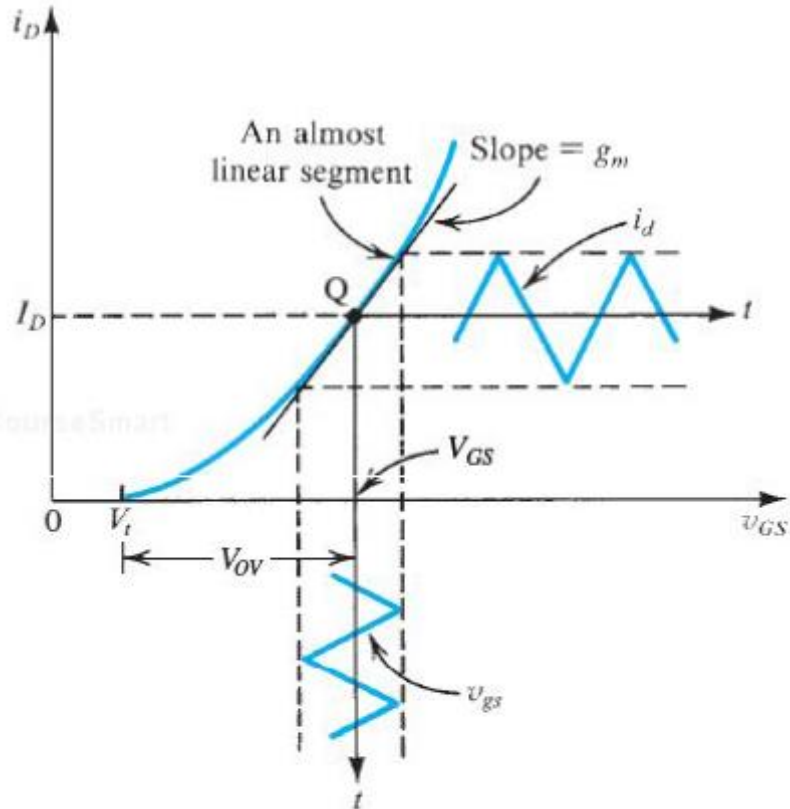


Basic MOSFETs Amplifier Configuration


11/12/2019

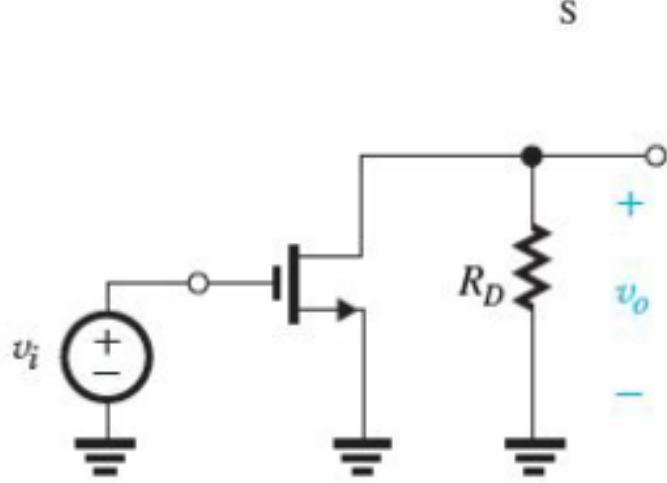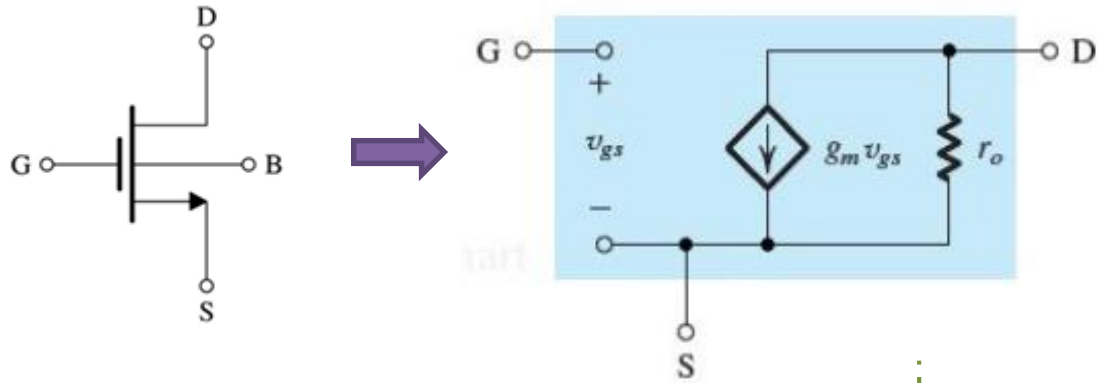

(a) Common Source (CS)

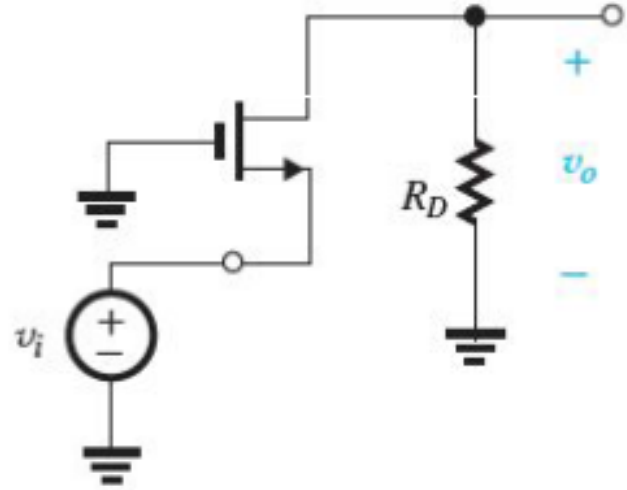


(b) Common Gate (CG)

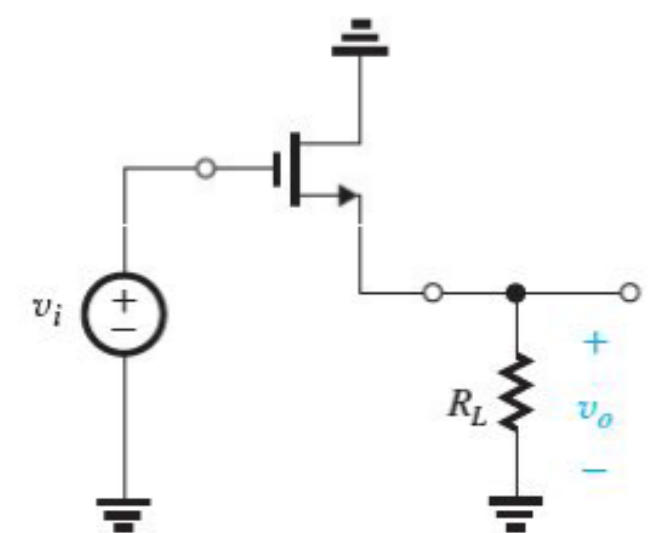


(c) Common Drain (CD)

MOS Amplifiers


11/12/2019

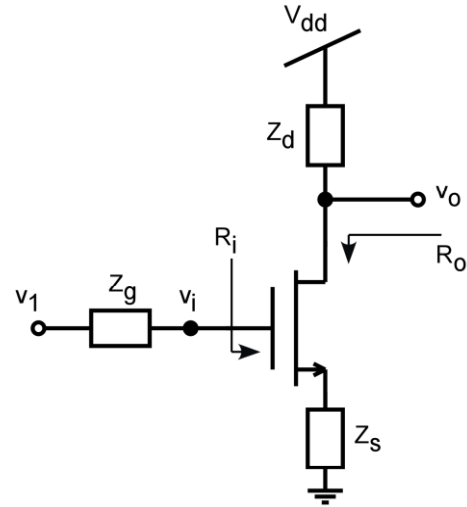

Common Source - CS

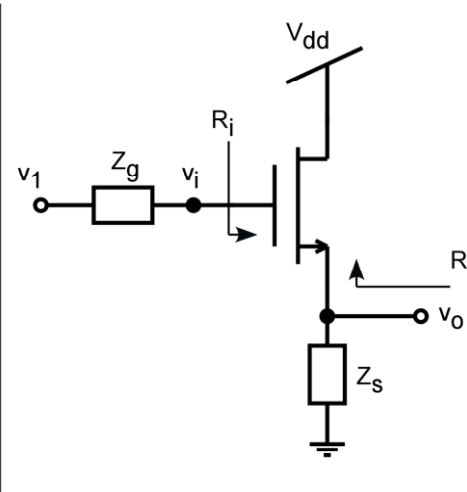

Common Drain - CD

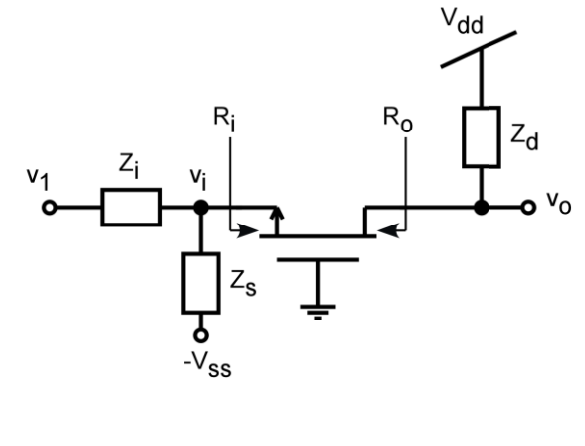

Common Gate - CG


Single Transistor MOS Amplifier	Common-Source	Common-Drain	Common-Gate
Voltage Gain $A_v = \frac{v_o}{v_i}$	$= -\frac{g_m}{1 + g_m Z_s} \cdot R_o // Z_d$	$= +\frac{g_m}{1 + g_m Z_s} \cdot Z_s$	$= +g_m R_o // Z_d$
Input Resistance R_i	$= \infty$	$= \infty$	$= \frac{1}{g_m}$
Output Resistance R_o	$= r_{ds}(1 + g_m Z_s)$	$= \frac{1}{g_m}$	$= r_{ds}[1 + g_m(Z_i // Z_s)]$

Exercise 5.38

11/12/2019

Consider the given amplifier with $g_m=1\text{mA/V}$, $r_o=150\text{k}\Omega$, $R_{\text{sig}}=100\text{k}\Omega$, and $R_L=15\text{k}\Omega$.

- Calculate R_{in} , $A_{v_{\text{cs}}}=V_o/V_i$, and R_o , both without and with r_o taken into account
- Calculate the overall voltage gain $G_v=v_o/v_{\text{sig}}$, with r_o taken into account
- Determine output signal v_o if v_{sig} is a 0.4-V peak-to-peak sinusoid.

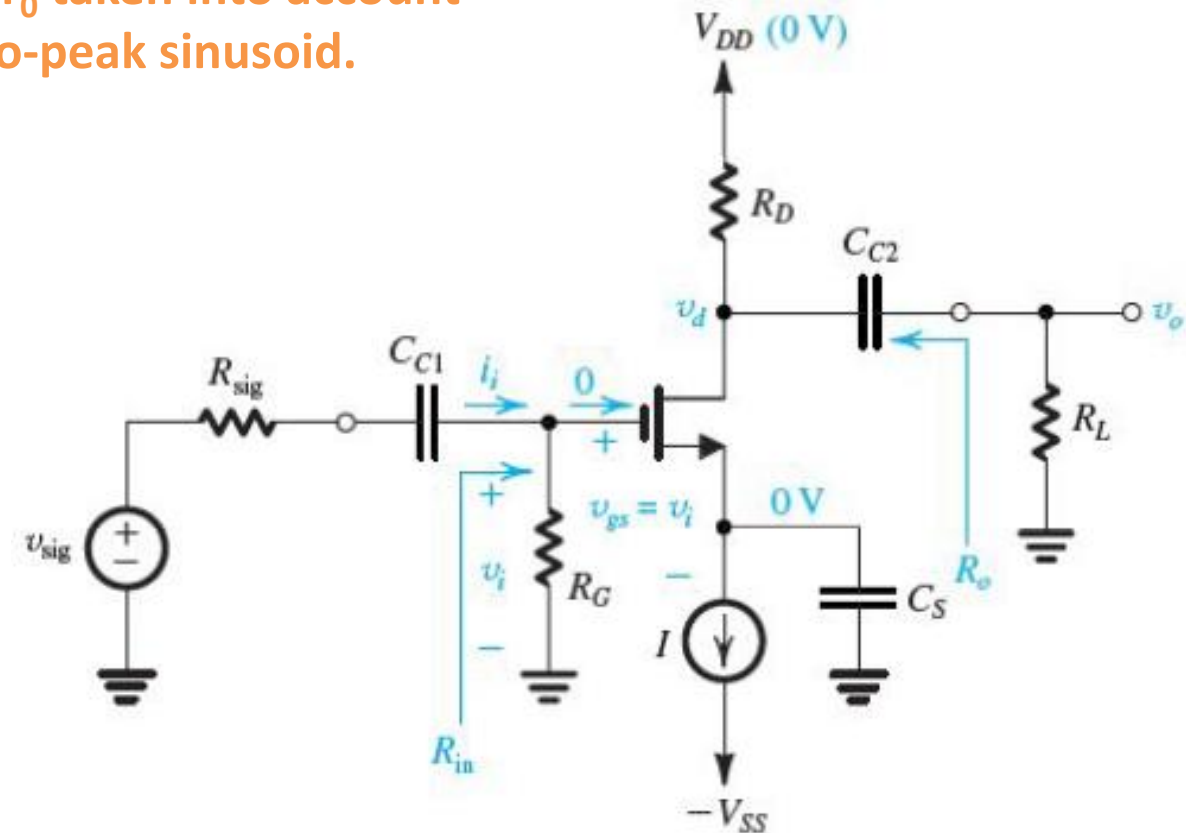


Exercise 5.41

11/12/2019

Consider the given common collector amplifier with $g_m=1\text{mA/V}$ and $r_o=150\text{k}\Omega$. Let $R_{\text{sig}}=1\text{M}\Omega$, $R_G=1\text{M}\Omega$, and $R_L=15\text{k}\Omega$,

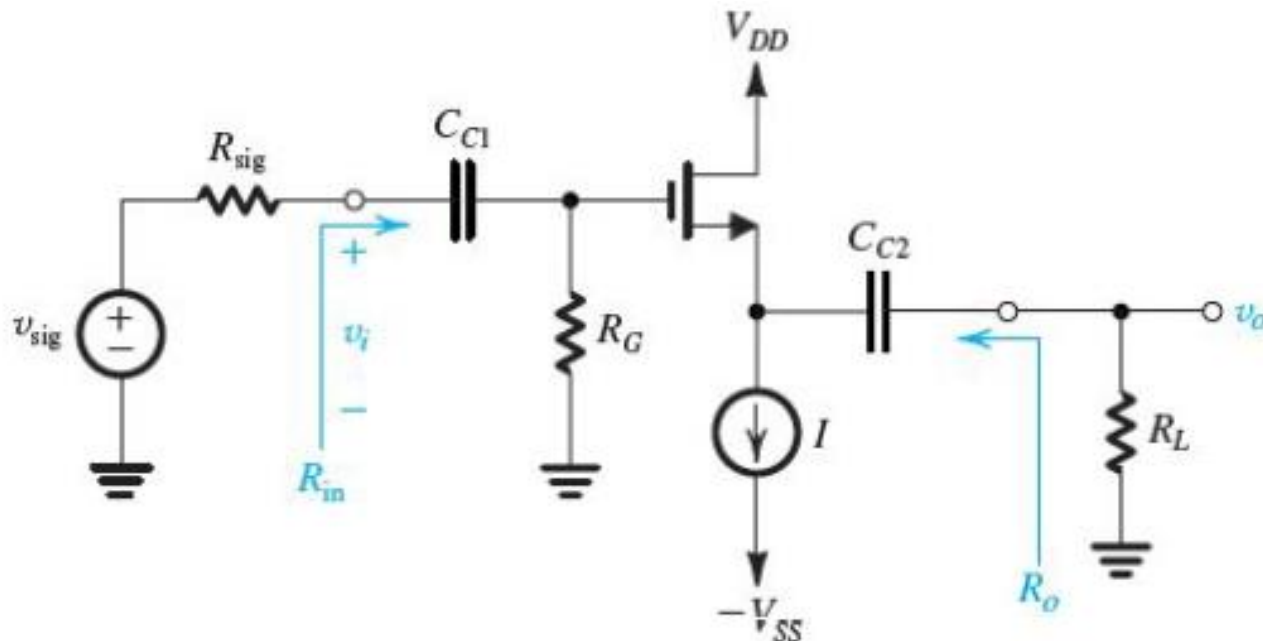- Find R_{in} , $A_v=V_o/V_i$, and R_o without and with r_o taken into account.
- Find the overall voltage gain $G_v=v_o/v_{\text{sig}}$ with r_o taken into account,



Problem

11/12/2019

An common source NMOS amplifier is to be designed to provide a 0.5V peak output signal across a 50k Ω load that can be used as a drain resistor. If a gain of at least -5V/V is needed, what g_m is required? Using a dc supply of 1.8V, what values of I_d and V_{ov} would you choose? What W/L ratio is required if $k_n'=200\mu\text{A}/\text{V}^2$? If $V_t=0.4\text{V}$, find V_{gs} .