
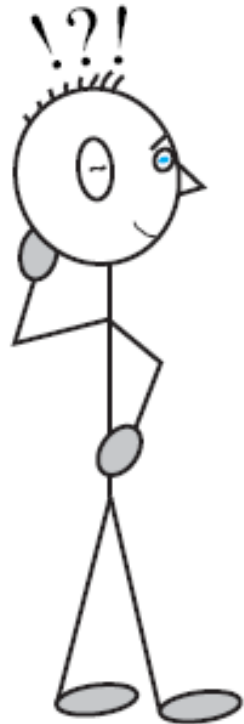


Course Objectives

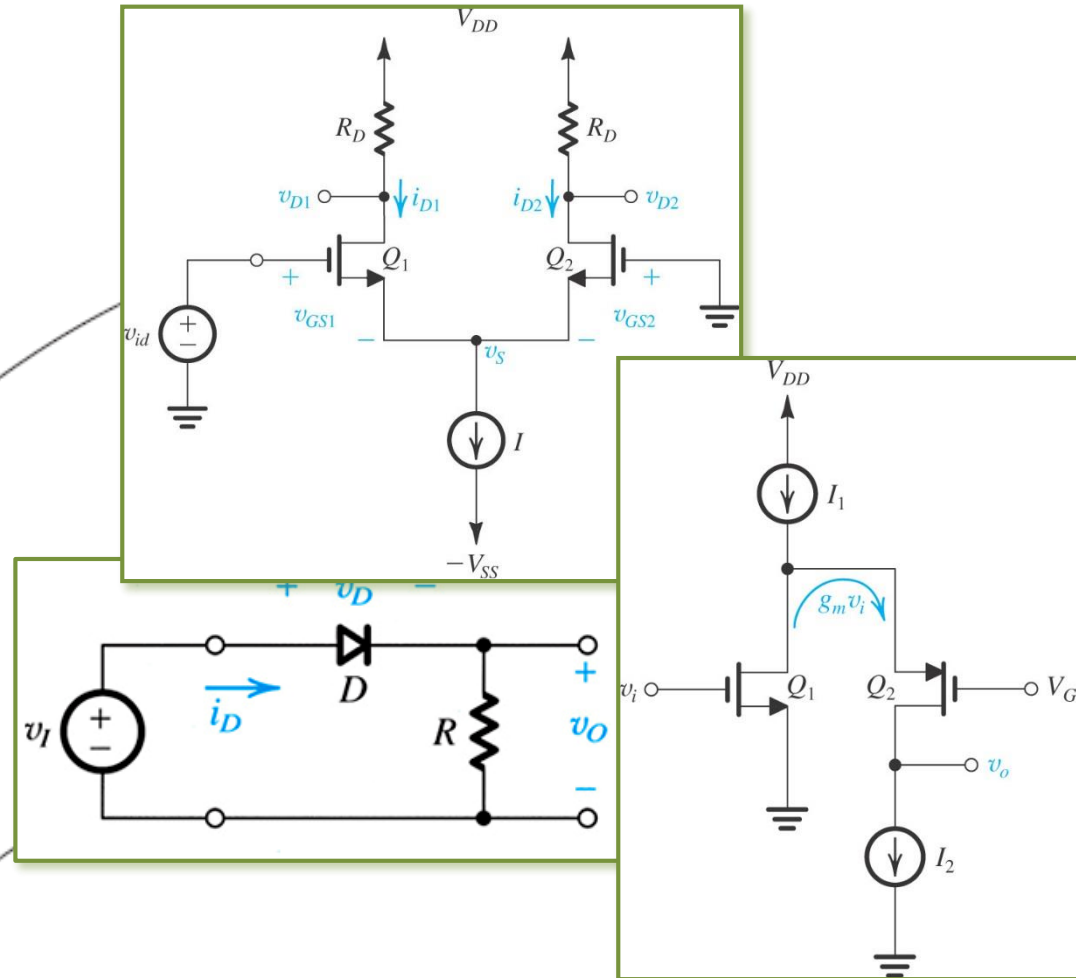This course teaches analysis techniques of basic electronic circuits with diodes and transistors.



SPECIFICATIONS




Electronic Systems → Chapter #1

- **Signal** - contains information
- **Transducer** – device which converts signal from non-electrical to electrical form
- **Process** – an operation which allow an observer to understand this information from a signal


*Process the electrical **signals** received from the **transducer** in some predetermine manner.*

Electrical Signal Representation

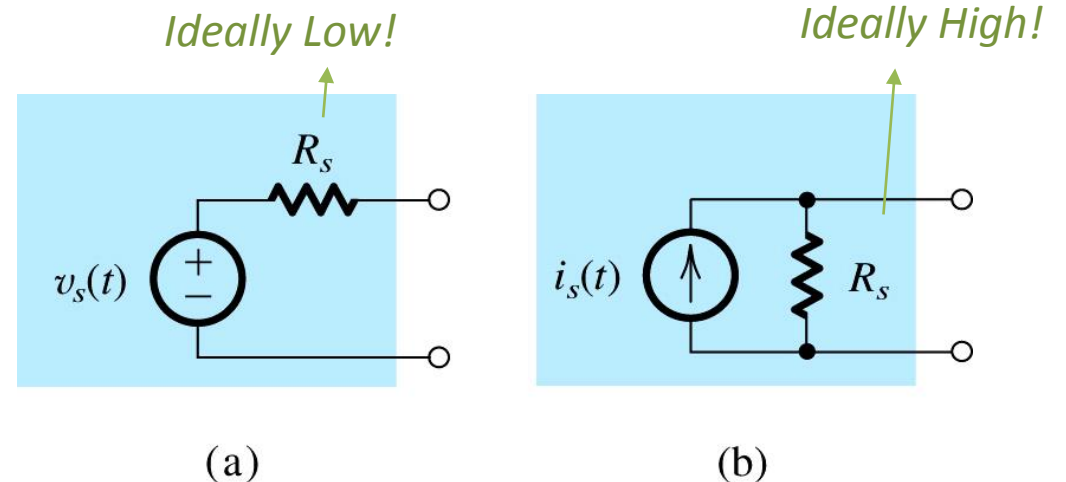
- Thevenin Form** – voltage source $v_s(t)$ with series resistance R_s
- Norton Form** – current source $i_s(t)$ with parallel resistance R_s



Basic Circuit Analysis → Example 1.1

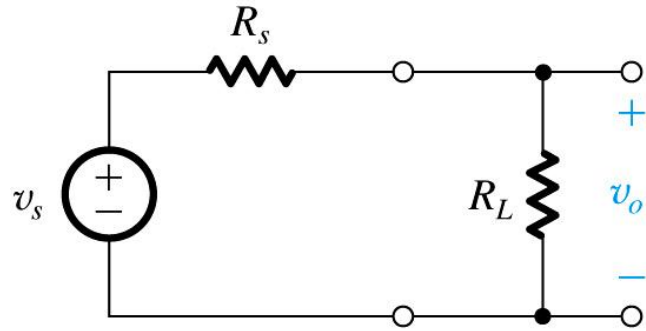

(a)


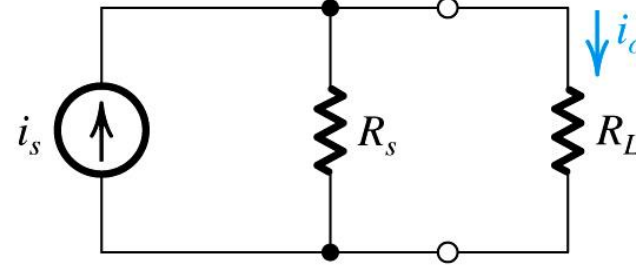


(b)

- How the output resistance of a source (R_s) **limits its ability to deliver a signal** at full strength?
- What is the relationship between the source and output when **maximum power** is delivered?

Concepts: *Power, Efficiency, Maxim Power Transfer*

Basic Circuit Analysis → Example 1.1

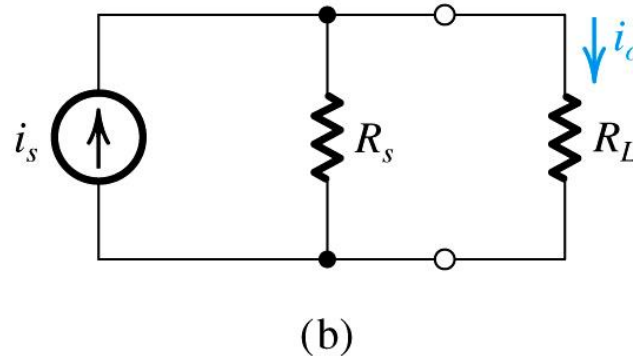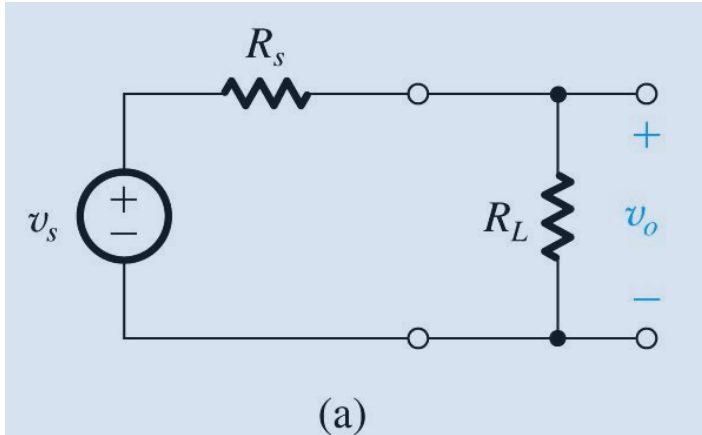

Application: maximum power transfer for solar cells

- Power** $P_L = V_o \cdot I_L = \frac{R_L}{(R_L + R_S)^2} V_s^2$

- Efficiency** $\eta = \frac{P_L}{P_{supply}} = \frac{R_L}{R_L + R_S}$

- Maximum Power**

$$\frac{\partial P_L}{\partial R_L} = 0 \quad @ R_L = R_S$$

