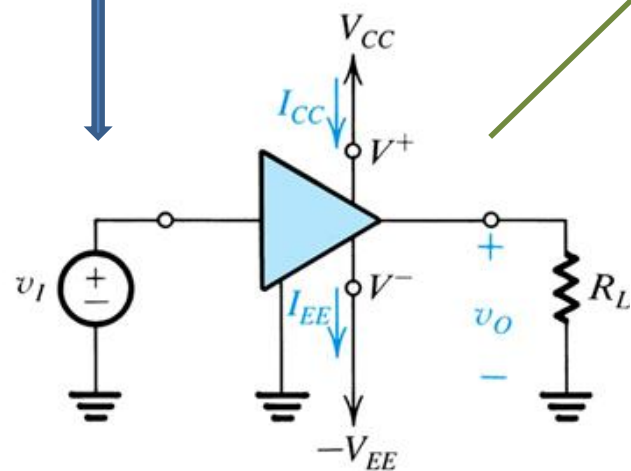


Last Lecture → Chapter 1.2-1.4

Concepts revisited...


- Frequency spectrum
- Fourier series
- Amplifier basics

- conservation of power
- efficiency
- model



Voltage Gain

$$V_{out}(t) = A_V \cdot V_{in}(t)$$

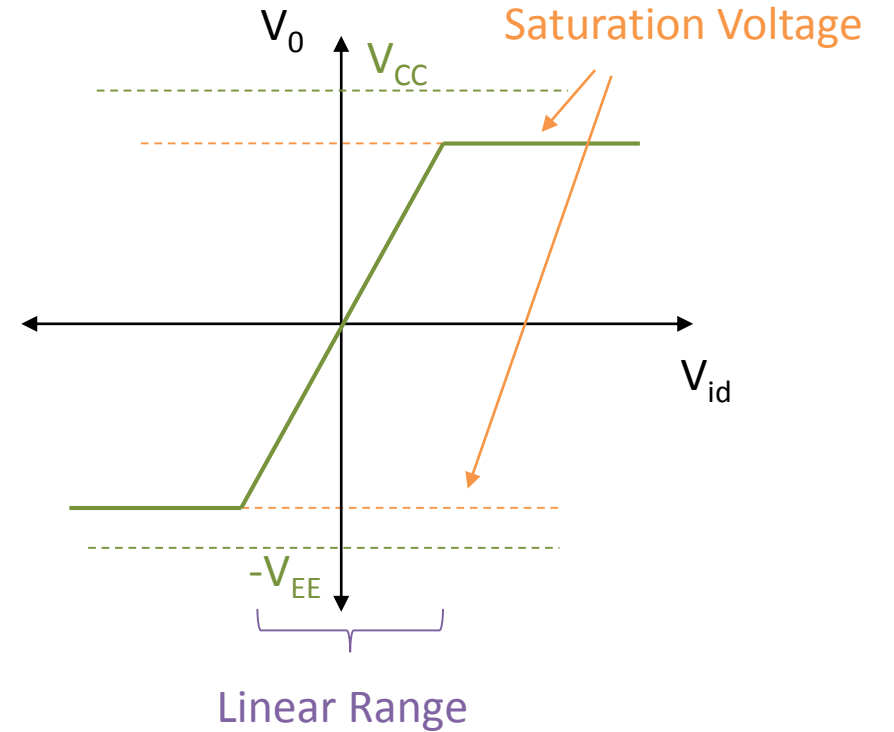

- Limited Linear Range
- Saturation Voltage
- Conservation of power
- Efficiency

$$P_{V_I} + P_{V_{CC}} + P_{V_{EE}} = P_L + P_{amp}$$

$$\eta = \frac{P_L}{P_{in}} = \frac{P_L}{P_{V_I} + P_{V_{CC}} + P_{V_{EE}}}$$

Amplifier Circuit Model → Chapter 1.5

... is the description of the amplifier's terminal behavior, neglecting internal operation / transistor design

model of amplifier input terminals


$$\text{input voltage} = v_i = \underbrace{(v_s)}_{\text{source volt.}} \underbrace{\frac{R_i}{R_i + R_s}}_{\text{source and input resistances}}$$

model of amplifier output terminals


$$\text{output voltage} = v_o = \underbrace{(A_{vo} v_i)}_{\text{open-ckt output voltage}} \underbrace{\frac{R_L}{R_L + R_o}}_{\text{output and load resistances}}$$

Voltage Gain
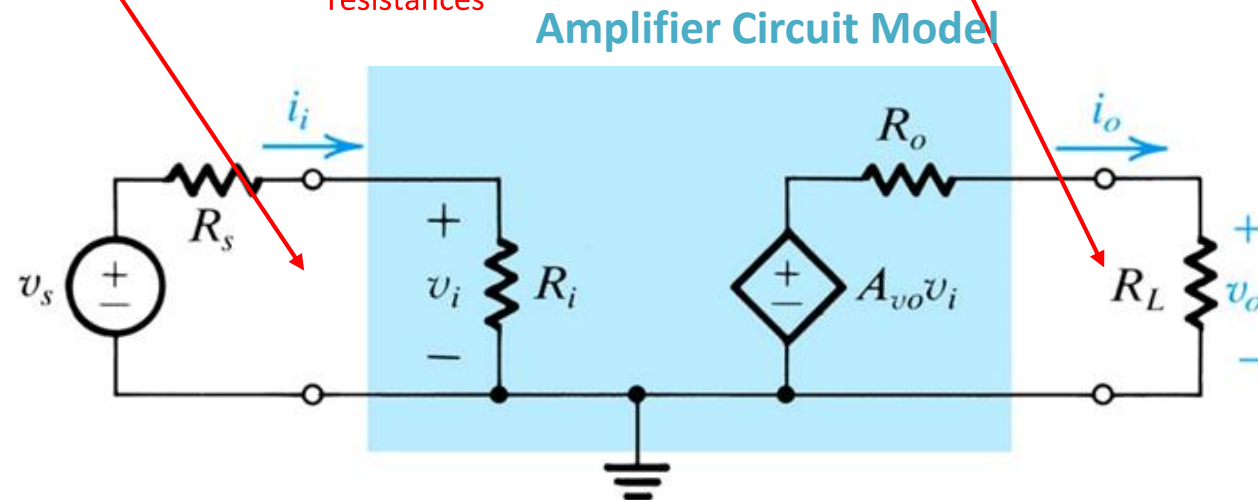
$$A_v = \frac{V_o}{V_s} = \underbrace{\left[\frac{V_i}{V_s} \right]}_{A_{v1}} \underbrace{\left[\frac{V_o}{V_i} \right]}_{A_{v2}}$$



Amplifier Circuit Model

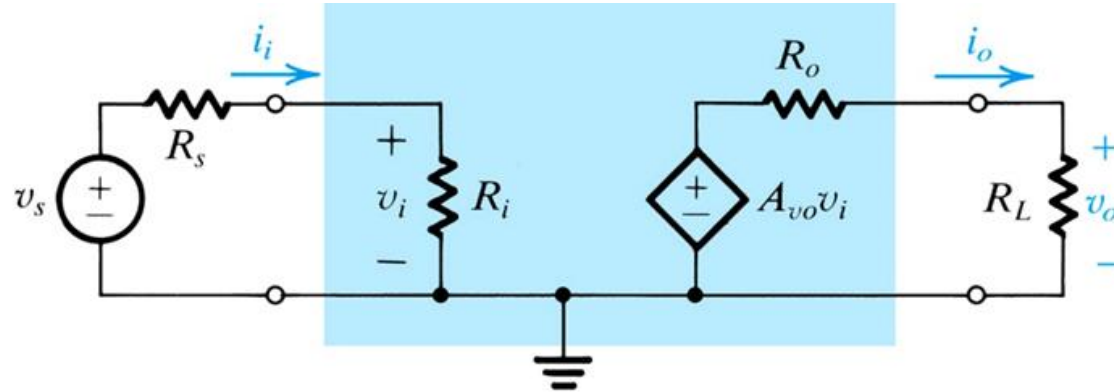

Ideal Assumptions...

- $R_i = \infty$ or $R_i \gg R_s$
- $R_o = 0$ or $R_o \ll R_L$



$$v_o = A_{vo} v_s \underbrace{\frac{R_i}{R_i + R_s} \frac{R_L}{R_L + R_o}}_{\text{non-ideal model}} = \underbrace{A_{vo} v_s}_{\text{ideal model}}$$

$$v_o = \underbrace{A_{vo} (v_s)}_{\text{source volt.}} \underbrace{\frac{R_i}{R_i + R_s}}_{\text{Attenuation: source and input resistances}} \underbrace{\frac{R_L}{R_L + R_o}}_{\text{Loading: output and load resistances}} = A_{vo} v_s \frac{R_i}{R_i + R_s} \frac{R_L}{R_L + R_o}$$

Gain is not constant, and dependent on input and load resistance!

Cascade Amplifiers

In real life, an amplifier is not ideal and will not have infinite input impedance or zero output impedance...

... cascading of amplifiers, however, may be used to emphasize desirable characteristics.




- **first amplifier** → high R_i , medium R_o
- **last amplifier** → medium R_i , low R_o
- **aggregate** → high R_i , low R_o




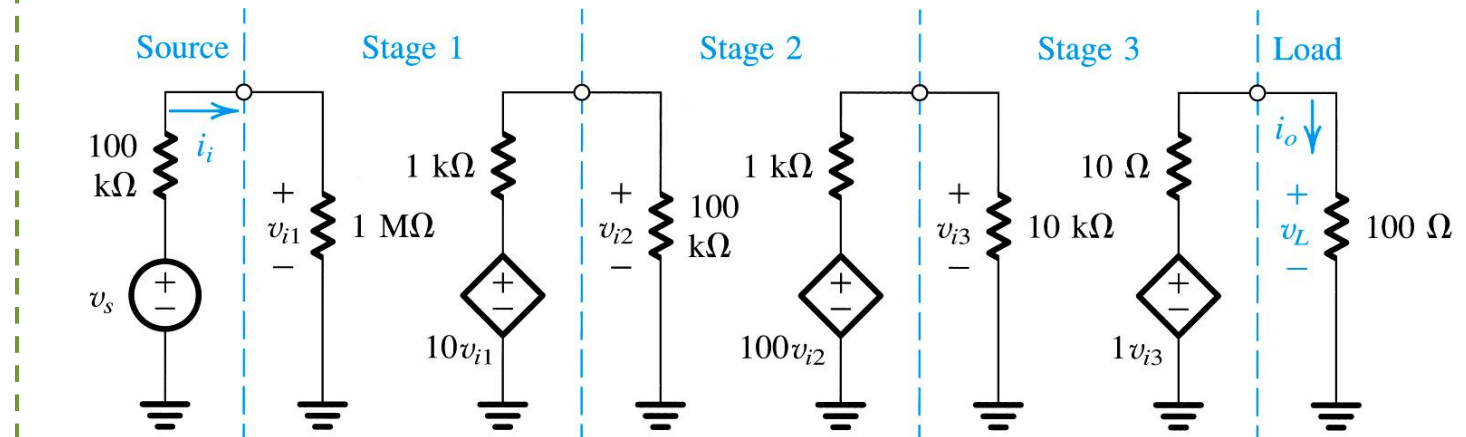
Example 1.3

Examine system of cascaded amplifiers....

- What is the overall voltage gain?
- What is the overall current gain?
- What is the overall power gain?



Different Types of Amplifiers

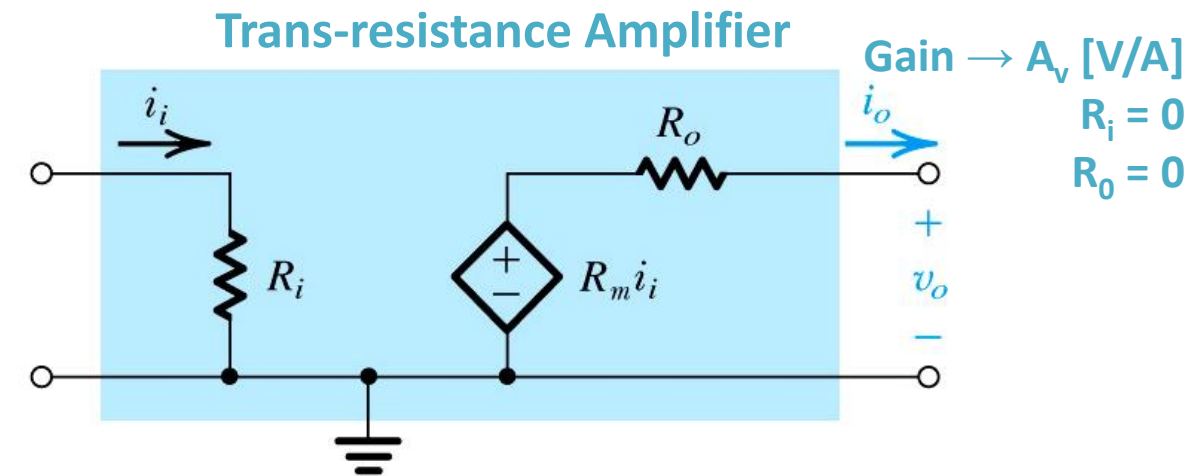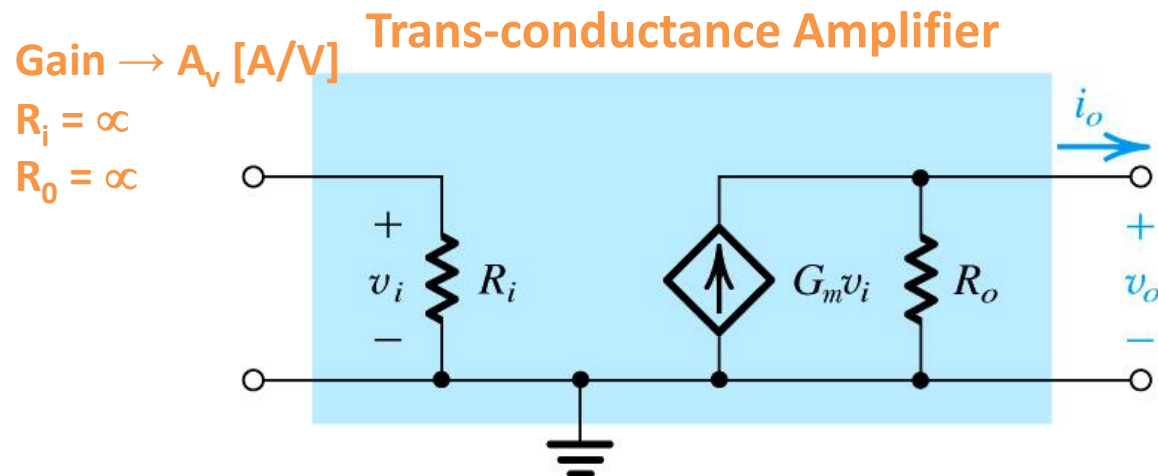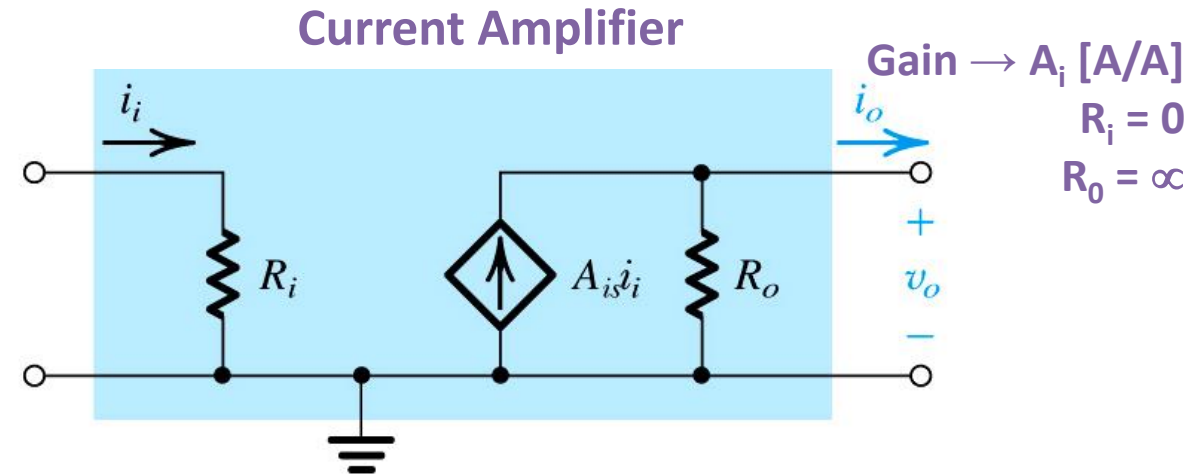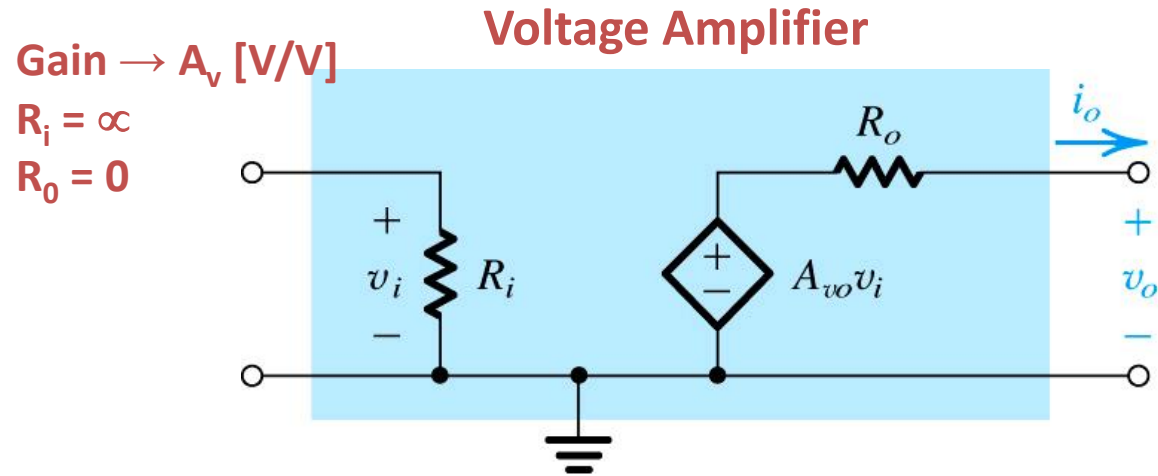

Problem D1.49

A designer has available voltage amplifiers with an input resistance of $10\text{k}\Omega$, an output resistance of $2\text{k}\Omega$, and an open-circuit voltage gain of 10V/V . The signal source has a $10\text{k}\Omega$ resistance and provides a $10\text{-mV}_{\text{rms}}$ signal, and it is required to provide a signal of at least 2V_{rms} to a $2\text{k}\Omega$ load. How many amplifier stages are required? What is the output voltage actually obtained?