


Last Lecture → Chapter 1.5

Concepts learned...

- **voltage amplifier circuit model**
 - ✓ ideal
 - ✓ non-ideal
- **circuit analysis**
- **other types of amplifiers models**
 - ✓ current amp.
 - ✓ trans-conductance amp.
 - ✓ trans-resistance amp.



Gain → A_v [V/V] $R_i = \infty$
 $R_o = 0$

Voltage Amplifier

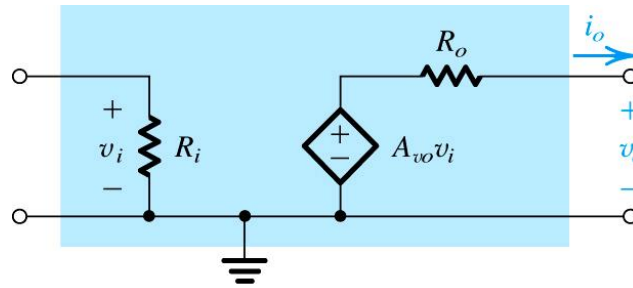


Gain → A_i [A/A] $R_i = 0$
 $R_o = \infty$

Current Amplifier

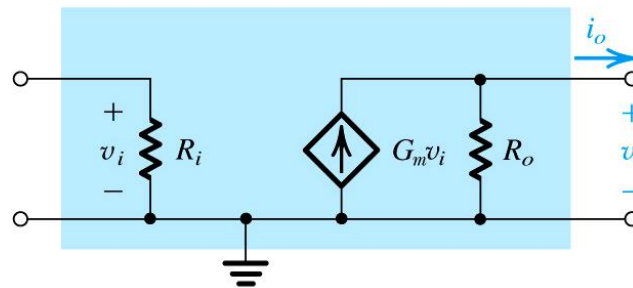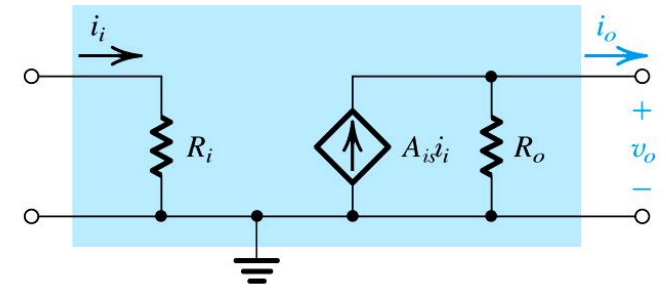

Trans-conductance Amplifier

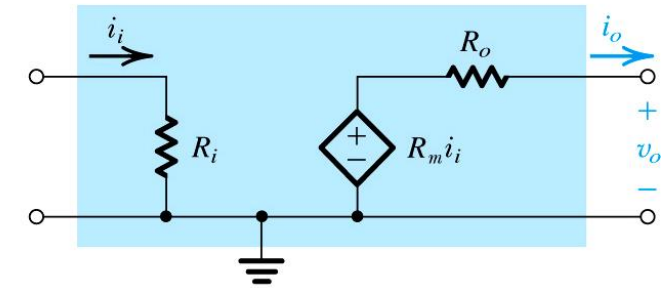Gain → G_m [A/V] $R_i = \infty$
 $R_o = \infty$



Trans-resistance Amplifier

Gain → R_m [V/A] $R_i = 0$
 $R_o = 0$

Last Lecture → Problem D1.49

A designer has available voltage amplifiers with an input resistance of $10\text{k}\Omega$, an output resistance of $2\text{k}\Omega$, and an open-circuit voltage gain of 10V/V . The signal source has a $10\text{k}\Omega$ resistance and provides a $10\text{-mV}_{\text{rms}}$ signal, and it is required to provide a signal of at least 2V_{rms} to a $2\text{k}\Omega$ load. How many amplifier stages are required? What is the output voltage actually obtained?


Input / Output Impedance of a Circuit

- How can one calculate input resistance from terminal behavior?

1. place a test source V_x at the input terminals
2. observe v_x and i_x
3. calculate via $R_{in} = v_x / i_x$


- How can one calculate output resistance from terminal behavior?

1. place a test source V_y at the output terminals
2. turn off the input source ($V_s=short!$, $I_s=open!$)
3. observe v_y and i_y
4. calculate via $R_{out} = v_y / i_y$

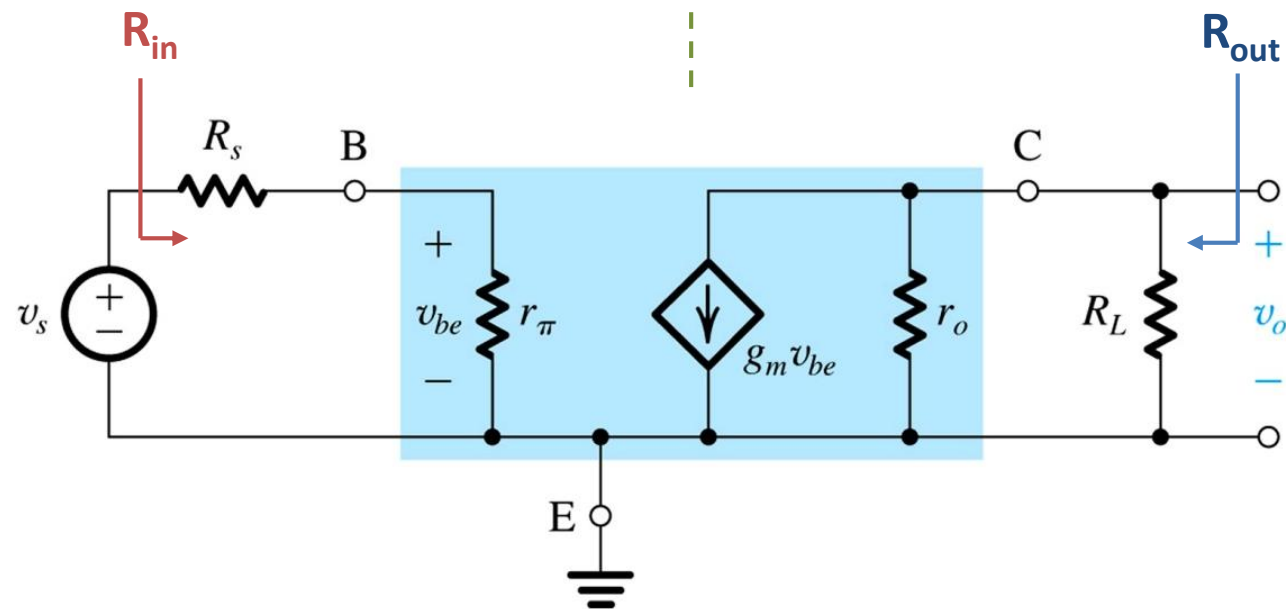

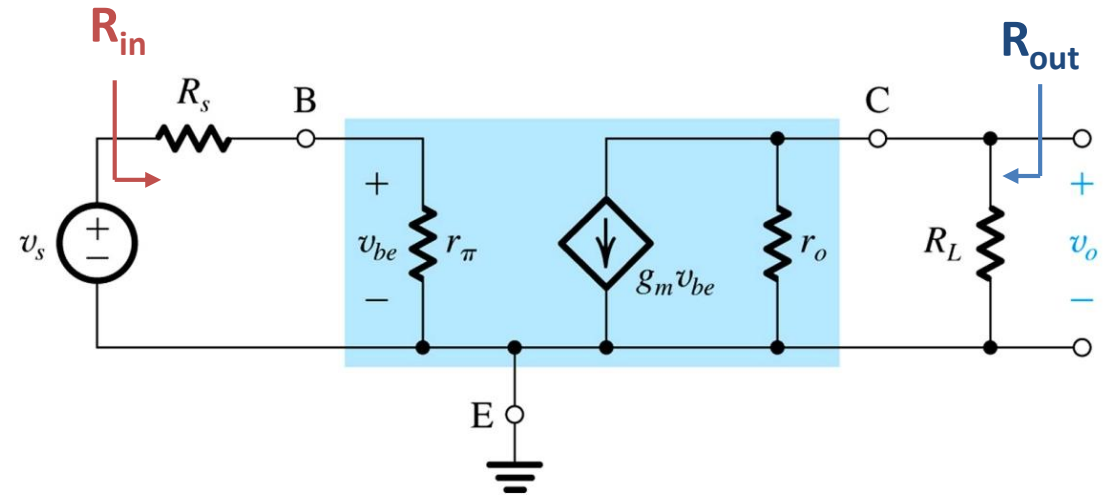Example 1.4

For the following circuit derive an expression for the voltage gain v_o/v_s , and evaluate its magnitude for the case $R_s=5\text{k}\Omega$, $r_\pi=2.5\text{k}\Omega$, $g_m=40\text{mA/V}$, $r_o=100\text{k}\Omega$, and $R_L=5\text{k}\Omega$. What would be the gain value if the effect of r_o were neglected? Calculate the value for the impedance seen by the source and at the output terminals.



$$A_v = \frac{v_o}{v_s} = \left[\frac{v_o}{v_{be}} \right] \left[\frac{v_{be}}{v_s} \right] = \left[\frac{r_\pi}{r_\pi + R_s} \right] [g_m r_o \parallel R_L] = [0.33][190] = 63 \text{ V/V}$$

$$\text{for } r_o = 0 \quad \rightarrow A_v = [0.33][200] = 66 \text{ V/V}$$


$$R_{in} = \frac{V_X}{I_x} = R_s + r_\pi = 7.5 \text{ k}\Omega$$

$$R_{out} = \frac{V_y}{I_y} = r_o \parallel R_L = 4.76 \text{ k}\Omega$$

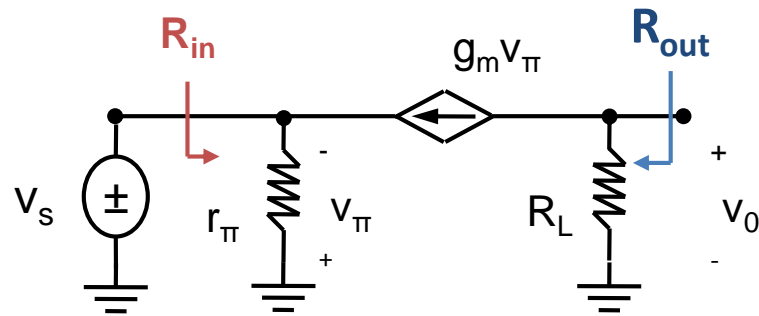Problem

For the circuit provided below find the expression for the

- Voltage gain V_0/V_s
- Output resistance R_{out} (assume the source exhibits a series resistance R_s not shown)
- Input resistance R_{in}



$$A_v = \frac{V_0}{V_s} = g_m R_L$$

$$R_{out} = \frac{V_y}{I_y} = R_L$$

$$R_{in} = \frac{V_X}{I_x} = \frac{1}{g_m} \left[\frac{1}{1 + \frac{1}{g_m r_\pi}} \right]$$

$$\text{for } g_m r_\pi \gg 1 \rightarrow R_{in} = \frac{V_X}{I_x} = \frac{1}{g_m}$$