

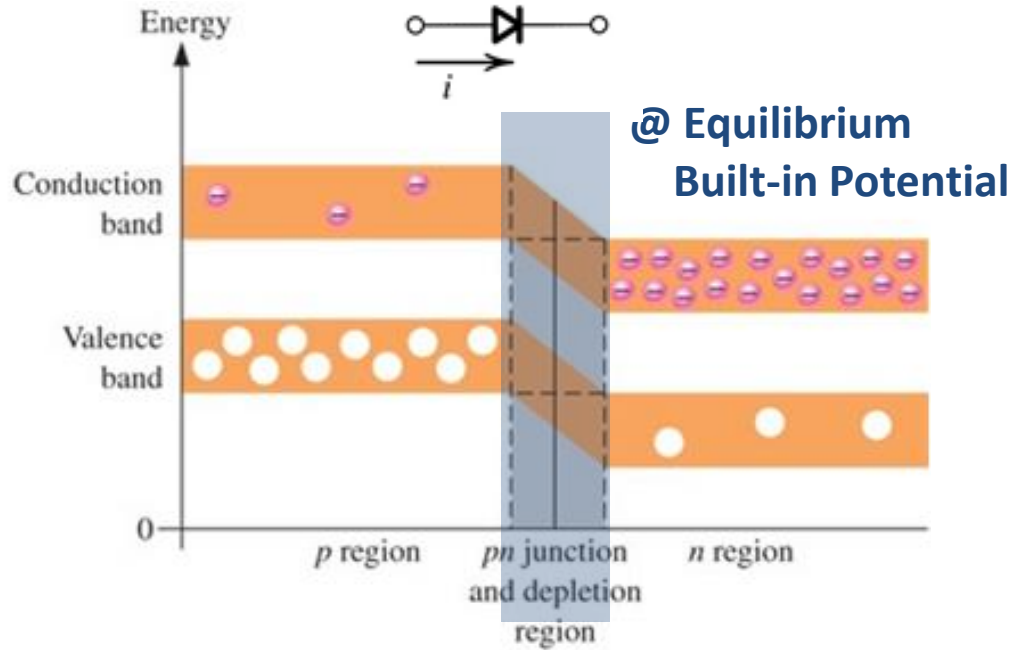
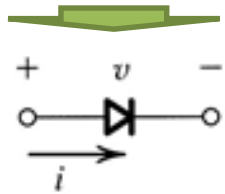



Last Lecture → PN Junction

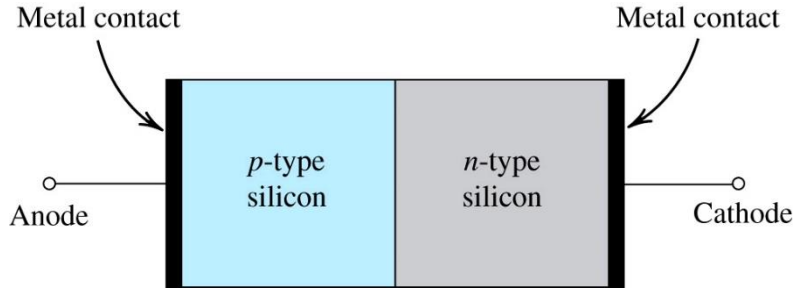



- *Reversed Biased* → $V_d < 0$

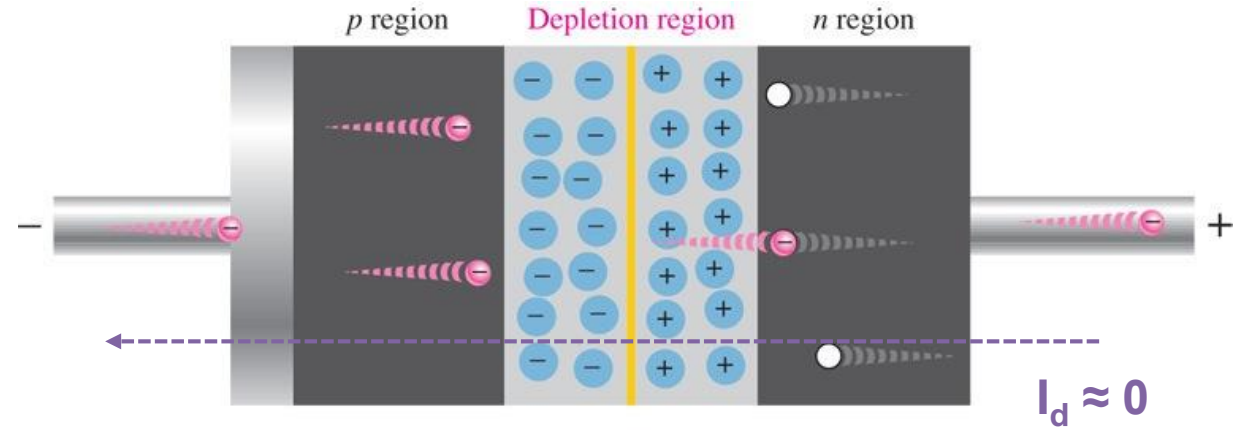

- *Forward Biased* → $V_d > V_0$

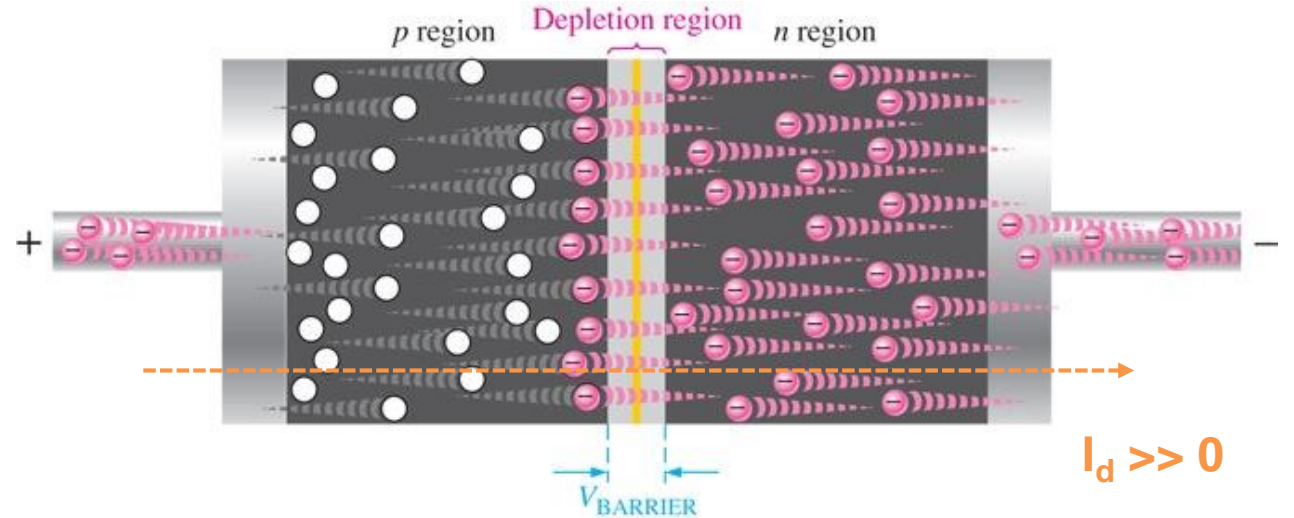


Terminal Characteristics of Diodes

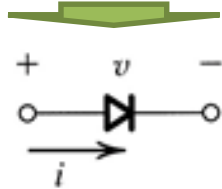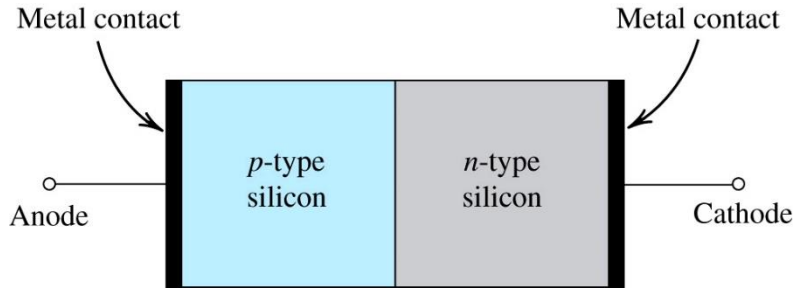

Characteristic Regions

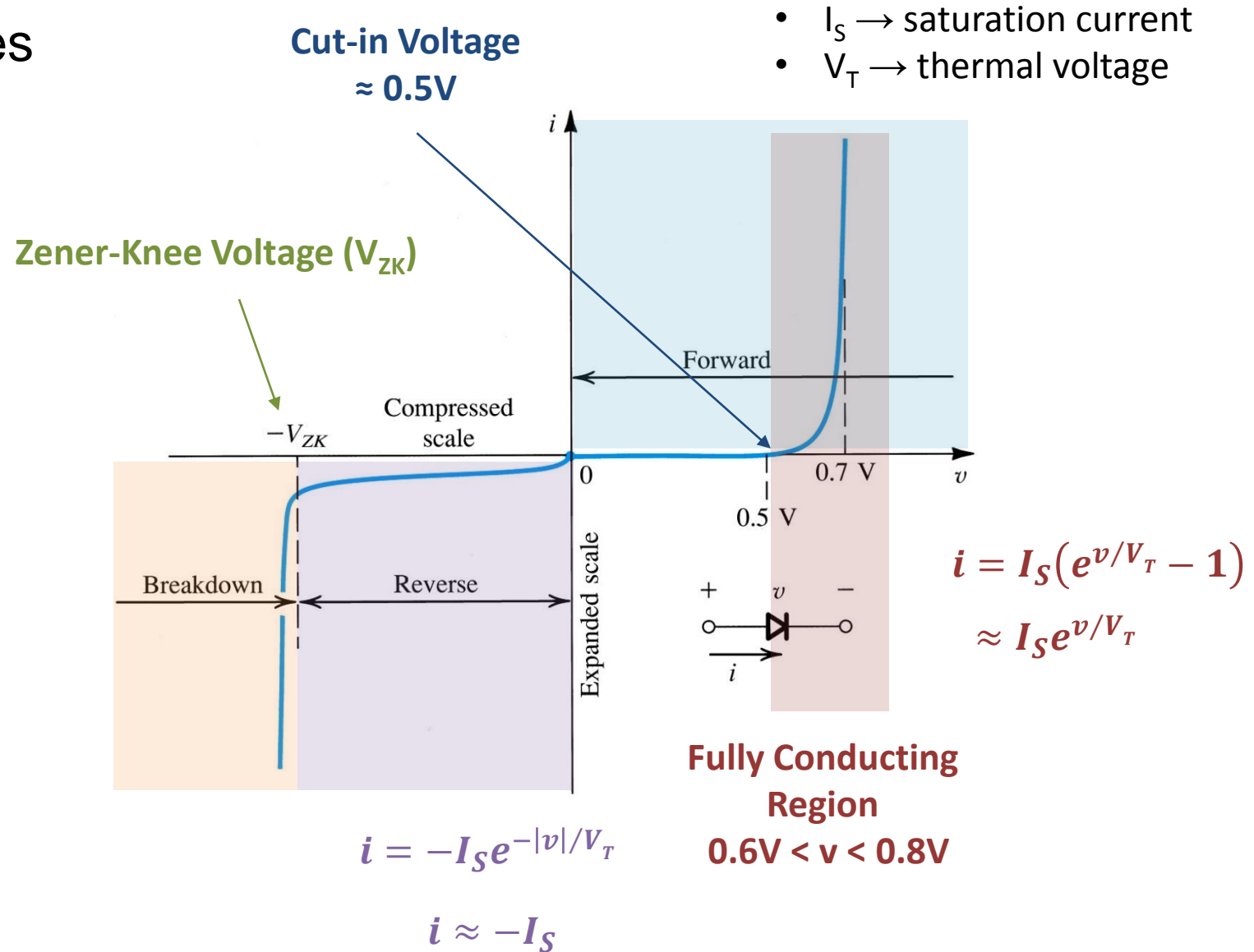
- **Forward Bias:** $v > 0$
- **Reverse Bias:** $v < 0$
- **Breakdown:** $v \ll 0$



Diode Models

- | | |
|----------------|-------------------------------|
| DC
Analysis | • Ideal Model |
| | • Constant-Voltage-Drop Model |
| | • Exponential Model |
| | ▪ Graphical Analysis |
| | ▪ Numerical Analysis |
| AC
Analysis | • Small Signal Model |

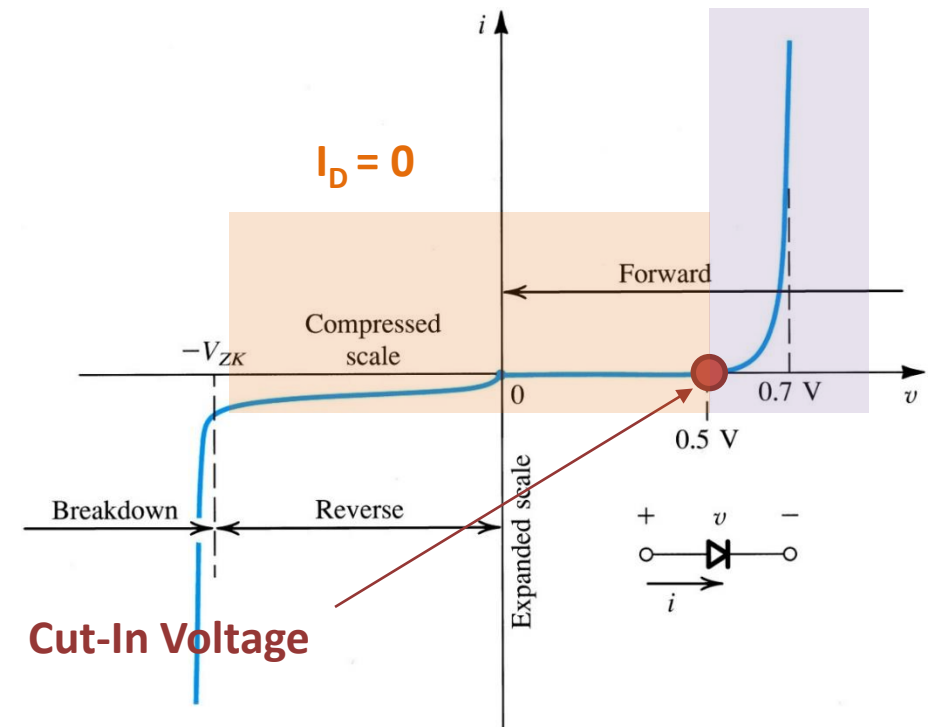Your simulation results are as good as your model!!!!




Exponential Model

$$\text{for } v < 0.5 \rightarrow I_D \approx 0$$

$$\text{for } v > 0.5 \rightarrow I_D \approx I_S e^{v_D/V_T}$$

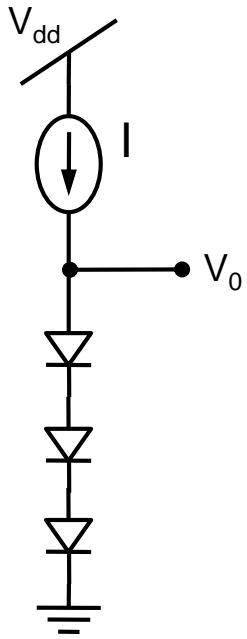Problem 4.23



The circuit provided below utilizes three identical diodes having $I_s = 10^{-16}\text{A}$. Find the value of the current I required to obtain an output voltage $V_o = 2.4\text{V}$. If a current of 1mA is drawn away from the output terminal by a load, what is the change in the output voltage.




Diode Models

- DC Analysis
 - Ideal Model
 - Constant-Voltage-Drop Model
 - Exponential Model
 - Graphical Analysis
 - Numerical Analysis
- AC Analysis
 - Small Signal Model

I_D is not a function of V_D

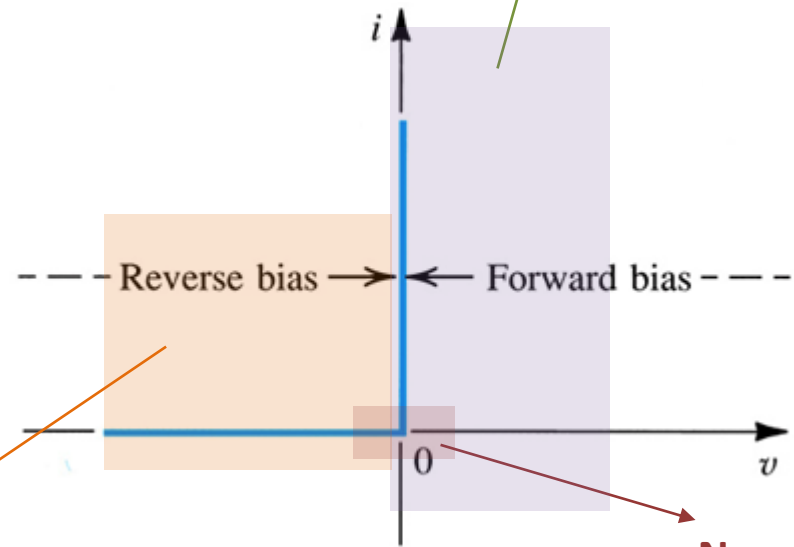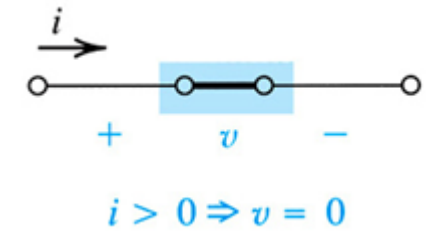

No reverse current

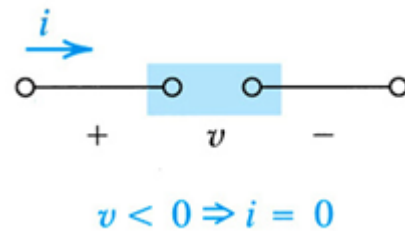

No voltage drop when conducting current

Ideal Model


for $v < 0 \rightarrow I_D = 0$

for $I_D > 0 \rightarrow v = 0$


Solving Circuits with Diodes

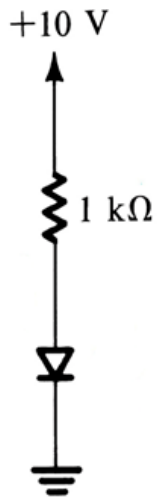1. Choose a model for the diode
2. Make an educated guess of the region of operation of the diode
3. Solve the circuit via mesh / nodal analysis
4. Verify if the condition of the region of operation are satisfied!

For the given circuits, determine the current flowing through the resistor.




(a)

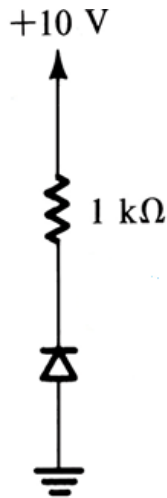

(b)

Assuming the diodes to be ideal, find the values of I and V in the given circuits ...



Example 4.2

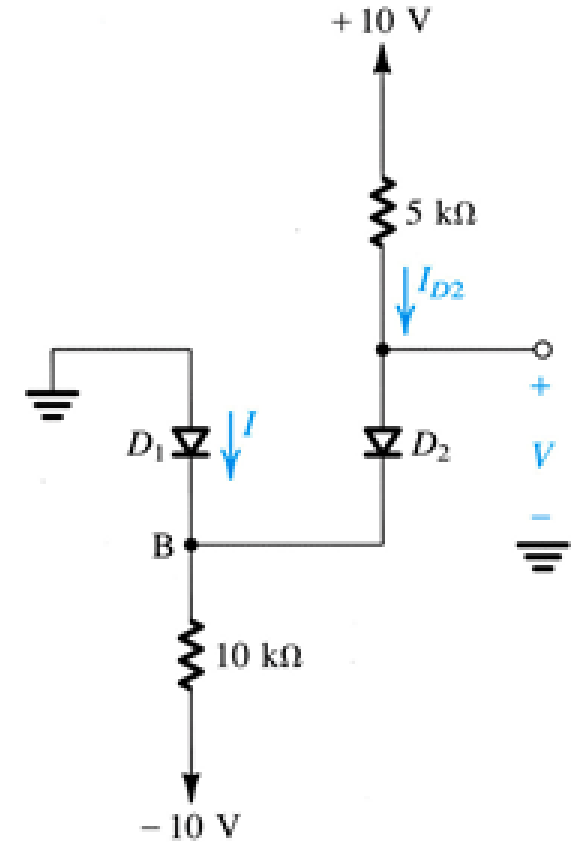

(b)



Diode Logic Gates

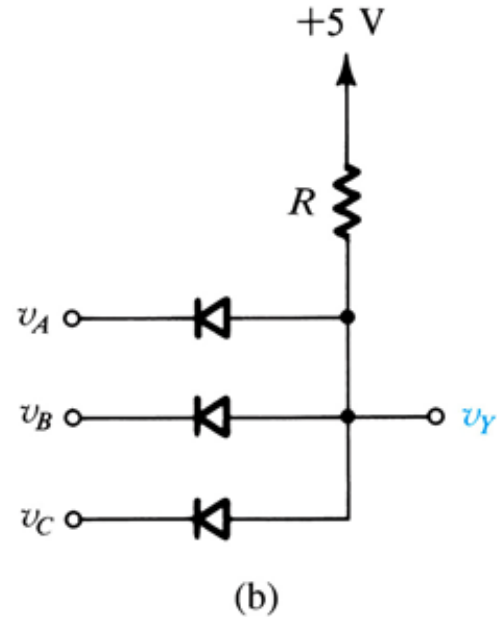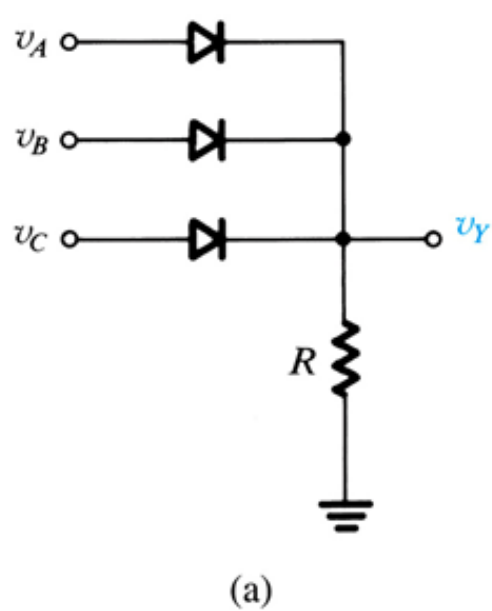Diodes together with resistors can be used to implement logic functions...



A Simple Application

→ The Rectifier

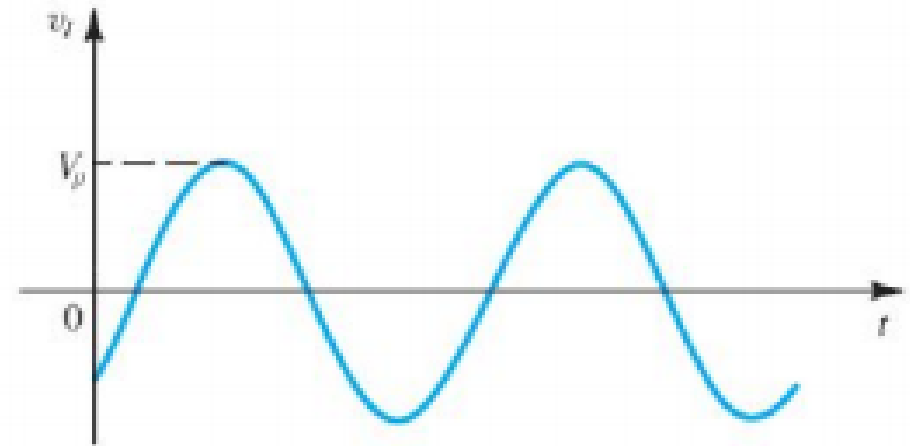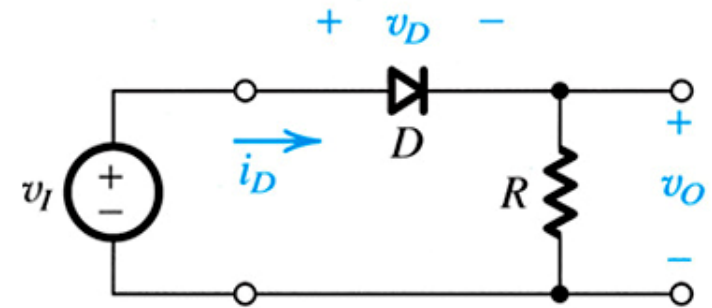

Example 4.1

For the following circuit, assuming v_s is a sinusoid with 24-V peak amplitude find

- the fraction of each cycle during which the diode conducts
- the peak value of the diode current
- The maximum reverse-bias voltage that appears across the diode

