
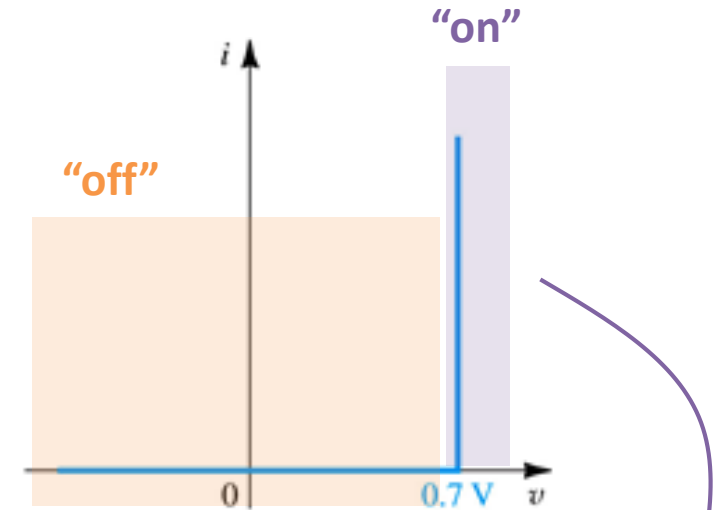

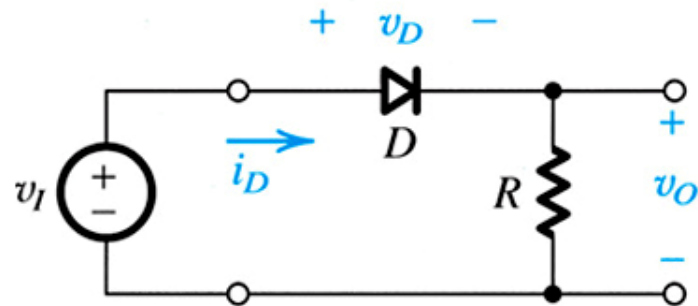
# Last Lecture → Constant-Voltage Drop Model

- DC Analysis
- ✓ Ideal Model
  - ✓ Constant-Voltage-Drop Model
  - ✓ Exponential Model
  - ✓ Graphical Analysis
  - ✓ Numerical Analysis




## Diode Application → Rectifier Circuit



### Problem Solving

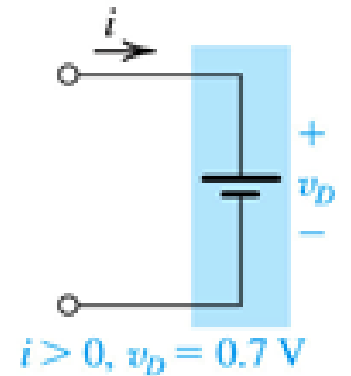
- 1) verify appropriate current direction as a function of the time varying source
- 2) Assume status of diode according the current direction

- If diode is "on"
  - $v_d = 0.7V$
  - ∴  $i_d > 0$
- If diode is "off"
  - $i_d = 0V$
  - ∴  $v_d < 0.7V$



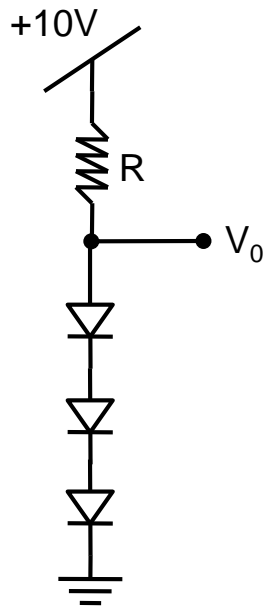
## Problem D 4.11

Design the given circuit to provide an output voltage of 2.4V. Assume that the diodes available have 0.7V drop at 1mA.



# Small-Signal Model

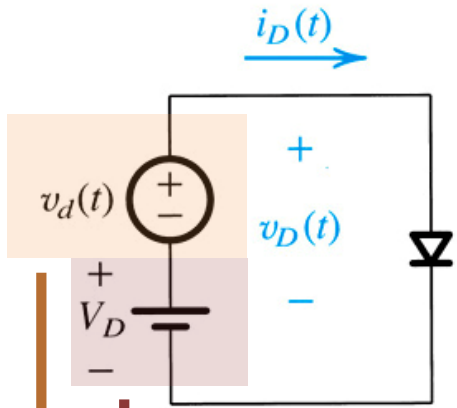

$$i_D = I_S e^{v_D/V_T}$$


$$\begin{aligned} i_D(t) &= I_S e^{v_D(t)/V_T} \\ &= I_S e^{(V_D + v_d(t))/V_T} \\ &= I_{bias} e^{v_d(t)/V_T} \end{aligned}$$

$$i_D(t) \approx I_{bias} + \frac{I_{bias}}{V_T} v_d(t)$$

DC Signal → establishes the bias point


AC Signal → small changes at the bias point
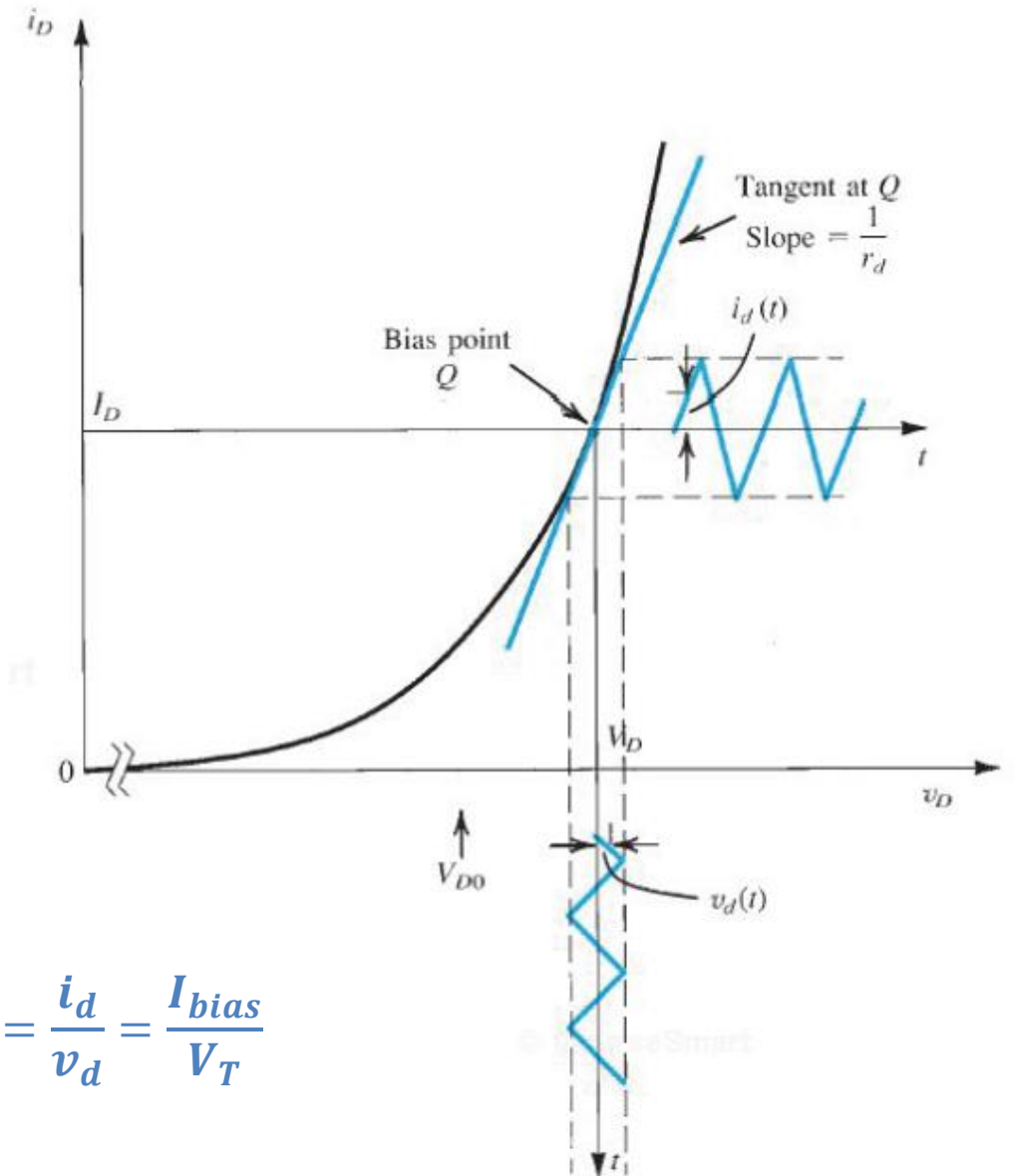
$$\frac{1}{r_d} = \frac{\Delta i_D}{\Delta v_D} = \frac{i_d}{v_d} = \frac{I_{bias}}{V_T}$$



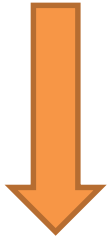
## Small-Signal Model

- Diode  $y$  modeled as a variable resistor
- Its value is defined via linearization of exponential model
- Around bias point defined by constant voltage drop model




The total instantaneous circuit is divided into steady-state and time varying components, which may be analyzed separately and solved via algebra.

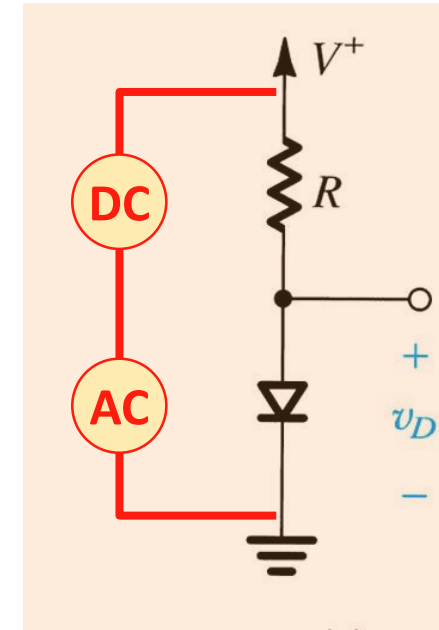
- 1) In steady-state, diode represented as CVDM.
- 2) In time-varying, diode represented as resistor.



(a)

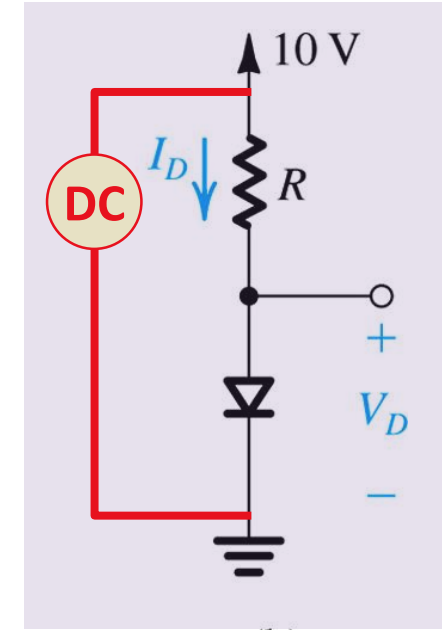

(b)

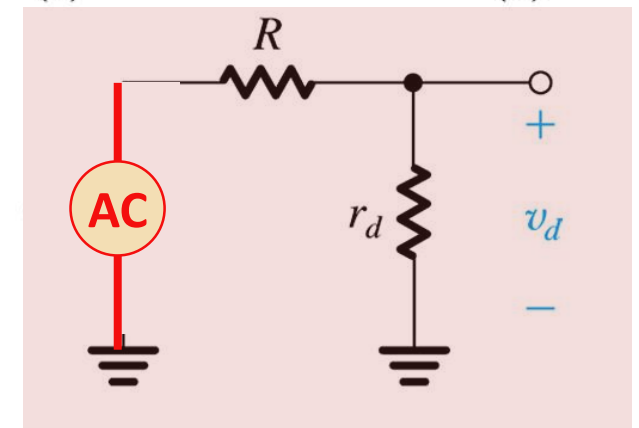

(c)


## Problem D 4.56

A particular design of a voltage regulator is shown below. Diodes  $D_1$  and  $D_2$  are 10-mA units; that is, each has a voltage drop of 0.7V at a current of 10mA. Use the diode exponential model and iterative analysis to answer the following questions:

- What is the regulator output voltage  $V_0$  with the  $150\Omega$  load connected?
- With the load connected, to what value can the 5V supply be lowered while maintaining the loaded output voltage within 0.1V / 0.01V / 0.001V of its nominal value?


**\*\* for part b) use both the large signal model (exponential) and the small signal**

$\Delta V_0$	large signal model	small signal model
0.1V		
0.01V		
0.001V		

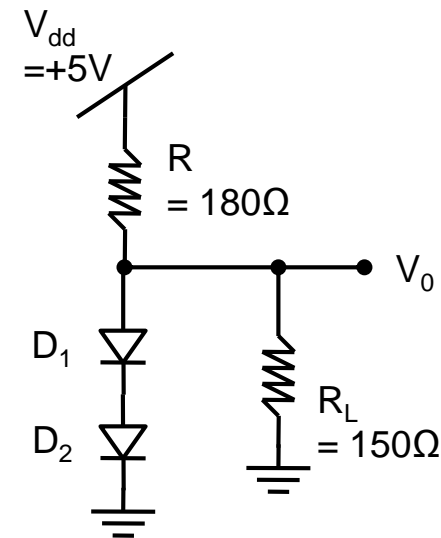
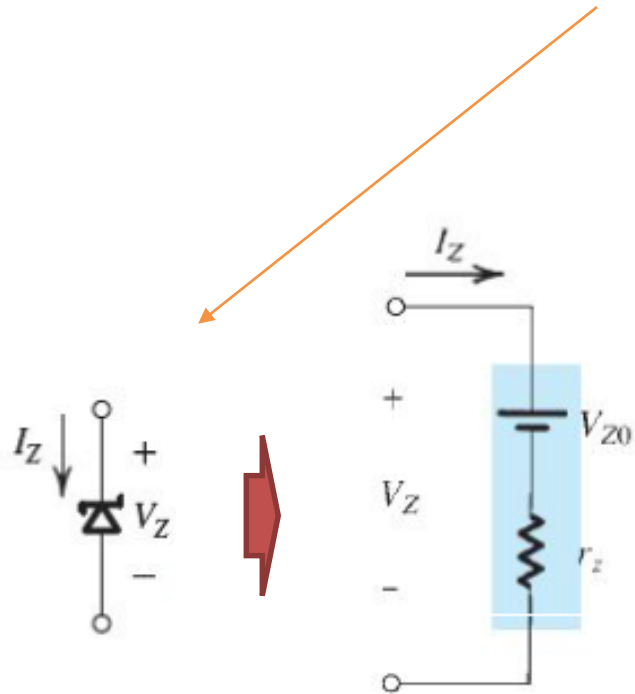
# Zener Diodes → Chapter 4.4

- Under certain circumstances, diodes may be intentionally used in the reverse breakdown region.
- These are referred to as **Zener Diodes**.



Zener-Knee Voltage ( $V_{ZK}$ )

$$V_Z = V_Z + r_z \cdot I_Z$$

\*\*\* for  $V_Z > V_{Z0}$   
 $I_Z > I_{ZK}$

