


Bate → Examen #1

Todo estudiante podrá traer su propio bate al examen. No obstante, dicho bate deberá circunscribirse a las siguientes características y normas establecidas:

1. Una hoja tamaño carta por ambos lados
2. Solo formulas
3. No se permiten:
 - problemas resueltos
 - esquemáticos
 - explicaciones
 - procedimientos
4. Deberá ser entregado junto a su examen

***** La falta de cumplimiento de dichas normas resultara en un reducción de la nota obtenida en proporción a dicha falta.**

Last Lecture → Small Signal Model

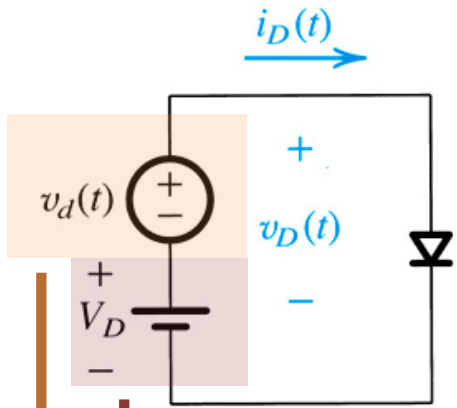


$$i_D = I_S e^{v_D/V_T}$$

$$\begin{aligned} i_D(t) &= I_S e^{v_D(t)/V_T} \\ &= I_S e^{(V_D + v_d(t))/V_T} \\ &= I_{bias} e^{v_d(t)/V_T} \end{aligned}$$

$$i_D(t) \approx I_{bias} + \frac{I_{bias}}{V_T} v_d(t)$$


$$\frac{1}{r_d} = \frac{\Delta i_D}{\Delta v_D} = \frac{i_d}{v_d} = \frac{I_{bias}}{V_T}$$

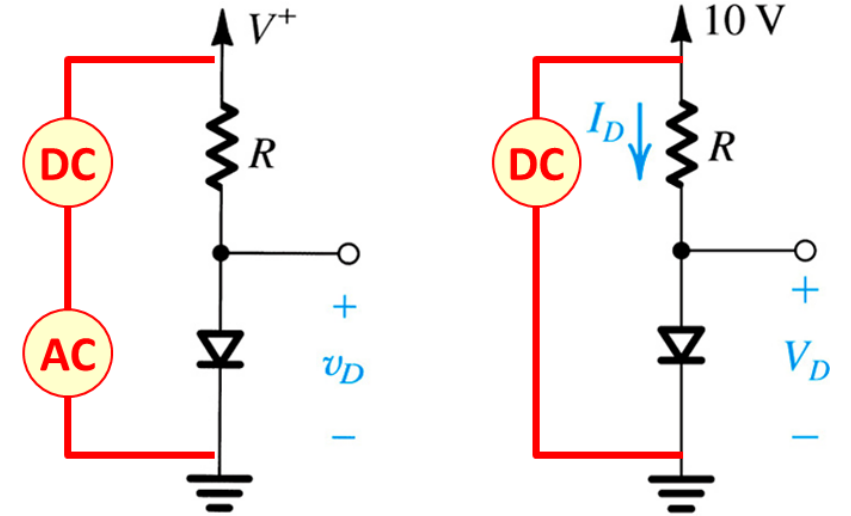DC Signal → establishes the bias point
 AC Signal → small changes at the bias point



(a)


(b)

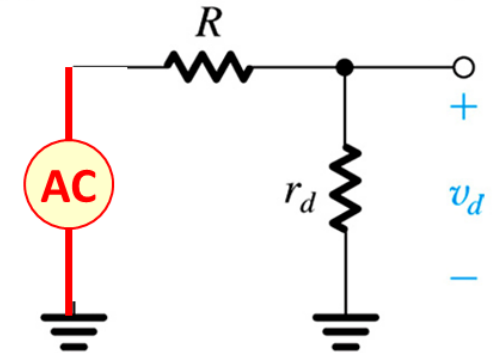

(c)

Zener Diodes → Chapter 4.4

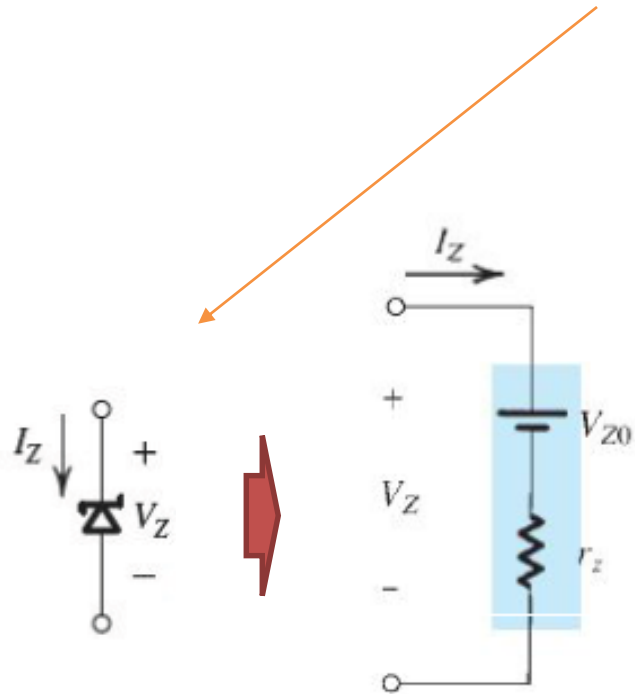
- Under certain circumstances, diodes may be intentionally used in the reverse breakdown region.
- These are referred to as **Zener Diodes**.



Zener-Knee Voltage (V_{ZK})

$$V_Z = V_Z + r_z \cdot I_Z$$

*** for $V_Z > V_{Z0}$
 $I_Z > I_{ZK}$

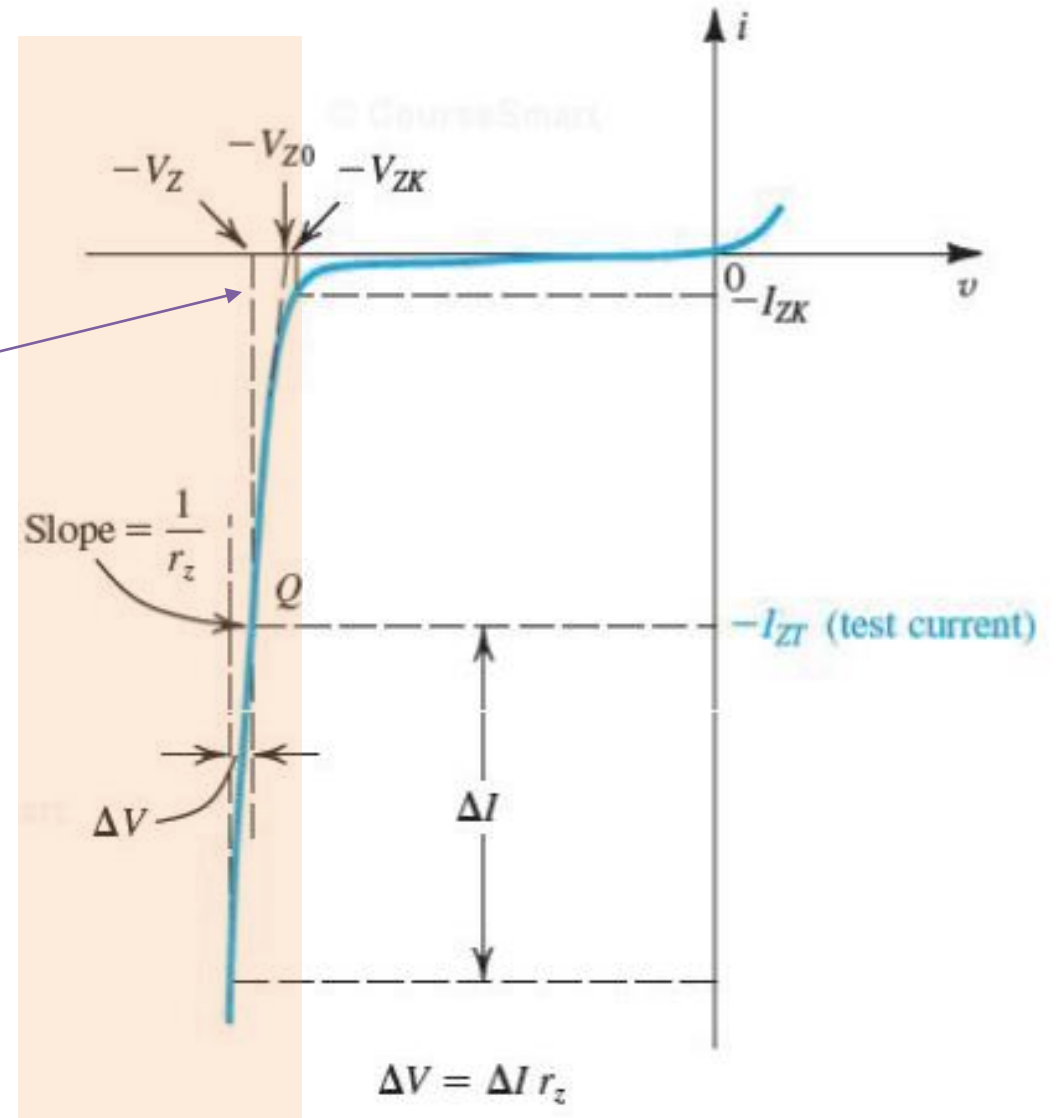


Exercise 4.17

A zener diode exhibit a constant voltage of 5.6V for current greater than five times the knee current. I_{ZK} is specified to be 1mA. The zener is to be used in the design of a shunt regulator fed from a 15-V supply. The load current varies over the range of 0mA to 15mA. Find a suitable value for the resistor R. What is the maximum power dissipation of the zener diode?


Rectifier Circuits → Chapter 4.5

DC Power Supply

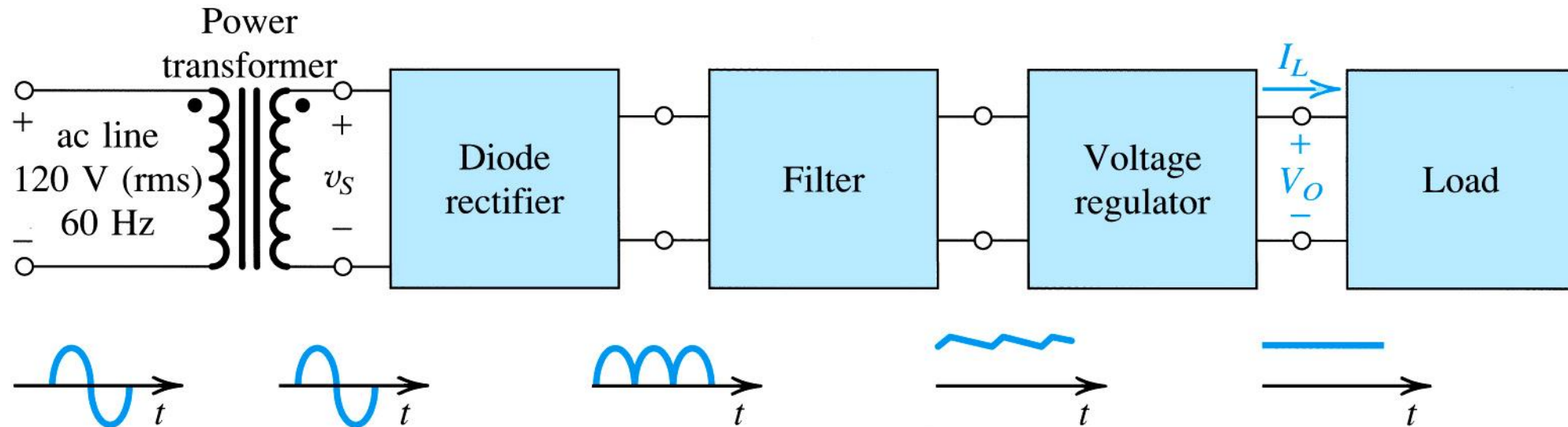
- **Power Transformer** – lowers down the 120V-AC input voltage and provides electrical isolation
- **Diode rectifiers** – converts the AC signal to an unipolar output
- **Filter** – reduces the voltage fluctuations of the rectified signal
- **Voltage Regulator** - reduces the ripple and stabilizes the output voltage from variations caused by changes in the load current




The Half-Wave Rectifier

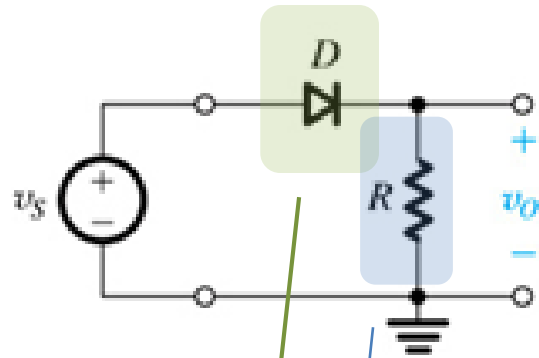

DC Response

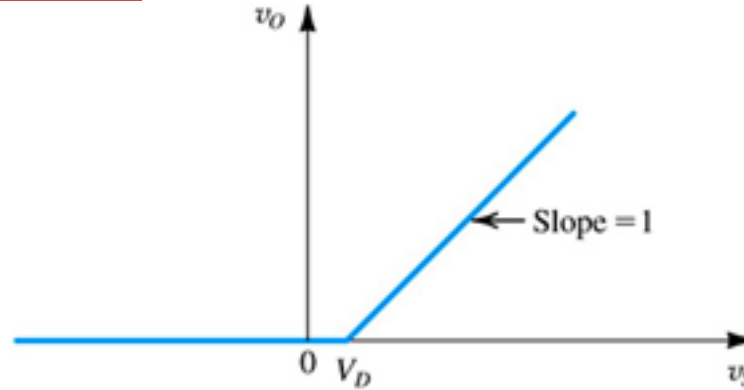

Transient Response

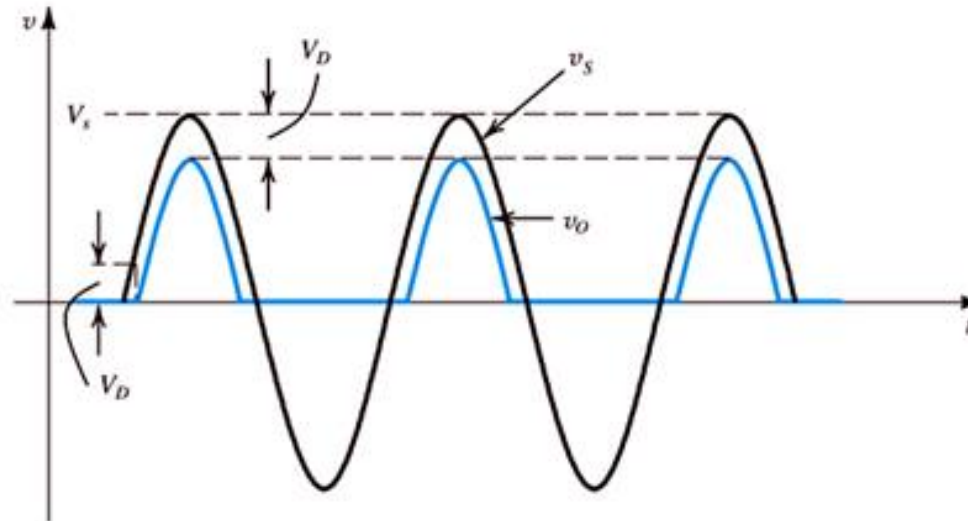

Diode Parameter Specifications:

- Current-handling capability – $I_{D(max)}$
- Peak inverse voltage – $PIV = V_{D(reverse(max))}$

Output Specifications:

- Average Voltage – $V_{O(avg)}$
- Average Current – $I_{L(avg)}$

Diode Ratings

$$I_{max} = \frac{V_S - V_D}{R}$$

$$PIV = V_S$$

Conduction Angle

$$\theta = \sin^{-1} \left(\frac{V_D}{V_S} \right)$$


$$\Delta\theta = \pi - 2\theta$$

Average Output


$$\bar{V}_O \approx \frac{V_S}{\pi} - \frac{V_D}{2}$$

$$\bar{I}_L \approx \frac{\bar{V}_O}{R}$$


The Full-Wave Rectifier

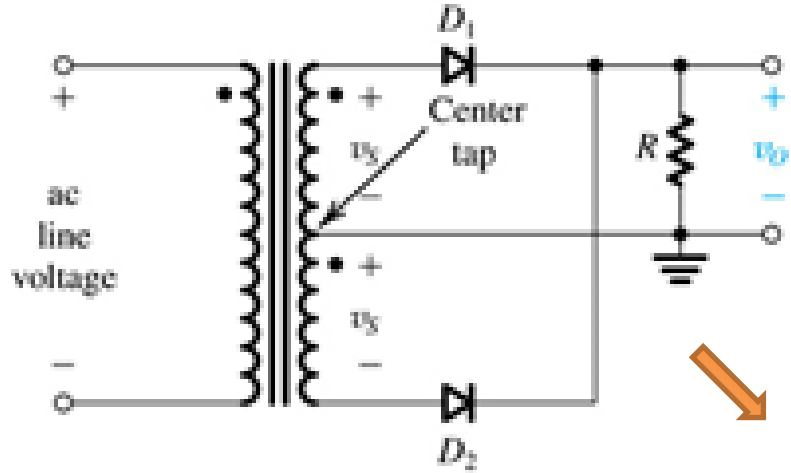

DC Response

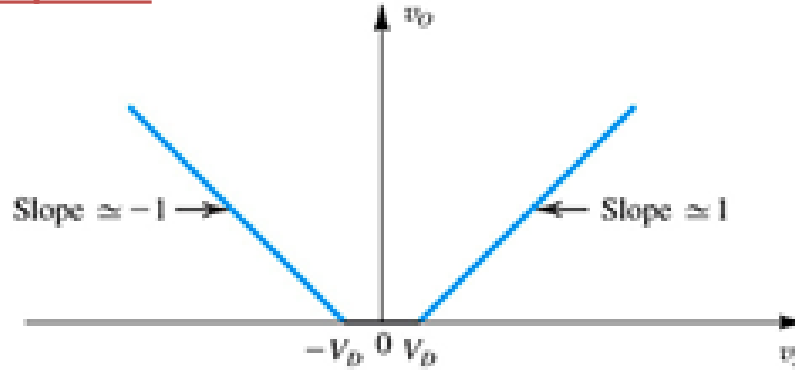

Transient Response

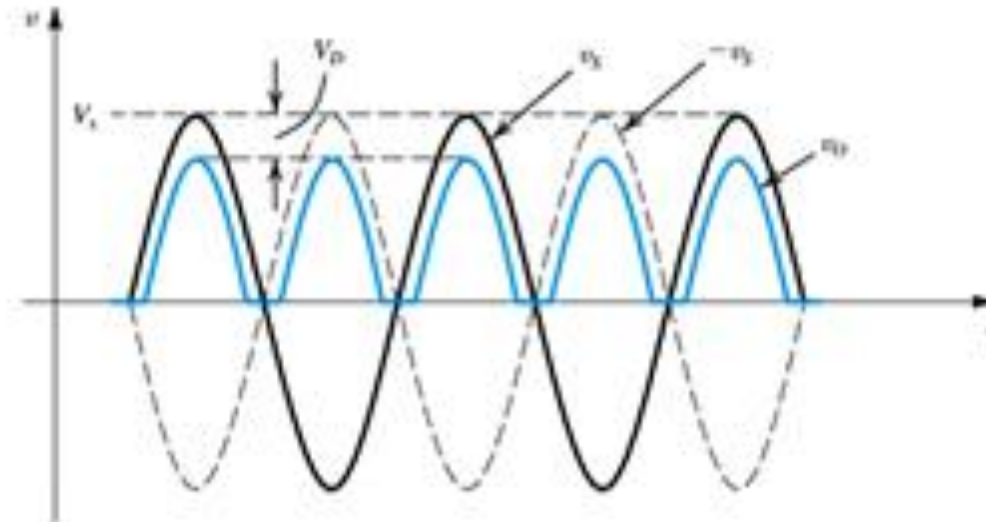

Diode Parameter Specifications:

- **Current-handling capability** – $I_{D(max)}$
- **Peak inverse voltage** – PIV

Output Specifications:

- **Average Voltage** – $V_{O(avg)}$
- **Average Current** – $I_{L(avg)}$

Diode Ratings

$$I_{max} = \frac{V_S - V_D}{R}$$

$$PIV = 2V_S - V_D$$

Conduction Angle

$$\theta = \sin^{-1} \left(\frac{V_D}{V_S} \right)$$


$$\Delta\theta = \pi - 2\theta$$

Average Output


$$\bar{V}_0 \approx \frac{2V_S}{\pi} - V_D$$

$$\bar{I}_L \approx \frac{\bar{V}_0}{R}$$

The Bridge Rectifier

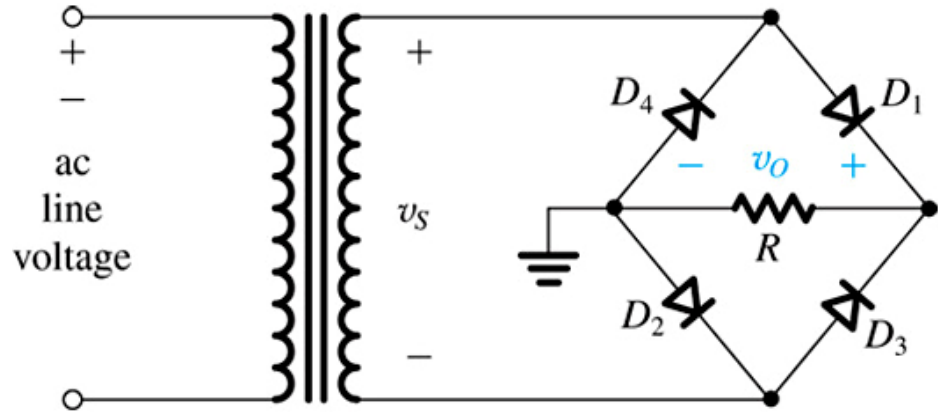

Transient Response

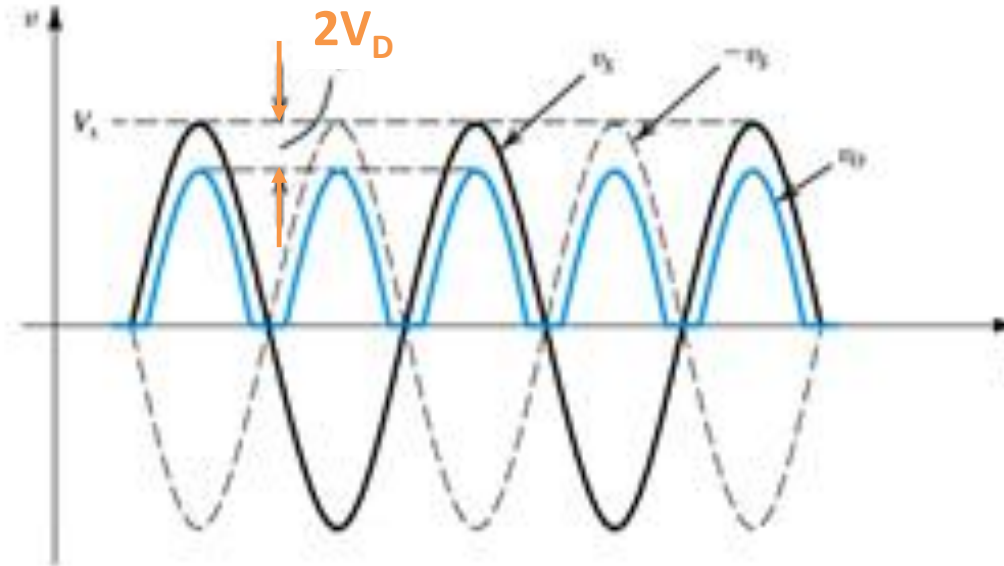

Diode Parameter Specifications:

- **Current-handling capability** – $I_{D(max)}$
- **Peak inverse voltage** – $PIV = V_{Dreverse(max)}$

Output Specifications:

- **Average Voltage** – $V_{O(avg)}$
- **Average Current** – $I_{L(avg)}$

• Diode Ratings

$$I_{max} = \frac{V_S - 2V_D}{R}$$

$$PIV = V_S - V_D$$

• Conduction Angle

$$\theta = \sin^{-1} \left(\frac{V_D}{V_S} \right)$$


$$\Delta\theta = \pi - 2\theta$$

• Average Output

$$\bar{V}_0 = \frac{2V_S}{\pi} - 2V_D$$


$$\bar{I}_L = \frac{\bar{V}_0}{R}$$

The Rectifier with a Filter Capacitor

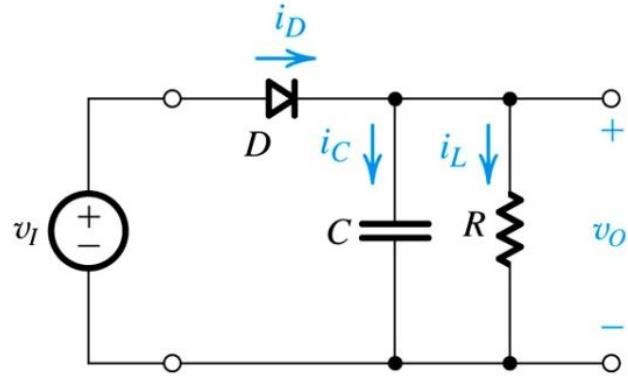

$$v_o(t) = V_S e^{-t/CR}$$

assume $CR \gg T$

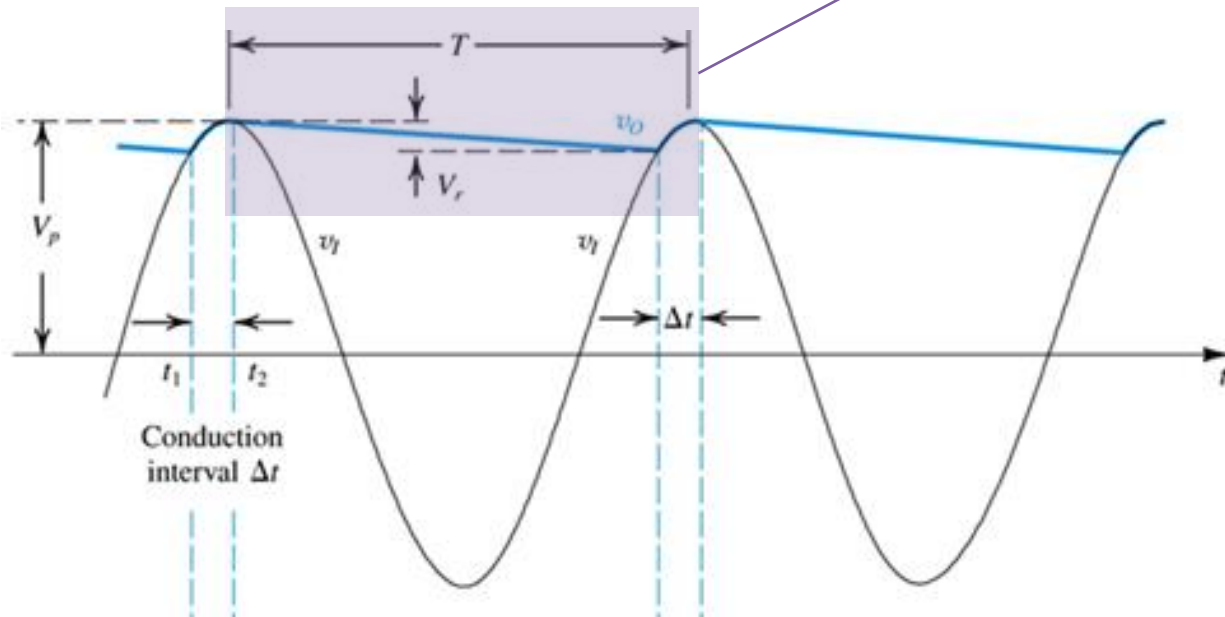

• Half-Wave

$$\bar{V}_0 = V_S - \frac{V_r}{2}$$

$$\bar{I}_L = \frac{\bar{V}_0}{R}$$

$$V_r = \frac{V_S}{fCR} \approx \frac{I_L}{fC}$$

$$\Delta\theta \approx \sqrt{2V_r/V_S}$$

$$i_{Davg} = I_L \left(1 + \pi\sqrt{2V_S/V_r} \right)$$

$$i_{Dmax} = I_L \left(1 + 2\pi\sqrt{2V_S/V_r} \right)$$

• Full-Wave

$$\bar{V}_0 = V_S - \frac{V_r}{2}$$

$$\bar{I}_L = \frac{\bar{V}_0}{R}$$

$$V_r = \frac{V_S}{2fCR} \approx \frac{I_L}{2fC}$$

$$\Delta\theta \approx \sqrt{2V_r/V_S}$$

$$i_{Davg} = I_L \left(1 + \pi\sqrt{V_S/2V_r} \right)$$

$$i_{Dmax} = I_L \left(1 + 2\pi\sqrt{V_S/2V_r} \right)$$