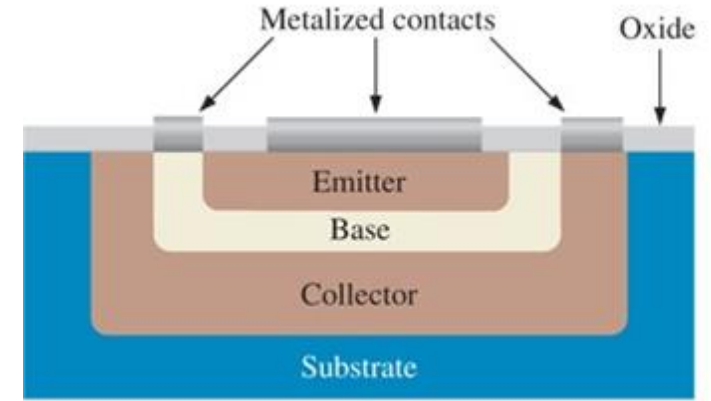



# Bipolar Junction Transistors → Chapter 6

- A three terminal device
- Invented in 1948 at Bell Telephone Laboratories
- Ushered in a new era of solid-state circuits
- Replaced by MOSFET as predominant transistors


*cross section* →


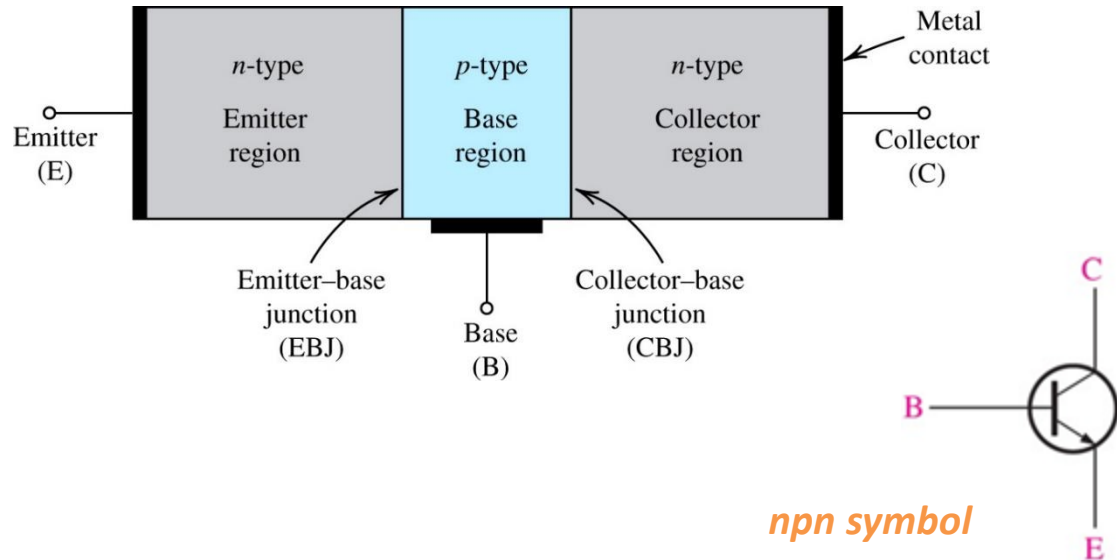
## • Simplified structure of the *npn* transistor


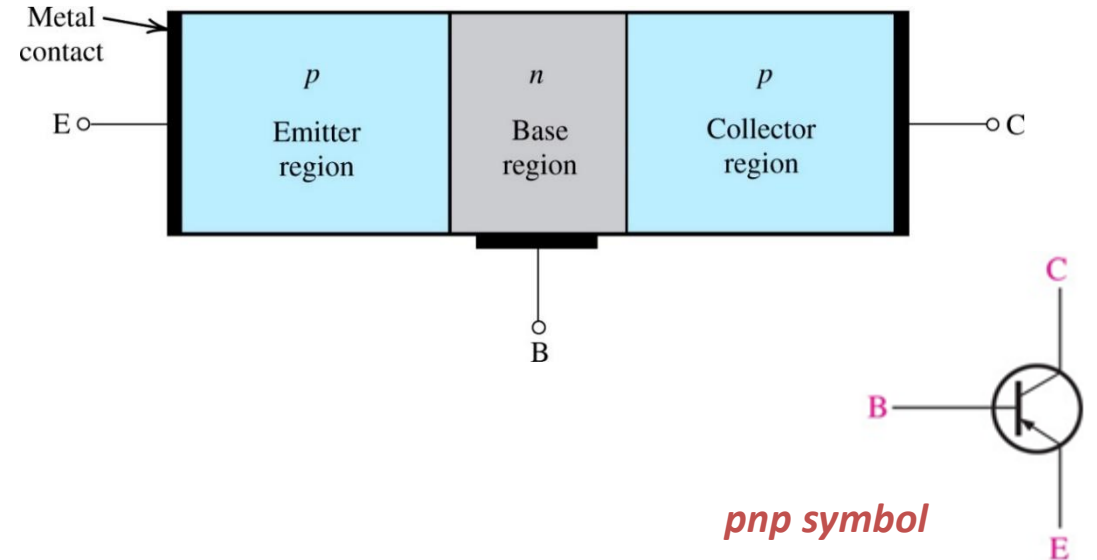
## • Simplified structure of the *pnp* transistor






# BJT Operation

- Two external voltage sources are required for biasing
- Three operation modes:

*used for switching!*

- 1) Cut-Off
- 2) Saturation
- 3) Active

*used for amplification!*

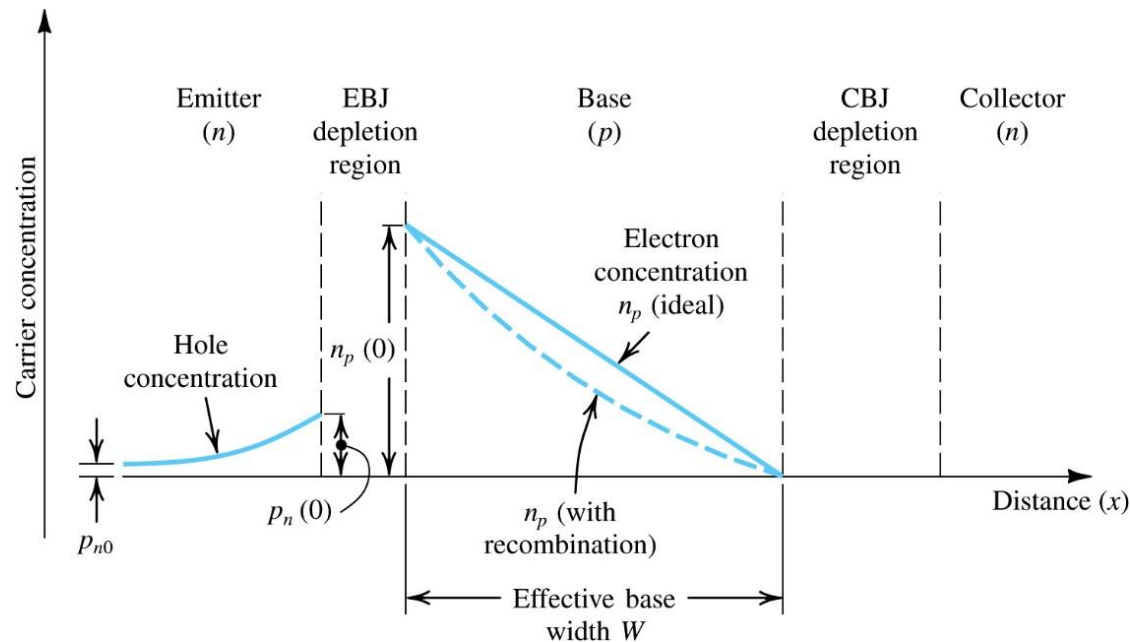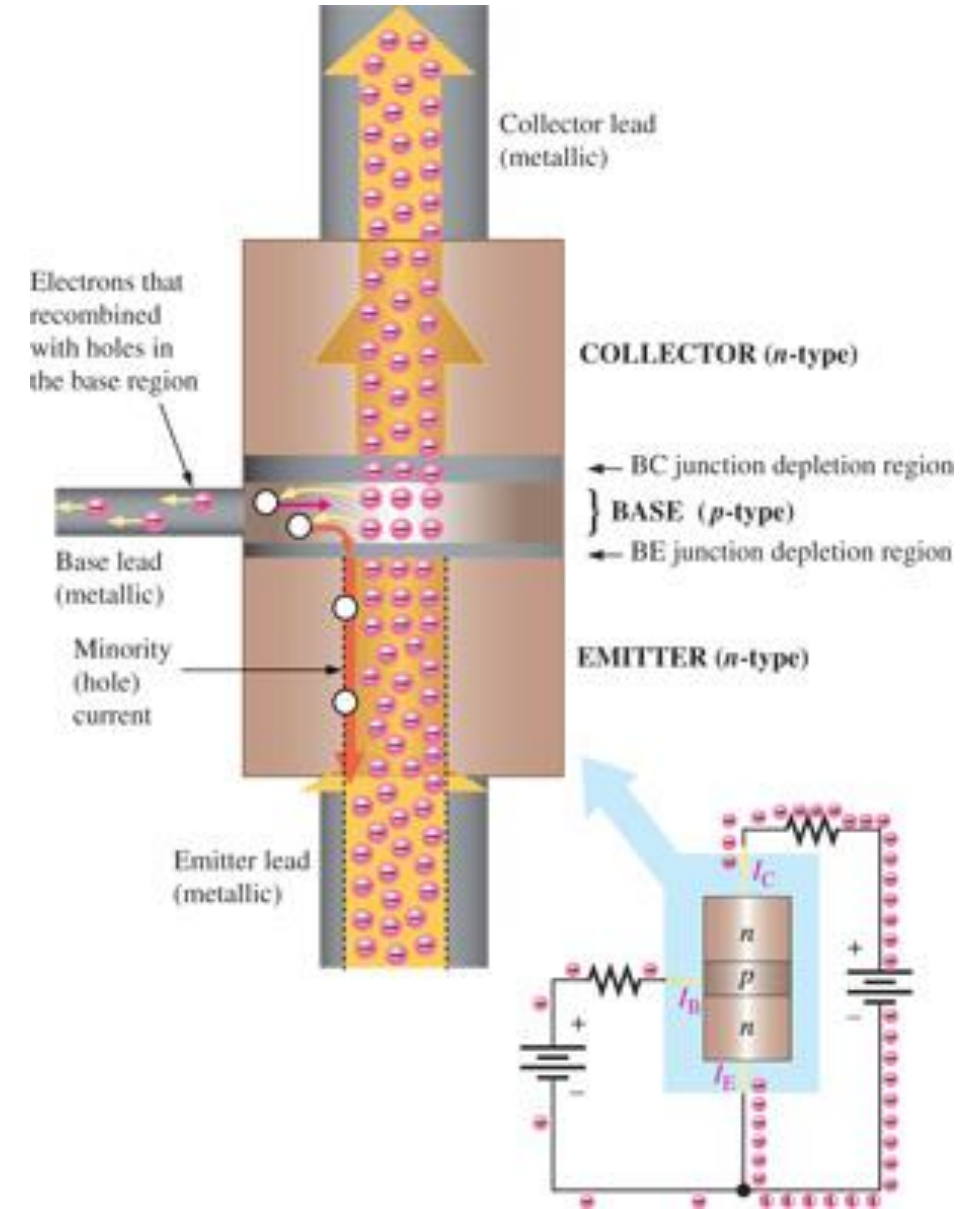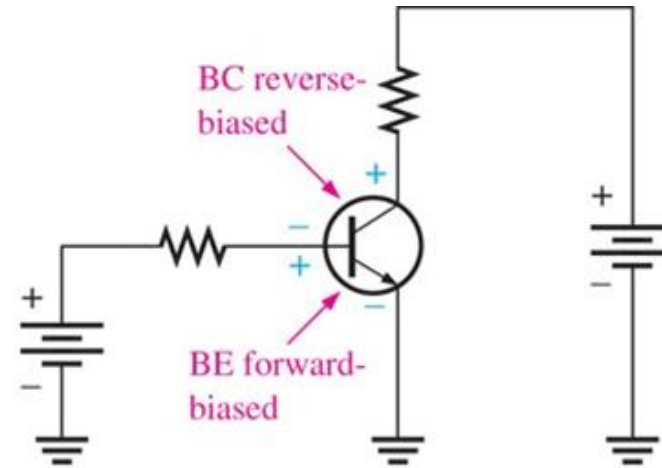



# BJT Operation

- Two external voltage sources are required for biasing
- Three operation modes:

*used for switching!*


- 1) Cut-Off
- 2) Saturation
- 3) Active

*used for amplification!*

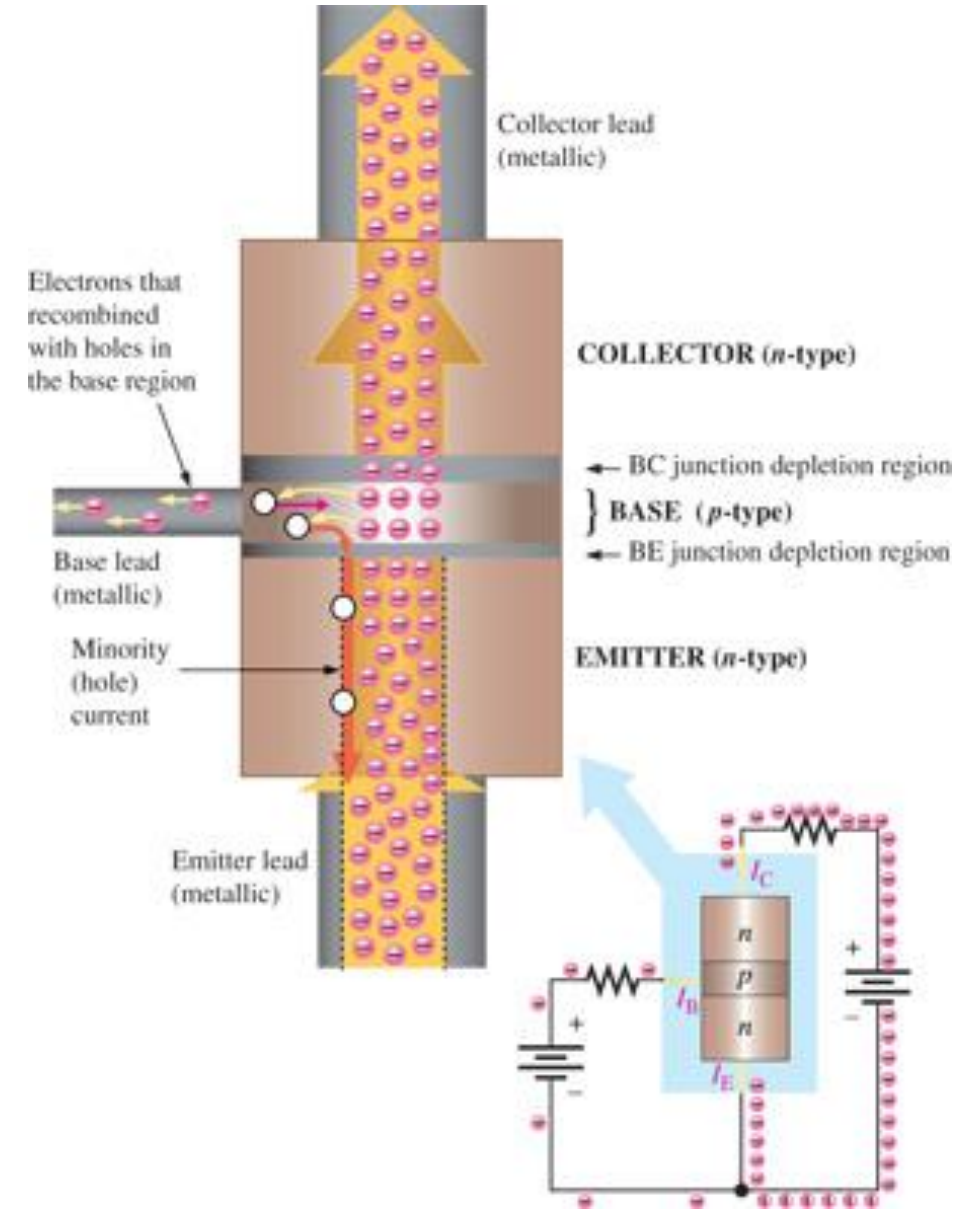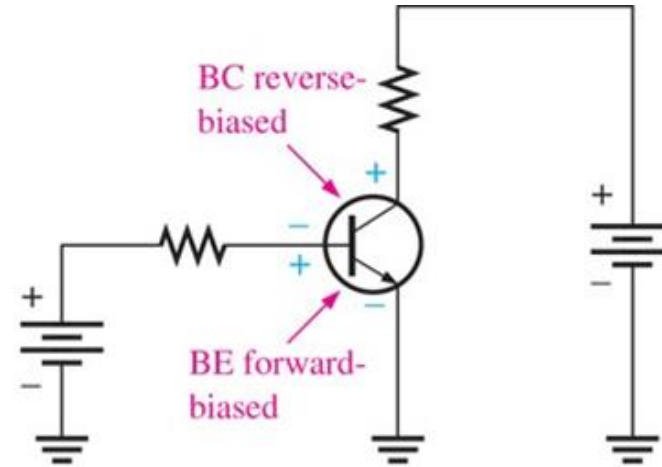


# BJT Mathematical Model → Active

- $i_C = f(v_{BE})$

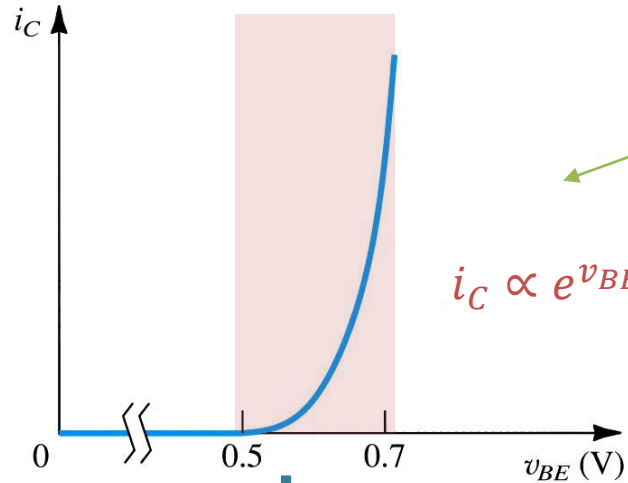


$$i_C \propto e^{v_{BE}/V_T}$$

- $i_C = f(v_{CE})$

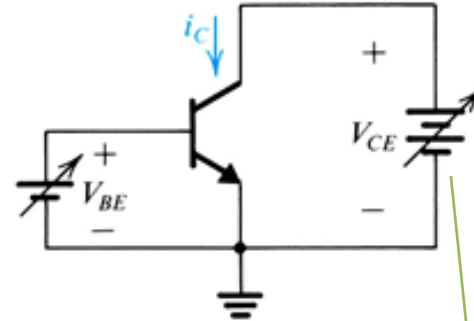

$$i_C \propto \frac{v_{CE}}{V_A}$$

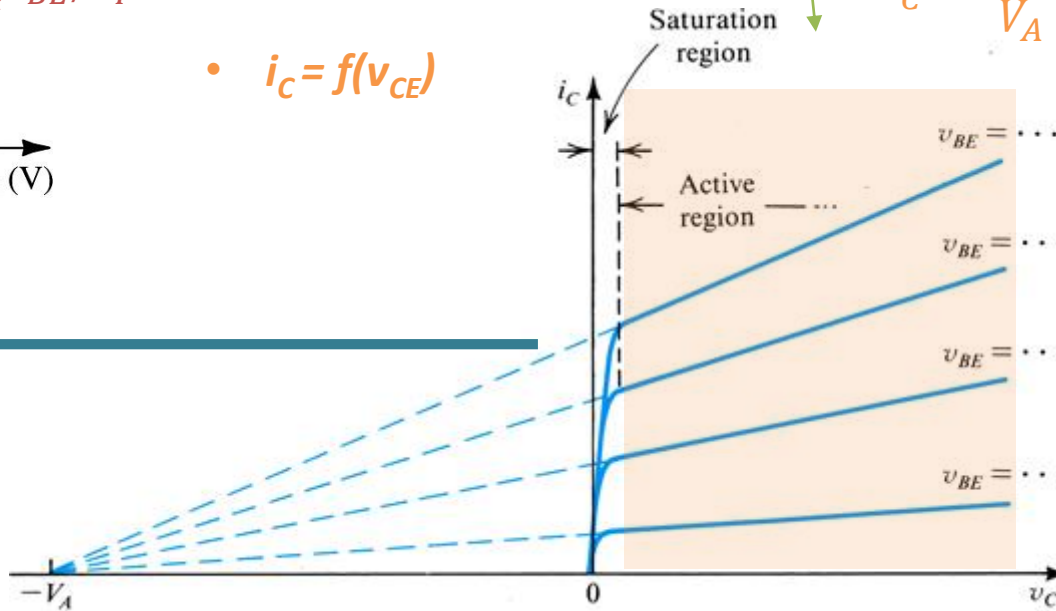

Collector Current

$$i_C = I_S e^{v_{BE}/V_T} \left( 1 + \frac{v_{CE}}{V_A} \right)$$

$$\approx I_S e^{v_{BE}/V_T}$$

Base / Emitter Currents

$$i_B = \frac{i_C}{\beta}$$

$$i_E = i_B + i_C = \frac{\beta + 1}{\beta} i_C = \frac{i_C}{\alpha}$$

$I_S$  - Saturation Current [ $10^{-12}$  -  $10^{-18}$ ] A

$$I_S = \frac{A_E q D_n n_i}{N_A W}$$

$\beta$  - Current Gain [50 - 200] A/A

$$\beta_{forced} = \frac{i_C}{i_B} |_{sat} \leq \beta$$

$\alpha$  - Constant

$$\alpha = \frac{\beta}{\beta + 1}$$

$V_A$  - Early Voltage [10 - 100] V



# Large Signal Model → npn

## Active Mode

- $v_{BE} \rightarrow$  forward bias
- $v_{BC} \rightarrow$  reverse bias
- $v_{CE} > 0.3V$
- $i_C = f(v_{BE})$

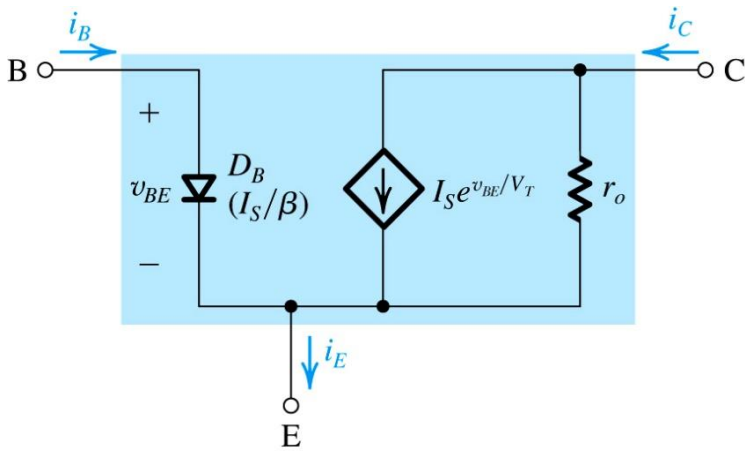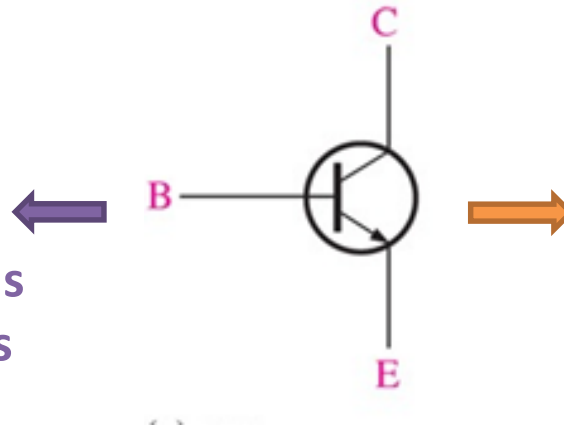
## Saturation Mode

- $v_{BE} \rightarrow$  forward bias
- $v_{BC} \rightarrow$  forward bias
- $i_C \neq f(v_{BE})$
- $i_C / i_B < \beta$




(a)

npn circuit model

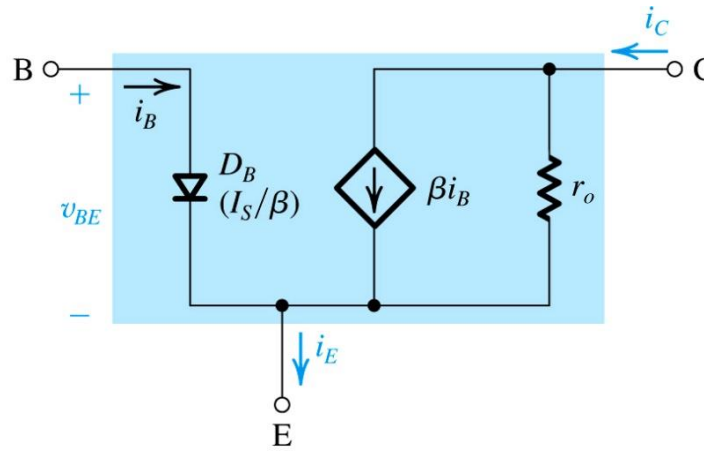

(b)

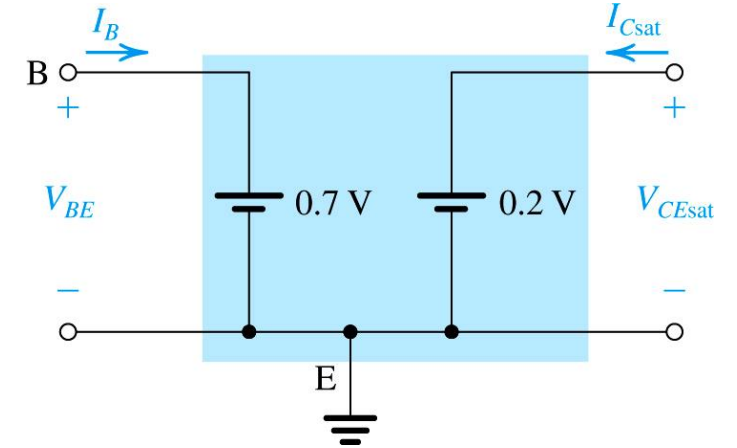

npn circuit model

## Example 6.1

An npn transistor having  $I_s = 10^{-15}\text{A}$ ,  $\beta = 100$ , and  $V_A = \infty$  is connected as follows: the emitter is grounded, the base is fed with a constant-current source supplying a dc current of  $10\mu\text{A}$ , and the collector is connected to a 5-V dc supply via a resistance  $R_C$  of  $3\text{k}\Omega$ . Assuming that the transistor is operating in the active mode, find  $V_{BE}$  and  $V_{CE}$ . Use these values to verify active-mode operation. Replace the current source with a resistance connected from the base to the 5-V dc supply. What resistance value is needed to result in the same operating conditions?

