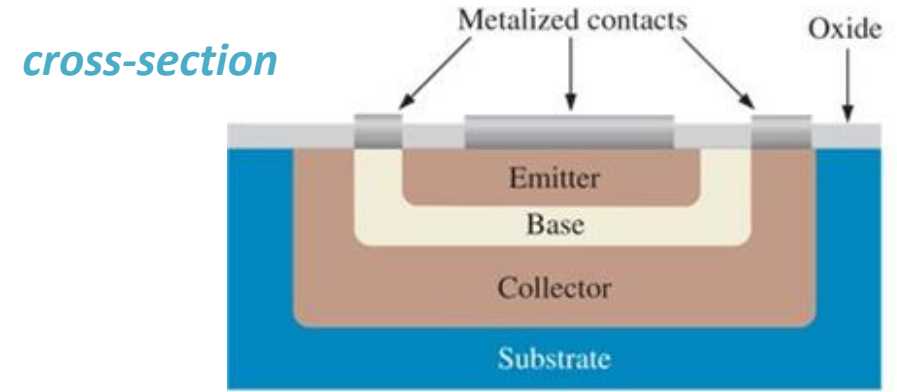



Last Lecture → BJTs - Chapter 6

- Two external voltage sources are required for biasing
- Three operation modes:


1) Cut-Off	<i>used for</i>
2) Saturation	<i>switching!</i>
3) Active	<i>used for amplification!</i>



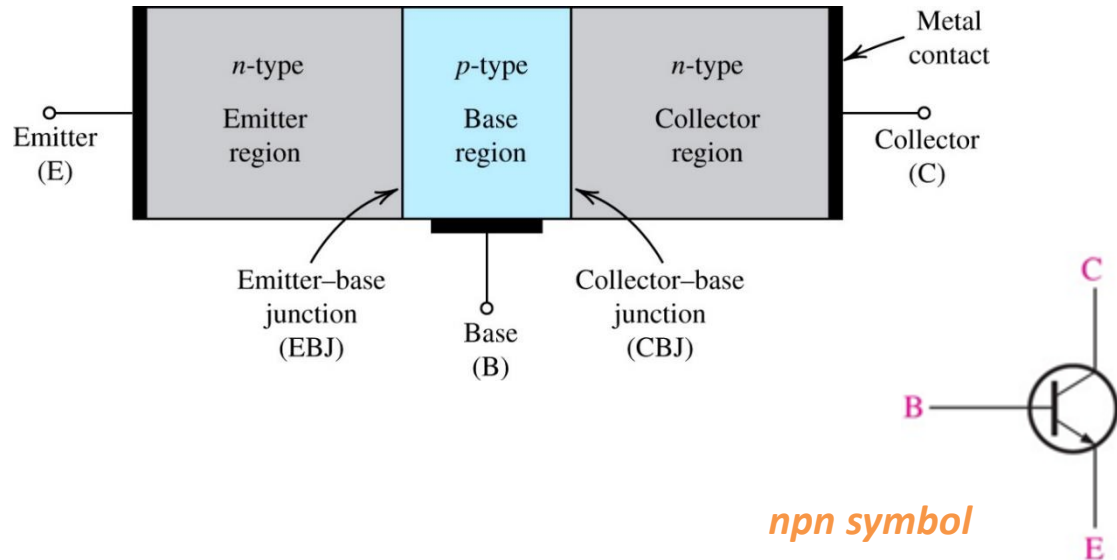• Simplified structure of the npn transistor




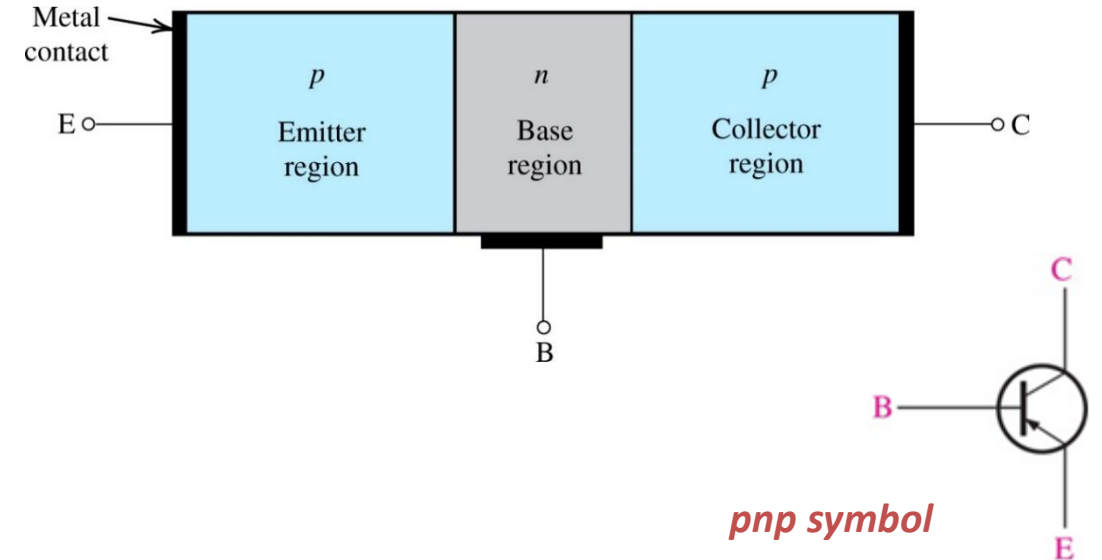• Simplified structure of the pnp transistor




Last Lecture → BJT (active)

- $i_C = f(v_{BE})$

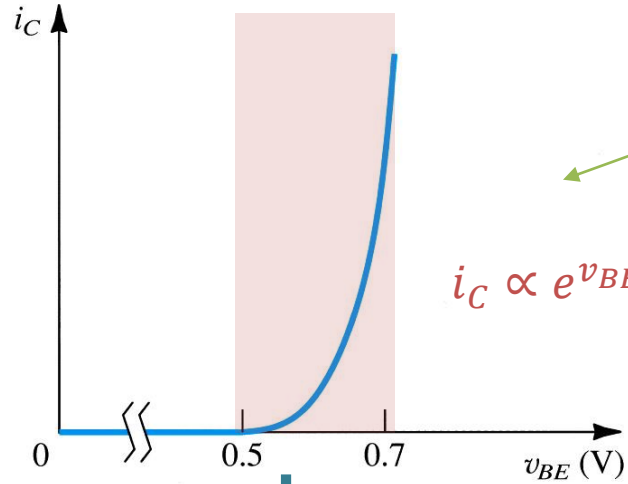


$$i_C \propto e^{v_{BE}/V_T}$$

- $i_C = f(v_{CE})$

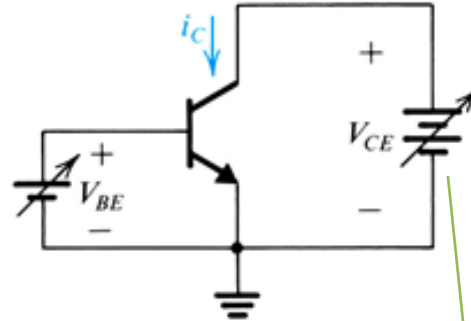

$$i_C \propto \frac{v_{CE}}{V_A}$$

Large Signal Model

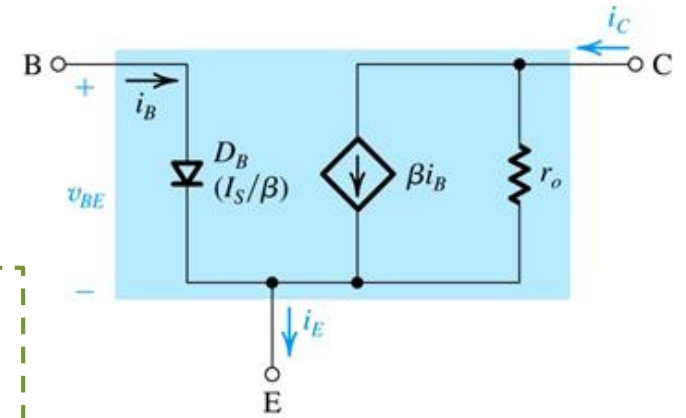


Base / Emitter Currents

$$i_B = \frac{i_C}{\beta}$$

$$i_E = i_B + i_C = \frac{\beta + 1}{\beta} i_C = \frac{i_C}{\alpha}$$



Collector Current
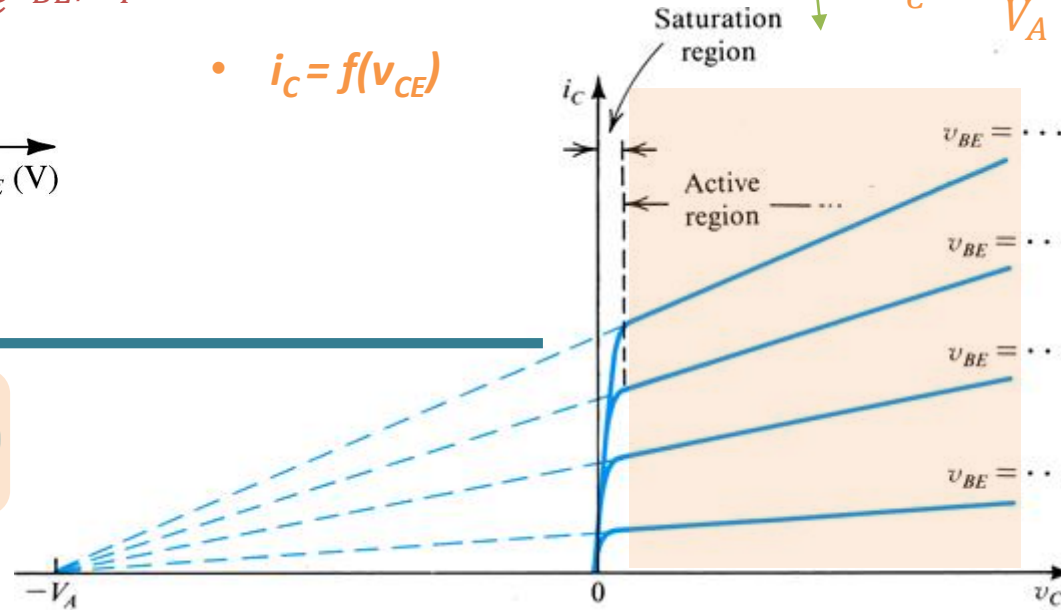
$$i_C = I_S e^{v_{BE}/V_T} \left(1 + \frac{v_{CE}}{V_A} \right) \approx I_S e^{v_{BE}/V_T}$$





Large Signal Model → Active-Mode

npn - transistor

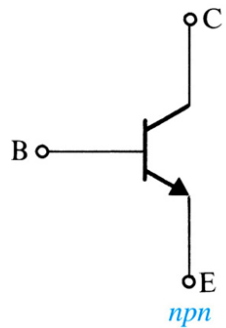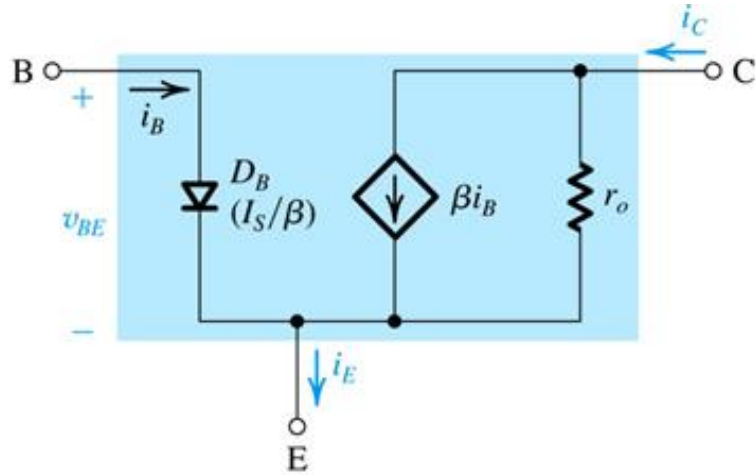

- BE Junction → forward bias
✓ $v_{BE} > 0.5V$
- BC Junction → reverse bias
✓ $v_{CE} > 0.3V$
- $i_C = f(v_{BE})$



pnp - transistor

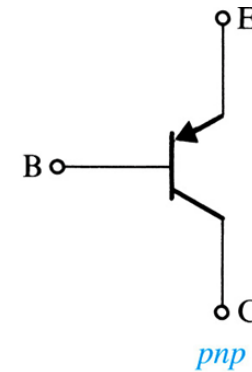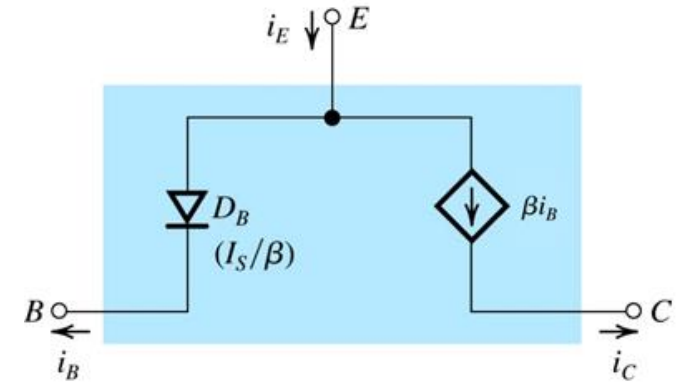

- EB Junction → forward bias
✓ $v_{EB} > 0.5V$
- CB Junction → reverse bias
✓ $v_{EC} > 0.3V$
- $i_C = f(v_{EB})$


Large Signal Model → Active-Mode

npn - transistor

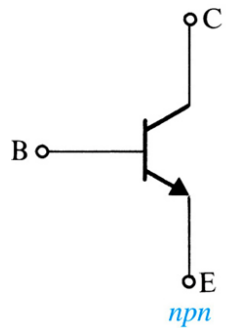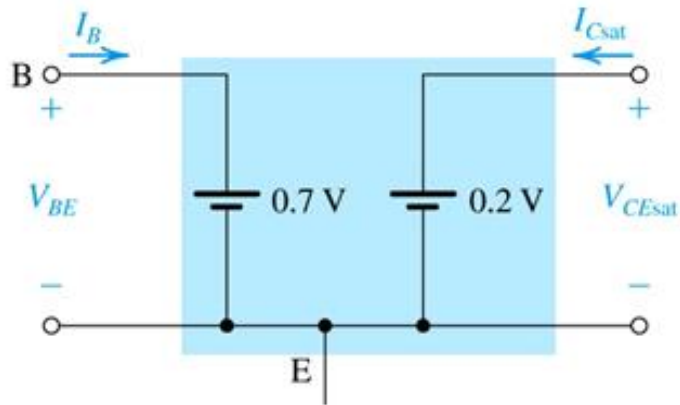

- BE Junction → forward bias
✓ $v_{BE} > 0.5V$
- BC Junction → reverse bias
✓ $v_{CE} < 0.3V$
- $i_C \neq f(v_{BE})$
✓ $i_C/i_B < \beta$

pnp - transistor

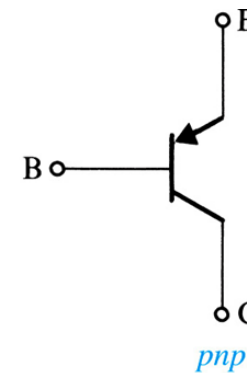

- EB Junction → forward bias
✓ $v_{EB} > 0.5V$
- CB Junction → reverse bias
✓ $v_{EC} < 0.3V$
- $i_C \neq f(v_{EB})$
✓ $i_C/i_B < \beta$

Large Signal Models

- 1) Cut-Off
- 2) Saturation
- 3) Active


Table 6.3 Conditions and Models for the Operation of the BJT in Various Modes

	npn	pnp
Cutoff EJB: Reverse Biased CBJ: Reverse Biased	<p> $I_B = 0$ $V_{BE} < 0.5\text{ V}$ $V_{CE} < 0.4\text{ V}$ $I_C = 0$ </p>	<p> $I_B = 0$ $V_{EB} < 0.5\text{ V}$ $V_{EC} < 0.4\text{ V}$ $I_C = 0$ </p>
Active EJB: Forward Biased CBJ: Reverse Biased	<p> $I_B > 0$ $V_{BE} = 0.7\text{ V}$ $V_{CE} < 0.4\text{ V}$ $I_C = \beta I_B$ </p>	<p> $I_B > 0$ $V_{EB} = 0.7\text{ V}$ $V_{EC} < 0.4\text{ V}$ $I_C = \beta I_B$ </p>
Saturation EJB: Forward Biased CBJ: Forward Biased	<p> $I_B > 0$ $V_{BE} = 0.7\text{ V}$ $V_{CE} = 0.2\text{ V}$ $I_C = \beta_{\text{sat}} I_B$ </p>	<p> $I_B > 0$ $V_{EB} = 0.7\text{ V}$ $V_{EC} = 0.2\text{ V}$ $I_C = \beta_{\text{sat}} I_B$ </p>

Example 6.3


For the given circuit ($R_B=10\text{k}\Omega$, $R_C=1\text{k}\Omega$, $V_{CC}=10\text{V}$) assuming V_{BE} remains constant at 0.7V and transistor β is specified to be 50, it is required to determine the value of the voltage V_{BB} that results in the transistor operating

- in the active mode with $V_{CE}=5\text{V}$
- at the edge of saturation ($V_{CEsat} = 0.3\text{V}$)
- deep in saturation ($V_{CEsat} = 0.2\text{V}$) with $\beta_{\text{forced}}=10$.

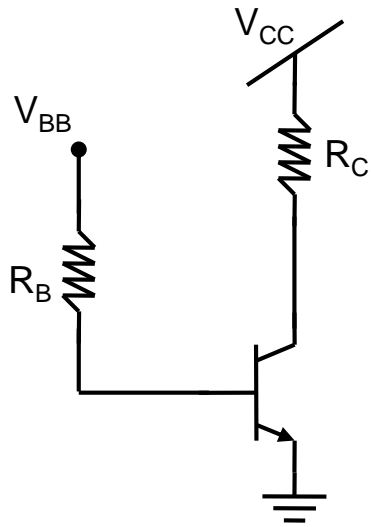


Example 6.5

For the given circuit ($R_C=4.7\text{k}\Omega$, $R_E=3.3\text{k}\Omega$, $V_{CC}=10\text{V}$, $V_B=6\text{V}$) determine the voltages at all nodes and the currents through all branches. Assume that the transistor β is specified to be at least 50 and $V_{BE}=0.7\text{V}$ for all currents.

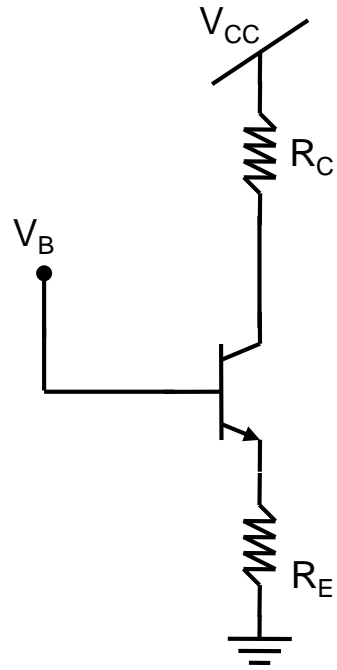

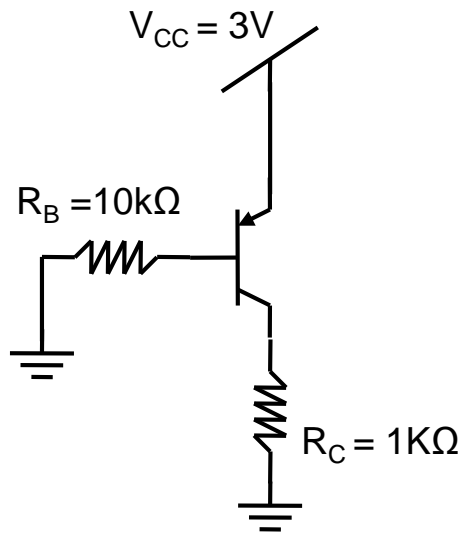Problem 6.51

For the following circuit, assuming $\beta=50$ and $V_{EB}=0.7V$ for all currents, determine the voltage V_c at the collector terminal. To what value should R_B be increased or decreased in order for the transistor to change operating modes.



Problem

For the following circuit determine the voltages at all nodes and the current through all branches assuming $V_{BE}=0.7V$, $\beta=100$, $V_{dd} = -V_{ss}=5V$, and $V_B = 5V$.

