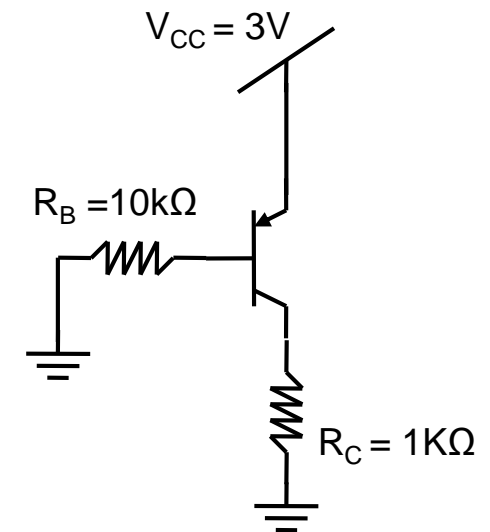


# Last Lecture → BJTs – Large Signal Analysis

## Procedure

- 1) When applicable, simplify the circuit
- 2) Determine if BE/EB junction is forward (transistor = “on”)
  - If reverse, transistor → cut off
  - If forward, transistor → active / saturation
 ∴ Make an educated guess of the region of operation
- 3) Substitute the appropriate model and or assumptions
- 4) Solve for the transistor operating point ( $I_C$  &  $V_{CE}$ )
- 5) Verify proper operation @ the assumed region
  - If cut off →  $V_{BE} < 0.5V$
  - If active →  $V_{CE} > 0.3V$
  - If saturation →  $I_C / I_B < \beta$

## Problem 6.51




For the following circuit, assuming  $\beta=50$  and  $V_{EB}=0.7V$  for all currents, determine the voltage  $V_C$  at the collector terminal. To what value should  $R_B$  be increased or decreased in order for the transistor to change operating modes.
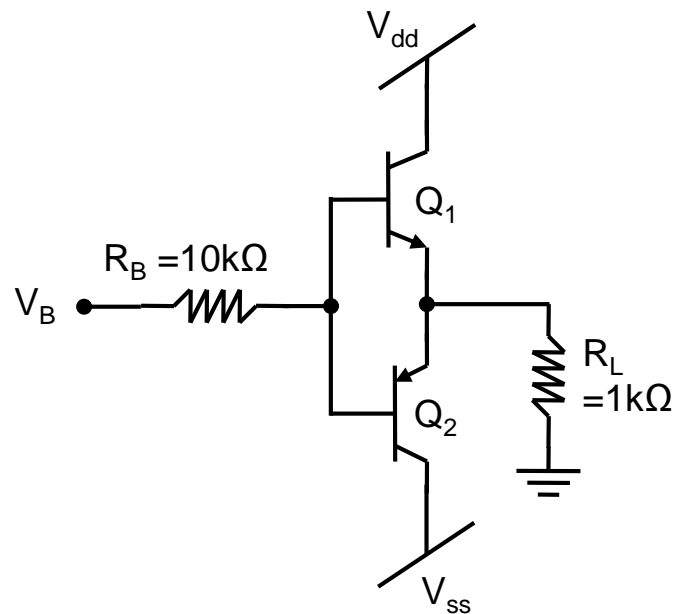
## Example 6.12

For the following circuit determine the voltages at all nodes and the current through all branches assuming:

- $V_{BE}=0.7V$ ,  $\beta=100$ ,  $V_{dd} = -V_{ss}=5V$ , and  $V_B = 5V$
- $V_{BE}=0.7V$ ,  $\beta=100$ ,  $V_{dd} = -V_{ss}=5V$ , and  $V_B = 0.3V$



## Example 6.11

For the following circuit determine the voltages at every node and the bias currents of transistors  $Q_1$  and  $Q_2$ . Assume  $V_{BE} = |V_{EB}| = 0.7$  and  $\beta = 100$ .

