
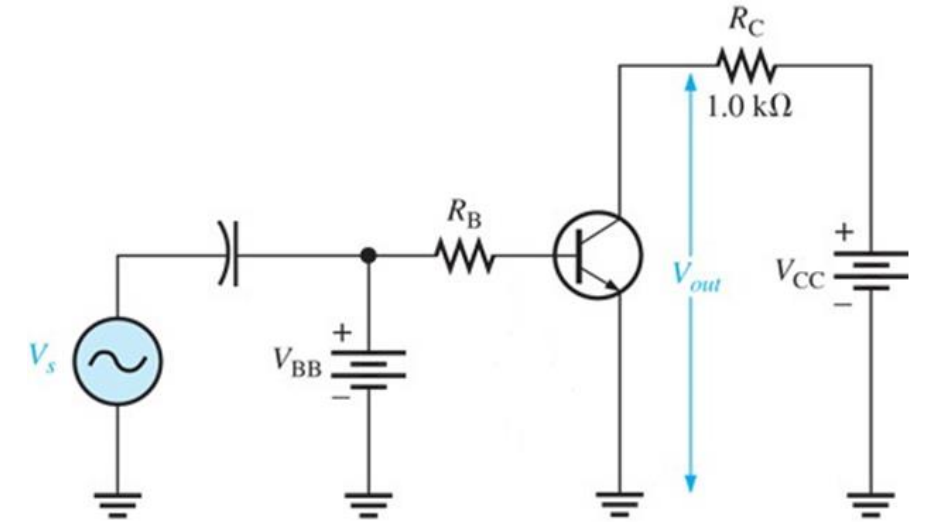



Large-Signal vs Small Signal Behavior

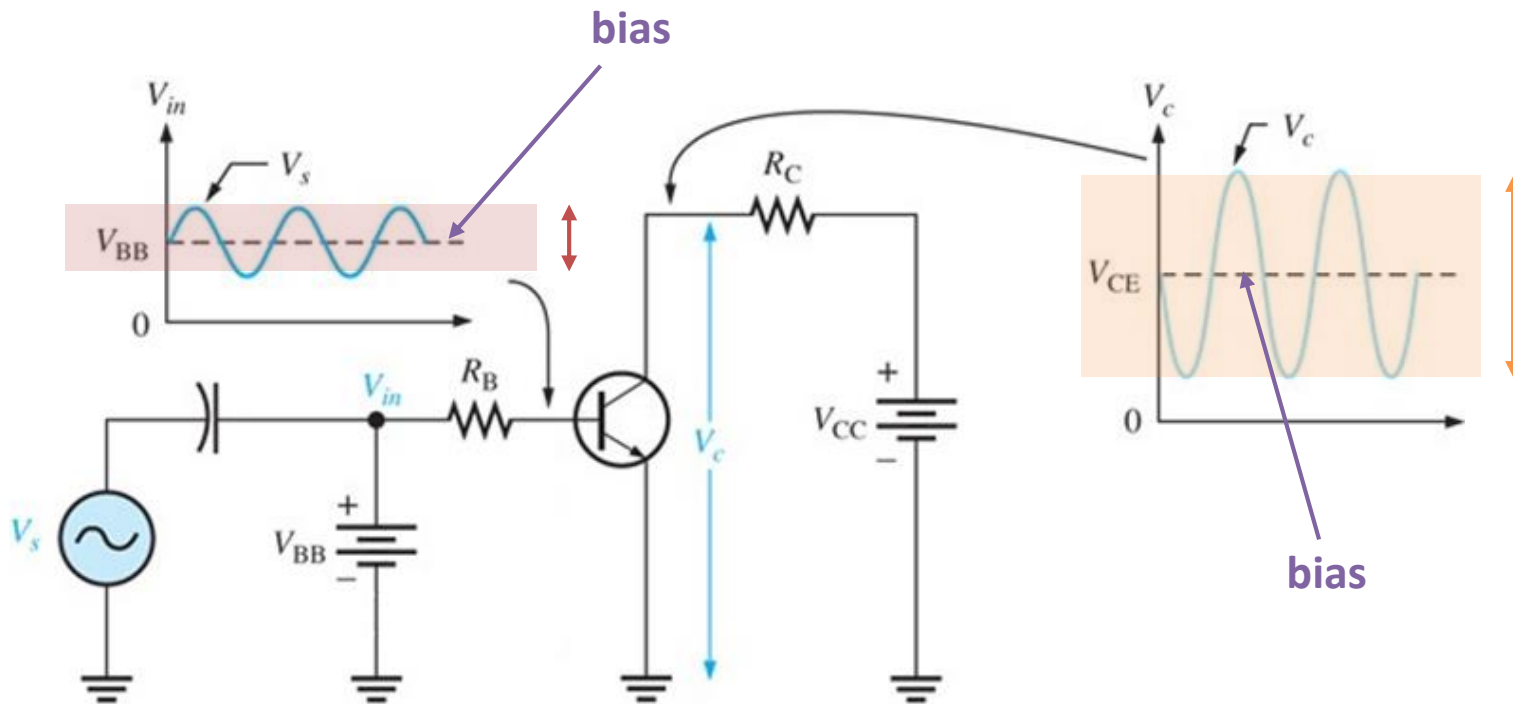- 1) Bias current is established through V_{BB} and supplied by V_{CC}
- 2) AC signal is coupled through the capacitor and superimposed to the DC signal
- 3) AC behavior will be determined by the circuit configuration and the DC bias




- Large-Signal – establishes the DC operating point of the circuit
- Small-Signal – determines the circuit behavior around the DC operating point

Small Signal Parameters

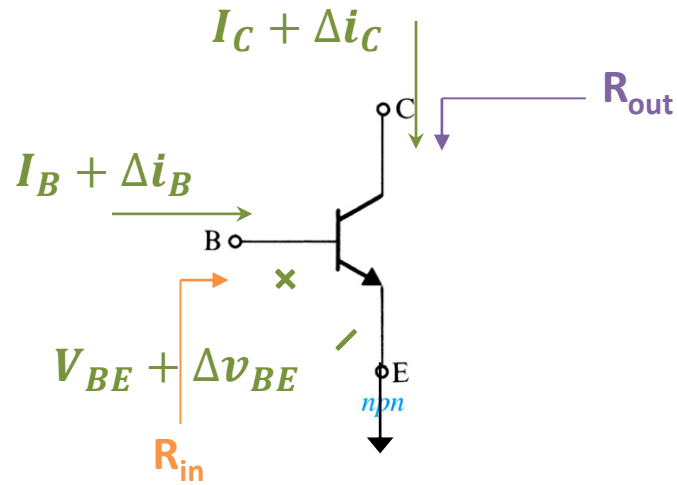


Output Impedance
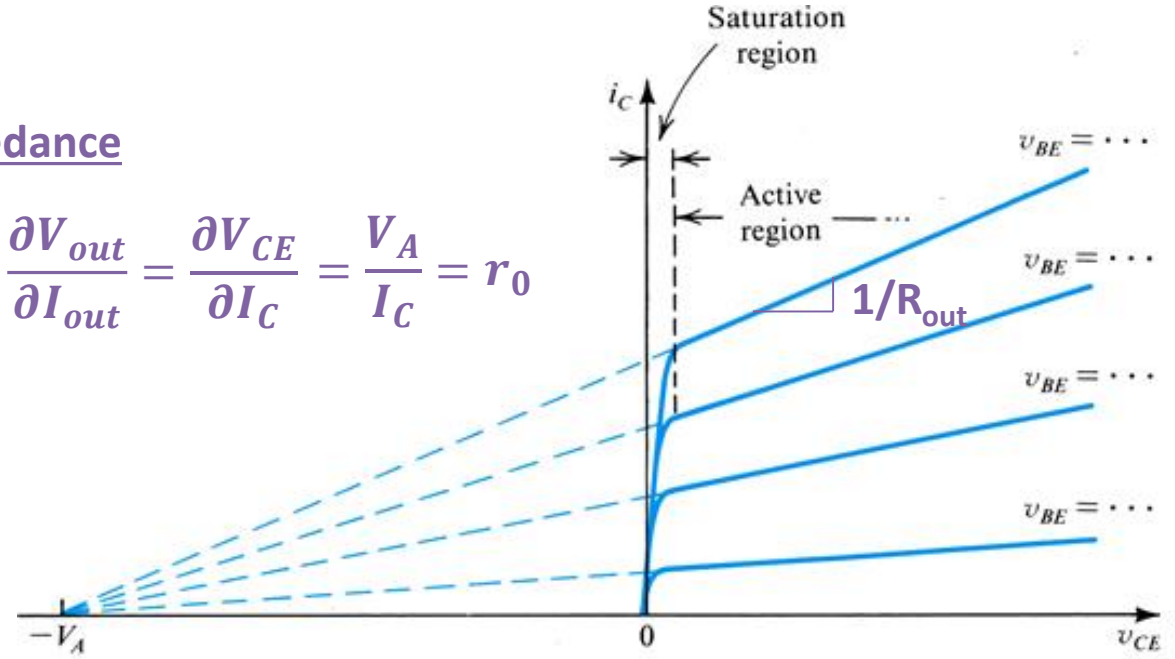
$$R_{out} = \frac{\partial V_{out}}{\partial I_{out}} = \frac{\partial V_{CE}}{\partial I_C} = \frac{V_A}{I_C} = r_o$$



Trans-conductance
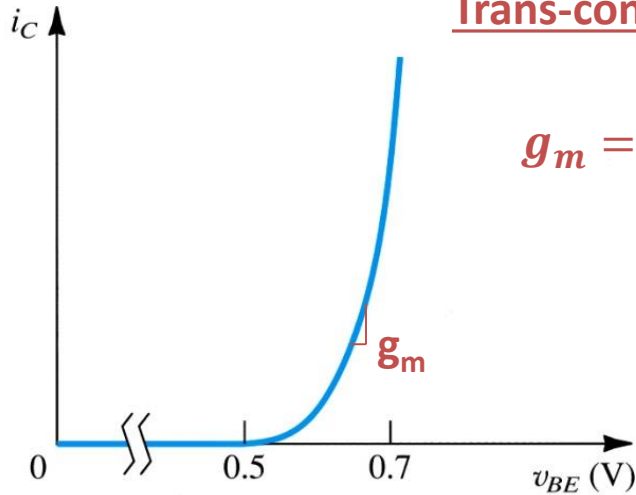
$$g_m = \frac{\partial I_{out}}{\partial V_{in}} = \frac{\partial I_C}{\partial V_{BE}} = \frac{I_C}{V_T}$$





Input Impedance



$$R_{in} = \frac{\partial V_{in}}{\partial I_{in}} = \frac{\partial V_{BE}}{\partial I_B} = \frac{\beta}{g_m} = r_{\pi}$$

Small Signal Equivalent Circuit

- npn transistor

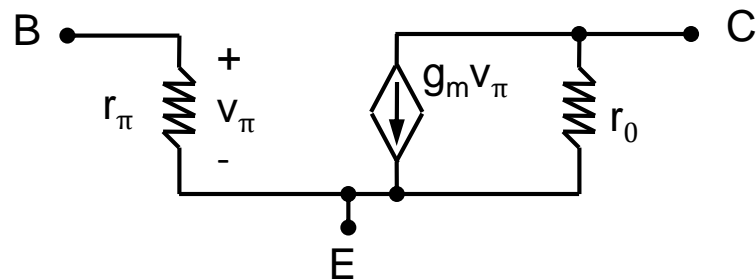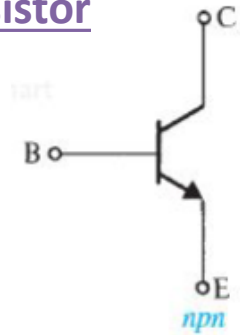


- pnp transistor

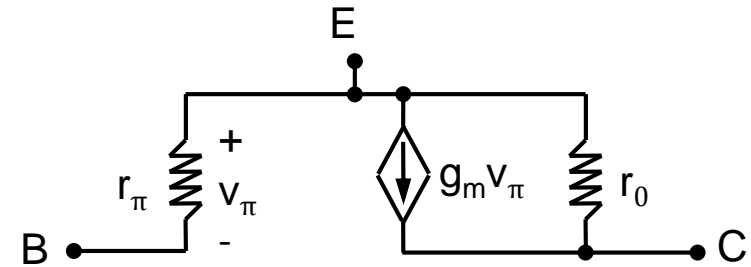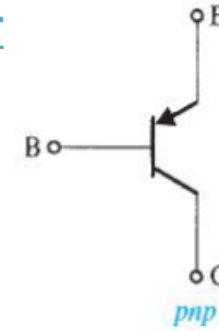

Small Signal Analysis

→ with the small-signal model

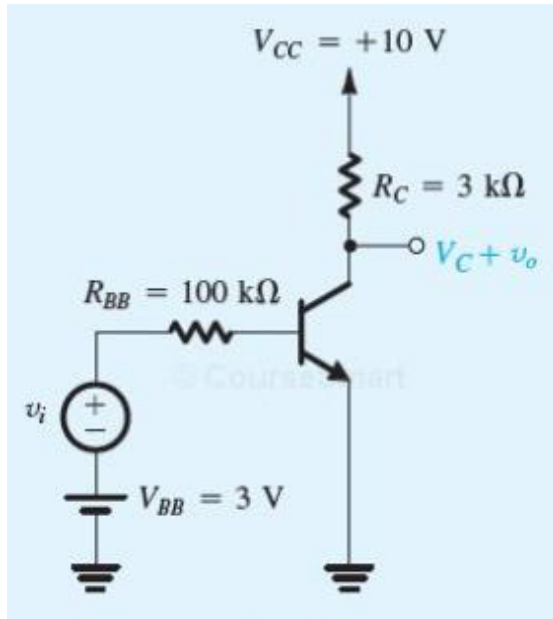Assuming $\beta=200$ and $V_{BE}=0.7V$ find the input resistances R_{in} (seen by v_s) and the overall voltage gain v_o/v_s .



Procedure

- 1) Determine the transistor bias current (DC Analysis)
- 2) Determine the small-signal parameters
- 3) Draw the small-signal equivalent circuit
 - All DC sources off!
 - Low freq. cap shorted!
- 4) Replace transistor with small-signal circuit
- 5) Calculate the desired specifications