
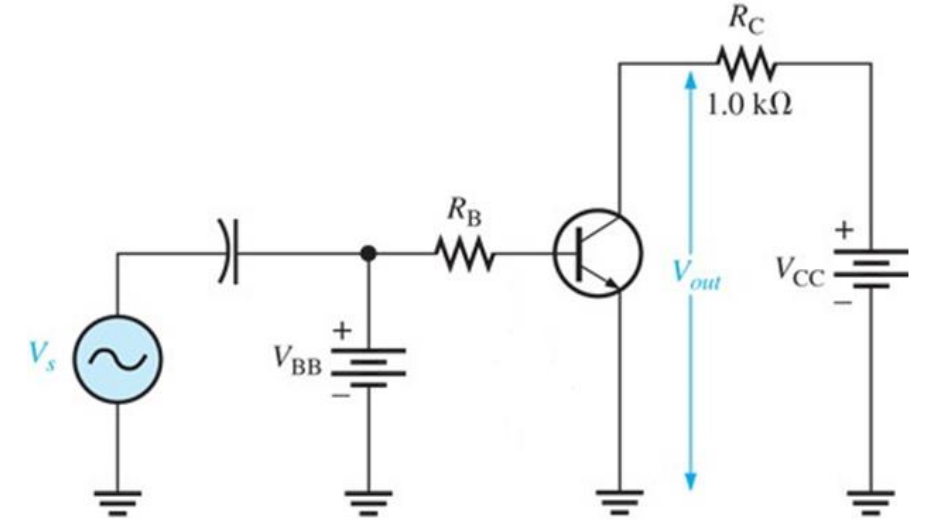


Large-Signal vs Small Signal Behavior

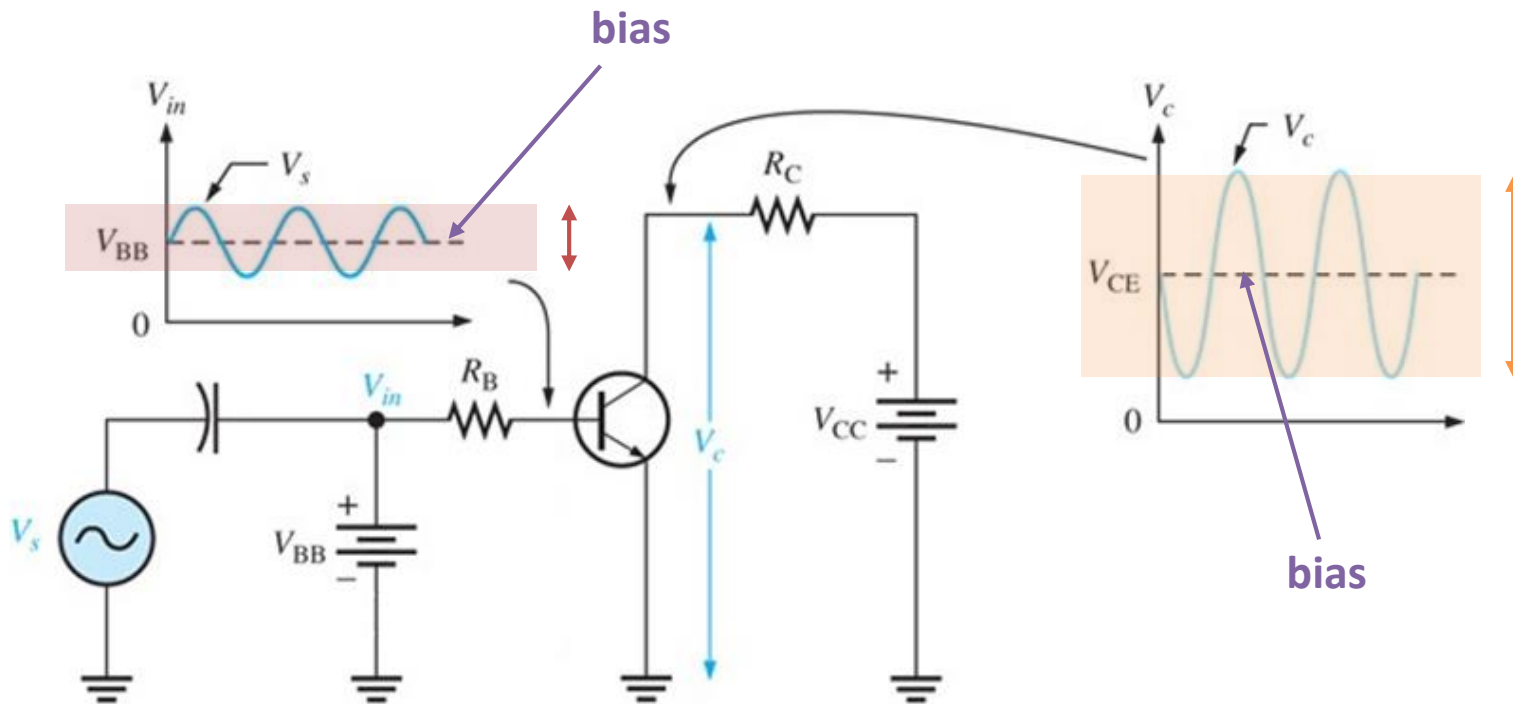- 1) Bias current is established through V_{BB} and supplied by V_{CC}
- 2) AC signal is coupled through the capacitor and superimposed to the DC signal
- 3) AC behavior will be determined by the circuit configuration and the DC bias




- Large-Signal – establishes the DC operating point of the circuit
- Small-Signal – determines the circuit behavior around the DC operating point

Common-Source Amplifier

↳ Source terminal connected at the common node! $\implies R_{in} = r_{\pi}$


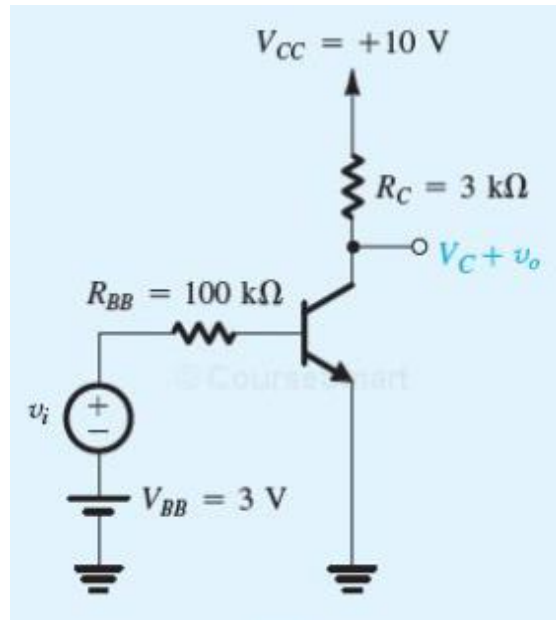
Assuming $\beta=200$ and $V_{BE}=0.7V$ find the input resistances R_{in} (seen by v_s) and the overall voltage gain v_o/v_s .



$$R_{out} = R_C // r_o$$


$$A_V = -g_m(R_C // r_o)$$

- High Gain!
- 180° Shift!

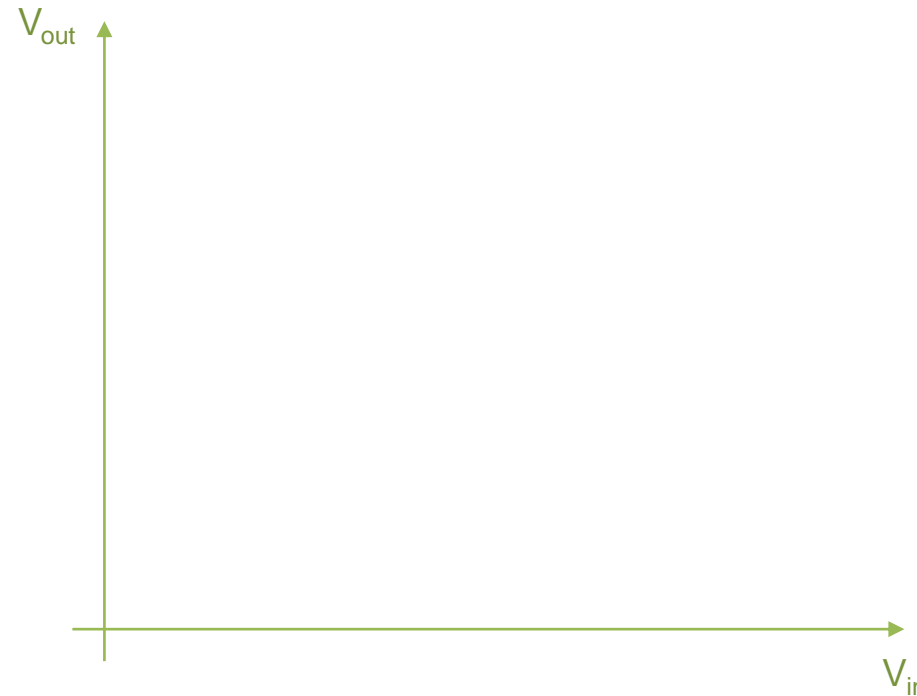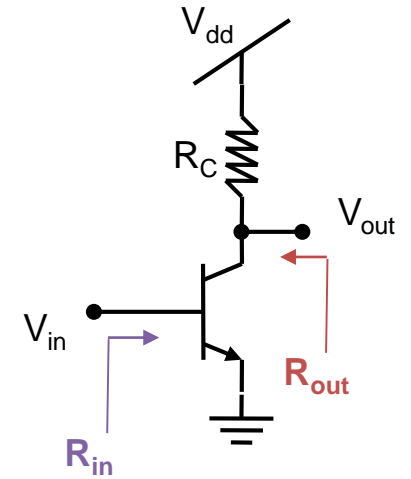

Problem 6.101

Assuming $\beta = 200$, what is the dc voltage at the collector. Find the input resistances R_{ib} and R_{in} and the overall voltage gain v_o/v_{sig} .

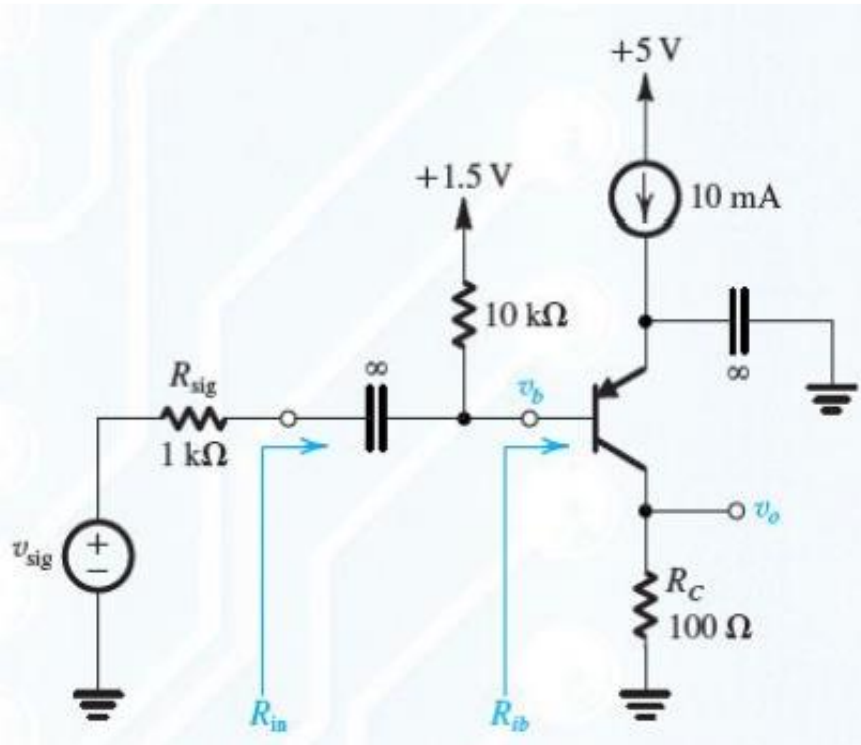

Problem 6.107

Assuming β is very large and the transistor is operating in active mode, find the collector bias current I_C . Using the small-signal model analyze the circuit to determine v_{o1}/v_i and v_{o2}/v_i .

