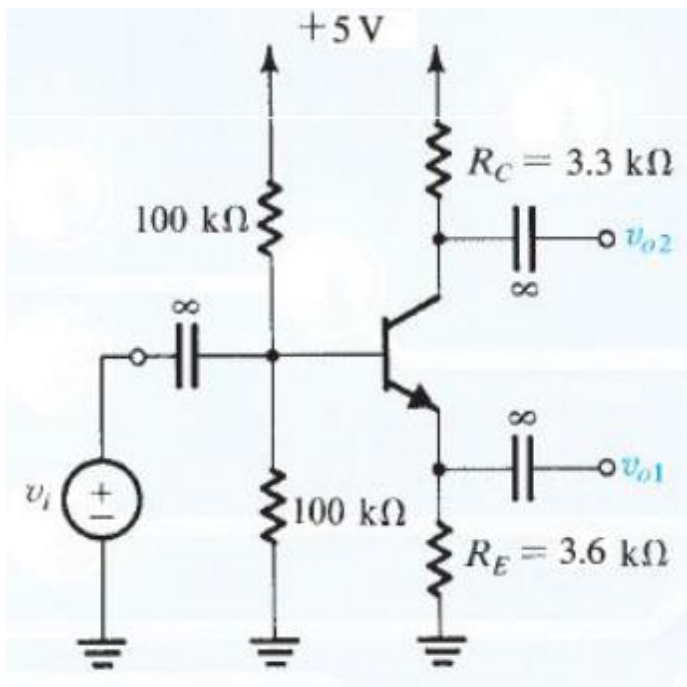


Last Lecture → Problem 6.107

Assuming β is very large and the transistor is operating in active mode, find the collector bias current I_C . Using the small-signal model analyze the circuit to determine v_{o1}/v_i and v_{o2}/v_i . Assuming $V_A = \infty$, determine the resistance seen by the input source and the output resistances from v_{o1} and v_{o2} .



$$V_E = V_{CC}/2 - V_{BE} = 1.8V \quad V_C = V_{CC} - R_C \cdot I_C = 3.35V$$

$$I_C = I_E = \frac{V_E}{R_E} = 0.5mA$$