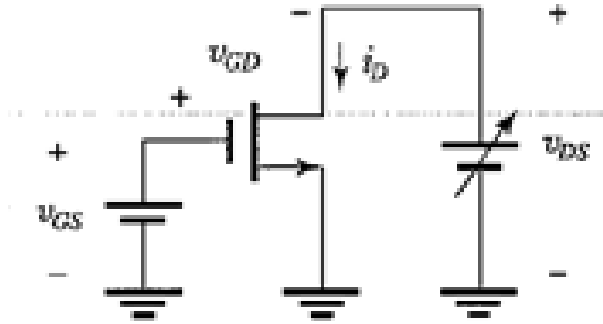


Last Lecture → MOS DC Analysis

- $V_{GS} > V_{th}$
- $V_{DS} > V_{GS} - V_{th} = V_{ov}$
- $i_G = 0$



- $V_{GS} > V_{th}$
- $V_{DS} < V_{GS} - V_{th} = V_{ov}$
- $i_G = 0$

Channel Length Modulation Parameter [1/V]

$$I_D = \frac{1}{2} K_n' \frac{W}{L} (V_{GS} - V_{th})^2 (1 + \lambda V_{DS})$$

$$\approx \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_{th})^2$$

Transconductance Parameter [A/V²]

$$k_n' = \mu_n C_{ox}$$


$$I_D = k_n' \frac{W}{L} \left[(V_{GS} - V_{th})(V_{DS}) - \frac{1}{2} V_{DS}^2 \right]$$

$$\approx k_n' \frac{W}{L} (V_{GS} - V_{th}) \cdot V_{DS}$$

$$r_{ds} = \frac{1}{k_n' \frac{W}{L} (V_{GS} - V_{th})}$$


Example 5.3

Assuming $\lambda=0$, design the circuit below, that is, determine the values of R_D and R_S , so that the transistor operates at $I_D=0.4\text{mA}$ and $V_D=0.5\text{V}$. The NMOS transistor has $V_{th}=0.7\text{V}$, $\mu_n C_{ox}=100\mu\text{A}/\text{V}^2$, and $W/L=32$.

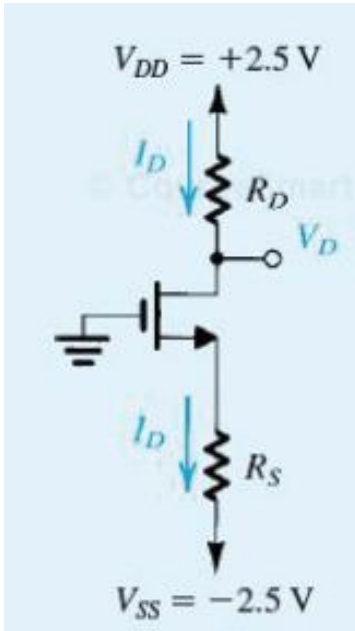

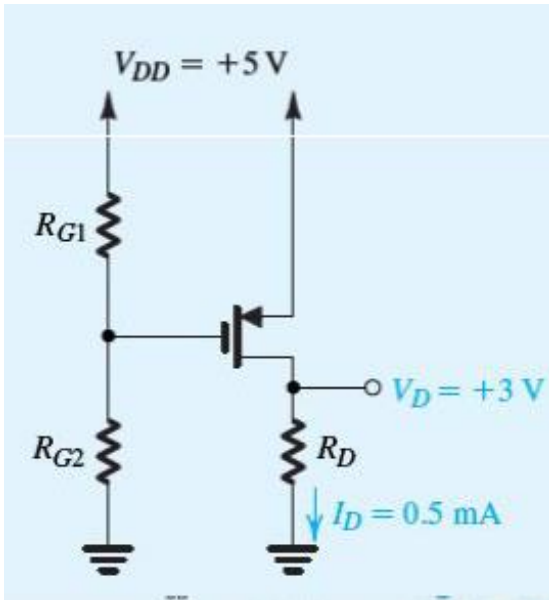Example 5.7


Assuming $\lambda=0$, design the circuit below, so that the transistor operates in saturation with $I_D=0.5\text{mA}$ and $V_D=3\text{V}$. The PMOS transistor has $V_{th}=-1\text{V}$, $K_p=1\text{mA/V}^2$. What is the largest value that R_D can have while maintaining saturation-region operation?




MOS Behavior → Intuitively

Choose the plot that best represents each circuit behavior!


Circuit (a)

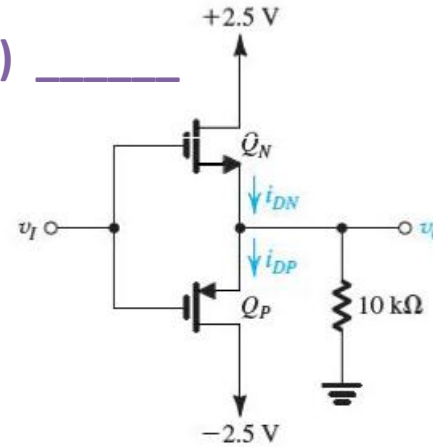


Circuit (b)

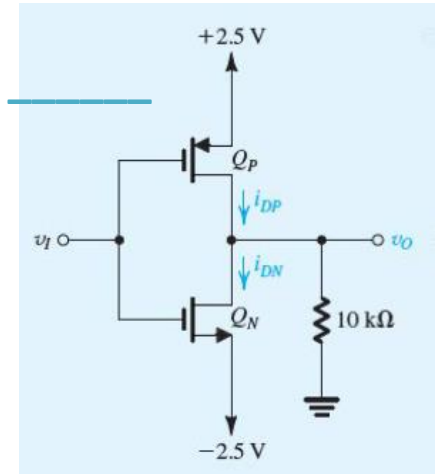


(1)

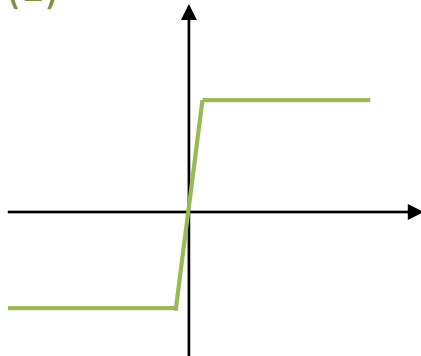

(2)

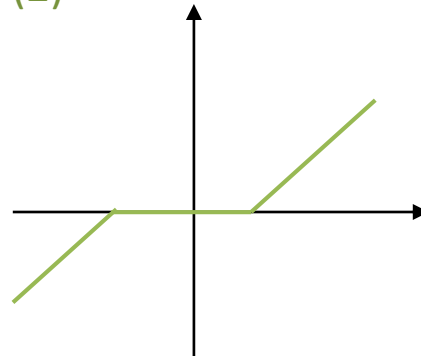

(3)

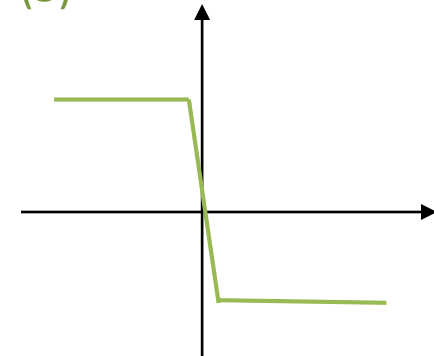

Example 5.8

Assuming matched NMOS and PMOS transistors with $V_{thn} = -V_{thp} = 1V$, $K_n = K_p = 1mA/V^2$ and $\lambda = 0$, find the drain currents I_{Dn} and I_{Dp} , as well as the voltage v_o , for $v_i = 0V$, $+2.5V$, and $-2.5V$.

