
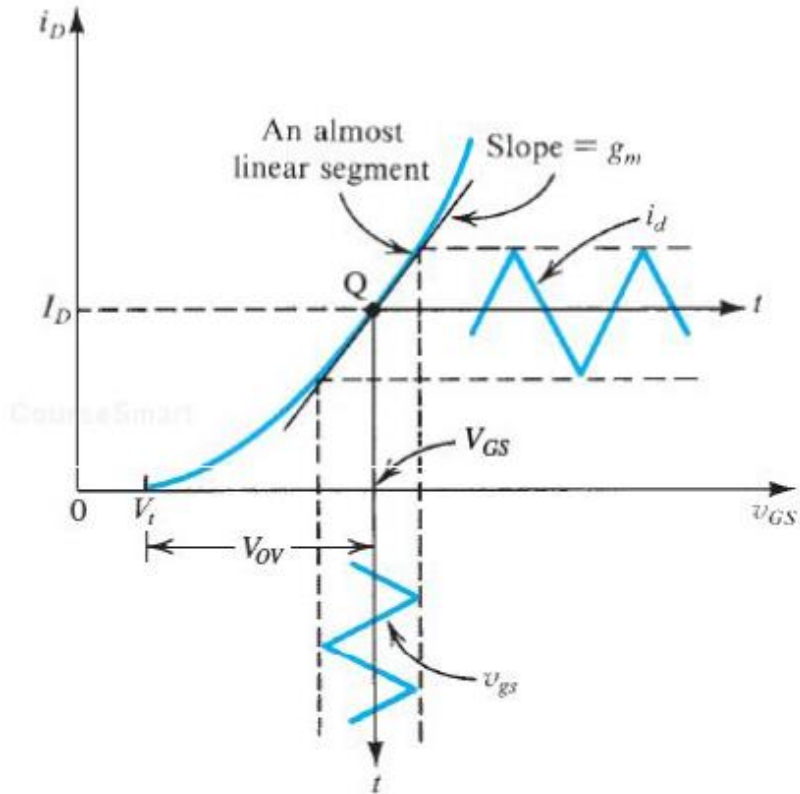



Last Lecture → MOS Small Signal Circuit

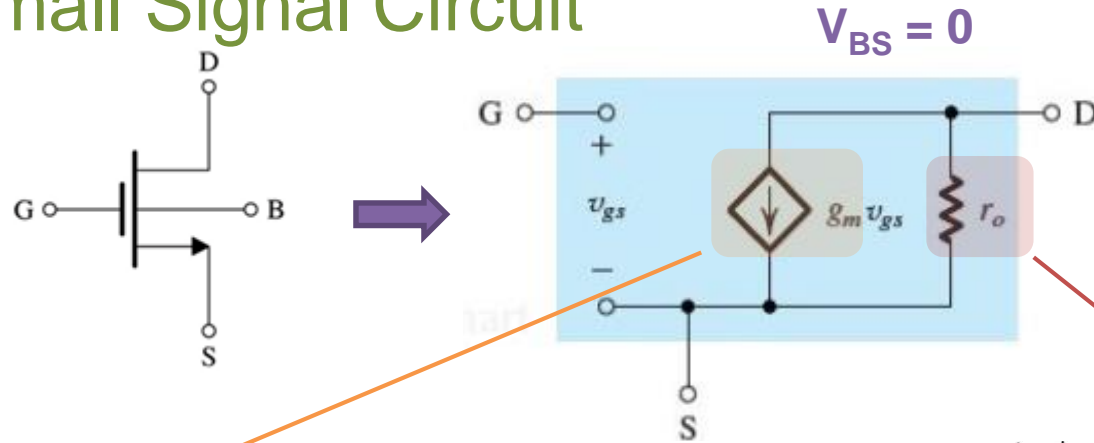- Trans-conductance (g_m)
- Output Impedance (r_o)
- Input Impedance




Small Signal Parameters

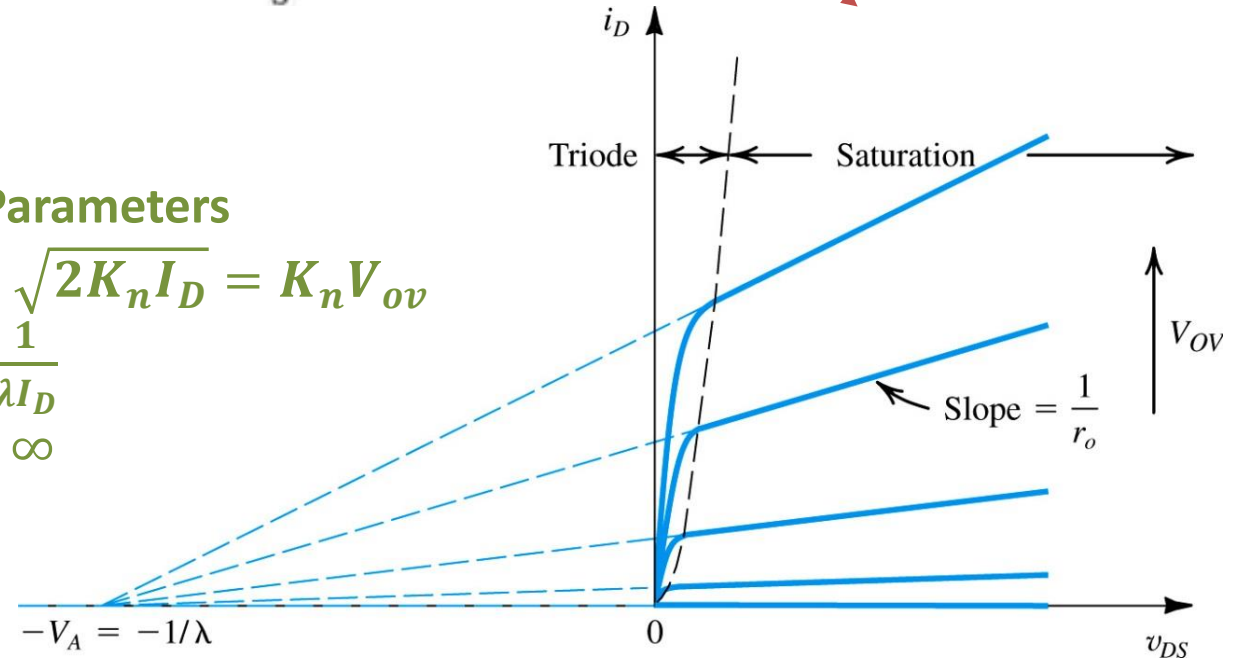
- $g_m = \sqrt{2K_n I_D} = K_n V_{ov}$
- $r_o = \frac{1}{\lambda I_D}$
- $r_{in} = \infty$




Basic MOSFETs Amplifier Configuration

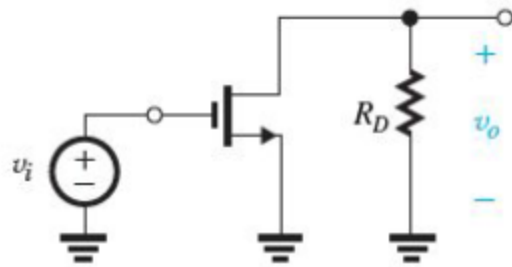

(a) Common Source (CS)

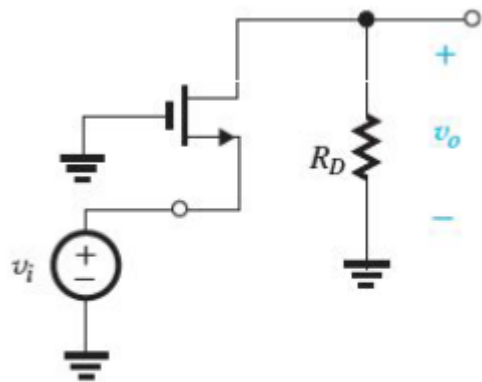

(b) Common Gate (CG)

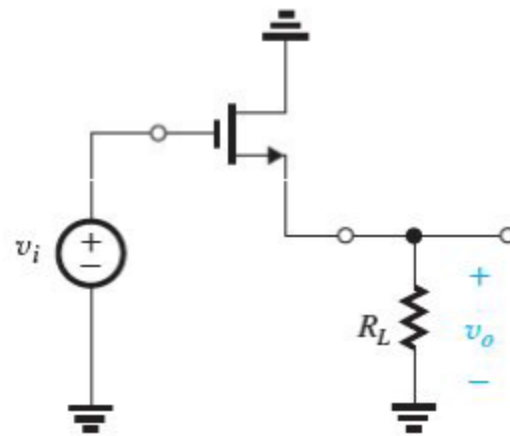


(c) Common Drain (CD)

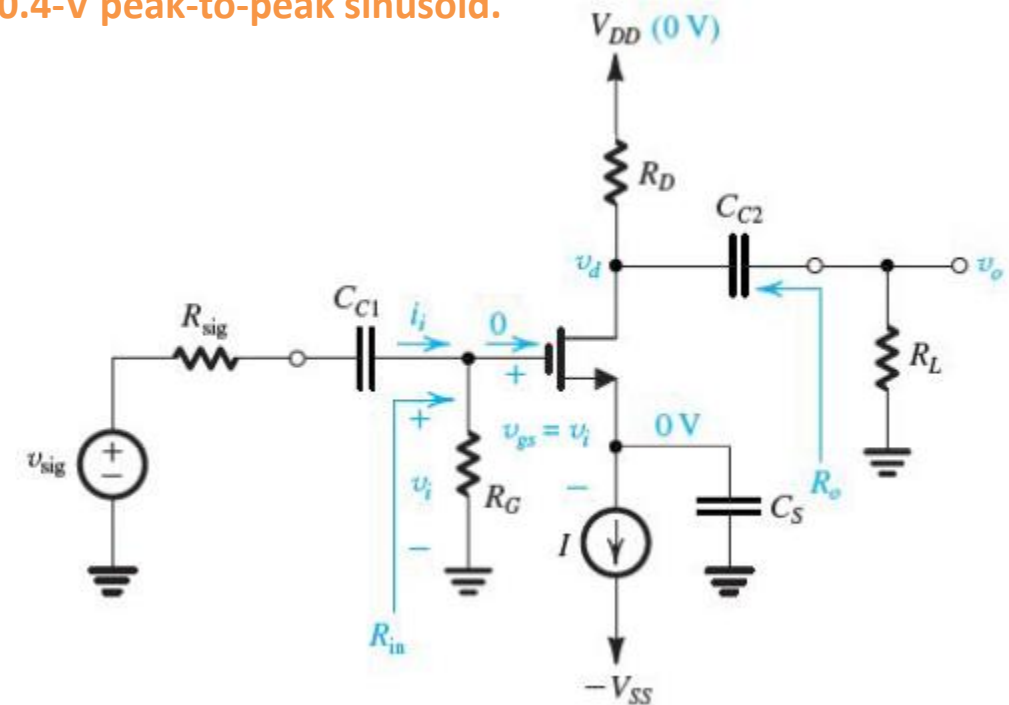Exercise 5.38

Consider the given common source amplifier with $g_m=1\text{mA/V}$, $r_o=150\text{k}\Omega$, $R_{\text{sig}}=100\text{k}\Omega$, and $R_L=15\text{k}\Omega$.

- Calculate R_{in} , $A_{v_cs}=V_o/V_i$, and R_o , both without and with r_o taken into account
- Calculate the overall voltage gain $G_v=v_o/v_{\text{sig}}$, with r_o taken into account
- Determine output signal v_o if v_{sig} is a 0.4-V peak-to-peak sinusoid.




Problem

An common source NMOS amplifier is to be designed to provide a 0.5V peak output signal across a 50k Ω load that can be used as a drain resistor. If a gain of at least -5V/V is needed, what g_m is required? Using a dc supply of 1.8V, what values of I_d and V_{ov} would you choose? What W/L ratio is required if $k_n' = 200\mu\text{A}/\text{V}^2$? If $V_t = 0.4\text{V}$, find V_{gs} .

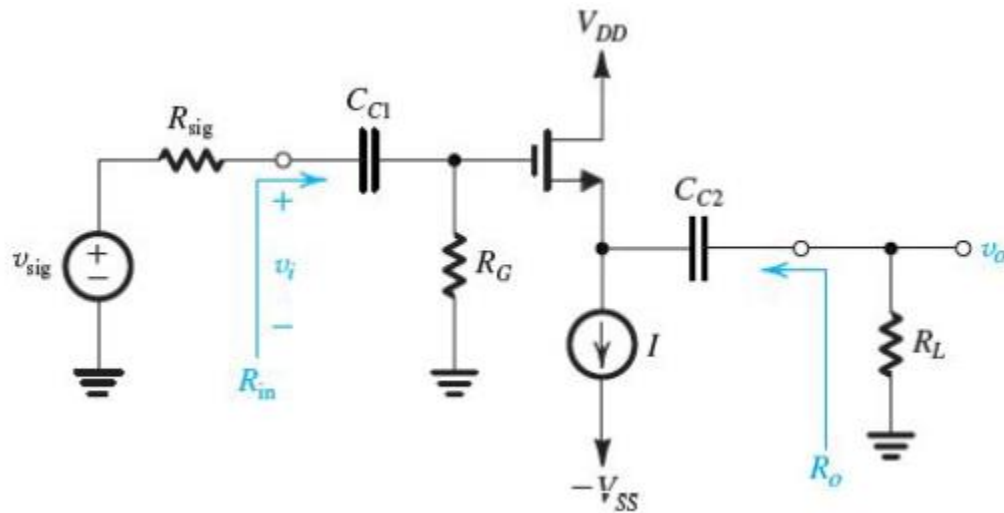Exercise 5.41

Consider the given common collector amplifier with $g_m = 1\text{mA/V}$ and $r_o = 150\text{k}\Omega$. Let $R_{\text{sig}} = 1\text{M}\Omega$, $R_G = 1\text{M}\Omega$, and $R_L = 15\text{k}\Omega$,

- Find R_{in} , $A_v = v_o/v_i$, and R_o without and with r_o taken into account.
- Find the overall voltage gain $G_v = v_o/v_{\text{sig}}$ with r_o taken into account,



Problem

Design the given circuit so that the transistor operates in saturation with V_{DS} biased 1V from the edge of the triode region, with $I_D=1\text{mA}$ and $V_D=3\text{V}$, for each of the following two devices (use a $10\mu\text{A}$ current in the voltage divider):

a) $|V_t|=1\text{V}$ and $K_p=0.5\text{mA/V}^2$

b) $|V_t|=2\text{V}$ and $K_p=1.25\text{mA/V}^2$

For each case, specify the values of V_G , V_D , V_S , R_1 , R_2 , R_S , and R_D .

