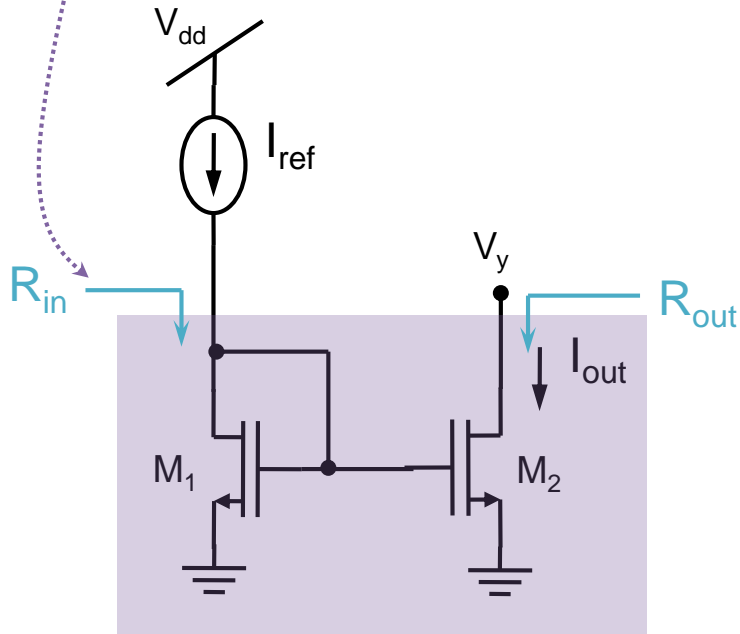


# Last Lecture → Current Mirrors

## - MOS Based



$$(W/L)_2 = N \cdot (W/L)_1$$

\* Remember  $I_D = \frac{K_n' W}{2 L} (V_{GS} - V_{th})^2 (1 + \lambda V_{DS})$

\* Assume  $\left. \begin{matrix} \mu_{01} = \mu_{02} \\ V_{th1} = V_{th2} \end{matrix} \right\} \text{M}_1 \text{ \& M}_2 \text{ matched transistors!}$

### DC Behavior

$$\frac{I_{out}}{I_{ref}} = \frac{(W/L)_2}{(W/L)_1} \frac{(1 + \lambda V_{ds2})}{(1 + \lambda V_{ds1})}$$

Gain error due to channel length modulation!

$\lambda = 0$

$$\frac{I_{out}}{I_{ref}} \approx \frac{(W/L)_2}{(W/L)_1} = N$$

### AC Behavior


$$R_{in} = \frac{1}{g_{m1}}$$

$$R_{out} = r_{o2}$$

$$A_i \approx \frac{(W/L)_2}{(W/L)_1}$$

# Last Lecture → Current Mirrors

- BJT Based
- $\beta$  Compensation

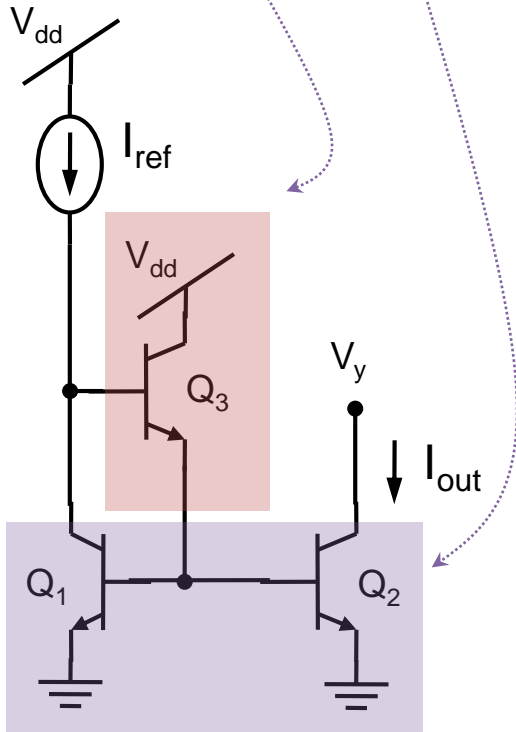

$$A_{E2} = N \cdot A_{E1}$$


## DC Behavior

$$\frac{I_{out}}{I_{ref}} = N \frac{1}{\left(1 + \frac{N+1}{\beta(\beta+1)}\right)}$$

Beta effective is much larger!


$$\beta = \infty \rightarrow \frac{I_{out}}{I_{ref}} \approx \frac{A_{E2}}{A_{E1}} = N$$

## Comparison

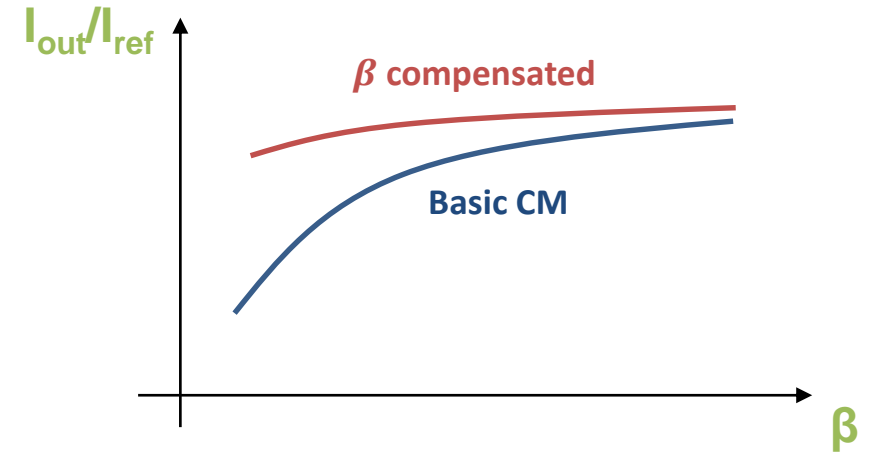


# Cascode Current Mirror

\* Assume matched transistors!

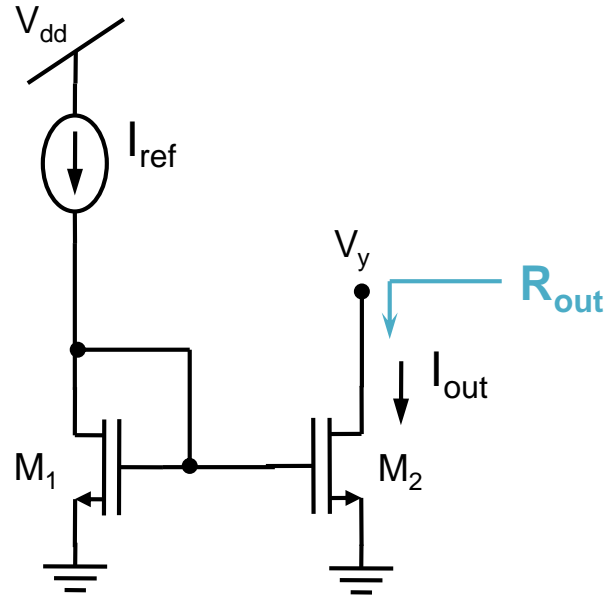
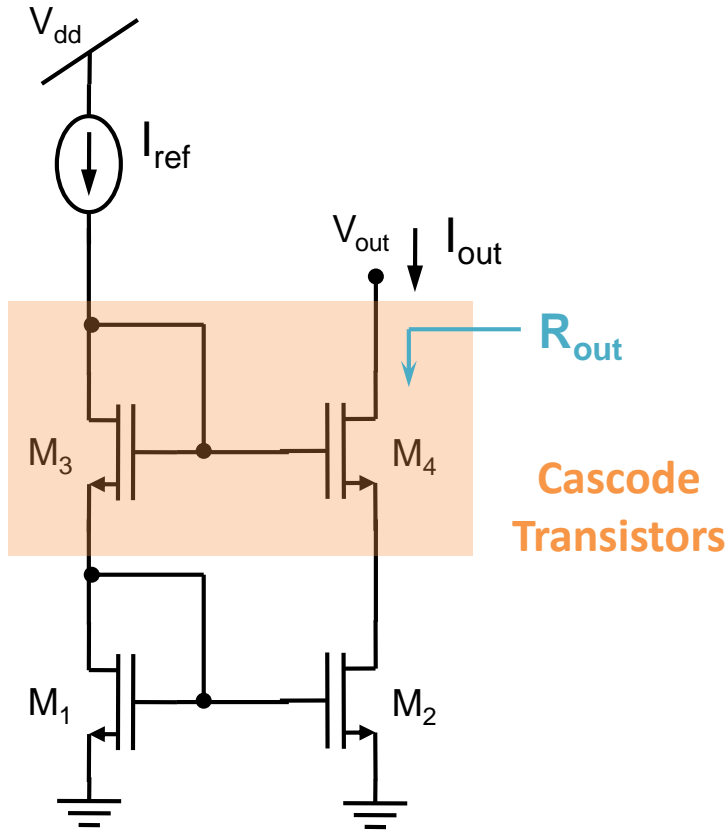
$$\frac{I_{out}}{I_{ref}} = \frac{(W/L)_2 (1 + \lambda V_{ds2})}{(W/L)_1 (1 + \lambda V_{ds1})}$$



$$(W/L)_2 = N \cdot (W/L)_1$$

$$(W/L)_4 = N \cdot (W/L)_3$$

## DC Behavior

$$V_{GS3} = V_{GS4}$$

$$\therefore V_{DS1} = V_{DS2}$$


$$\therefore \frac{I_{out}}{I_{ref}} = \frac{(W/L)_2}{(W/L)_1}$$

## AC Behavior


$$R_{in} = \frac{1}{g_{m1}} + \frac{1}{g_{m3}}$$

$$R_{out} = r_{o4}(1 + g_{m4}r_{o2})$$


# nMOS Current Mirrors

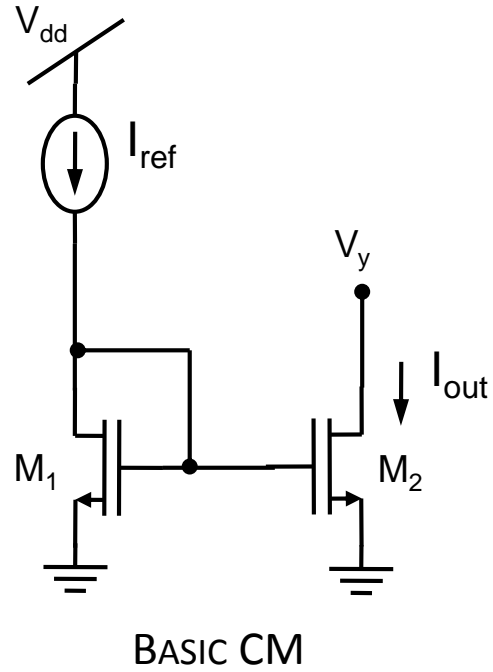
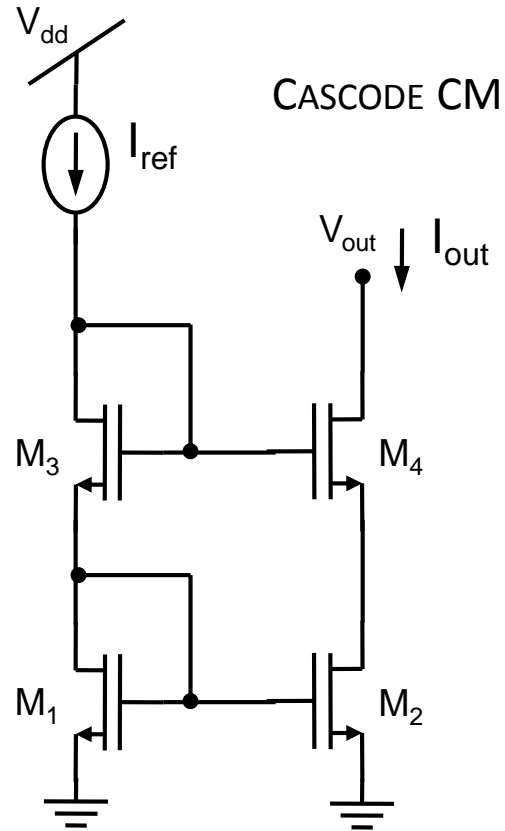
$$\frac{I_{out}}{I_{ref}} = \frac{W_2/L_2}{W_1/L_1} \frac{(1 + \lambda V_y)}{(1 + \lambda V_x)}$$


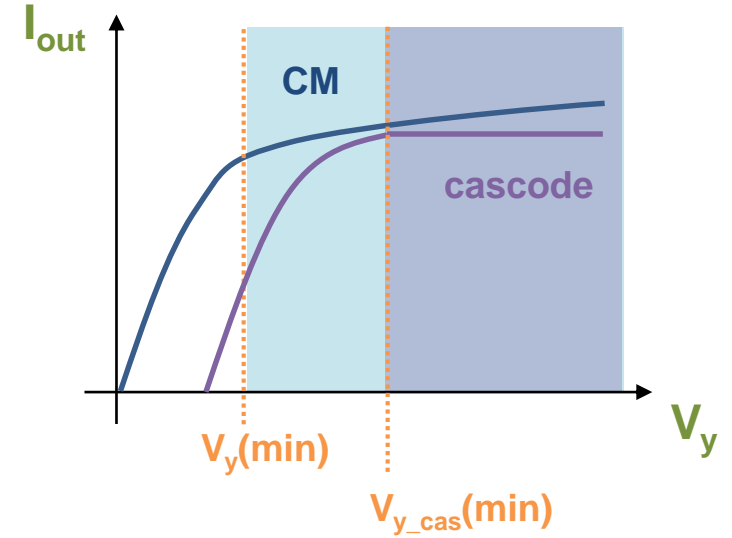
$$\frac{I_{out}}{I_{ref}} = \frac{W_2/L_2}{W_1/L_1}$$




$$R_{out} = r_{o2}$$

$$R_{out} = r_{o4}(1 + g_{m4}r_{o2})$$

## Problem P7.60

For the circuit below, assuming matched transistors,  $|V_{be}| = 0.7$  and  $\beta = \infty$ , find  $I$ ,  $V_1$ ,  $V_2$ ,  $V_3$ ,  $V_4$ , and  $V_5$  for

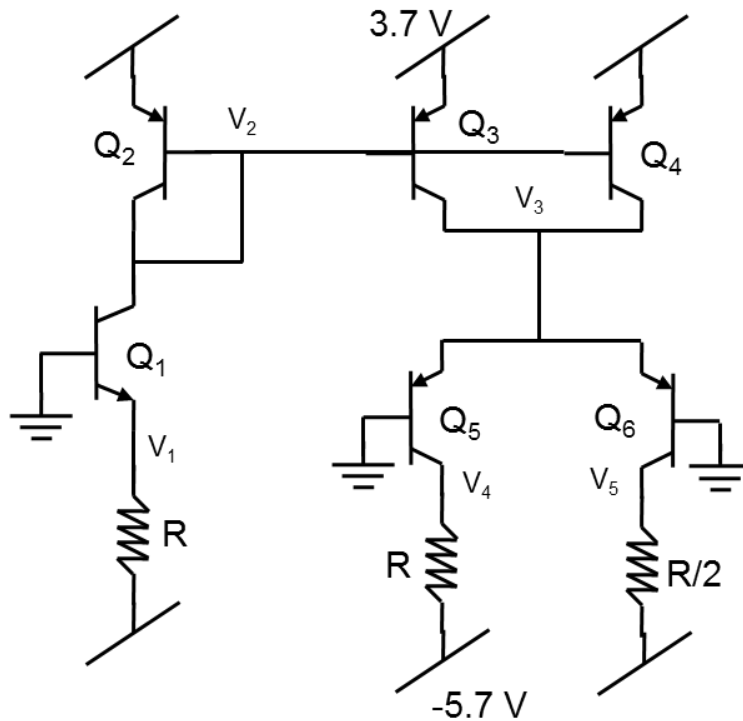- $R = 10\text{k}\Omega$
- $R = 100\text{k}\Omega$ .



## Problem P7.71

For the circuit below, assuming all transistors to be matched with current gain  $\beta$ ,

- Assuming  $\beta = \infty$  find  $I_{01}$  and  $I_{02}$  in terms of  $I_{ref}$
- Use this idea to design a circuit that generates currents of 0.1mA, 0.2mA, and 0.4mA, using a reference current source of 0.7mA.
- What are the actual values of the current generated for  $\beta = 50$ ?

