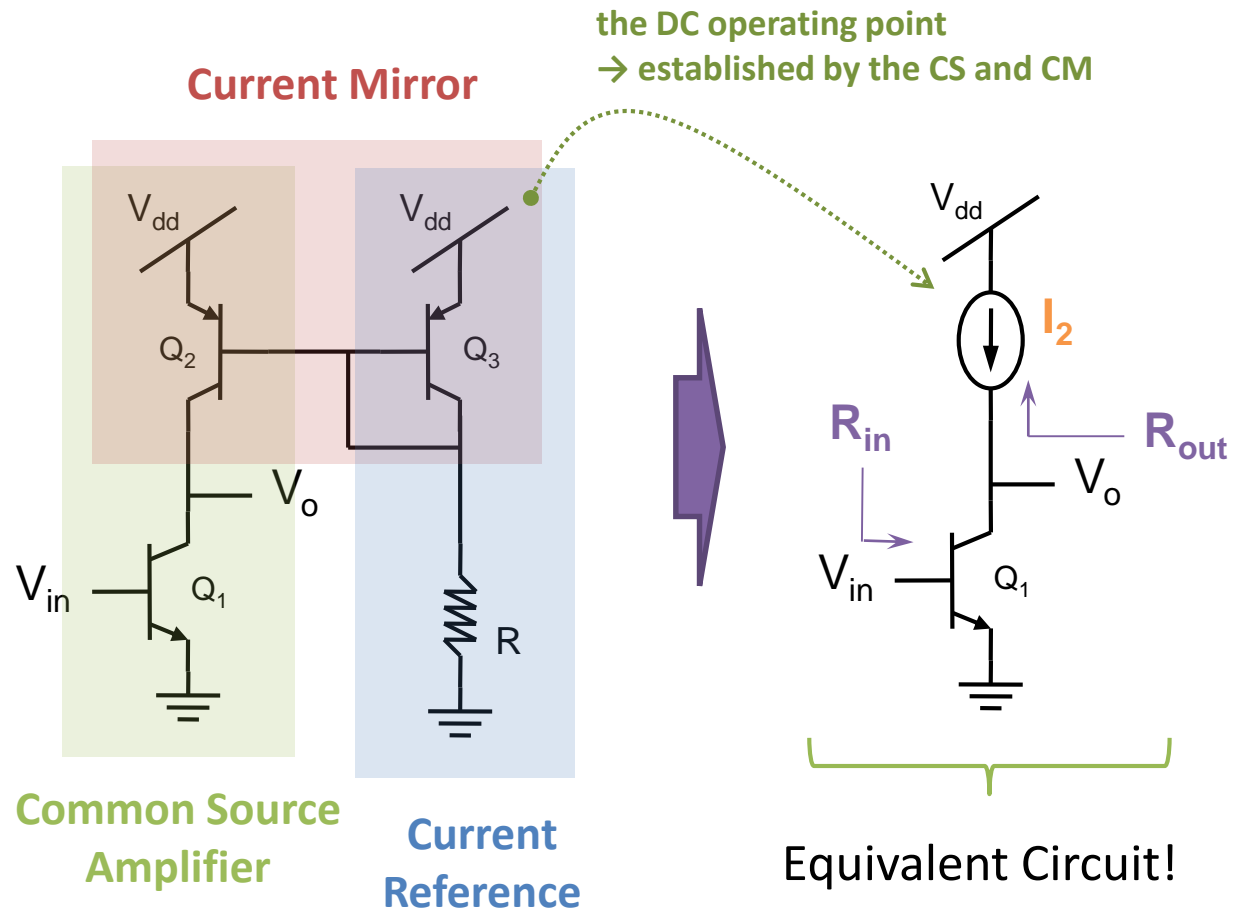


Amplifier with Active Load



- DC Behavior

$$I_R = I_3 = ?$$

$$I_2 = ?$$


- AC Behavior

$$A_v = V_o / V_{in} = ?$$

$$R_{in} = ?$$

$$R_{out} = ?$$

Differential Amplifiers

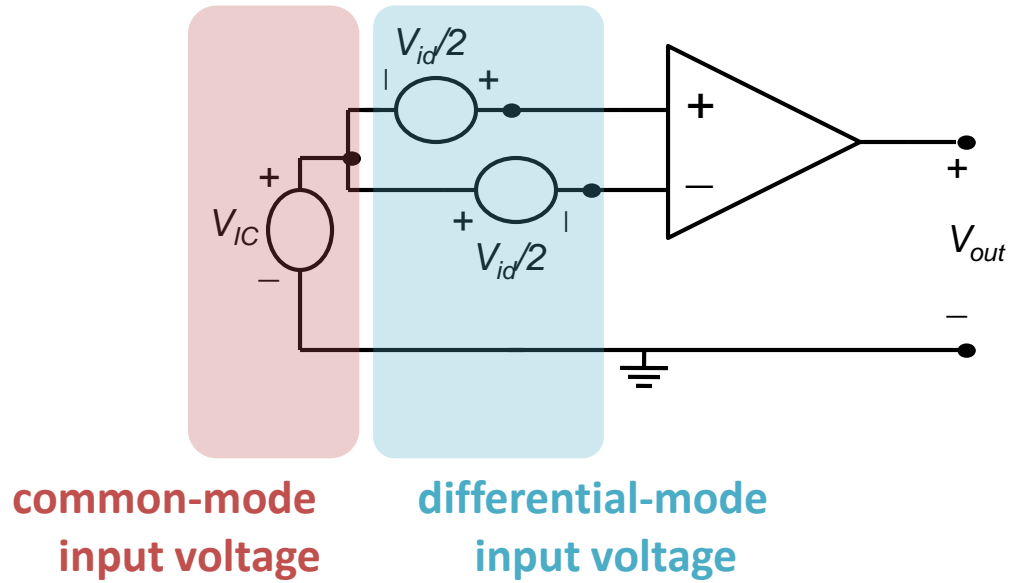

Analysis:

- Common-mode → small signal
- Differential-mode → large signal & small signal

$$V_{out} = A_{vd} v_{id} \pm A_{vc} v_{ic}$$


$A_{vd}(\text{ideal}) = \infty$
 A_{vd} – Differential Mode Gain
 • $V_+ = -V_- \rightarrow$ small signal
 A_{vc} – Common Mode Gain
 • $V_+ = V_- \rightarrow$ small signal
 $A_{vc}(\text{ideal}) = 0$

CMRR – Common Mode Rejection Ratio

$$CMRR = 20 \log \left(\frac{A_{vd}}{A_{vc}} \right)$$

Differential Pair → Chp #8

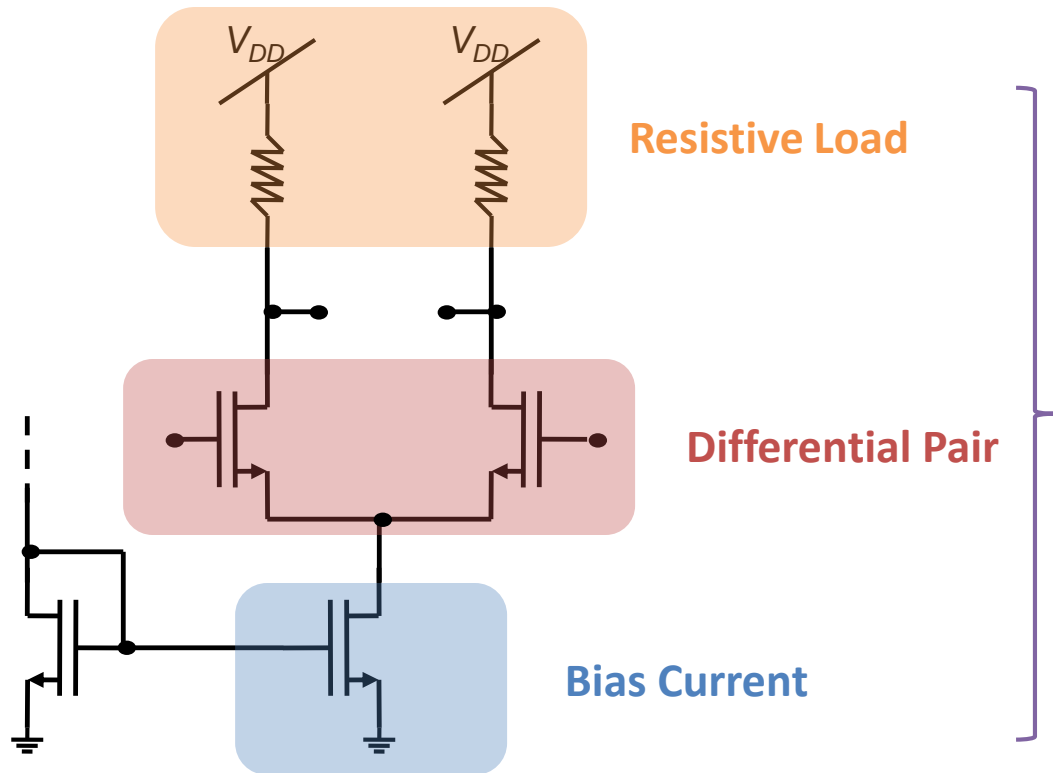
- Converts the differential input signal into a differential current
- Input stage to almost every amplifier architecture



Amplifier Analysis


- DC Behavior ?
 - Common Mode
- AC Behavior
 - Common Mode
 - Differential Mode

Differential Pair Behavior

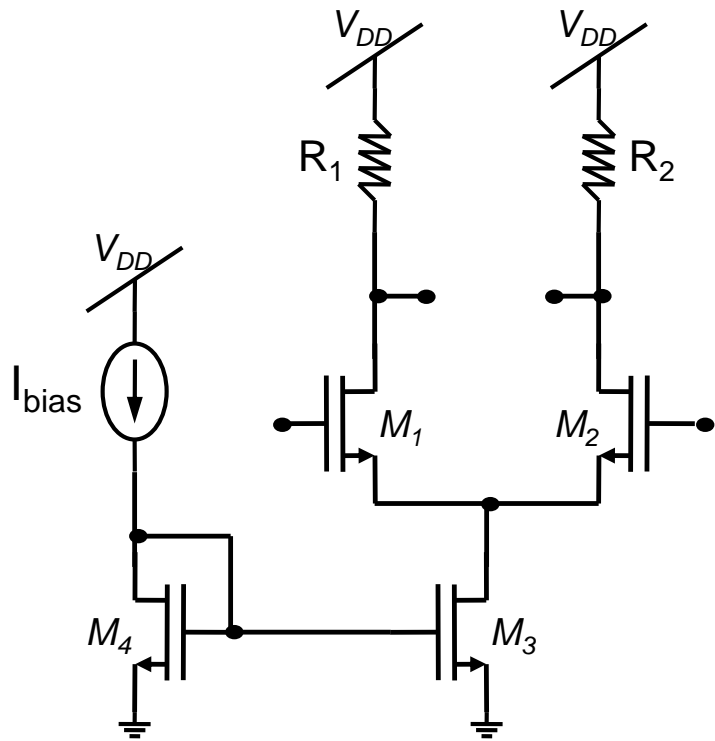


Assume circuit is symmetric with matched parameters

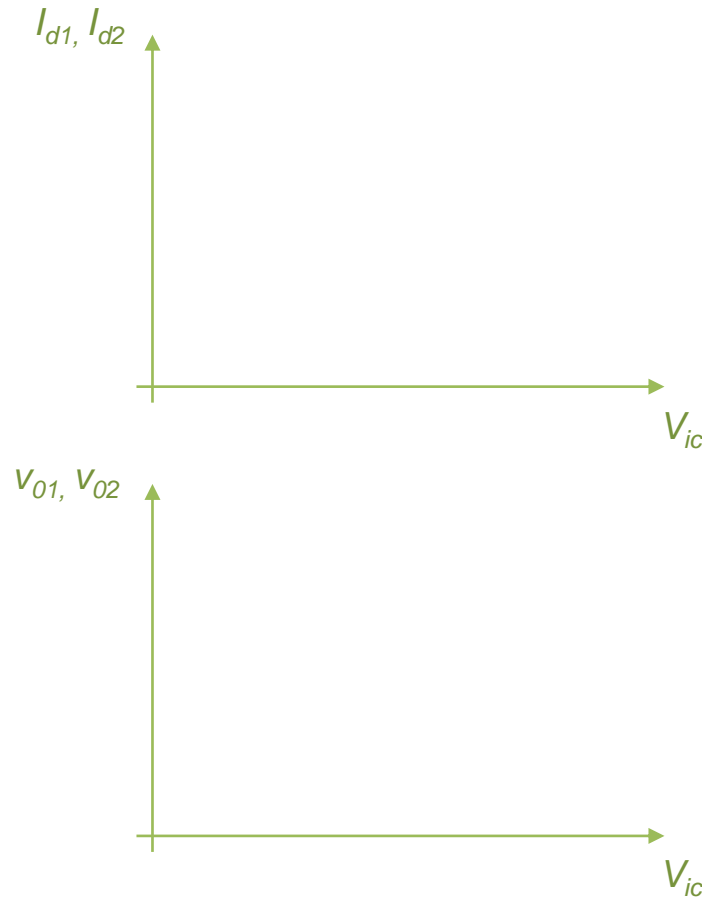
Common-Mode Behavior
 $V_1 = V_2 = V_{ic}$



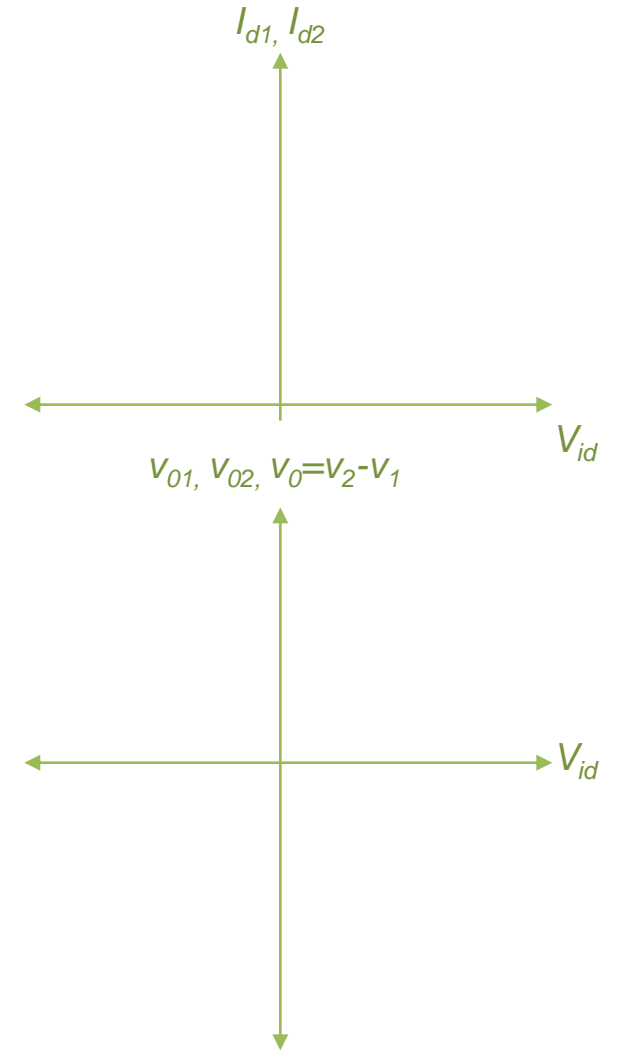
Differential-Mode Behavior
 $V_1 = -V_2 = V_{id}/2$




Diff. Pair → Small Signal Analysis

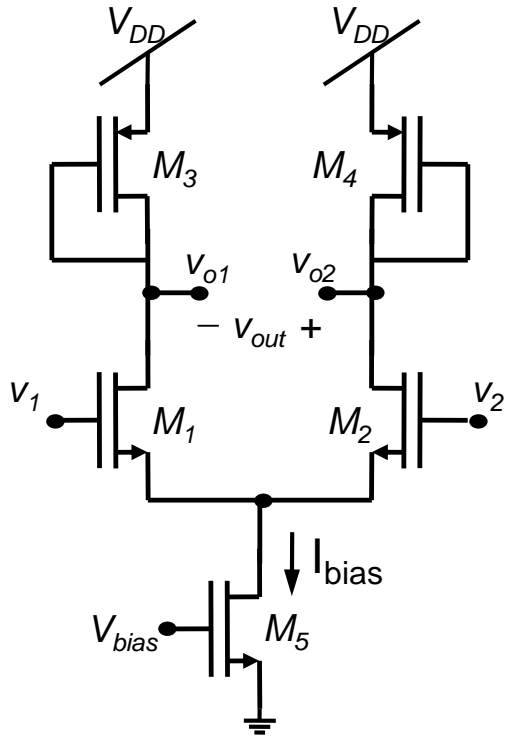

Differential-Mode Circuit

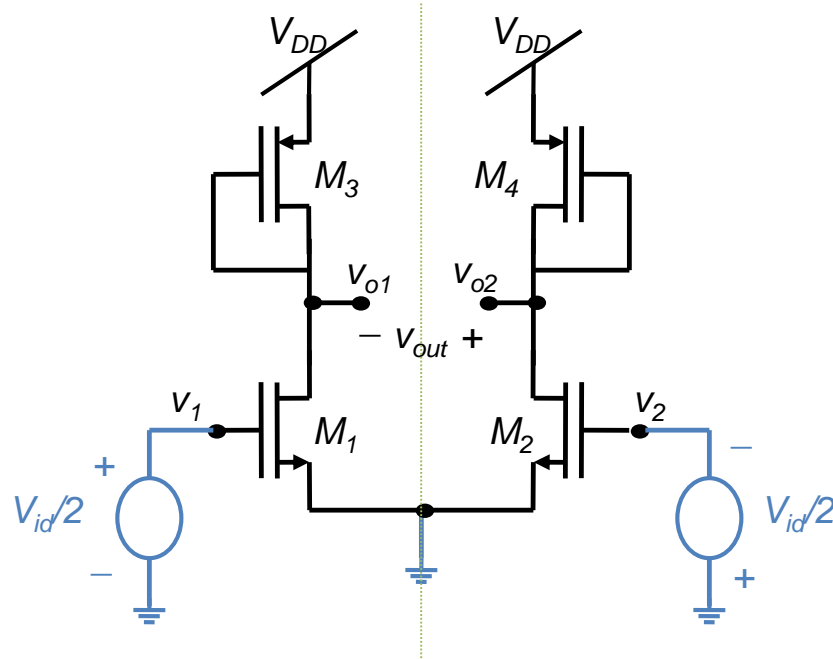

Common-Mode Circuit

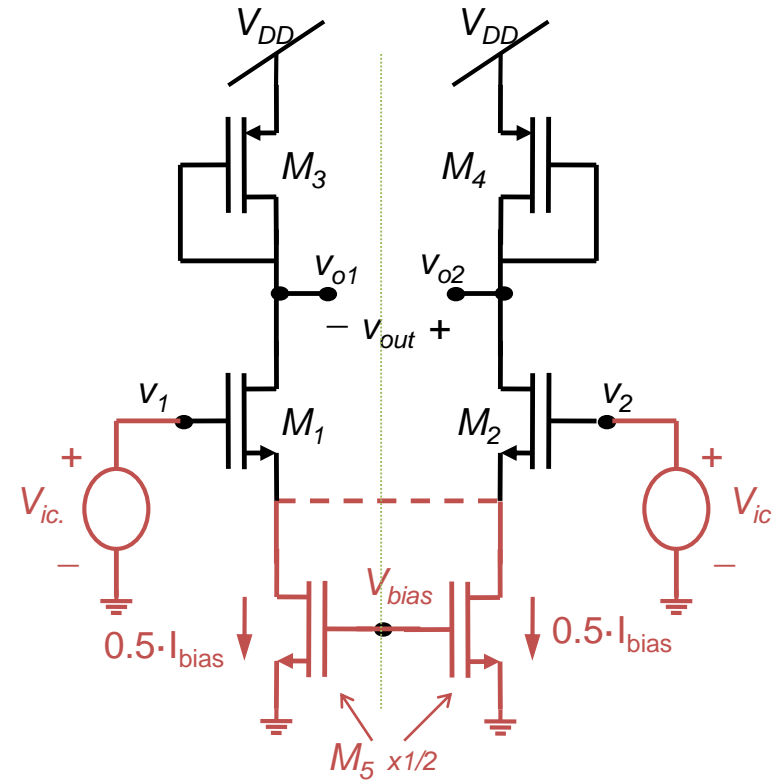


1. Draw symmetric circuit
2. Point in the line of symmetry are equivalent to an **short circuit / open circuit**
3. Analyze half circuit

$$A_{vc} = \frac{V_{o2} - V_{o1}}{V_{ic}} = ?$$

$$A_{vd} = \frac{V_{o2} - V_{o1}}{V_{id}} = ?$$

Differential Pair

→ with current source load

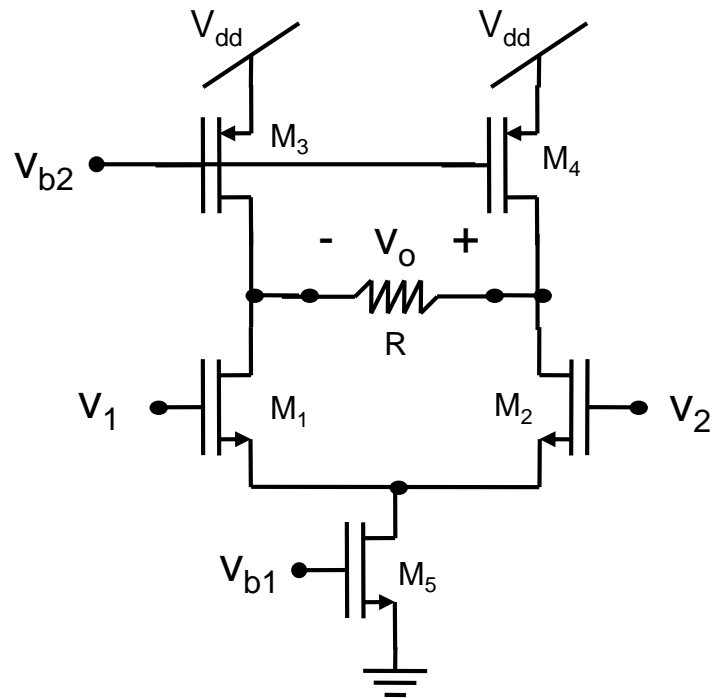

Find the expression for:

- $A_{id} = ?$
- $A_{cm} = ?$

Assume:

- circuit is symmetric with matched parameters
- V_{b1} and V_{b2} are DC voltages