


Problem – D8.120

For the circuit below assume all transistors have $|V_{BE}|=0.7\text{V}$, $V_A=200\text{V}$, and $\beta=100$.

a) Perform a bias calculation assuming $|V_{BE}| = 0.7\text{V}$, $V_A = \infty$, $\beta = \infty$, $v_+ = v_- = 0$ and v_o is stabilized by feedback to about 0V . Find R so that the reference current I_{ref} is $100\mu\text{A}$. What are the voltages at all the labeled nodes?


b) Provide the bias current in all transistors together with g_m and r_o .

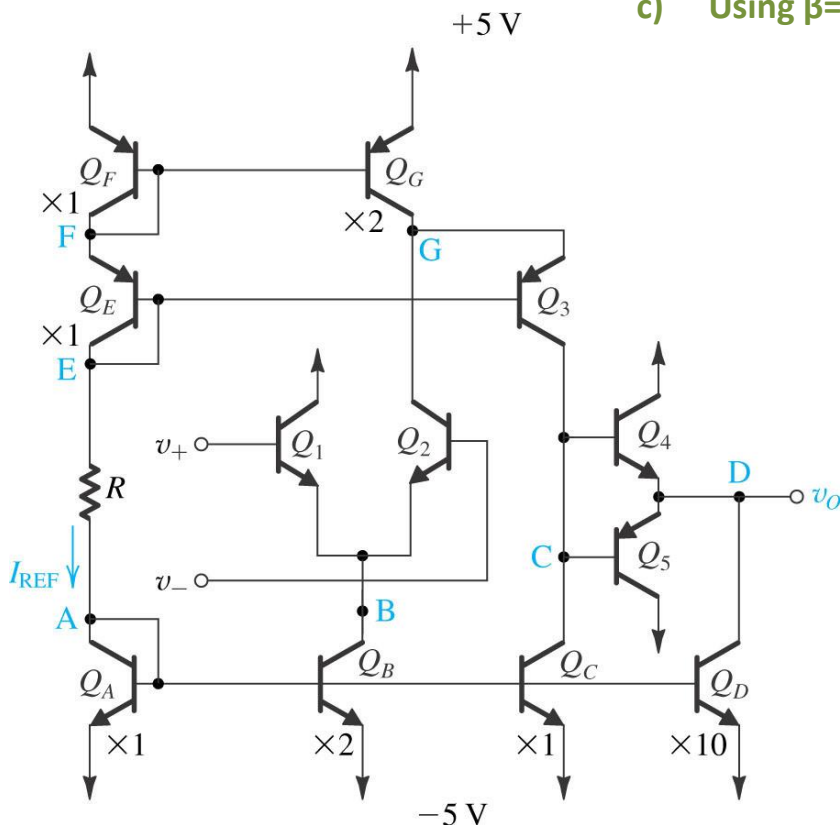c) Using $\beta=100$, find the voltage gain v_o/v_{id}




Small-Signal Gain


Bipolar

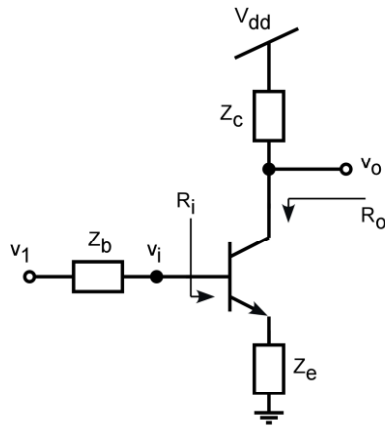

Common Emitter - CE

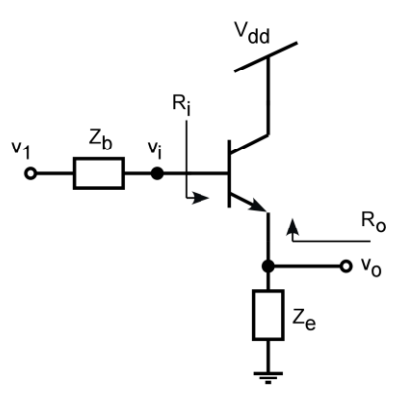

Common Collector - CC

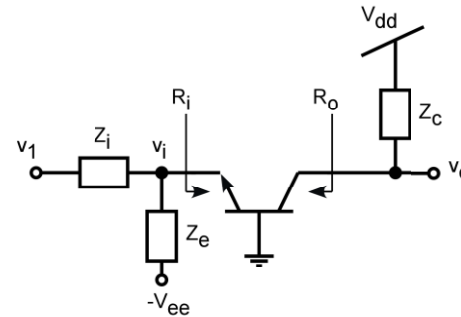


Common Base - CB

Single Transistor Bipolar Amplifier	Common-Emmitter CE	Common-Collector CC	Common-Base CB
Voltage Gain $A_v = \frac{v_o}{v_i}$	$\cong -\frac{g_m}{1 + g_m Z_e} \cdot R_o // Z_c$	$\cong +\frac{g_m}{1 + g_m Z_e} \cdot Z_e$	$= +g_m \cdot R_o // Z_c$
Input Resistance R_i	$= r_\pi (1 + g_m Z_e)$	$= r_\pi (1 + g_m Z_e)$	$\cong \frac{1}{g_m}$
Output Resistance R_o	$= r_o (1 + g_m Z_e)$	$\cong \frac{1}{g_m} + \frac{Z_b}{\beta_o + 1}$	$= r_o [1 + g_m (Z_i // Z_e)]$

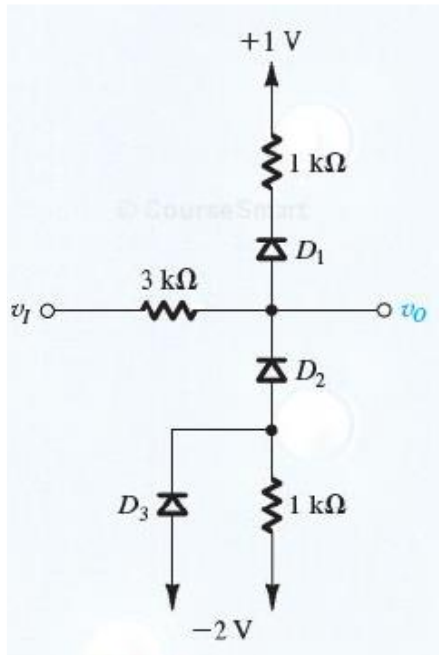
Problem – 4.93

Sketch and label the voltage transfer characteristic v_o versus v_i of the circuit provided below over a $\pm 10\text{-V}$ range of input signals. Assume a constant voltage drop of 0.7V for all diodes. What are the slopes of the characteristic at the extreme $\pm 10\text{-V}$ levels?



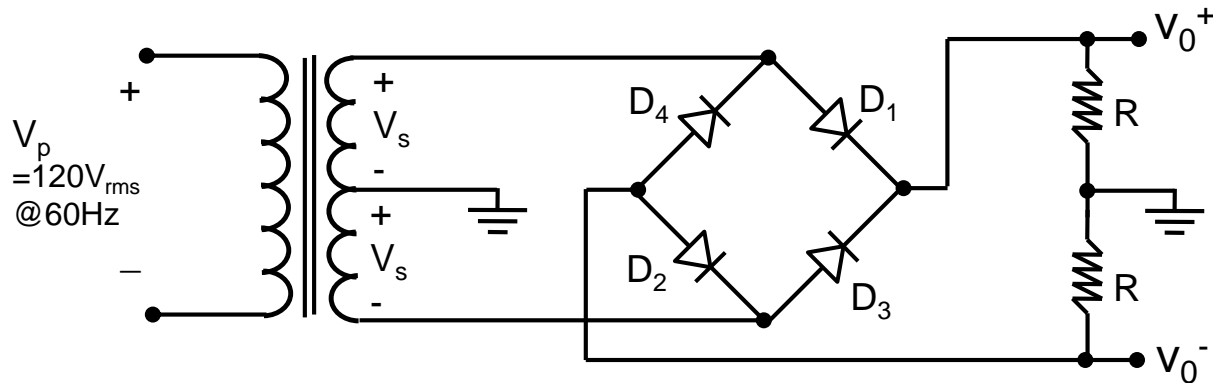Problem – D4.82

Consider the circuit below with two equal filter capacitors placed across the load resistors R . Assume that the diodes available exhibit a 0.7-V drop when conducting. Design the circuit to provide $\pm 15V$ dc output voltages with a peak-to-peak ripple no greater than 1V. Each supply should be capable of providing 200mA dc current to its load resistor R . Completely specify the capacitors, diodes and the transformer.



Capacitor: _____ mF _____ volts

Diodes- DC current rating: _____ A Breakdown voltage: _____ Volts

I surge: _____ A Peak current: _____ A

Transformer- Prim/sec: _____ / _____

Rectifiers

- **Half-Wave Sine ($T=0 \rightarrow \pi$)**

$$\overline{V_0} = 2 \frac{V_{peak}}{\pi}$$

- **Half-Wave (filtered)**

$$V_r = \frac{V_S}{fCR} \approx \frac{I_L}{fC}$$

$$\Delta\theta \approx \sqrt{2V_r/V_S}$$

$$i_{Davg} = I_L \left(1 + \pi\sqrt{2V_S/V_r} \right)$$

$$i_{Dmax} = I_L \left(1 + 2\pi\sqrt{2V_S/V_r} \right)$$

- **Full-Wave (filtered)**

$$V_r = \frac{V_S}{2fCR} \approx \frac{I_L}{2fC}$$

$$\Delta\theta \approx \sqrt{2V_r/V_S}$$

$$i_{Davg} = I_L \left(1 + \pi\sqrt{V_S/2V_r} \right)$$

$$i_{Dmax} = I_L \left(1 + 2\pi\sqrt{V_S/2V_r} \right)$$