

1. Mencione 4 razones por que estudiantes de otras ingenierías necesitan aprender los fundamentos de la ingeniería eléctrica.

1. para revalida
2. para trabajo en equipo
3. para comunicarse bien con otros
4. para poder evaluar a otros bien
5. para que no los engañen

3. Con un amperímetro mides la corriente que fluye por un cable y lees -5A. ¿Qué significa el signo negativo? ¿Cuánta carga fluye por una sección transversal del cable en 3 segundos?



El negativo significa que los contactos se pusieron al revés

$$I = \frac{\Delta Q}{\Delta t} \Rightarrow \Delta Q = I \Delta t$$
$$= (5A)(3s) = 15C$$
$$=$$

$$\Delta Q = 15C$$

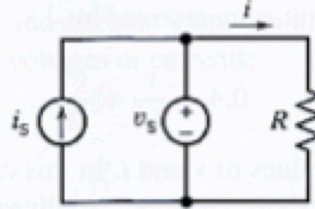


FIGURE P 2.5-1

P2.5-1 A current source and a voltage source are connected in parallel with a resistor as shown in Figure P2.5-1. All of the elements connected in parallel have

the same voltage, v_s in this circuit. Suppose that $v_s = 15\text{ V}$, $i_s = 3\text{ A}$, and $R = 5\ \Omega$.

(a) Calculate the current i in the resistor and the power absorbed by the resistor.

(b) Change the current source current to $i_s = 5\text{ A}$ and recalculate the current, i , in the resistor and the power absorbed by the resistor.


$$V = IR \quad \text{Ley de Ohm}$$

$$a) \quad i = \frac{v_s}{R} = \frac{15\text{V}}{5\Omega} = 3\text{A}$$

$$P_R = v_s i = (15\text{V})(3\text{A}) = 45\text{W}$$

$$P_{v_s} = v_s(0) = 0\text{W}$$
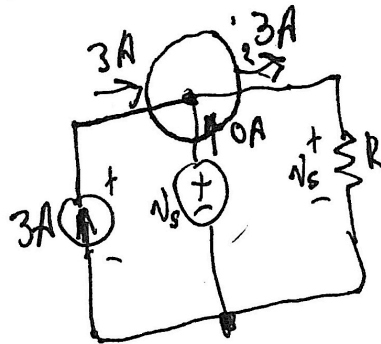
$$P_{i_s} = -(15\text{V})(3\text{A}) = -45\text{W}$$



formula no cambia


formula no cambia

$$b) \quad i = \frac{v_s}{R} = \frac{15\text{V}}{5\Omega} = 3\text{A}$$

$$P_R = v_s i = (15\text{V})(3\text{A}) = 45\text{W}$$


$$P_{v_s} = v_s(2\text{A}) = 15(2) = 30\text{W}$$
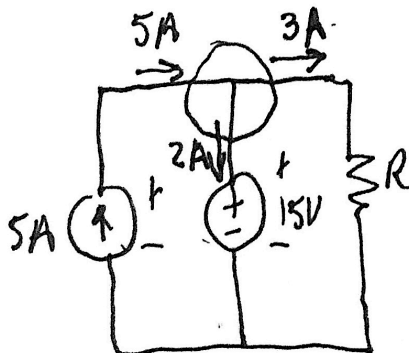
$$P_{i_s} = (15\text{V})(-5) = -75\text{W}$$



Buscamos las potencias para las fuentes y vemos que cambio

FIGURE P 2.5-2

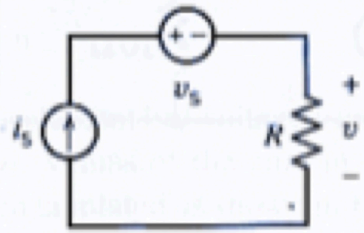

P2.5-2 A current source and a voltage source are connected in series with a resistor as shown in Figure P 2.5-2. All of the elements connected in series have the same current, i_s , in this circuit. Suppose that $v_s = 10 \text{ V}$, $i_s = 2 \text{ A}$, and $R = 5 \Omega$.

(a)

Calculate the voltage v across the resistor and the power absorbed by the resistor.

(b) Change the voltage source voltage to $v_s = 5 \text{ V}$ and recalculate the voltage, v , across the resistor and the power absorbed by the resistor.

$$a) \quad v = i_s R = (2 \text{ A})(5 \Omega) = 10 \text{ V} \quad , \quad P_R = v i_s = (10 \text{ V})(2 \text{ A}) = 20 \text{ W}$$

$$P_{v_s} = (10 \text{ V})(2 \text{ A}) = 20 \text{ W}$$

$$P_{i_s} = (10 \text{ V} + 10 \text{ V})(-2 \text{ A}) = -40 \text{ W}$$

formula no cambia


formula no cambia

$$b) \quad v = i_s R = 10 \text{ V} \quad , \quad P_R = v i_s = 20 \text{ W}$$

$$P_{v_s} = (5 \text{ V})(2 \text{ A}) = 10 \text{ W}$$

$$P_{i_s} = (5 + 10)(-2 \text{ A}) = -30 \text{ W}$$

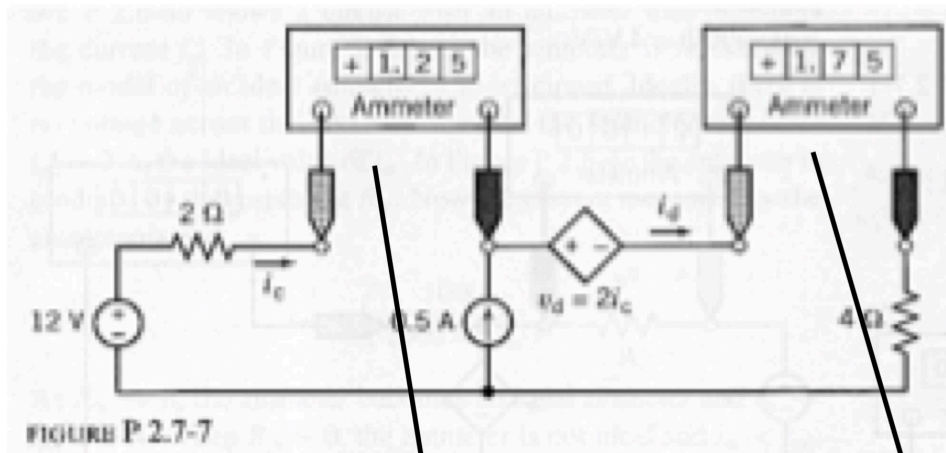
Buscamos las potencias para las fuentes
y vemos que cambio



P 2.7-7 Find the power absorbed by the CCVS in Figure P 2.7-7.

Sustituir valores
de las corrientes

entra por
el terminal positivo

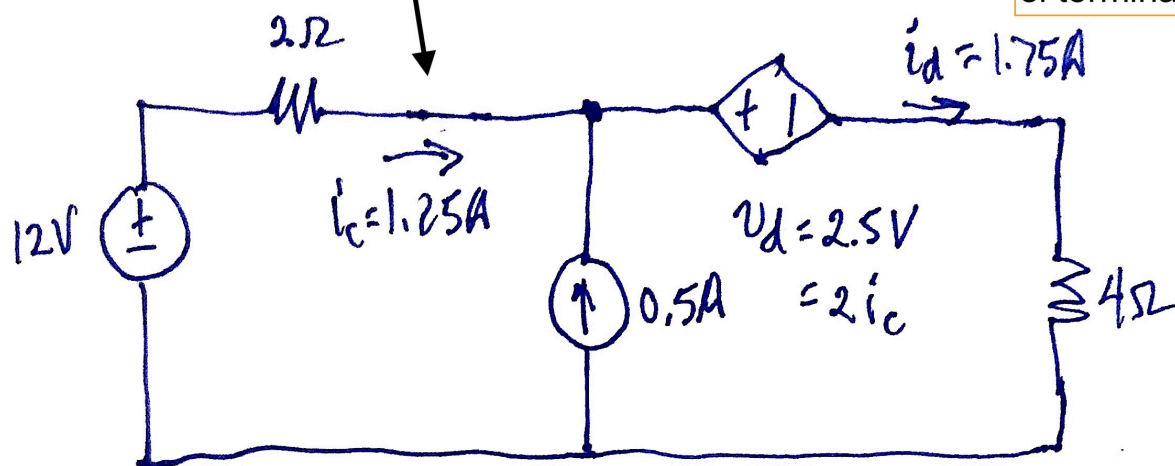

$$P_{v_d} = (2.5V)(1.75A) = 4.375W$$

cifras correctas son
las que menos
aparecen.

4.4
4.38

P2.34. The 9-V source in Figure P2.34 is delivering 27 W of power. All three resistors have the same value R . Find the value of R .

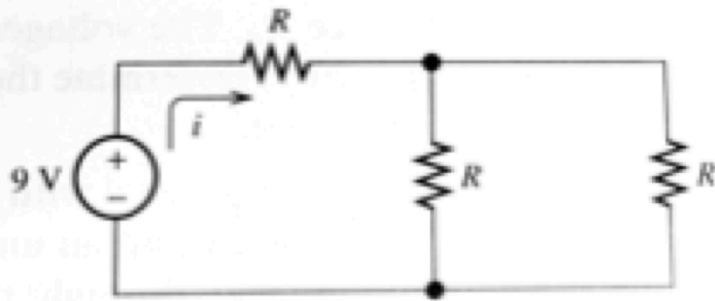



Figure P2.34

$$P = 27 \text{ W}$$

$$V = 9 \text{ V}$$

$$i = \frac{P}{V} = \frac{27 \text{ W}}{9 \text{ V}} = 3 \text{ A}$$

$$p = vi$$

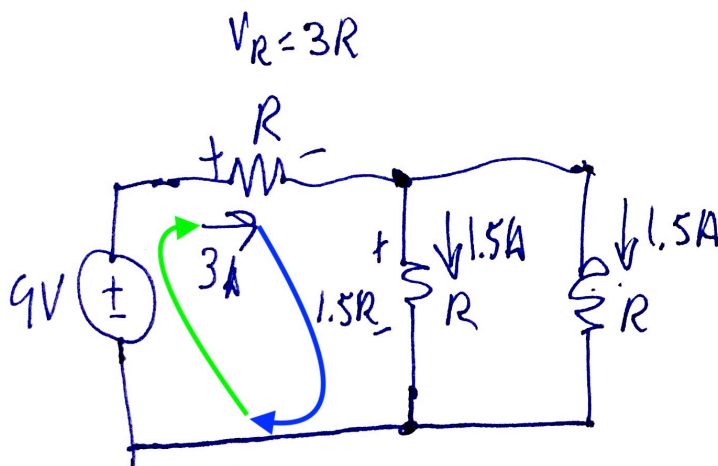

Voltajes

$$\underline{9 \text{ V}} = \underline{3R + 1.5R} = 4.5R$$

$$R = \frac{9 \text{ V}}{4.5} = 2 \Omega$$

Verificando usando
potencias da igual

Potencias $p = i^2 R$

$$27 \text{ W} = 9R + 2.25R(2) + 4.5R$$

$$27 = 13.5R$$

$$2R = R$$

*P2.47. Write equations and solve for the node voltages shown in Figure P2.47. Then, find the value of i_1 .

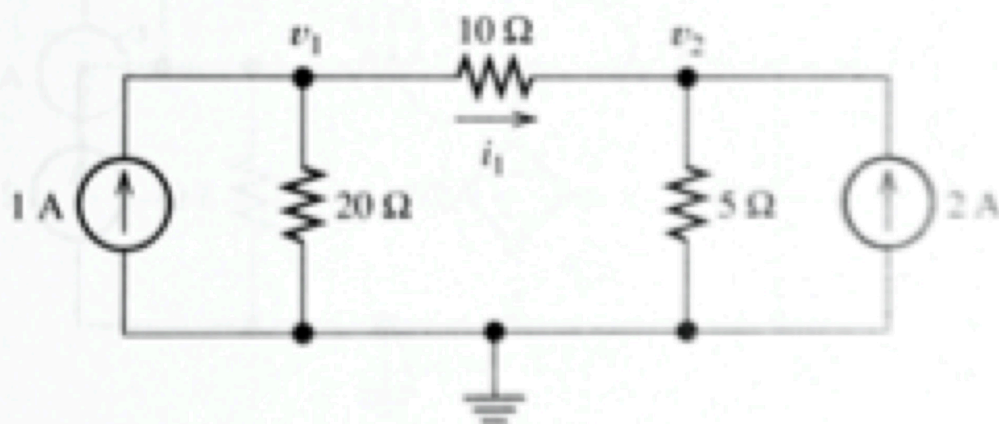


Figure P2.47

$$V_1: \quad 1 = V_1 \left(\frac{1}{20} + \frac{1}{10} \right) - V_2 \left(\frac{1}{10} \right)$$

$$V_2: \quad 2 = V_2 \left(\frac{1}{5} + \frac{1}{10} \right) - V_1 \left(\frac{1}{10} \right)$$

$$i_1 = \frac{V_1 - V_2}{10}$$

$$V_1 = 14.28 \text{ V}, \quad V_2 = 11.43 \text{ V}, \quad i_1 = 0.285 \text{ A}$$

P2.62. Solve for the power delivered by the voltage source in Figure P2.62, using the mesh-current method.

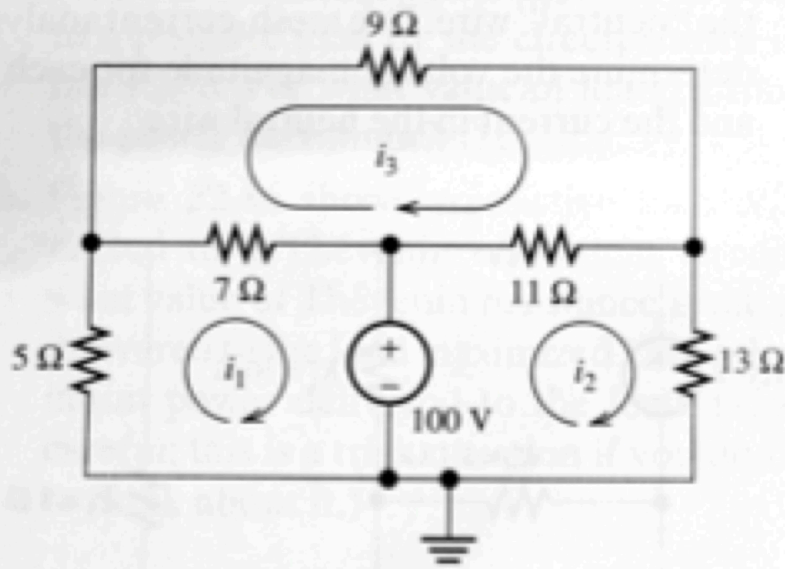


Figure P2.62

$$i_1: -100 = i_1(5+7) - i_3(7)$$

$$i_2: 100 = i_2(11+13) - i_3(11)$$

$$i_3: 0 = i_3(7+9+11) - i_1(7) - i_2(11)$$

$$P_{100V} = (100)(i_2 - i_1)$$

$$i_1 = -8.734A \quad i_2 = 3.847A \quad i_3 = -0.697A \quad P_{100V} = 1260W$$