
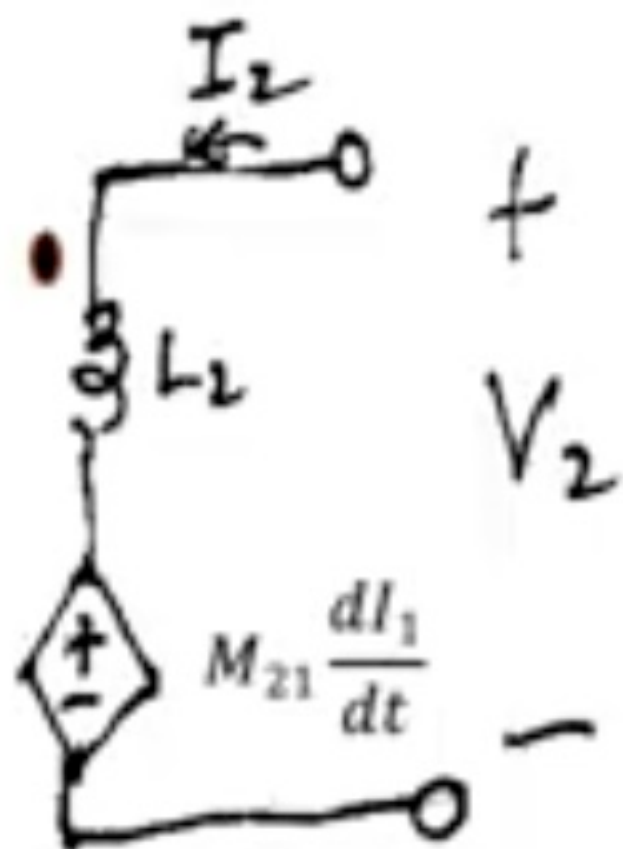


Inductancia mutua

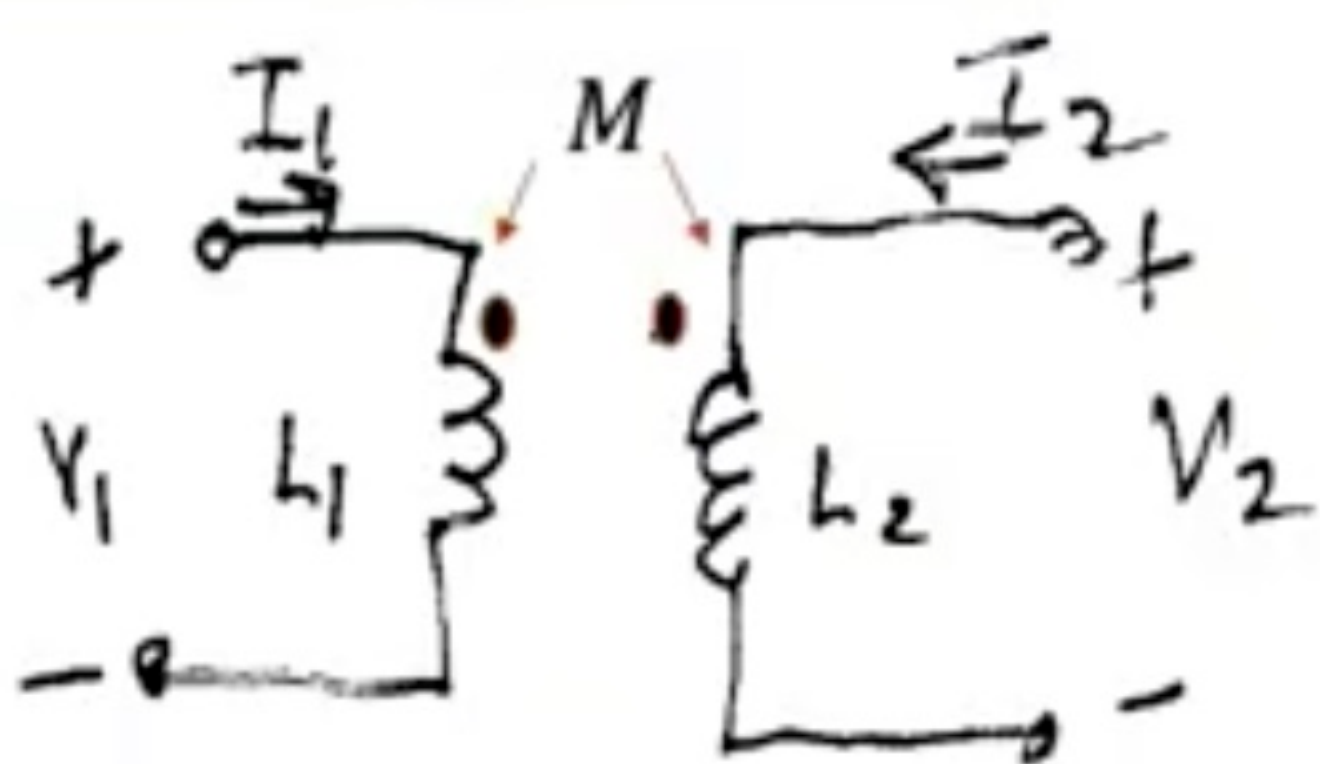




$$V_1 = L_1 \frac{dI_1}{dt} + M_{12} \frac{dI_2}{dt}$$

$$V_2 = L_2 \frac{dI_2}{dt} + M_{21} \frac{dI_1}{dt}$$

$$\text{Si } M_{12} \approx M_{21} = M = k\sqrt{L_1 L_2} \quad 0 \leq k \leq 1$$

Transformacion fasorial de inductores acoplados

PC4075_3_5

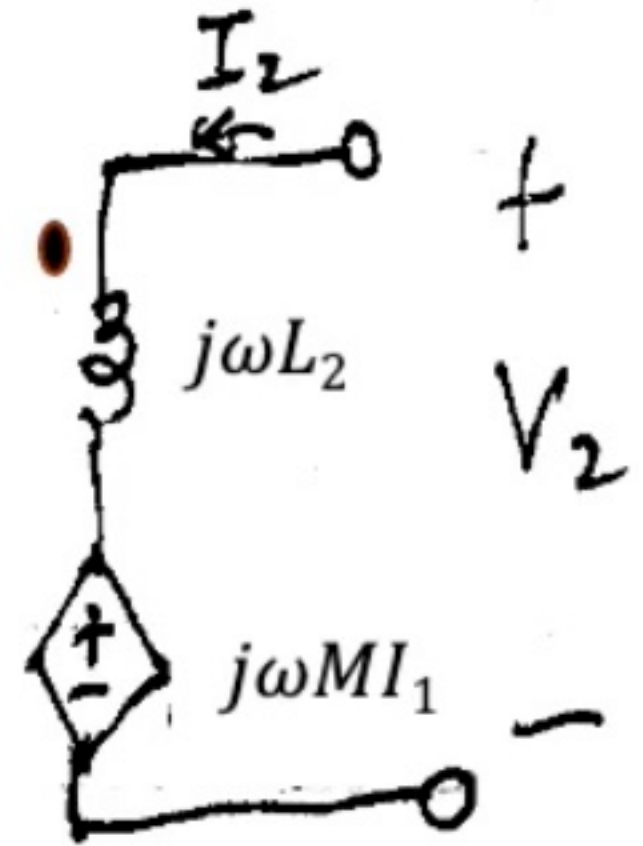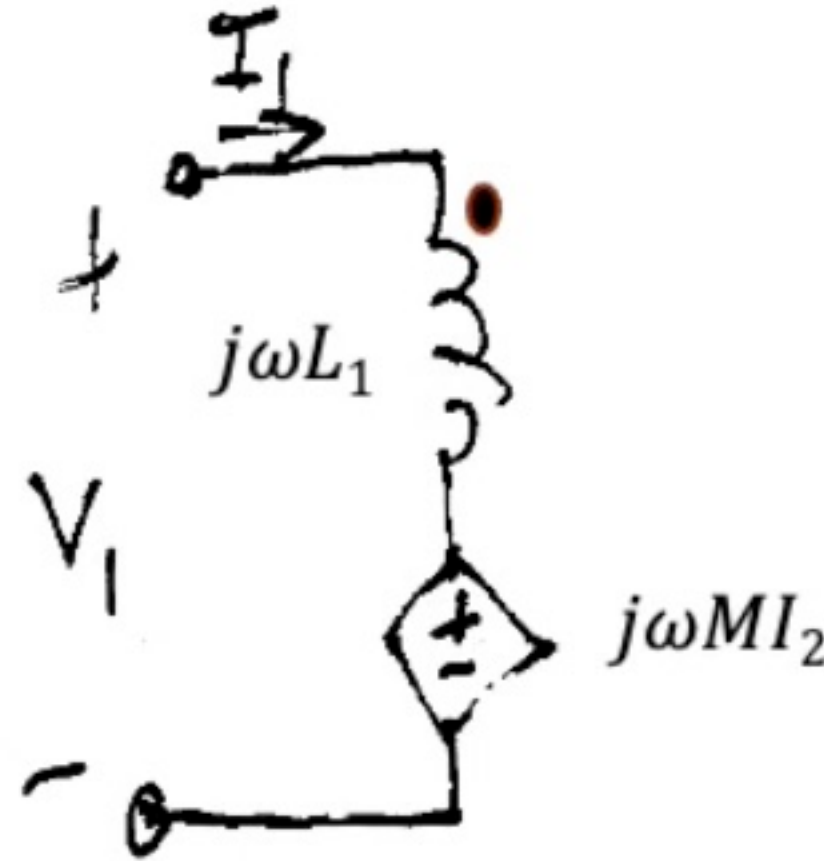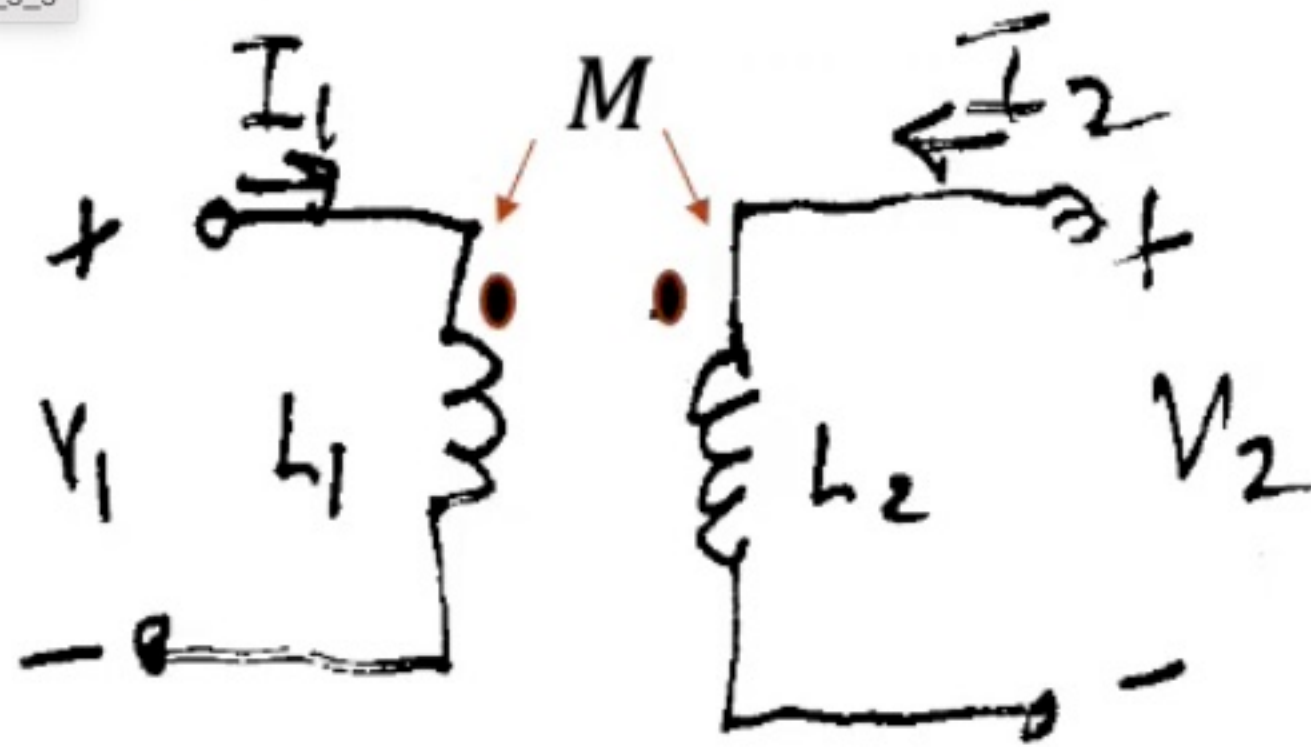


$$V_1 = j\omega L_1 I_1 + j\omega M I_2$$

$$V_2 = j\omega L_2 I_2 + j\omega M I_1$$


The input to the circuit shown in Figure 11.9-6a is the voltage of the voltage source,

$$v_s(t) = 5.94 \cos(3t + 140^\circ) \text{ V}$$

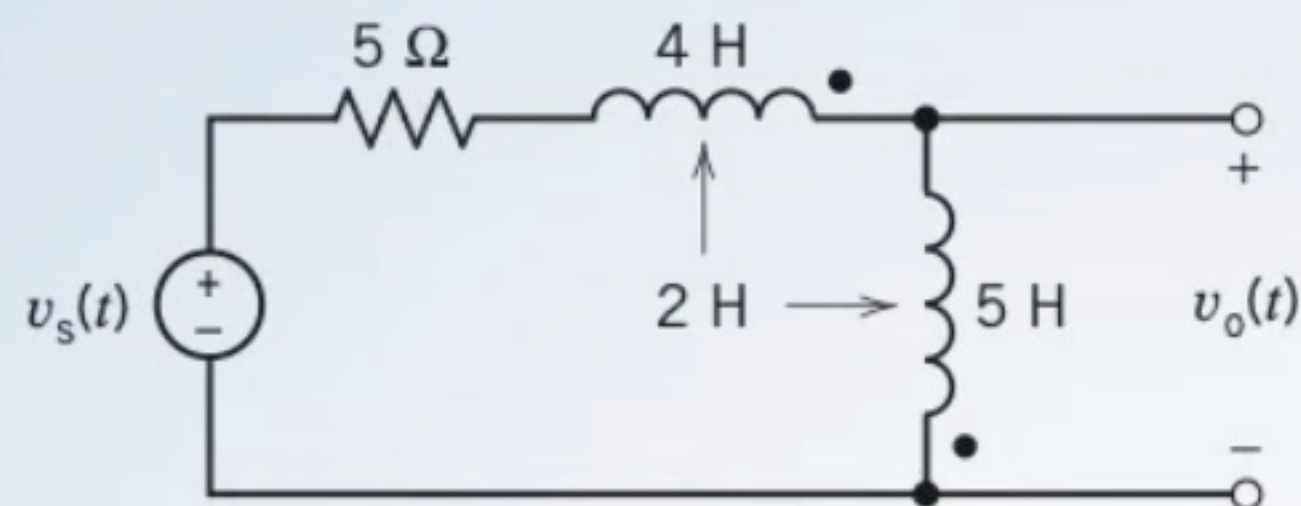The output is the voltage across the right-hand coil, $v_o(t)$. Determine the output voltage $v_o(t)$.



(a)

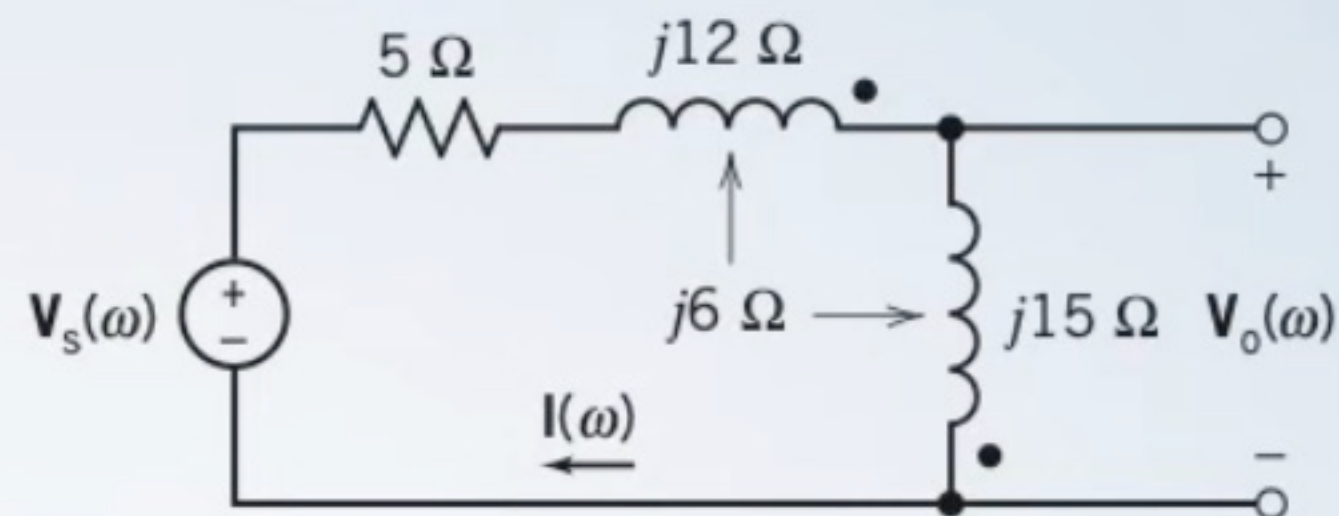


(b)


FIGURE 11.9-6 The circuit considered in Example 11.9-2 represented (a) in the time domain and (b) in the frequency domain.

$$\mathbf{V}_s(\omega) = 5.94 \angle 140^\circ \text{ V} \quad \mathbf{I}(\omega) = \frac{5.94 \angle 140^\circ}{5 + j(12 + 6 + 6 + 15)} = \frac{5.94 \angle 140^\circ}{5 + j39} = \frac{5.94 \angle 140^\circ}{39.3 \angle 83^\circ} = 0.151 \angle 57^\circ \text{ A}$$
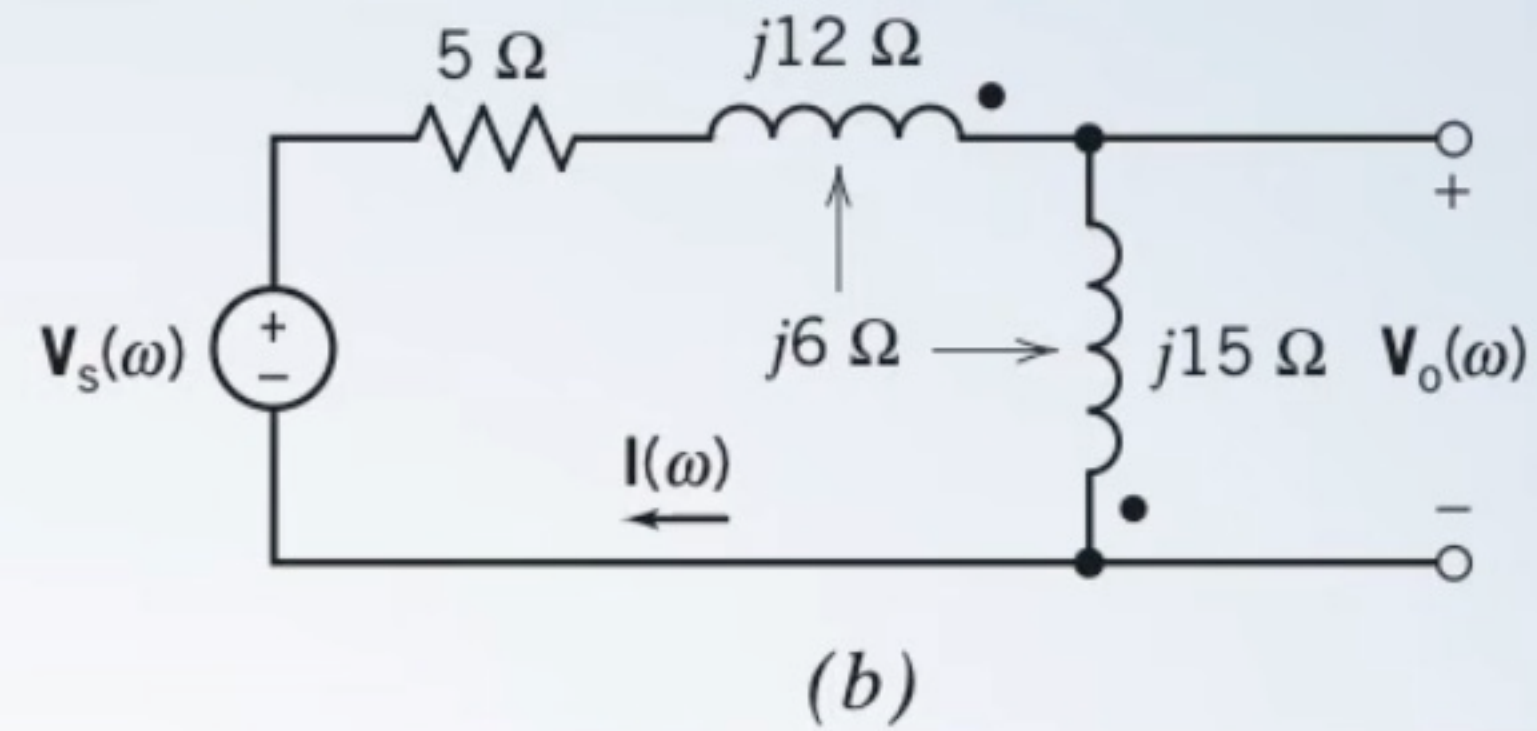
$$\begin{aligned} \mathbf{V}_o(\omega) &= j15 \mathbf{I}(\omega) + j6 \mathbf{I}(\omega) = j21 \mathbf{I}(\omega) = j21(0.151 \angle 57^\circ) \\ &= (21 \angle 90^\circ)(0.151 \angle 57^\circ) \\ &= 3.17 \angle 147^\circ \text{ V} \end{aligned}$$


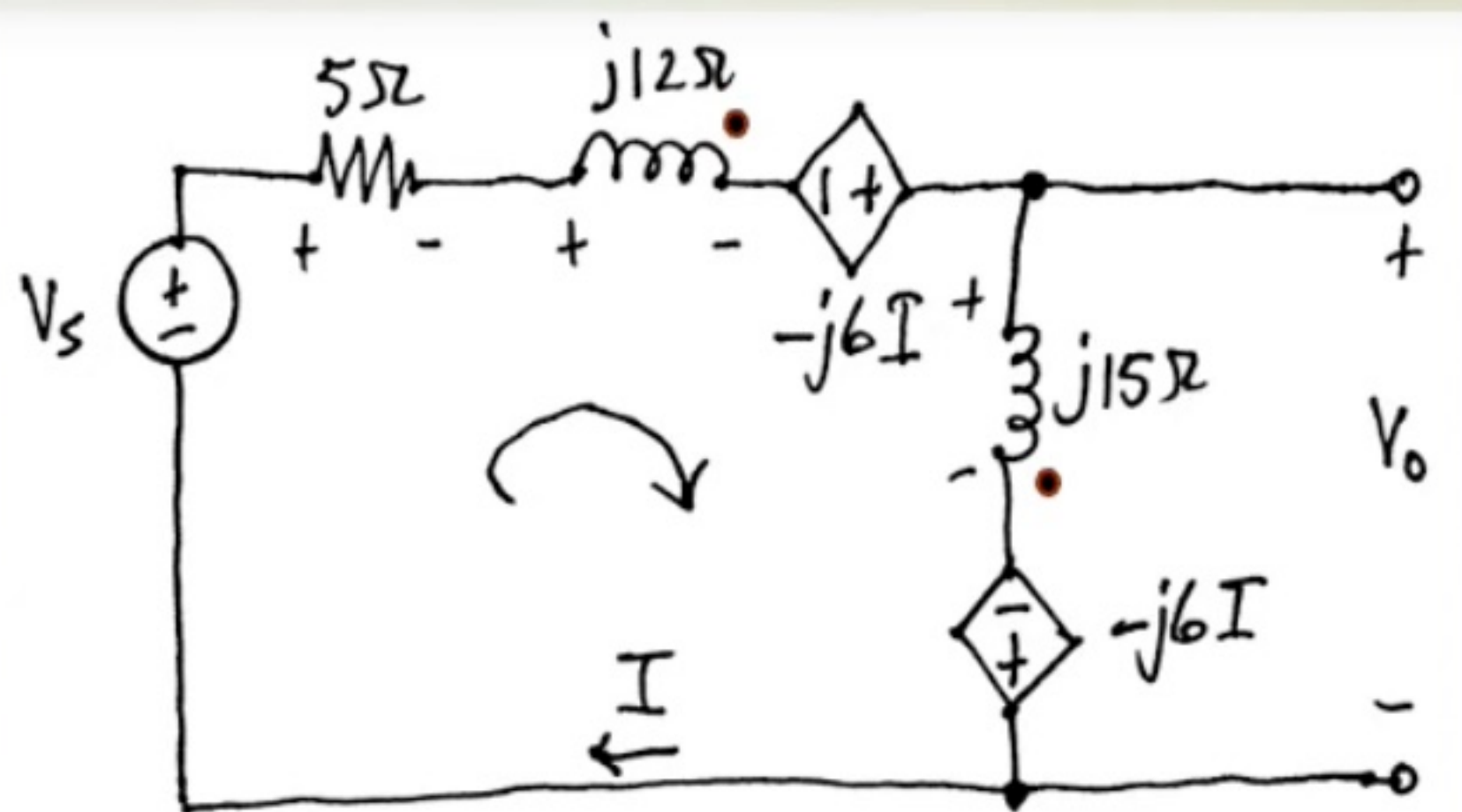
$$V_s(\omega) = 5.94 \angle 140^\circ \text{ V}$$



Por mallas con las fuentes dependientes


$$V_s - j6I - j6I = (5 + j12 + j15)I$$

$$I = \frac{V_s}{5 + j12 + j15 + j6 + j6} = \frac{5.94 \angle 140^\circ}{5 + j39}$$

$$V_o = j15I - (-j6I) = j21I$$

$$v_o(t) = 3.17 \cos(3t + 147^\circ) \text{ V}$$

Ideal Transformer

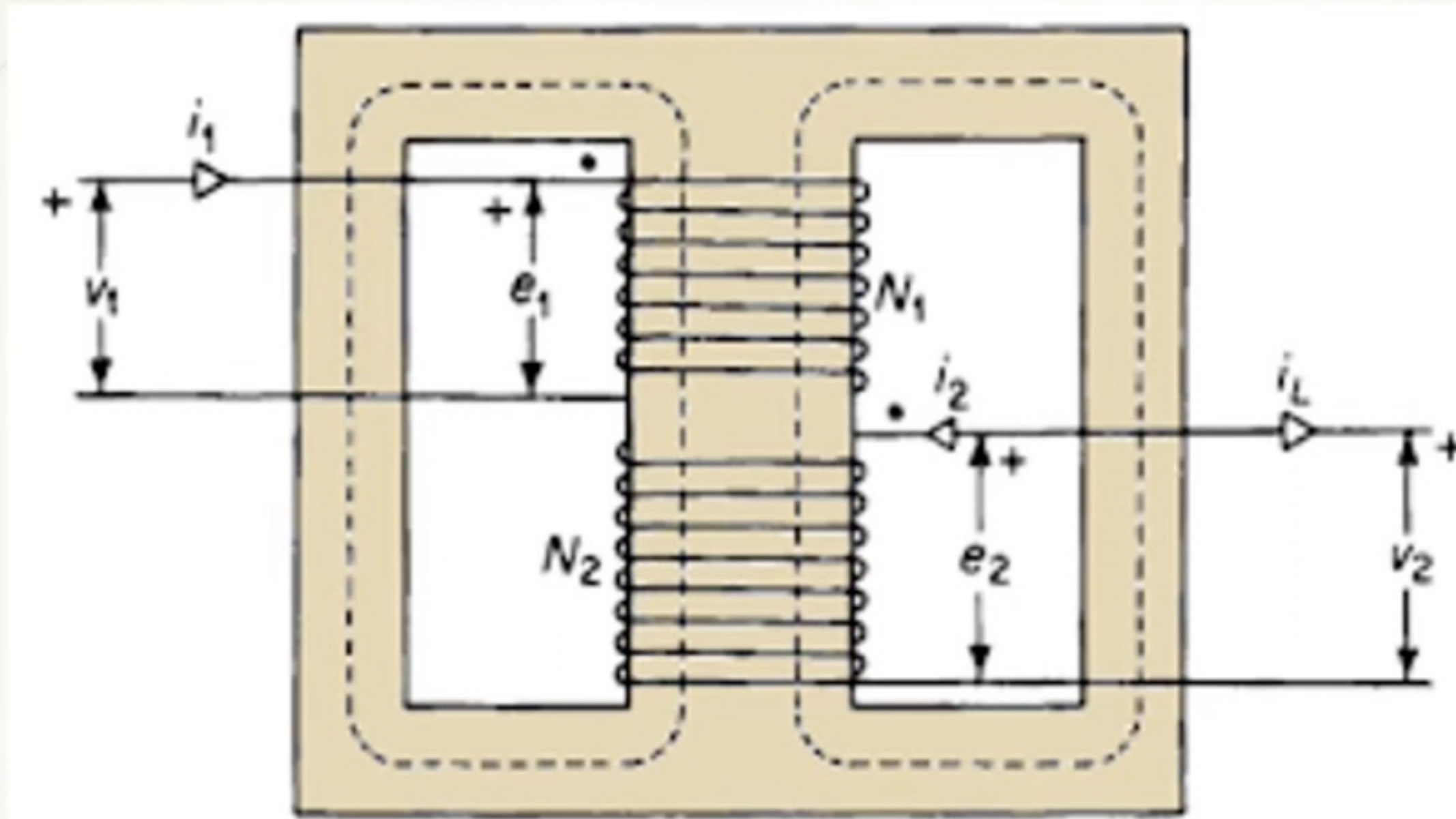

$$v_1 = -N_1 \frac{d\phi}{dt}$$

$$v_2 = -N_2 \frac{d\phi}{dt}$$

$$\frac{v_1}{N_1} = -\frac{d\phi}{dt} = \frac{v_2}{N_2}$$

$$\frac{v_2}{v_1} = \frac{N_2}{N_1} = -\frac{i_1}{i_2} = \frac{i_1}{i_L}$$


$$v_2(t) = \frac{N_2}{N_1} v_1(t)$$

$$p_1(t) = v_1(t)i_1(t)$$

$$i_1(t) = -\frac{N_2}{N_1} i_2(t)$$

$$p_2(t) = -v_2(t)i_2(t) = -\frac{N_2}{N_1} v_1(t) \left[-\frac{N_1}{N_2} i_1(t) \right] = v_1(t)i_1(t)$$

Ideal Transformer

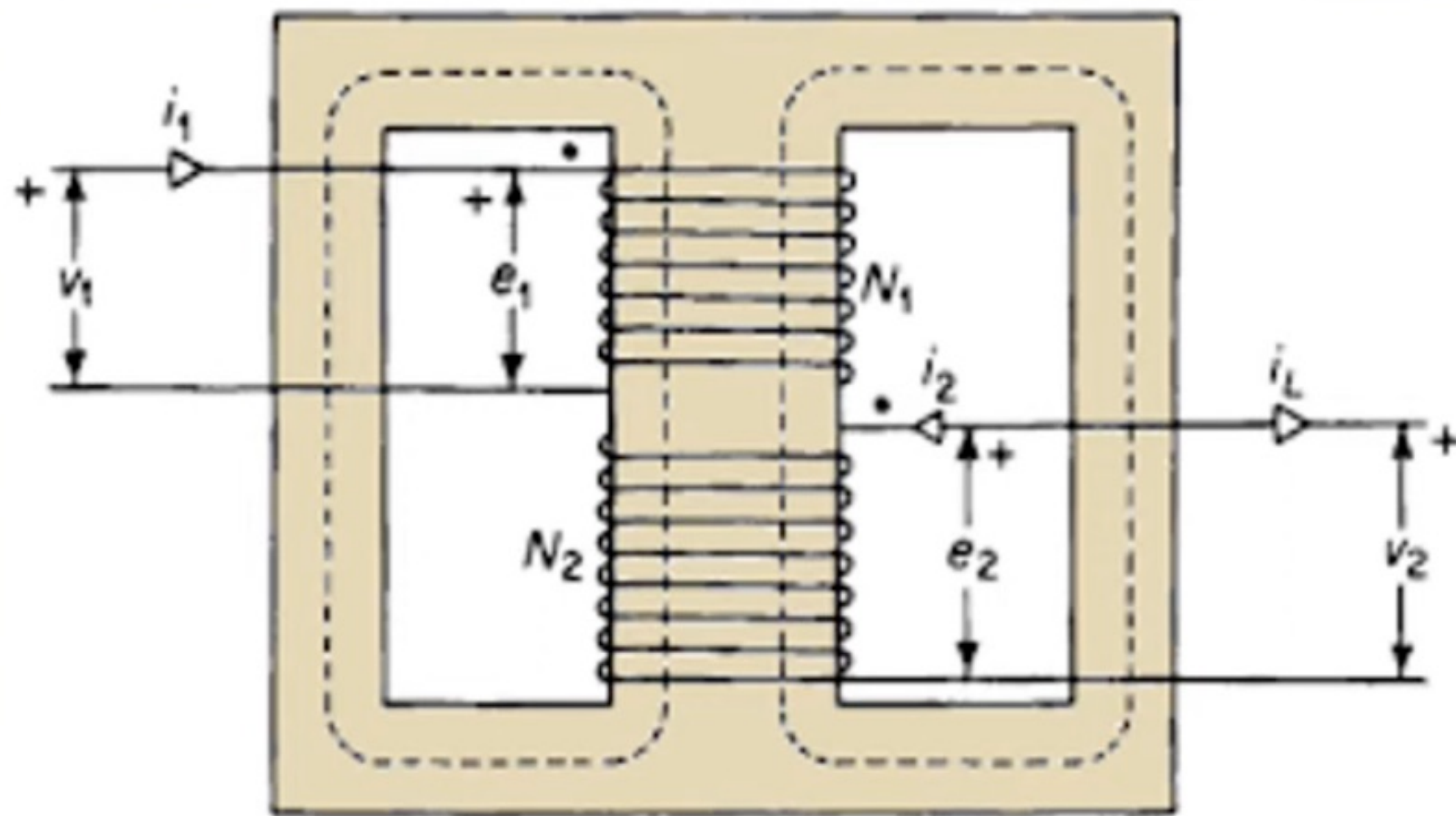

$$v_1 = -N_1 \frac{d\phi}{dt}$$

$$v_2 = -N_2 \frac{d\phi}{dt}$$

$$\frac{v_1}{N_1} = -\frac{d\phi}{dt} = \frac{v_2}{N_2}$$

$$\frac{v_2}{v_1} = \frac{N_2}{N_1} = -\frac{i_1}{i_2} = \frac{i_1}{i_L}$$


$$v_2(t) = \frac{N_2}{N_1} v_1(t)$$

$$p_1(t) = v_1(t) i_1(t)$$

$$i_1(t) = -\frac{N_2}{N_1} i_2(t)$$

$$p_2(t) = -v_2(t) i_2(t) = -\frac{N_2}{N_1} v_1(t) \left[-\frac{N_1}{N_2} i_1(t) \right] = v_1(t) i_1(t)$$

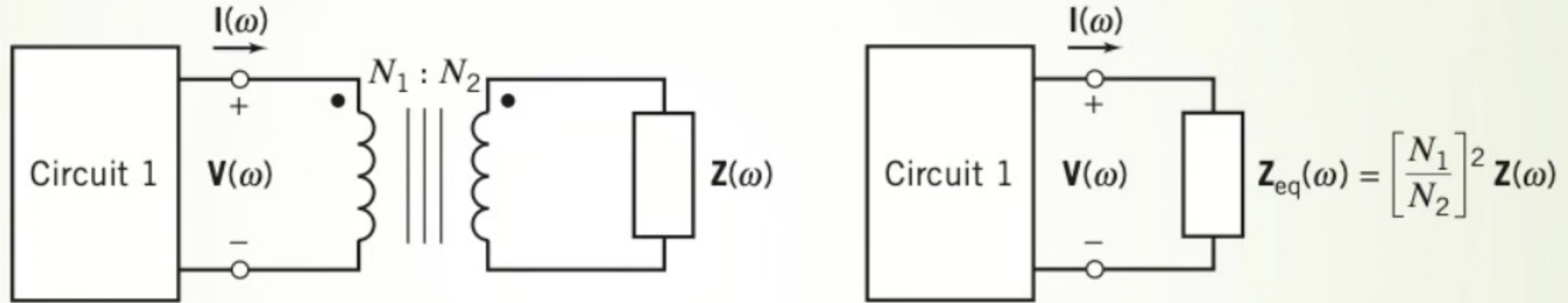Usando el transformador para impedance matching



$$\mathbf{Z}_{eq}(\omega) = \left(\frac{N_1}{N_2} \right)^2 \mathbf{Z}(\omega) = \frac{1}{n^2} \mathbf{Z}(\omega) = a^2 \mathbf{Z}(\omega)$$

Example 13.8

For the ideal transformer circuit of Fig. 13.37, find: (a) the source current $\mathbf{I}_1$, (b) the output voltage $\mathbf{V}_o$, and (c) the complex power supplied by the source.


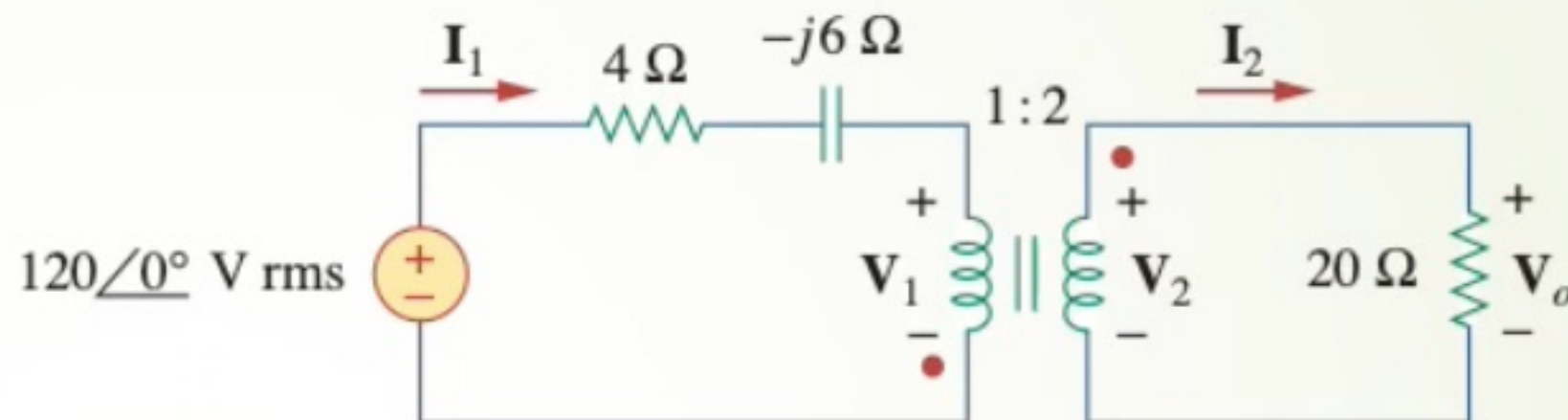


Figure 13.37

For Example 13.8.

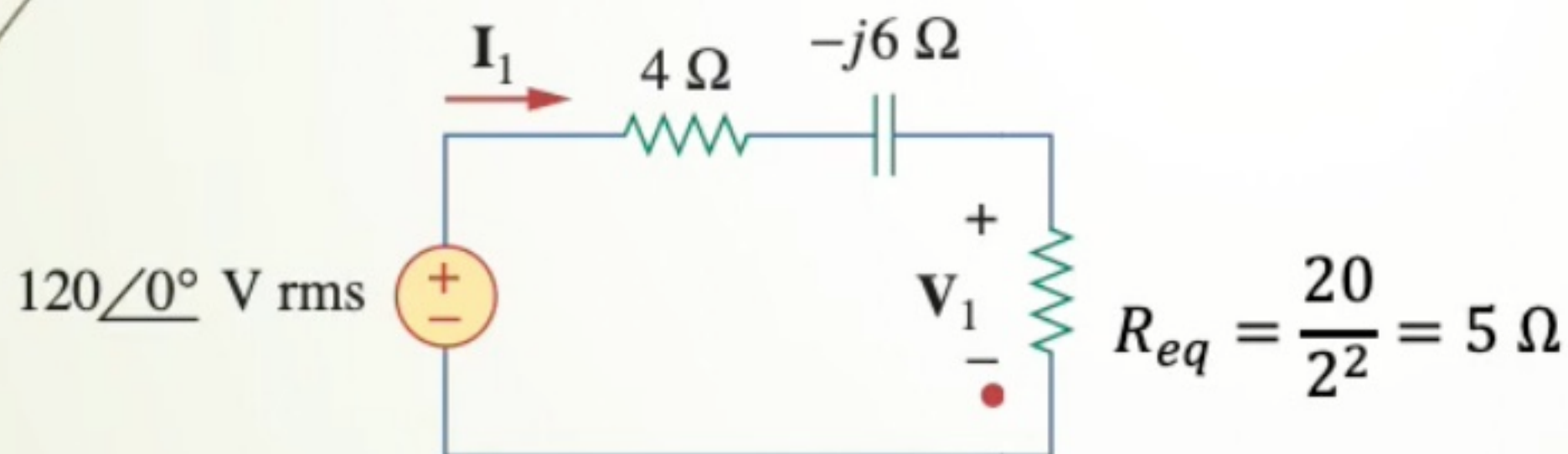

$$\mathbf{I}_1 = \frac{120}{4 + 5 - j6} = 11.09 \angle 33.69^\circ \text{ A}$$

$$\mathbf{I}_2 = -\frac{1}{2} (11.09 \angle 33.69^\circ) = -5.55 \angle 33.69^\circ \text{ A}$$

$$\mathbf{V}_o = 20 \mathbf{I}_2 = 110.9 \angle -146.31^\circ \text{ V}$$

$$\begin{aligned} S &= 120 (11.09 \angle -33.69^\circ) \\ &= 1330.8 \angle -33.69^\circ \text{ VA} \end{aligned}$$