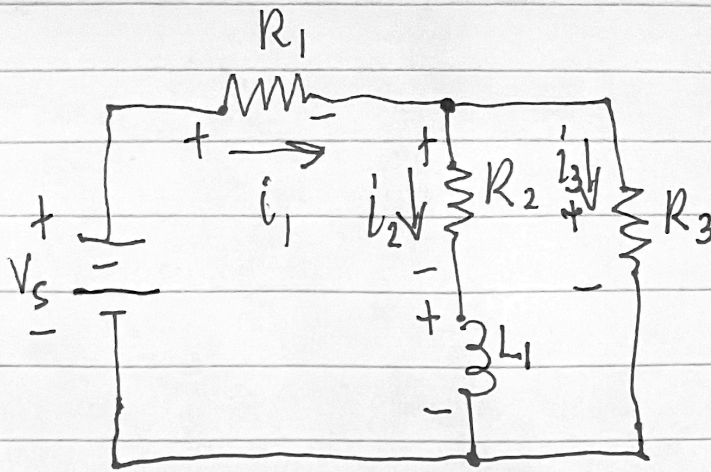




$$\rightarrow V_s = R_1 i_1 + R_2 i_2 + L_1 \frac{di_2}{dt}$$

$$i_1 = i_2 + i_3$$

$$R_2 i_2 + L_1 \frac{di_2}{dt} = R_3 i_3$$

$$i_3 = \frac{R_2}{R_3} i_2 + \frac{L_1}{R_3} \frac{di_2}{dt}$$

$$V_s = R_1 (i_2 + i_3) + R_2 i_2 + L_1 \frac{di_2}{dt}$$

$$V_s = R_1 i_3 + (R_1 + R_2) i_2 + L_1 \frac{di_2}{dt}$$

$$V_s = \frac{R_1 R_2}{R_3} i_2 + \frac{R_1 L_1}{R_3} \frac{di_2}{dt} + (R_1 + R_2) i_2 + L_1 \frac{di_2}{dt}$$

$$V_s = \underbrace{\left(R_1 + R_2 + \frac{R_1 R_2}{R_3} \right)}_a i_2 + \underbrace{\left(\frac{R_1}{R_3} + 1 \right) L_1}_b \frac{di_2}{dt}$$

$$V_s = a i_2 + b \frac{di_2}{dt}$$

$$i_2 = i_{2p} + i_{2h}$$

$$i_{2p} = k \quad V_s = ak + 0$$

$$i_{2p} = \frac{V_s}{a}$$

$$i_{2h}: 0 = a i_2 + b \frac{di_2}{dt}$$

$$-a i_2 = b \frac{di_2}{dt}$$

$$-\frac{a}{b} \int_0^t dt = \int_{i_0}^{i_2} \frac{di_2}{i_2}$$

$$-\frac{a}{b} t = \ln \frac{i_2}{i_0}$$

$$e^{-\frac{a}{b} t} = \frac{i_2}{i_0}$$

$$\underline{i_{2h} = i_0 e^{-\frac{a}{b} t}}$$

$$i_2 = \frac{V_s}{a} + i_0 e^{-\frac{a}{b} t}$$

$$i_2(t=0) = 0 = \frac{V_s}{a} + i_0(1) \quad i_0 = -\frac{V_s}{a}$$

$$i_2(t) = \frac{V_s}{a} (1 - e^{-\frac{a}{b} t}), t \geq 0$$

$$i_2(\infty) = 1.23 \text{ mA} \stackrel{?}{=} \frac{V_s}{a} = \frac{12}{9.75 \text{ k}} = 1.23 \text{ mA} \quad e^{-t/\tau}$$


$$a = R_1 + R_2 + \frac{R_1 R_2}{R_3} =$$

$$1.5 \text{ k} + 3.3 \text{ k} + \frac{(1.5 \text{ k})(3.3 \text{ k})}{(1 \text{ k})} = 18.3 \text{ k}$$

$$= 9.75 \text{ k}$$

$$b = \left(\frac{1.5 \text{ k}}{1.0 \text{ k}} + 1 \right) 1 \text{ m}$$

$$b = 2.5 \text{ m}$$

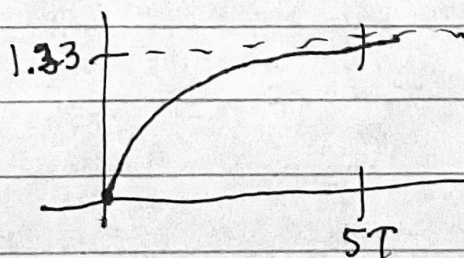

$$\tau = \frac{b}{a} = \frac{2.5 \text{ m}}{9.75 \text{ k}} = 0.256 \mu \text{ s}$$