

Universidad de Puerto Rico
Recinto Universitario de Mayagüez
Departamento de Ingeniería Eléctrica y Computadoras


INEL 4075 Asignacion #3:

Semana de lunes 12 de septiembre de 2011.


Nombre: _____

Sección: _____

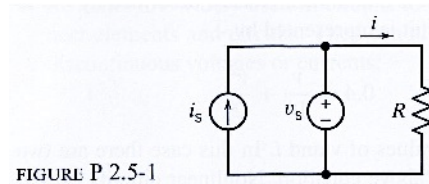1. Una batería tipo D cuesta \$0.50 y es capaz de producir 1.2V a 0.1A durante un intervalo de 75 horas. Determine el costo energético (en \$/kW-hr) y compáralo con el costo energético de tu proveedor de energía eléctrica local y el costo promedio nacional (\$0.12/kW-hr).



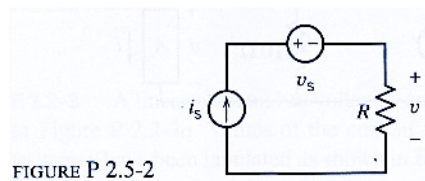2. A current source and a voltage source are connected in parallel with a resistor as shown in Figure P2.5-1. All of the elements connected in parallel have the same voltage, v_s in this circuit. Suppose that $v_s = 15\text{ V}$, $i_s = 3\text{ A}$, and $R = 5\ \Omega$. (a) Calculate the current i in the resistor and the power absorbed by the resistor. (b) Change the current source current to $i_s = 5\text{ A}$ and recalculate the current, i , in the resistor and the power absorbed by the resistor.



3. A current source and a voltage source are connected in series with a resistor as shown in Figure P 2.5-2. All of the elements connected in series have the same current, i_s , in this circuit. Suppose that $v_s = 10\text{ V}$, $i_s = 2\text{ A}$, and $R = 5\ \Omega$. (a) Calculate the voltage v across the resistor and the power absorbed by the resistor. (b) Change the voltage source voltage to $v_s = 5\text{ V}$ and recalculate the voltage, v , across the resistor and the power absorbed by the resistor.