

Fundamentos de Transformadores y Máquinas Eléctricas

Dr. Lionel R. Orama Exclusa, PE

Clase 19


Motores DC

- Se comparan por % SR - regulación de velocidad

$$\% SR = \frac{\omega_{NL} - \omega_{FL}}{\omega_{FL}} \times 100 = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100$$

Voltaje de entrada (DC) se presume constante

Circuito
Equivalente

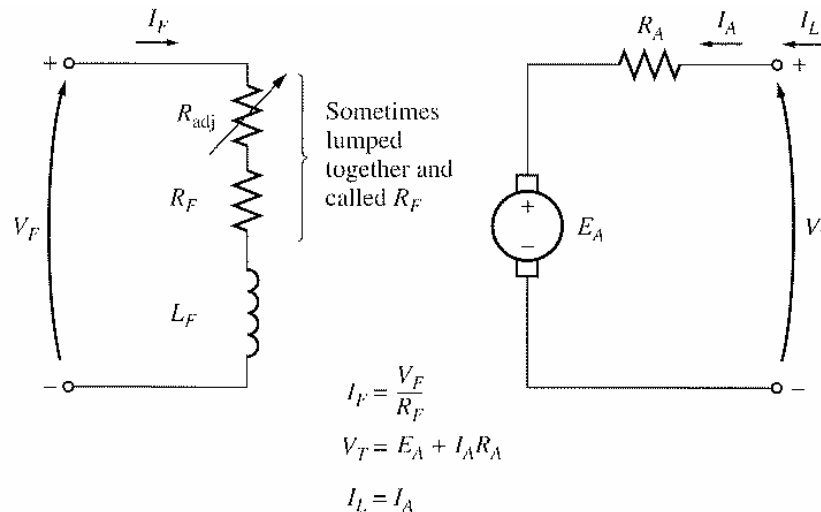


$E_A = K\phi\omega$, voltaje inducido o interno

$T_{ind} = K\phi I_A$, torque inducido

Motor DC Exitado por Separado

Separately Exited

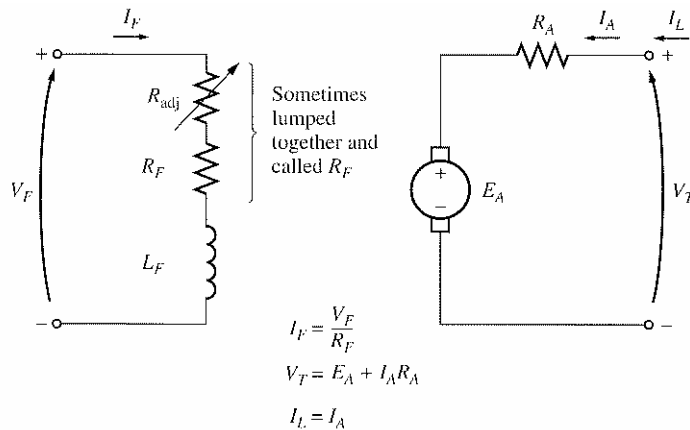

$$V_T = E_A + R_A I_A$$

$$I_L = I_A$$


$$I_F = \frac{V_F}{R_{F_T}}$$

$$E_A = K\phi\omega, \quad \text{voltage inducido o interno}$$

$$\tau_{ind} = K\phi I_A, \quad \text{torque inducido}$$

Motor Excitado en Paralelo

Shunt DC Motor

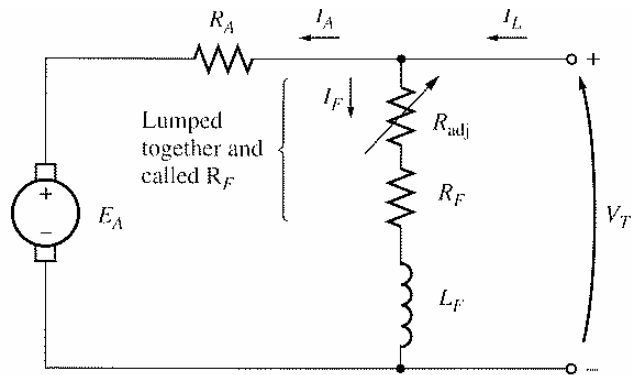

$$I_F = \frac{V_T}{R_F}$$

$$V_T = E_A + I_A R_A$$

$$I_L = I_A + I_F$$

$$V_T = E_A + R_A I_A$$

$$I_L = I_A + I_F \quad I_F = \frac{V_T}{R_F}$$

* Si el voltaje que se suministra al motor es constante
no hay diferencia en el comportamiento de ambos.

Característica de Terminal

Aumento en Carga

$\tau_{load} \uparrow \gg \tau_{ind} \therefore \omega \downarrow$

$$E_A = K \phi \omega \downarrow$$

$$I_A = \frac{V_T - E_A}{R_A} \uparrow$$

$$\tau_{ind} = K \phi I_A \uparrow$$

$\tau_{ind} \cong \tau_{load}$ a una ω menor.


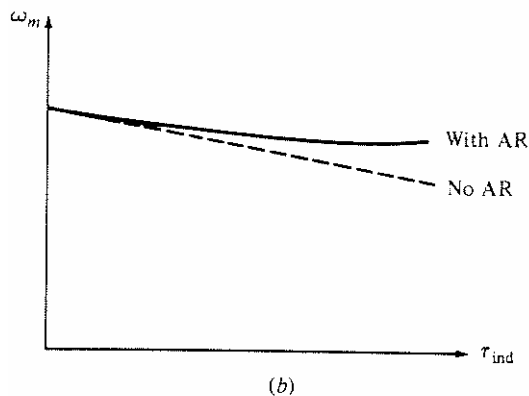
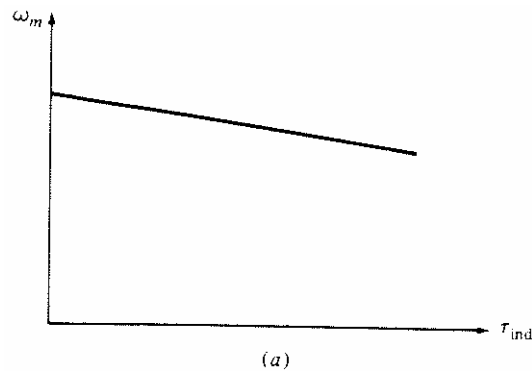


Figure 6-4 (a) Torque-speed characteristic of a shunt or separately excited dc motor with compensating windings to eliminate armature reaction. (b) Torque-speed characteristic of the motor with armature reaction present.

Control de Velocidad

$E_A = K\phi\omega$, voltaje inducido o interno

$T_{ind} = K\phi I_A$, torque inducido

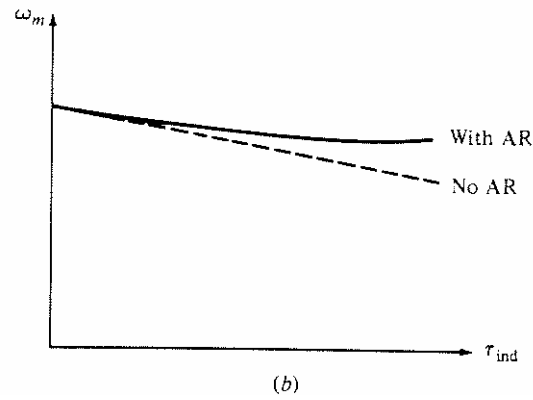


1) $E_A = K\phi\omega \rightarrow R_F \downarrow, I_F \uparrow \therefore E_A \uparrow$

2) $V_T \uparrow, I_A \uparrow \therefore T_{ind} \uparrow$

Motor DC en Serie

Series DC Motor

Figure 8-40 | The equivalent circuit of a series DC motor.

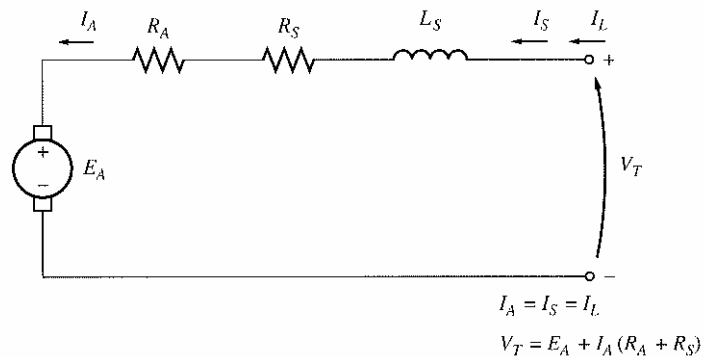

$$V_T = E_A + I_A(R_A + R_S)$$

$$I_A = I_S = I_L$$

Característica de Terminal

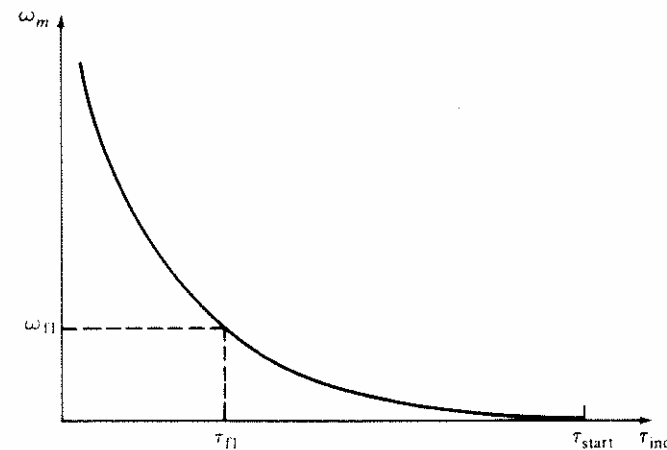


Figure 6-16 The torque-speed characteristic of a series dc motor.

- ω varía aproximadamente con la $\sqrt{\tau}$
- * desventaja, $\tau = 0 \quad \omega \rightarrow \infty$
- * ventaja, $\uparrow$ arranque alto

Control de Velocidad


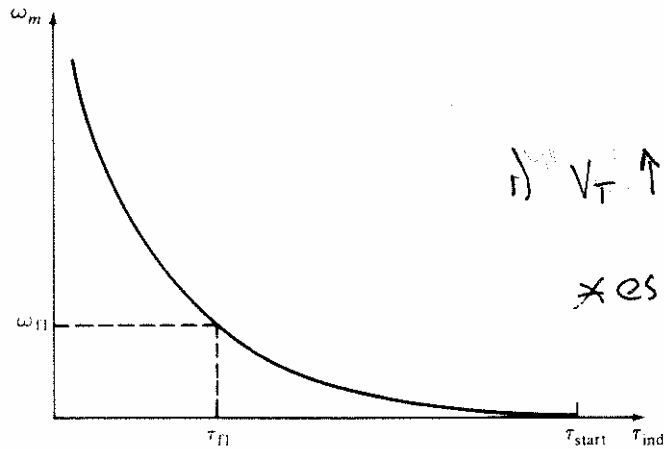


Figure 6-16 The torque-speed characteristic of a series dc motor.

1) $V_T \uparrow$, $E_A \uparrow \therefore \omega \uparrow$

es la única forma efectiva de controlar velocidad

Figure 8-40 The equivalent circuit of a series DC motor.

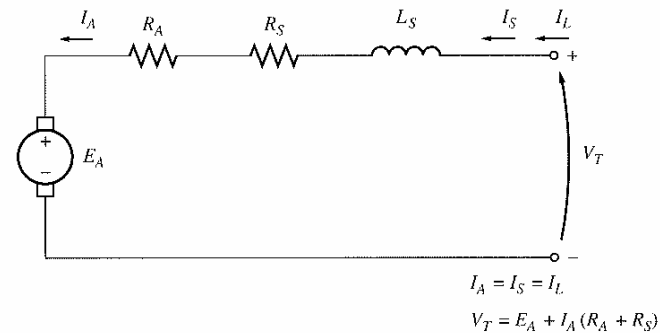

Motor DC Compuesto


Cumulative Compounded

$$V_T = E_A + I_A (R_A + R_S)$$

$$I_A = I_L - I_F$$

$$I_F = V_T / R_F$$

Figure 8-44 | The equivalent circuit of compounded DC motors: (a) connection; (b) short-shunt connection.

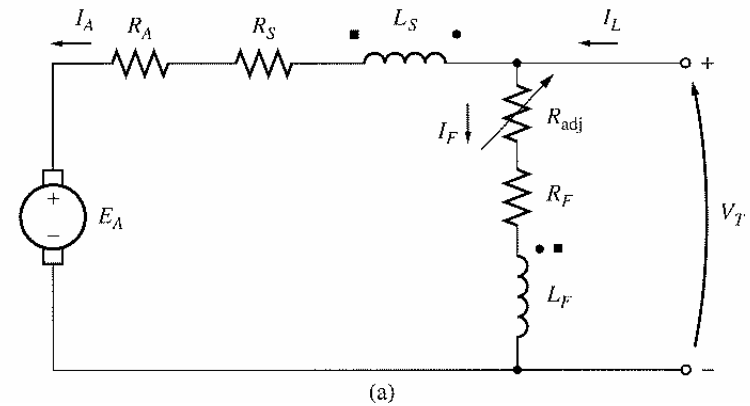

Característica de Terminal

Hay una I_F constante, $I_s \propto I_A$; $\tau_s < \tau_{\text{START}} < \tau_{se}$

$\therefore$ Tiene lo bueno de ambos (shunt y el series)

1) Series - τ_{start} alto

2) shunt - $\tau \rightarrow$, ω es finita

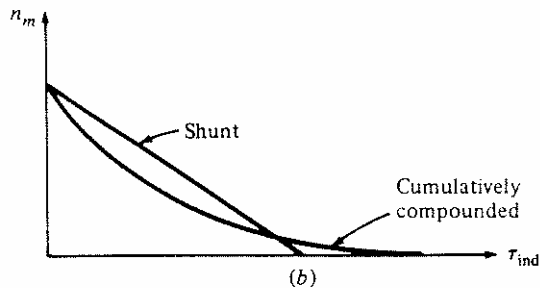
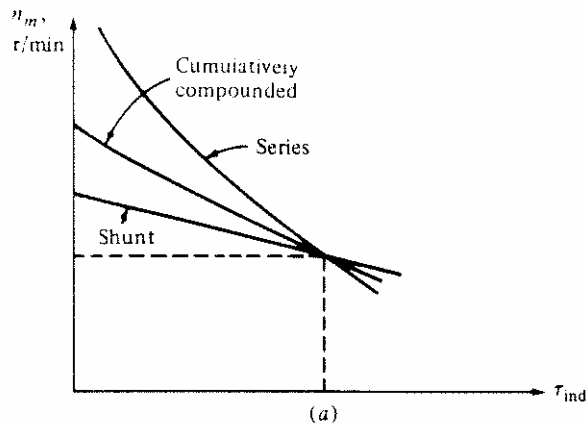


Figure 6-20 (a) The torque-speed characteristic of a cumulatively compounded motor compared to series and shunt motors with the same full-load rating. (b) The torque-speed characteristic of a cumulatively compounded dc motor compared to a shunt motor with the same no-load speed.