

Problem 2.8.

C1 has been charged to 500kV

The gap sparks and generates an impulse voltage at A-B.

$C1=2\mu\text{F}$, $C2=0.05\mu\text{F}$

$R1=10\Omega$, $R2=100\Omega$


Maximum spark current= 50kA

Maximum voltage across C2= 454kV in about 2 μs (4 time constants)



At 0.5 μs voltage is close to 453.95kV


At 50 μs voltage is close to 453.64kV

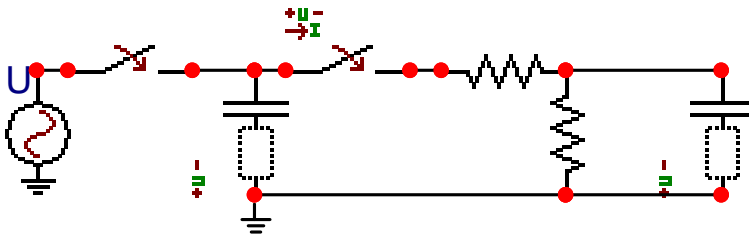For simulation we have to first charge C1 to 500kV and then switch the source off at the same time the gap sparks-over. This can be done in an unsophisticated approach by simulating the spark as an ideal switch. The circuit in ATP becomes:



The results are shown on the next page.

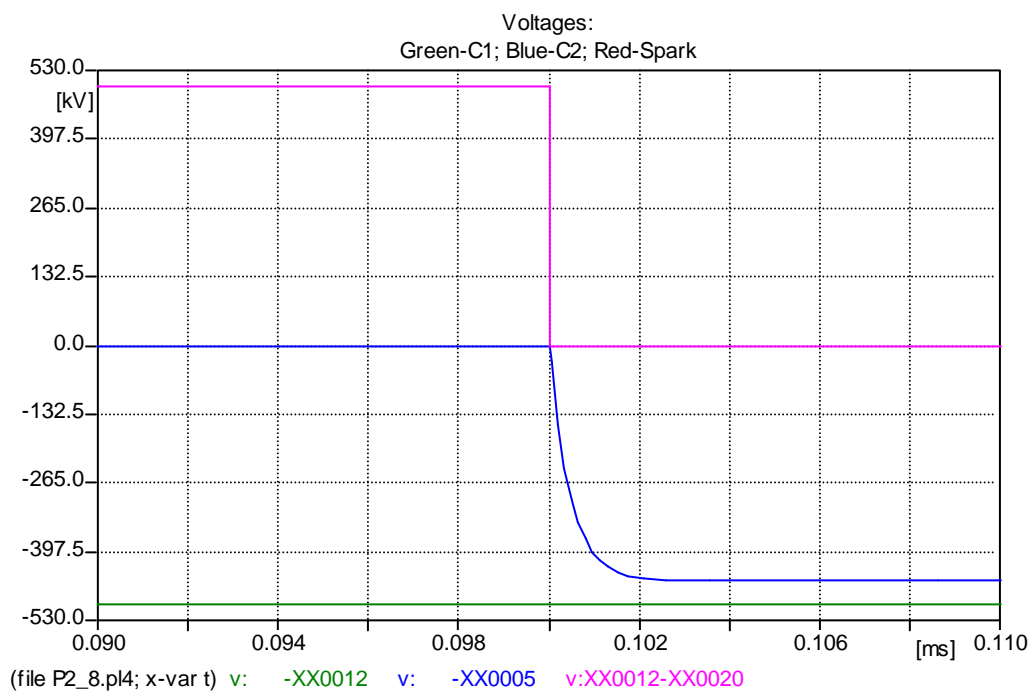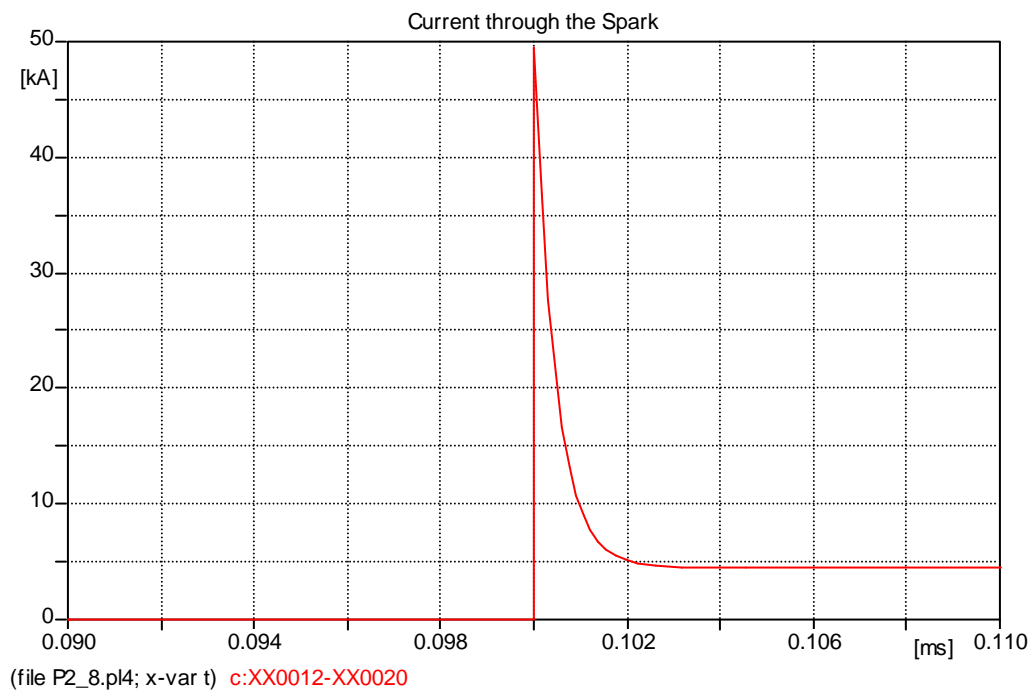

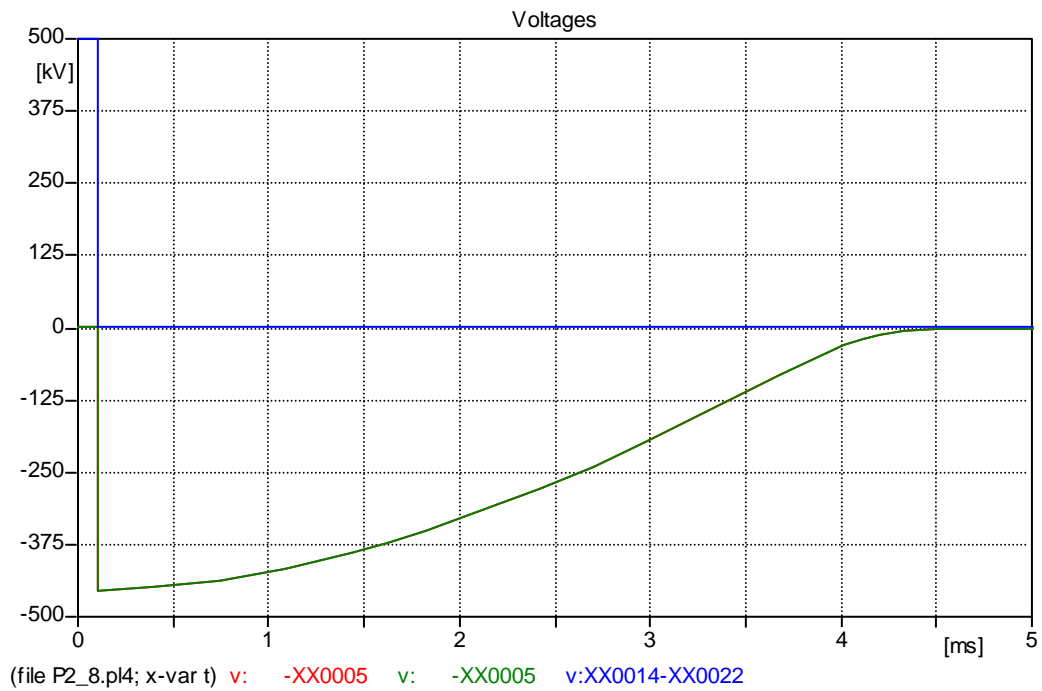

This is the result at time equals infinity in the simulated circuit. The voltage will drop down to zero since there is no forcing function to re-energize the circuit.