

Prob 2.4 $X_L = 5\Omega$ $\omega L = X_L$ $L = \frac{X_L}{\omega} = \frac{5}{2\pi(60)}$

$$L = 13.26 \text{ mH}$$

$$C_1 = 60 \mu\text{F} \quad C_2 = 40 \mu\text{F} \quad ; \quad C_e = 24 \mu\text{F}$$

$$Z_0 = \sqrt{\frac{L}{C_e}} = \sqrt{\frac{13.26 \text{ mH}}{24 \mu\text{F}}} = 23.5 \Omega$$

$$\omega_0 = \frac{1}{\sqrt{LC_e}} = \frac{1}{\sqrt{(13.26 \text{ m})(24 \mu)}} = 1772.5 \text{ [rad/s]}$$

(a) Instantaneous Current when Switch closes.

$I(0) = 0$, because I can not change instantaneously in an inductor

(b) Peak Current

$$I_{\text{peak}} = \frac{V_1(0) - V_2(0)}{Z_0} = \frac{16.67 \text{ kV}}{23.5 \Omega} = 709 \text{ [A]}$$

(c) Energy stored in L after 1 ms .

$$I(t) = I_{\text{peak}} \sin \omega_0 t = 709 \sin 1773 t \text{ [A]}$$

$$I(1 \text{ ms}) = 709 \sin 1773(1 \text{ ms}) = 695 \text{ [A]}$$

$$E_L = \frac{1}{2} I^2 L = \frac{1}{2} (695 \text{ A})^2 (13.26 \text{ mH}) = 3200 \text{ [J]}$$

(d) Energy stored in C_1 at the same time.

$$E_{C_1}(0) = \frac{1}{2} C_1 [V_1(0)]^2 = \frac{1}{2} (60 \mu\text{F}) (16.67 \text{ kV})^2 = 8334 \text{ [J]}$$

$$E_{C_1}(1 \text{ ms}) = E_{C_1}(0) - E_L(1 \text{ ms}) = 8334 \text{ [J]} - 3200 \text{ [J]}$$

$$= 5134 \text{ [J]}$$