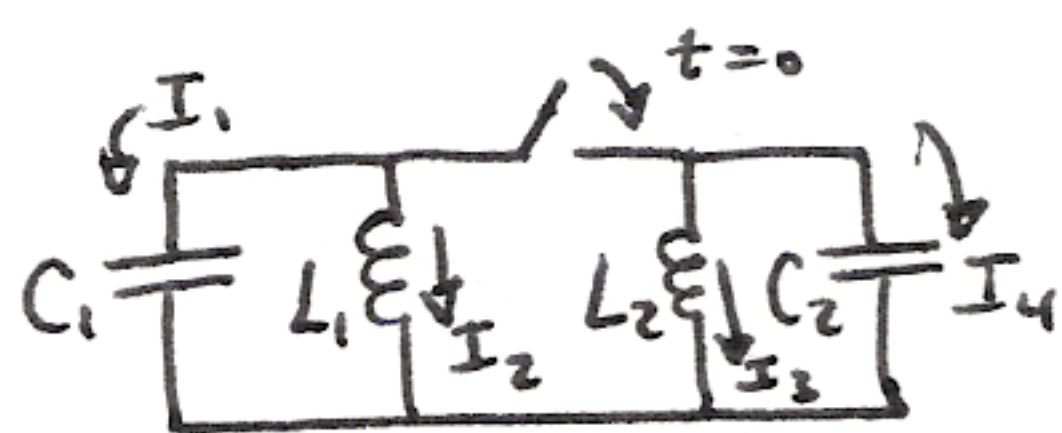


P 3.12



$$C_1 = 100 \mu F \quad L_1 = 10 \text{ mH}$$

$$C_2 = 40 \mu F \quad L_2 = 20 \text{ mH}$$

When switch closes all elements have common voltage

$$V = \frac{1}{C_1} \int I_1 dt = L_1 \frac{dI_2}{dt} = L_2 \frac{dI_3}{dt} = \frac{1}{C_2} \int I_4 dt \quad \text{and}$$

$$I_1 + I_2 + I_3 + I_4 = 0 \quad \text{therefore,}$$

$$C_1 \frac{d^2 V}{dt^2} + \frac{V}{L_1} + \frac{V}{L_2} + C_2 \frac{d^2 V}{dt^2} = 0$$

$$(C_1 + C_2) V'' + \left( \frac{1}{L_1} + \frac{1}{L_2} \right) V = 0 \quad ; \quad \frac{L_1 + L_2}{L_1 L_2} = \frac{1}{L_1} + \frac{1}{L_2}$$

$$\left\{ V'' + \left( \frac{L_1 + L_2}{L_1 L_2 (C_1 + C_2)} \right) V = 0 \right\} \quad ; \quad \omega_0^2 = \frac{L_1 + L_2}{L_1 L_2 (C_1 + C_2)}$$

$$s^2 V(s) - s V(0) - V'(0) + \omega_0^2 V(s) = 0$$

$V(0) = 0$  as established by the problem.

$$-I_2(0) = (C_1 + C_2) \frac{dV}{dt} \quad \text{then} \quad V'(0) = -\frac{I_2(0)}{C_1 + C_2}$$

then

$$V(s) = -\frac{I_2(0)}{C_1 + C_2} \cdot \frac{1}{s^2 + \omega_0^2}$$

that gives,  $V(t) = \frac{-I_2(0)}{\omega_0 (C_1 + C_2)} \sin \omega_0 t \quad ; \quad \omega_0 = \sqrt{\frac{L_1 + L_2}{L_1 L_2 (C_1 + C_2)}} = 1035 \text{ rad/s}$

(a)

$$V_{\max} = 3450 \text{ V}$$

$$I_3 = \frac{1}{L_2} \int V dt = \frac{1}{L_2} \left( \frac{-I_2(0)}{\omega_0^2 (C_1 + C_2)} \right) \cos \omega_0 t + \text{const.}$$

$$t=0 \quad I_3 = 0 \quad \text{then} \quad I_3 = \frac{-I_2(0)}{L_2 \omega_0^2 (C_1 + C_2)} (\cos \omega_0 t - 1)$$

$$I_{\text{peak}} = (166 \text{ A})^2, \text{ when } \omega_0 t = \pi$$

$$I_{\text{peak}} = 332 \text{ A}$$

(b)

(c)

The circuit has only one frequency:  $f_0 = \frac{\omega_0}{2\pi} = 164.7 \text{ Hz}$

(d)

Before  $t=0$ ,  $Z_0 = \left( \frac{10 \text{ m}}{100 \mu} \right)^{1/2} = 10 \Omega \quad V_{\text{peak}} = 500 \text{ V} = 5 \text{ KV}$