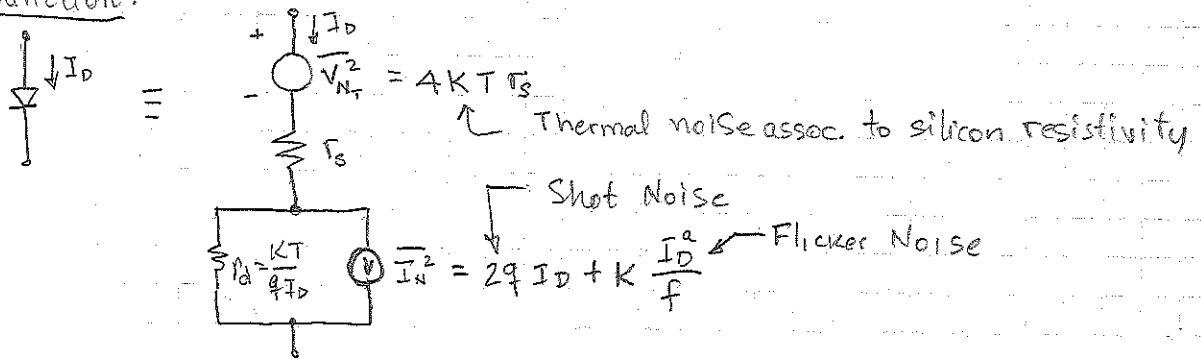


Noise Models for IC components


PN Junction:



N-11

Bipolar Transistors:

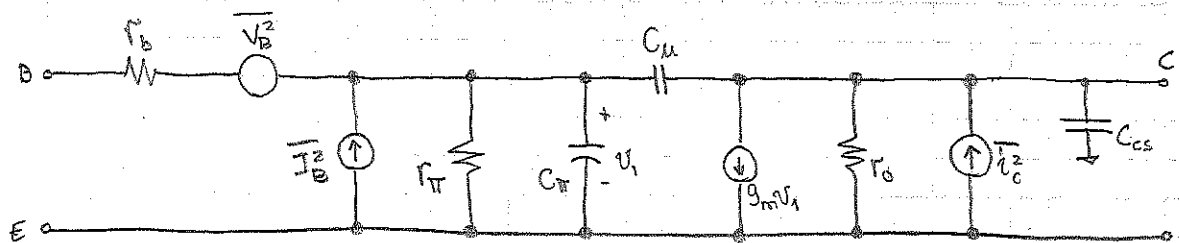- The collector current I_C is made-up of a series of random current pulses. Thus I_C exhibits shot noise.
- I_B also exhibits shot noise due to the random nature of recombination and carrier injection.



I_B^2 = Combined effect of shot noise, flicker noise, and burst noise

$$I_B^2 = \underbrace{2qI_B}_{\text{Shot}} + \underbrace{K_1 \frac{I_B^2}{f}}_{\text{Flicker}} + \underbrace{K_2 \frac{I_B^2}{1+(f/f_c)^2}}_{\text{Burst}}$$

V_B^2 = Thermal noise in r_b


$$V_B^2 = 4KT r_b$$

I_C^2 = shot noise in I_C $I_C^2 = 2qI_C$

- r_o and r_{π} are model resistances (not real). Therefore do not generate thermal noise



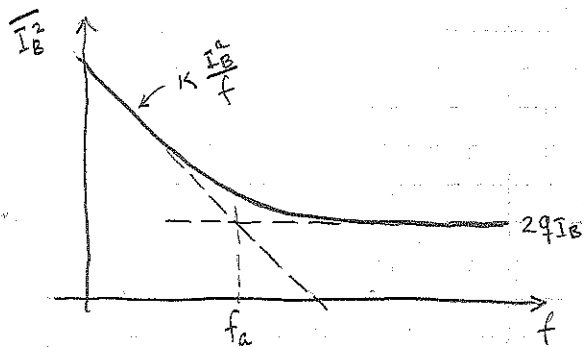- All noise sources in BJT analysis are ^{considered} independent.
- The interception between flicker and shot noise PSDs happens at f_a (corner frequency)




- Circuit model valid for NPN & PNP BJTs
- f_a can be 100Hz \rightarrow 10MHz

N-12

MOS Transistors

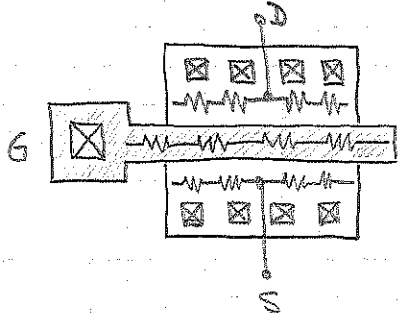- Major sources of noise in MOSFETs are thermal and flicker noise.
- In a lesser degree, the gate leakage current produces shot noise
- Thermal Noise is associated to the resistivity of the terminals (Gate, Source, Drain)



MOS TERMINAL RESISTANCE

- Channel resistance is the major source of thermal noise with PSD


$$\overline{I_N^2} = 4KT \gamma g_m$$

where $\gamma = \frac{2}{3}$ for long channel devices and higher for small channel MOSFETs

- Resistances R_G , R_S and R_D are typically negligible. Gate resistance is large in wide transistors.

- Flicker Noise is associated to the gate-oxide interface.
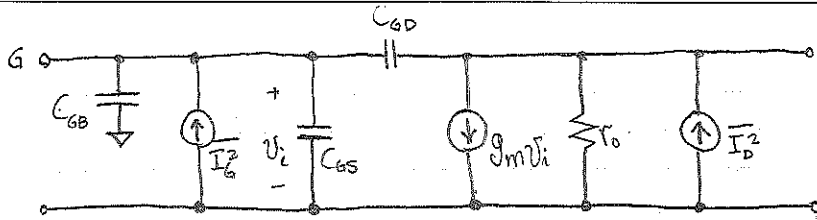
$$\overline{I_{nf}^2} = \frac{K}{C_{ox}WL} \frac{1}{f} g_m^2$$



$$\overline{I_G^2} = 2q I_G \left\{ \text{SHOT NOISE} \right.$$


$$\overline{I_D^2} = \underbrace{4KT \left(\frac{2}{3} g_m \right)}_{\text{THERMAL NOISE}} + \underbrace{\frac{K}{C_{ox}WL} \frac{1}{f} g_m^2}_{\text{FLICKER NOISE}}$$

• All NOISE sources in FETs can be considered independent

• Passive Components: Resistors, Inductors, and capacitors.

• When the element series resistance is considered, introduce thermal noise

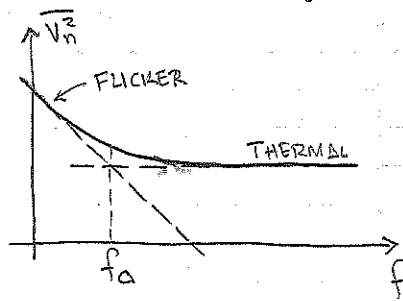The comparative flicker and thermal noise effects in MOSFETs can be viewed by superimposing their PSDs



• Allows to visualize in which portion of the spectrum each is dominant

• At f_c (corner frequency)

$$\overline{I_{n_f}^2} = \overline{I_{n_t}^2}$$

$$\text{So } 4KT \left(\frac{2}{3} g_m \right) = \frac{K}{C_{ox}WL} \cdot \frac{1}{f_c} \cdot g_m^2$$

$$\text{So } f_c = \frac{K}{C_{ox}WL} \frac{g_m \cdot 3}{8KT}$$

Example:

For an NMOS current source, calculate the total thermal & 1/f noise in I_D in a band from 1kHz to 1MHz

$$\overline{I_{n_{Th}}^2} = 4KT \left(\frac{2}{3} g_m \right) \Delta f \approx 4KT \left(\frac{2}{3} g_m \right) \times 10^6 \text{ A}^2$$

$$\overline{I_{n_{1/f}}^2} = \frac{K}{C_{ox}WL} \cdot \frac{1}{f} g_m^2 \quad \leftarrow \text{single frequency}$$

$$\overline{I_{n_{1/f}}^2}_{\text{total}} = \int_{f_1}^{f_2} \overline{I_{n_{1/f}}^2} df$$

$$= \frac{K g_m^2}{C_{ox}WL} \int_{1k}^{1M} \frac{df}{f} = \frac{K g_m^2}{C_{ox}WL} \ln \left[\frac{10^6}{10^3} \right] = \frac{6.91 K g_m^2}{C_{ox}WL}$$

