

- $Z_L \neq Z_0$ creates a potential inconsistency at the termination leading to a $V_B \neq 0$ and $i_B \neq 0$




Reflection Coefficient

$$\Gamma = \frac{V_B}{V_F} \Big|_{\text{right end}} = \frac{V_F}{V_B} \Big|_{\text{left end}} = \frac{\frac{Z_L}{Z_0} - 1}{\frac{Z_L}{Z_0} + 1} = \frac{Z_L - Z_0}{Z_L + Z_0} \quad (13)$$

$$|\Gamma| \leq 1$$

Note that for $Z_L = \infty \Rightarrow \Gamma \rightarrow 1$ and $Z_L = 0 \Rightarrow \Gamma \rightarrow -1$

Case analysis:

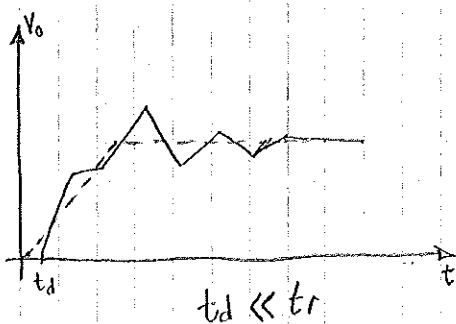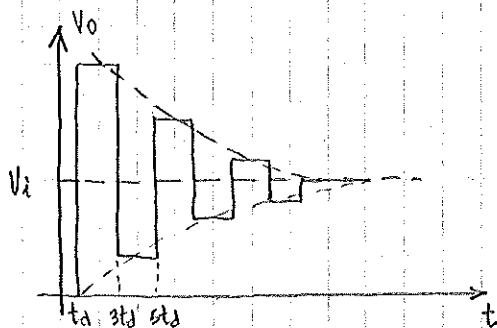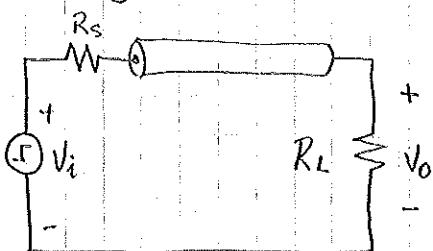

For this circuit

$$\begin{aligned} R_s &\approx 10 \Omega \\ R_L &= 10 \text{ k}\Omega \\ R_0 &= 100 \Omega \end{aligned}$$

- $R_s \ll R_0 \ll R_L$
- Assuming $t_r \ll t_d$
- V_o will be a damped oscillation
- V_o could be interpreted as multiple oscillations.
- Oscillations are avoided by terminating the line with Z_0
- Propagation delay per unit length of an unloaded transmission line

$$\delta = \frac{t_d}{l} = \sqrt{LC} \quad \delta = \frac{1}{v}$$

- In an homogeneous medium

$$\delta = \sqrt{\mu \epsilon}$$

$\mu = \mu_r \mu_0 \rightarrow$ permeability (magnetic response)

$\epsilon = \epsilon_r \epsilon_0 \rightarrow$ permittivity (electric field response)

For digital lines $\mu_r \approx 1$, $\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$, and $\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$

$$\text{Thus } \delta = 33.35 \sqrt{\epsilon_r} \text{ ps/cm}$$




- If neither the source or load impedance match Z_0 then multiple reflections will occur

Let T_L and T_S be the reflection indices of load & source, respectively

When T_S and T_L have opposite signs, reflections alternate causing ringing

Traces on PCBs (strips & microstrips)

- Microstrip

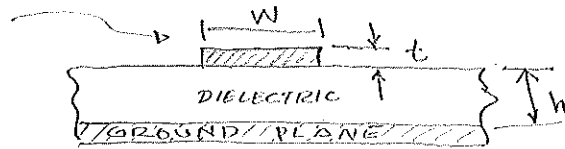

$$Z_0 = \frac{87 \ln \left(\frac{5.89h}{0.8w+t} \right)}{\sqrt{\epsilon_r + 1.41}}$$


ϵ_r = relative dielectric constant of insulator

Valid for $0.1 < w/h < 0.3$
 $1 < \epsilon_r < 15$

The propagation delay is dependent only on ϵ_r

$$S = 33.35 \sqrt{0.475 \epsilon_r + 0.67} \text{ ps/cm}$$

- Strip

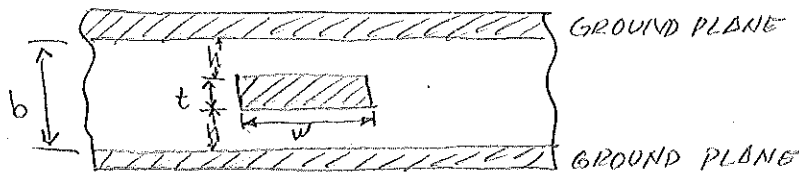


$$Z_0 = \frac{60}{\sqrt{\epsilon_r}} \ln \left[\frac{4b}{0.67\pi(0.8w+t)} \right]$$

Valid for $\frac{w}{(b-t)} < 0.35$ and $t/b < 0.25$

$$S = 33.35 \sqrt{0.475 \epsilon_r + 0.67}$$

- On PCBs traces are highly predictable
- Transverse electromagnetic mode: operation of strip & pstrip

Example:

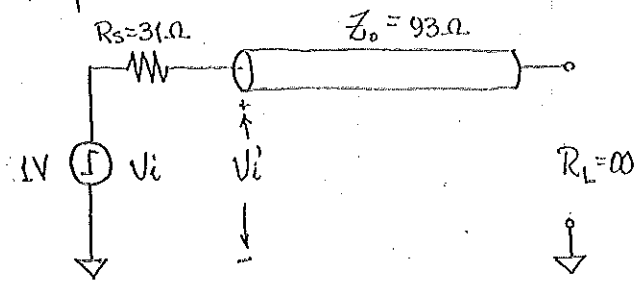

- Mismatched line at both ends
- Lattice diagram used to keep track of
 - Magnitude
 - Polarity
 - Time

Assuming step is applied at $t=t_0$


$$V_i' = \frac{Z_o}{Z_o + R_s} V_i = \frac{93}{93 + 31} \times 1 = 0.75V \leftarrow \text{This is } V_f \text{ for } t_0$$

Since $R_s \neq Z_o \neq R_L \Rightarrow$ Reflections will develop

$$\Gamma_l = \frac{\infty - 93}{\infty + 93} = +1$$

$$\Gamma_s = \frac{31 - 93}{31 + 93} = -0.5$$

Lattice Diagram:

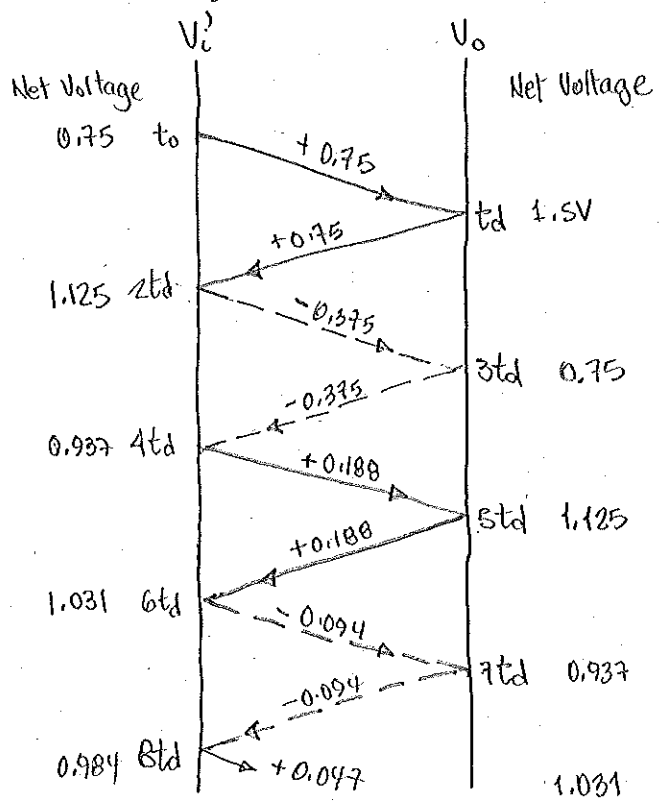

- Input @ t_0 is 0.75V
- After t_d , V_o' is $V_i' + \Gamma_l(V_i') = 1.5V$
- After $2t_d$ the voltage at source

$$V_i + \Gamma_s V_i + \Gamma_s \Gamma_l V_i = 1.125$$

$\underbrace{V_i}_{V_r} \quad \underbrace{\Gamma_s \Gamma_l V_i}_{\text{reflexion } \Gamma_s \Gamma_l V_i}$
- After $3t_d$ at the load

$$V_o^2 = V_i^2 + \Gamma_l V_r = 1.125 - 0.375 = 0.75$$



and so on

Termination Techniques for Fast circuits :

- Parallel Termination
- Serial Termination

Parallel Termination : Eliminates reflections at the end of the transmission line.

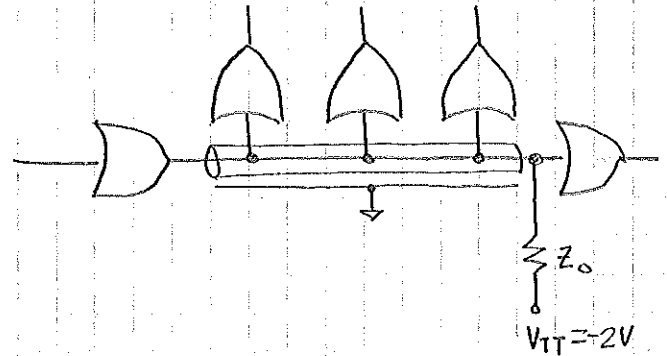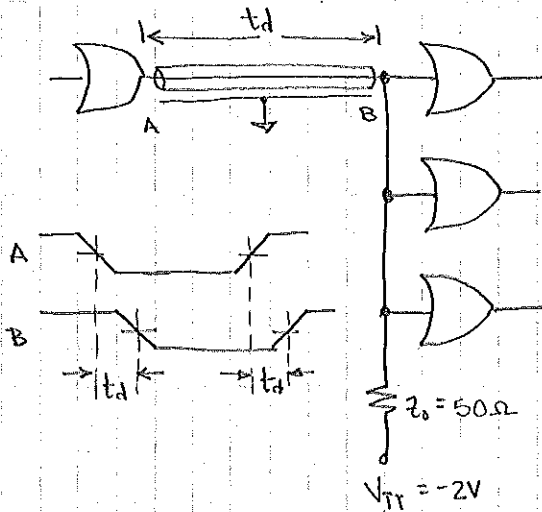loads can be lumped at the end of the line or distributed along the line



- ECL output stage designed to drive a 50Ω line terminated with Z₀ with no reflections (lumped load model). Auxiliary supply V_{TT} required
- In distributed load model, the edge propagation decreases with x along the TL due to the distributed load capacitance

In this case the propagation delay and characteristic impedance will be:


$$\delta = \sqrt{L(C+C_d)} = \sqrt{1 + \frac{C_d}{C}} \delta$$

$$\text{and } Z'_0 = \sqrt{\frac{L}{C+C_d}} = \left(\frac{1}{\sqrt{1 + \frac{C_d}{C}}} \right) Z_0$$

} where C_d is the gate input capacitance (distributed load)

*** See example ***

- An alternative using a single supply :

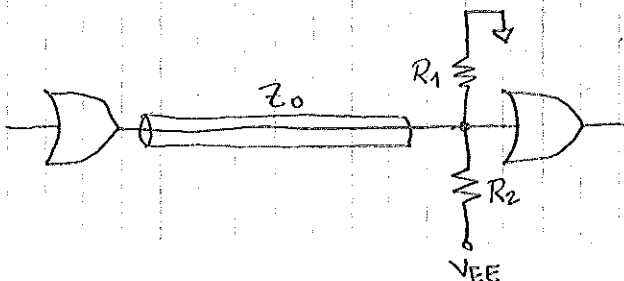

$$R_2 = \frac{V_{EE}}{V_{TT}} Z_0 = 2.6 Z_0$$

$$R_1 = \text{selected such that } R_1 \parallel R_2 = Z_0$$

$$R_1 = \frac{R_2}{1.6}$$


22-141 50 SHEETS
22-142 100 SHEETS
22-144 200 SHEETS



Parallel Termination Example:

- Four identical ECL gates
 - Total capacitance 13 pF
 - Spaced at 5cm intervals
 - 20cm-long microstrip
 - $Z_0 = 68 \Omega$
 - $\epsilon_r = 5$

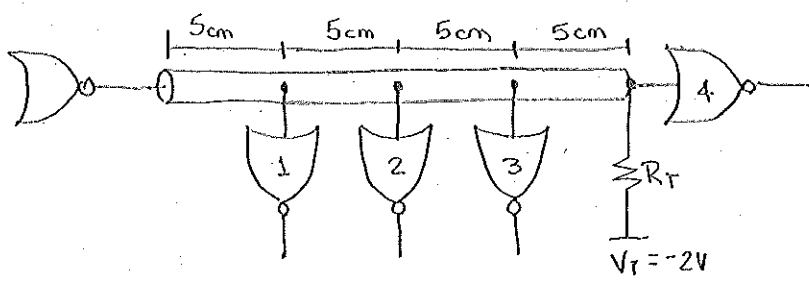• Find the parallel terminating resistor for no reflection @ end



22-141 50 SHEETS
 22-142 100 SHEETS
 22-144 200 SHEETS


1) Line capacitance $C = \frac{\delta}{Z_0}$

$$\delta = 33.35 \sqrt{0.475 \epsilon_r + 0.67} = 33.35 \sqrt{3.045} = 58.19$$

$$C = \frac{58.19}{68} = 0.86 \text{ pF/cm}$$



$$C_d = \frac{C_{total}}{L} = \frac{13 \text{ pF}}{20 \text{ cm}} = 0.65 \text{ pF/cm}$$

$$Z_o' = \frac{Z_0}{\sqrt{1 + C_d/C}} = \frac{68}{\sqrt{1 + \frac{0.65}{0.86}}} = 51.26 \Omega$$


$$\boxed{R_T = 51 \Omega}$$

Series termination: Eliminates reflections at the transmitting end of the line.

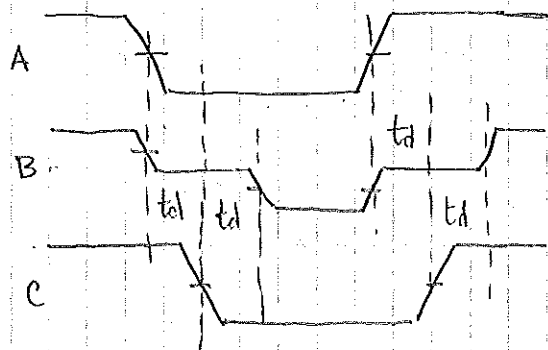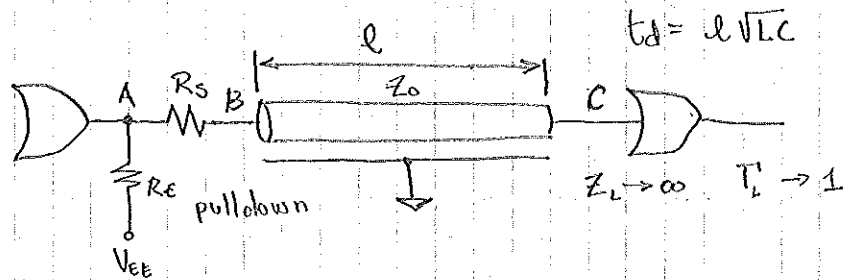Inserts a SERIES resistor to the driver output



- The series termination is useful for open-ended lines or load impedances very high
- The sum of R_s plus the driver output impedance are matched to Z_0
- Reduced crosstalk and reduced power dissipation. Single supply
- Cannot be used with distributed load (half logic swing propagating down the line)
- Slower than parallel termination (larger series impedance)
- Parallel lines used to improve speed

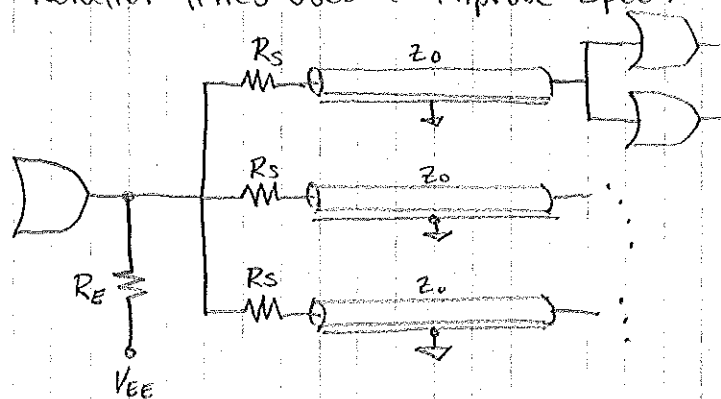

- A low-impedance parallel-terminated line has shorter t_d than a series terminated line with equivalent fan-out. However multiple series terminated operate faster.


22-141 50 SHEETS
22-142 100 SHEETS
22-144 200 SHEETS




- A capacitive load at the end of a T.L. inserts an additional delay to the signal propagation. (Slows down the rising time)

$$t_d' = t_d + \Delta t_d$$

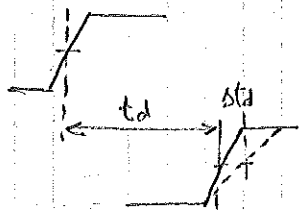
The additional delay can be computed with an RC model in either the series or parallel model.



Series

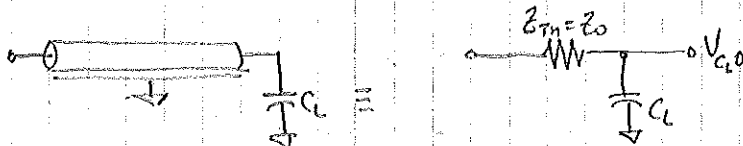

Parallel

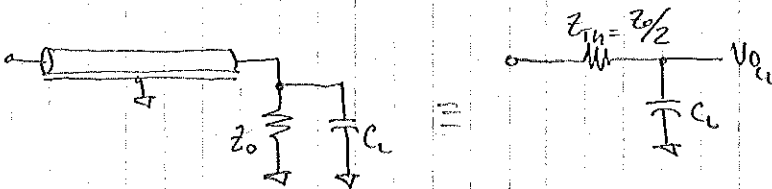

Solution found using Laplace

$$t_{rise, input} = 0.69 \alpha ; \alpha \leftarrow \text{Ramp time}$$

22-141 50 SHEETS
22-142 100 SHEETS
22-144 200 SHEETS

