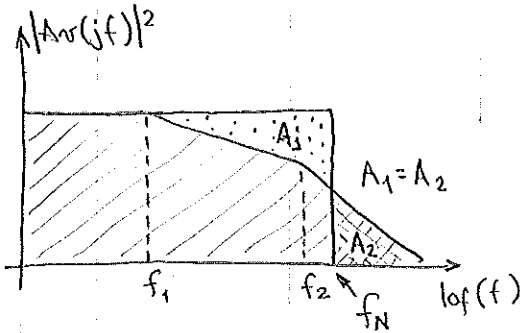
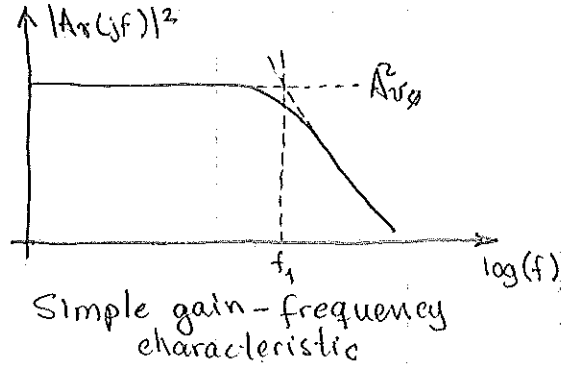


# Noise Bandwidth

- The total noise corrupting a signal in a circuit results from all of the frequency components falling in the circuit BW.
- Not all circuits have a simple gain frequency characteristic
- Consider a multipole circuit with a frequency response:



← In this case the noise component above  $f_1$  cannot be neglected and the total output noise needs to be computed as:

$$\overline{v_{oT}^2} = \int_0^{\infty} S_o(f) df = \int_0^{\infty} |A_v(jf)|^2 S_i(f) df \quad (1)$$

If we consider the EIG to have a white spectrum, i.e.

$$S_i(f) = S_{i0} \leftarrow \text{constant}$$

Then

$$\overline{v_{oT}^2} = S_{i0} \int_0^{\infty} |A_v(jf)|^2 df \quad (2)$$

This integral grows in complexity as the circuit complexity increases.

If consider the response of an equivalent circuit whose transfer function shows a sharp edge at  $f_N$  and with low-frequency gain  $A_{v0}$ , and  $f_N$  computed such that  $\overline{v_{oT}^2} = \overline{v_{oN}^2}$ , then we can write

$$\overline{v_{oT}^2} = S_{i0} A_{v0}^2 f_N \quad (3)$$

and therefore

$$f_N = \frac{1}{A_{v0}^2} \int_0^{\infty} |A_v(jf)|^2 df \quad (4)$$

$f_N$  is the equivalent noise bandwidth of the circuit