

Electrical and I/O Design

Conditions leading to malfunctioning in CMOS gates

- 1) Incorrect supply levels or power noise
- 2) Input noise
- 3) Faulty transistors / connections to transistors
- 4) Incorrect ratios
- 5) Charge sharing in clocked schemes

• CMOS will tolerate limited levels of power supply noise when powered by a well designed supply.

• It was shown that

$$t_{HL} \approx t_{LH} \approx K \cdot \frac{C_L}{\beta V_{DD}}$$

Recall $t_{s,f} = \frac{C_L V_{DD}}{\beta_{EFF} (V_{DD} - V_T)^2}$

β_{EFF} { Transistor geometry
of transistors in series or parallel

C_L { Driver size
No. of load gates
Wiring

Fan-In and Fan-out:

Fan-in: Number of inputs in a single gate

Fan-out: Number of inputs being fed by a single output

Stage Ratio: Increase in transistor size in successive logic gates

The larger the fan-in the larger the stage ratio and the worse the delay because of the larger number of series transistors.

$$t_r = \frac{R_P}{n} (m n C_d + C_w + k C_G)$$

R_p = Effective pull-up resistance
 n = Width multiplier for p-devices
 k = fan-out
 m = fan-in
 $C_G + C_D + C_W = C_L$

Excluding C_w














$$t_r = R_p C_G m r + \frac{R_p C_G}{n} f(k) + \frac{R_p C_G}{n} k$$

with

$$r = \frac{C_d}{C_G}$$

$f(k)$ = a function of the fan-out

             
22-141 50 SHEETS
 22-142 100 SHEETS
 22-144 200 SHEETS




I/O Structures

- The design of I/O pads is a critical stage due to the large off-chip capacitances it typically drives.
- In most cases, pads are selected from a library, according to the process being used.
- Pad size is a function of the bonding wire size to be attached
Typical sizes 100 to 150 μ sq.
- Pad spacing determined by the minimum pitch at which the bonding machine can operate. Typical spaces 150 to 200 μ .
- High pad counts achieved through interdigitation
- Pad styles:

 
CORE LIMITED: Associated I/O circuitry on pad sides
 PAD LIMITED: " " " under pad towards IC center
 ANYWHERE: Placed anywhere on the chip



(a)

 


(b)

 

(c)



(d)

 


(e)

22-141 50 SHEETS
 22-142 100 SHEETS
 22-144 200 SHEETS



- The widths of VDD and ground rails are computed from a worst case power dissipation analysis
- Multiple power supply pads provided to improve noise immunity
- Multiple vias on the interconnect reduces contact resistance
- In the I/O frame it is common practice to place the ground rail in the outermost trace

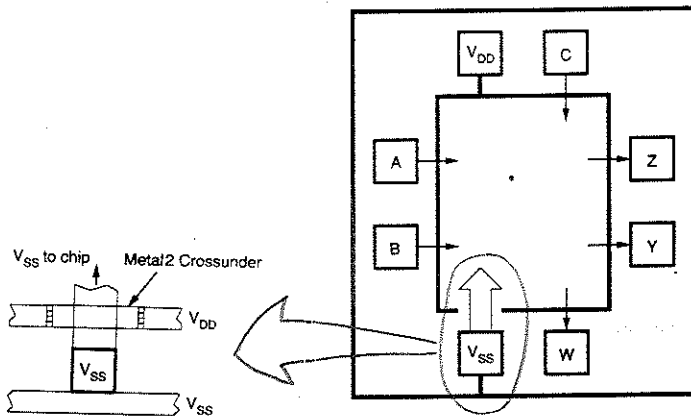22-141 50 SHEETS
22-142 100 SHEETS
22-144 200 SHEETS



Sample I/O pad config with

- Power rails
 - VDD
 - GND

- Input Output signals
 - A • W
 - B • Y
 - C • Z


- Output Pads must have sufficient drive capability to achieve adequate rise and fall times.

Recall $t_p = \frac{C_L V_{swing}}{I_{av}} \Rightarrow$ The larger C_L the larger I_{av} to maintain the same t_p

- Proper I_{av} achieved through transistor sizing

Recall $I_{av} \propto \beta = C_{ox} \mu \frac{W}{L} \rightarrow$ transistor size

 - The large size of the pad driver usually requires an additional buffer to present a small capacitance to the internal circuit



- Due to large I/O currents, guard rings necessary around transistors to prevent latchup
- Large I/O transistors built from parallel smaller transistors
 - Why? - Shorter gate (poly) lines.
 - Parallel metal connections to avoid electro migration

Example layout of an output pad driver.

 


Figure 8.17 Layout of final stage of bonding-pad driver. The plot on the right side is a magnification of the NMOS transistor connected between GND and Out. See also Colorplate 13.

 


Figure 3.3 A bonding pad using metal1 and metal2.

22-141 50 SHEETS
22-142 100 SHEETS
22-144 200 SHEETS




Input Pads

- Input buffers required to withstand/provide
 - High voltages
 - Static discharges } protection required
 - High input impedance ($10^{12} - 10^{13} \Omega$)
- Large voltage accumulation due to input capacitance

$$V = \frac{I \cdot \Delta t}{C_g}$$

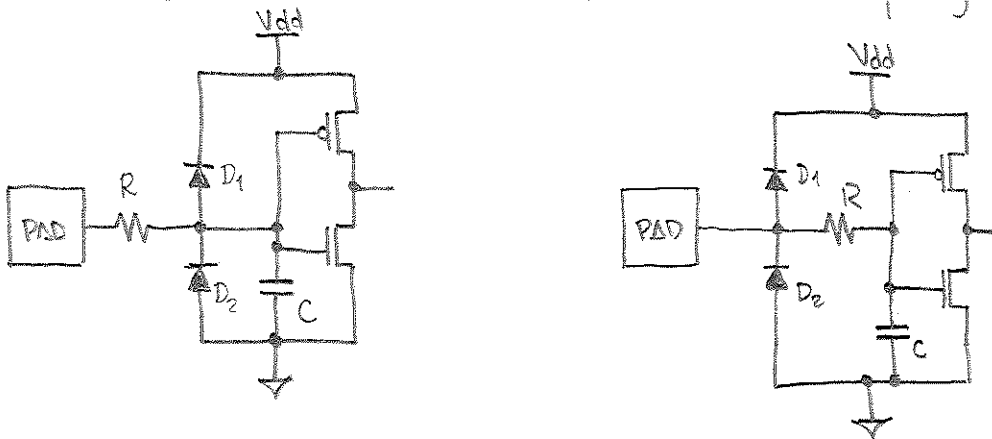Example: $I = 10 \mu A$ $C_g = 0.03 pF$, $\Delta t = 1 \mu s \Rightarrow V = 330V !!!$


- Protective circuit based on resistors & clamping diodes



- Diodes clamp the input voltage above V_{dd} and below V_{ss}
- Resistor limits the peak current
 - $R \approx 200 \Omega$ to $3K \Omega$
- Capacitor symbolizes input capacitance. Note that
 - RC time constant induced at input
 - Must be considered in the design of high-speed inputs.

• Construction:

 
- R: Polysilicon resistor
- Diodes formed with p+ diff on an n+ substrate
- Double guard rings used around input transistors



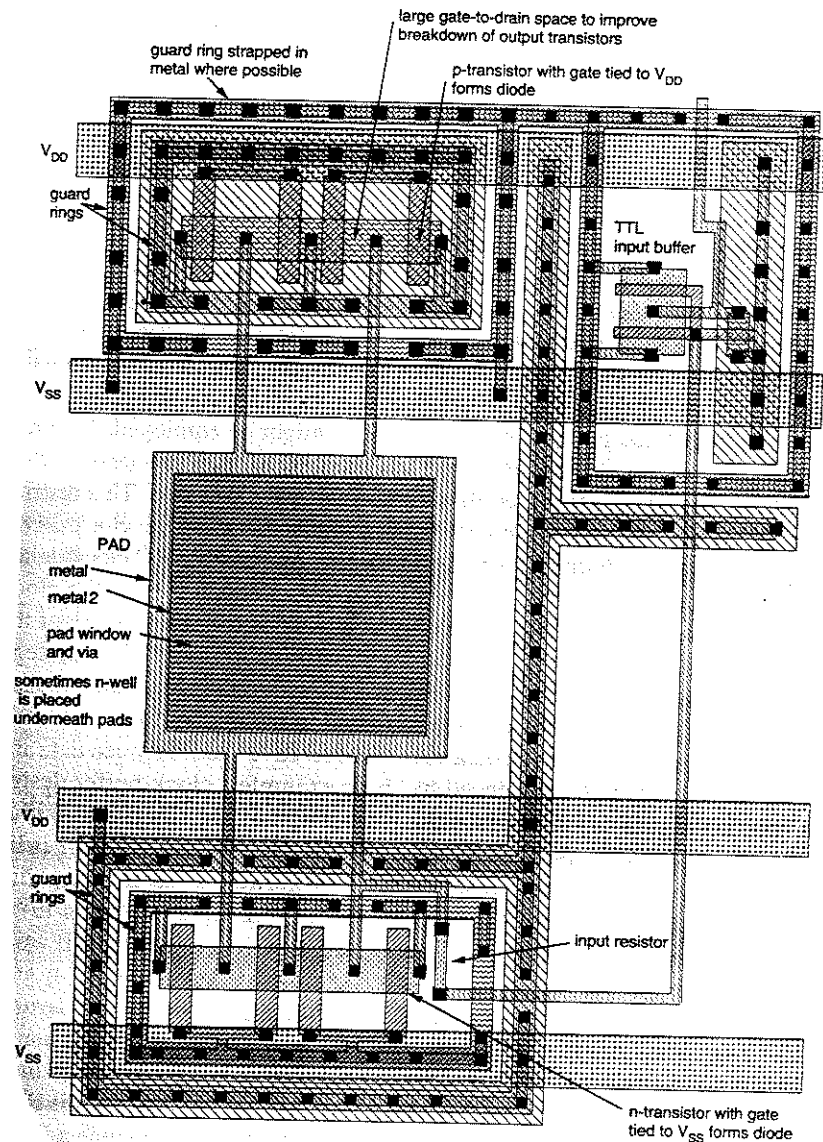22-141 50 SHEETS
22-142 100 SHEETS
22-144 200 SHEETS




- Gate length (L) longer than usual to control breakdown ($\sim 50V$)
- A symbolic input pad layout



- Input pads for clock signals require special considerations:
 - Large internal loading
 - Fast rise and fall time requirements
- Techniques like
 - PLL-based clock re-synchronization & early clock inputs
 - Tri-state buffered multi clock inputs
 - Centralized, chip-wide clock driver

Approaches

 

22-141 50 SHEETS
22-142 100 SHEETS
22-144 200 SHEETS




In a layout, the usual order is:


- 1) Power rails (V_{DD} and GND)
- 2) Clock distribution networks
- 3) Internal logic.

Tri-state & Bidirectional pads

Necessary for bus contending signals

 


(a) Tri-state pad

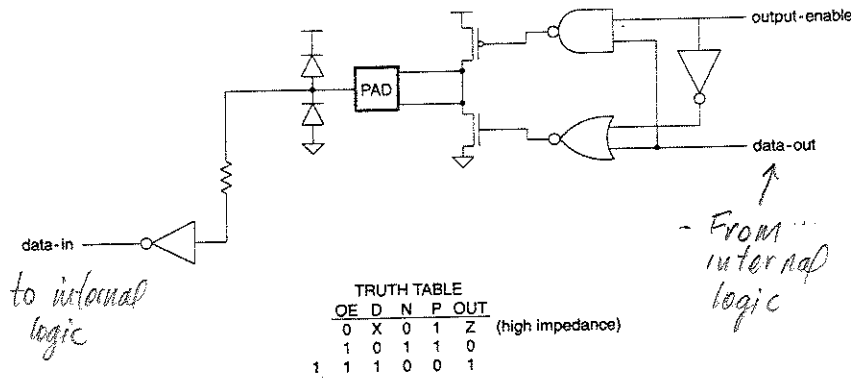

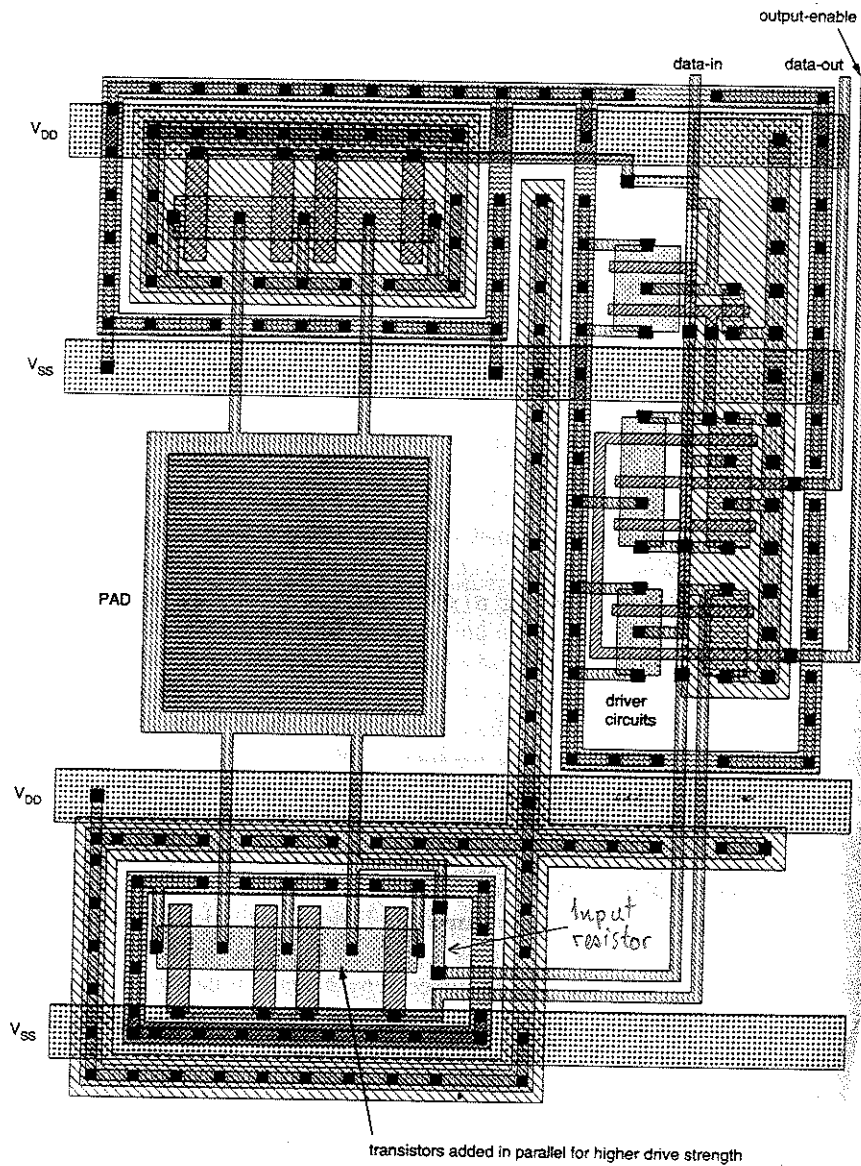(b) Bidirectional pad

- Tri-state configuration makes out to float when OE = 0
- Bi-directional buffer combines input and tri-state pads

- Tri-state pads can be conveniently used as
 - Input pads
 - Output pads
 - Tri-state pads
 } To reduce library size/maintenance
- Symbolic layout of a tri-state pad




 22-141 50 SHEETS
 22-142 100 SHEETS
 22-144 200 SHEETS




Other types of pads

- Discretionary wiring pads
 - Pull-up or Pull-down based on long gate MOS
- Low set-up and hold times
 - Latch integrated in input pad
- Pads with hysteresis
 - Based on schmitt trigger circuit



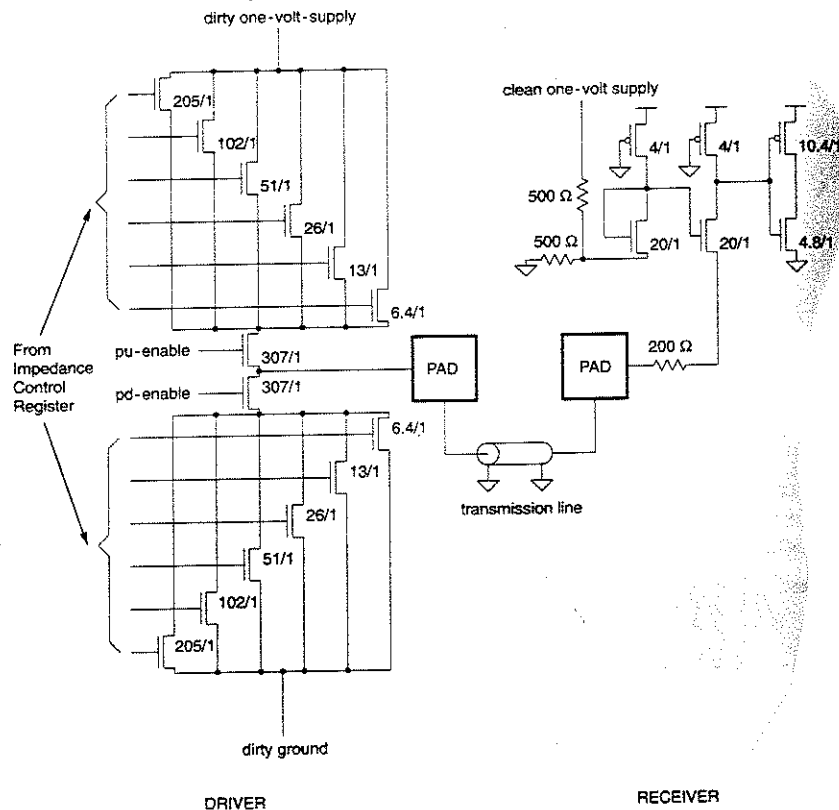- Operation based on different threshold voltages for PUN & PDN
- Reduced Voltage-swing pads used for fast transitions (ECL pads)



22-141 50 SHEETS
22-142 100 SHEETS
22-144 200 SHEETS



Stage Ratio Calculation

Consider the propagation delay of a CMOS inverter

$$t_p = \frac{t_{PLH} + t_{PHL}}{2}$$

$$= \frac{C_L V_{DD}}{2} \left(\frac{1}{K_n (V_{DD} - V_{TN})^2} + \frac{1}{K_p (V_{DD} - |V_{TP}|)^2} \right)$$


Assuming $V_{DD} \gg |V_T|$

$$t_p \approx \frac{C_L}{2V_{DD}} \left(\frac{1}{K_n} + \frac{1}{K_p} \right) \Rightarrow \text{Driver circuit required to handle large loads (large } C_L)$$

Cascading Inverter Stages:

t_p optimization ($t_{PLH} = t_{PHL}$) achieved sizing K_p & K_n according to the $\epsilon = \mu_n/\mu_p$ ratio. \leftarrow True only for a single gate

When multiple inverters are cascaded:

 

$$C_L = (C_{gp1} + C_{dn1}) + (C_{gp2} + C_{on2}) + C_W$$

Assuming PMOS α times wider than NMOS

$$\alpha = \frac{W_P/L_P}{W_n/L_n} \Rightarrow C_{gp} = \alpha C_{gn}, C_{gp} = \alpha C_{gn}$$

$$\Rightarrow C_L = (1 + \alpha)(C_{dn} + C_{gn}) + C_W = (1 + \alpha)C_n + C_W$$

where $C_n = C_{dn} + C_{gn}$


$$\Rightarrow t_p = \frac{(1 + \alpha)C_n + C_W}{2V_{DD}} \left(\frac{1}{K_n} + \frac{1}{K_p} \right) = \frac{(1 + \alpha)C_n + C_W}{2V_{DD} K_n} \left(1 + \frac{\epsilon}{\alpha} \right) \left\{ \begin{array}{l} \text{Using } \frac{W_P}{L_P} = \alpha \frac{W_n}{L_n} \\ \text{and } \mu_p = \mu_n/\epsilon \\ K_p = \frac{\alpha}{\epsilon} K_n \end{array} \right.$$

taking $\partial t_p / \partial \alpha = 0$ and isolating α^* $\alpha^* = \sqrt{\epsilon \left(1 + \frac{C_W}{C_n} \right)}$

When $C_W \ll C_n$, $\alpha^* \rightarrow \sqrt{\epsilon}$ \leftarrow True in inverter chains.

Note that for $\epsilon = 2.5$, $\alpha^* = 1.6 \Rightarrow$ Optimal t_p does not occur for the symmetrical case.

Single Inverter as Driver

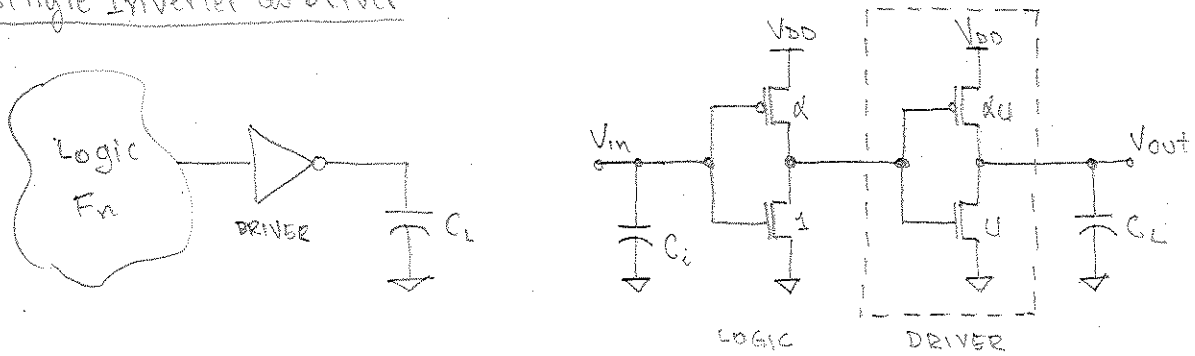

Assume: $C_L = x C_i$, $W_p = \alpha W_n$

Driver transistors are u times larger than logic

Find the value of u that optimizes $t_p = t_{p, \text{logic}} + t_{p, \text{drv}}$

Let t_{p0} be the propagation delay of a minimum-size gate with a unit fan-out. Then

$$t_p \approx \underbrace{u t_{p0}}_{\text{logic}} + \underbrace{\frac{x}{u} t_{p0}}_{\text{driver}} = \left(u + \frac{x}{u}\right) t_{p0}$$

- The logic stage will be u times slower because of the increased driver size
- The driver itself benefits from u to drive the x -times larger load.

To find the optimal size make $\frac{\partial t_p}{\partial u} = 0$ and solve for u^*

$$\frac{\partial t_p}{\partial u} = \left(1 - \frac{x}{u^2}\right) t_{p0} \therefore u^* = \sqrt{x} \quad \text{making } t_p^* = 2\sqrt{x} t_{p0}$$

When deciding whether or not to introduce a buffer-driver, just compare the single delay case versus the logic-driver case.

So it'll be worth only if $x t_{p0} > 2\sqrt{x} t_{p0} \therefore x > 4$ justifies the buffer insertion


Multi-stage Buffer-driver

When C_L is too large, a single buffer might still yield poor t_p

Example: $x = 1000$: $t_p^* = 2\sqrt{1000} t_{p0} = \underline{\underline{64 t_{p0}}} < 1000 t_{p0}$

↑ still large

Solution: Insert N stages.

 

- Divide the delay equally by N stages. Achieved by scaling-up all stages by a constant factor u .

Thus for each stage $t_{p_{stg}} = u \cdot t_{p0}$, where $u = C_{out}/C_{in}$

- For the last stage, $C_L = x C_{in} = u^N C_{in}$, yielding

$$t_p = N \cdot u \cdot t_{p0}, \text{ and } N = \frac{\ln(x)}{\ln(u)}$$

- Make

$$\frac{\partial t}{\partial u} = \frac{\partial}{\partial u} \left[u \cdot \frac{\ln(x)}{\ln(u)} \right] t_{p0} = 0 \quad \therefore u^* = e = 2.7182$$

and $t_p^* = e \ln(x) t_{p0} = e \ln\left(\frac{C_L}{C_i}\right) t_{p0}$

Optimal Buffer Design: Consecutive stages scale-up exponentially.

In practice, $u=3$ or $u=4$ are rather accepted:

 


Figure 8.13 t_p/t_{p0} versus u for various values of x .

Table 8.4 t_{op}/t_{p0} versus x for various driver configurations.

x	Unbuffered	Single Buffer	Cascaded Buffers
10	10	6.3	6.3
100	100	20	12.5
1000	1000	63	18.8
10,000	10,000	200	25.0

22.141 50 SHEETS
22.142 100 SHEETS
22.144 200 SHEETS

