

MOS Inverters

Digital Electronics - INEL 4207



Prof. Manuel Jiménez

With contributions by:
Rafael A. Arce Nazario



Objectives:

- Introduce MOS Inverter Styles
 - Resistor Load
 - Enhancement Load – Saturated / Linear
 - Depletion
 - Complementary (CMOS)
- Perform DC analysis of the circuits

Ideal Inverter

  


MOS Devices

  

- Operation regions (Enhancement)

- $V_{GS} < V_T$: cutoff, $V_{out} = V_{DD}$
- $V_{GS} > V_T, V_{DS} > V_{GS} - V_T$: saturation
- $V_{GS} > V_T, V_{DS} < V_{GS} - V_T$: linear

MOS Devices

 

K = device transconductance
 λ = channel-length modulation

• Operation regions

- $V_{GS} < V_T$: cutoff, $V_{out} = V_{DD}$

$$I_D \approx 0$$

- $V_{GS} > V_T, V_{DS} < (V_{GS} - V_T)$: linear


$$I_D = \frac{k}{2} [2(V_{GS} - V_T)V_{DS} - V_{DS}^2]$$

- $V_{GS} > V_T, V_{DS} > (V_{GS} - V_T)$: saturation


$$I_D = \frac{k}{2} (V_{GS} - V_T)^2$$

$$I_D = \frac{k}{2} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

Static Parameters

 


 
- **VOH** = max output voltage when output is “1”
- **VOL** = min output voltage when output is “0”
- **VIL** = max input voltage which can be interpreted as “0”
- **VIH** = min input voltage which can be interpreted as “1”



$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$


MOS Inverter - Resistor Load

  

$|V_{GS}| < V_T$ device is open circuit



$|V_{GS}| > V_T$ device conducts with resistance R_{ON}

 

MOS Inverter - Resistor Load : Parameters

V_{OH}

$$V_{OH} = V_{DD}$$

V_{OL}

Assumption: Must verify latter

$$I_{D(lin)} = I_R$$

$$k \left[(V_{DD} - V_T)V_{OL} - \frac{V_{OL}^2}{2} \right] = \frac{V_{DD} - V_{OL}}{R_L}$$

$$\Rightarrow V_{OL} \cong \frac{V_{DD}}{1 + kR_L(V_{DD} - V_T)}$$

MOS Inverter - Resistor Load : Parameters - V_{IL}

$$\frac{k}{2}(V_{GS} - V_T)^2 = \frac{V_{DD} - V_{out}}{R_L}$$

$$\frac{dV_{out}}{dV_{in}} = -1$$

$$\frac{dV_{out}}{dV_{in}} = -\frac{dI_D}{dV_{in}} \frac{dV_{out}}{dI_D} = -1$$

$$\frac{dI_D}{dV_{in}} = \frac{d}{dV_{in}} \frac{k}{2} (V_{in} - V_T)^2 = k(V_{in} - V_T)$$

$$\frac{dV_{out}}{dI_D} = \left(\frac{dI_D}{dV_{out}} \right)^{-1} = \left(\frac{d}{dV_{out}} \left(\frac{V_{DD} - V_{out}}{R_L} \right) \right)^{-1} = -R_L$$

$$\frac{dV_{out}}{dV_{in}} = -\frac{dI_D}{dV_{in}} \frac{dV_{out}}{dI_D} = -k(V_{in} - V_T)R_L = -1$$

$$V_{IL} = V_T + \frac{1}{kR_L}$$

MOS Inverter - Resistor Load : Parameters - V_{IH}

$$\frac{k}{2} \left[2(V_{IH} - V_T)V_{out} - V_{out}^2 \right] V_{out} = \frac{V_{DD} - V_{out}}{R_L} \quad (1)$$

$$\frac{dV_{out}}{dV_{in}} = - \frac{dI_D}{dV_{in}} \frac{dV_{out}}{dI_D} = -1.0$$

$$\frac{dV_{out}}{dV_{in}} = - \frac{dI_D}{dV_{GS}} \frac{dV_{DS}}{dI_D} = - \frac{kV_{DS}}{k[V_{GS} - V_T - V_{DS}]} = -1.0$$

$$V_{out} = \frac{(V_{in} - V_T)}{2}$$

...substitute in (1)

$$k \left[(V_{IH} - V_T) \left(\frac{V_{IH} - V_T}{2} \right) - \frac{1}{2} \left(\frac{V_{IH} - V_T}{2} \right)^2 \right] = \frac{V_{DD}}{R_L} - \frac{V_{IH} - V_T}{2R_L}$$

...solve quadratic expression by V_{IH}

MOS Inverter - Resistor Load : Parameters - V_M

$$V_M$$


$$I_{DS} = \frac{k}{2} (V_{GS} - V_T)^2 = I_R = \frac{V_{DD} - V_{DS}}{R}$$

$$\frac{k}{2} (V_M - V_T)^2 = \frac{V_{DD} - V_M}{R}$$

$$V_M^2 - 2V_M \left(V_T - \frac{1}{kR_L} \right) + \left(V_T^2 - \frac{2V_{DD}}{kR_L} \right) = 0$$

$$\Rightarrow V_M = V_T + \frac{\sqrt{1 + 2kR_L (V_{DD} - V_T)} - 1}{kR_L} \cong V_T + \sqrt{\frac{2(V_{DD} - V_T)}{kR_L}}$$

Effect of R_L on VTC

 

But putting a larger resistance would also mean:



- larger resistor length
- greater switching delays

main disadvantage of resistor load:


- occupies too much chip area (10s or 100s times the area of a single transistor!)

Using enhancement transistors as load devices

  - Justification: Since VLSI resistors occupy too much chip space → use transistor in either saturation or linear region instead of resistor




Saturated enhancement load

 


- Enhancement NMOS with $V_{GS} = V_{DS}$
 - while $V_{OUT} < V_{DD} - V_T$
the transistor will be in **saturation**
because $V_{GS} > V_T$ & $V_{DS} > V_{GS} - V_T$
 - If V_{OUT} tries to go above $V_{DD} - V_T$,
transistor goes **cutoff**
(because $V_{GS} < V_T$)

Saturated enhancement load - VTC

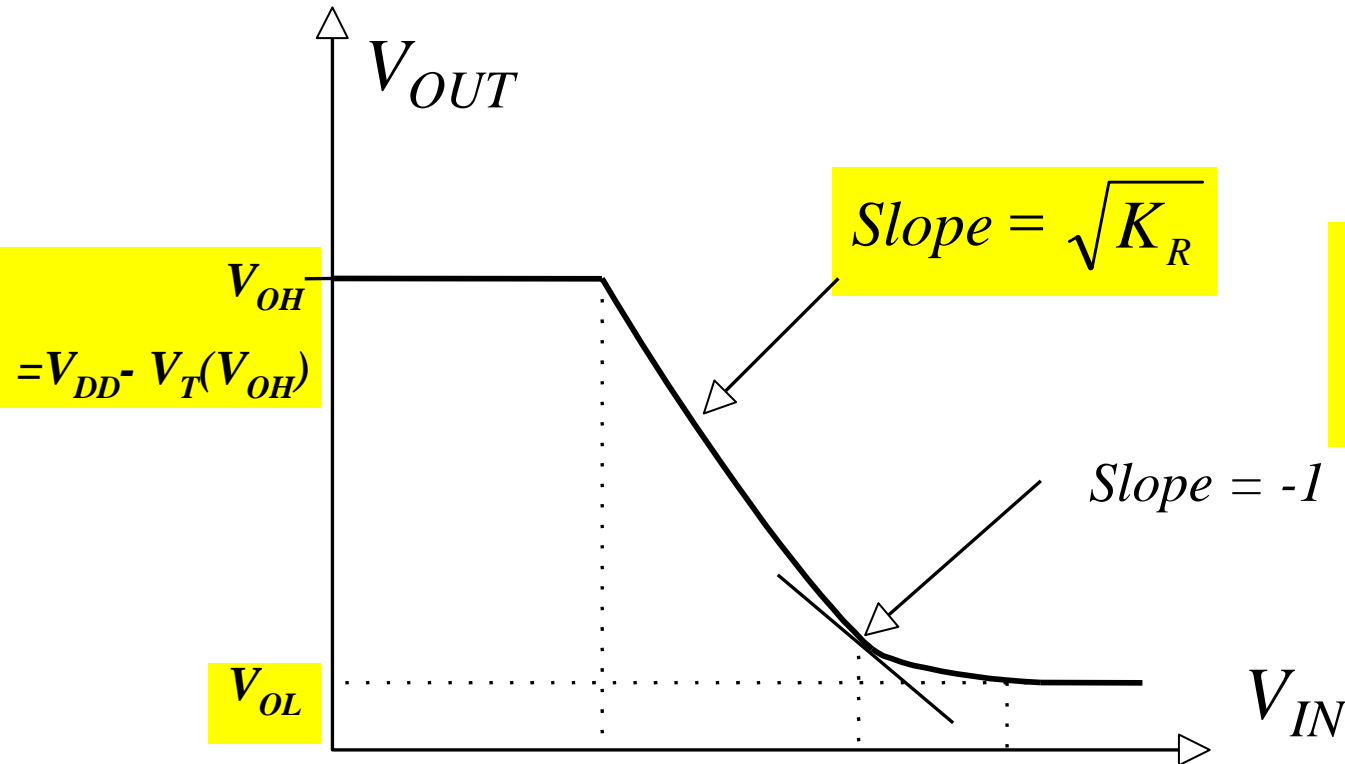


$$K_R = \frac{(W/L)_{inverter}}{(W/L)_{load}}$$
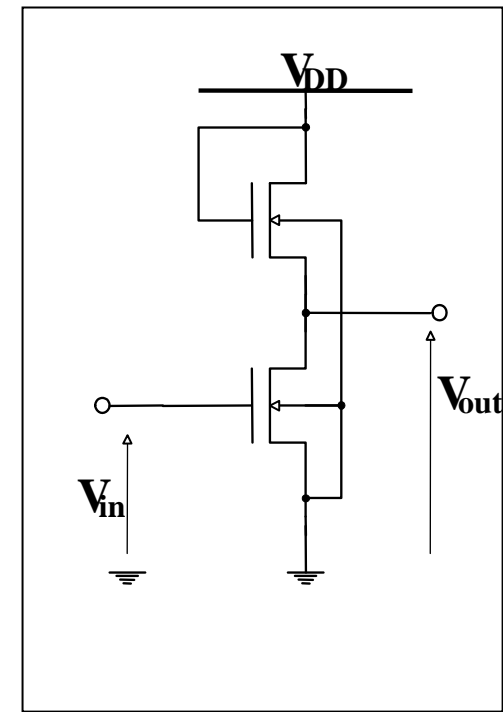
$$V_T = V_{T0} + \gamma \left(\sqrt{V_{SB} + 2\phi_F} - \sqrt{2\phi_F} \right)$$




Linear enhancement load

 

- Enhancement NMOS with $V_{GG} > V_{DD} + V_T$
- since $V_{DS} = V_{DD} - V_{OUT}$
and $V_{GS} = V_{GG} - V_{OUT} > V_{DD} + V_T - V_{OUT}$
→ $V_{DS} < V_{GS} - V_T$

since $V_{GS} > V_T$:
the load is always on **linear region**

Linear enhancement load - VTC

 

Pro:

- $V_{OH} = V_{DD}$



Disadvantage:

- Additional voltage source
- K_R must be even larger than for saturated load for decent slope


Depletion load

- Depletion NMOS with $V_{GS} = 0$


→ $V_{GS} > V_T$: always **conducting**

 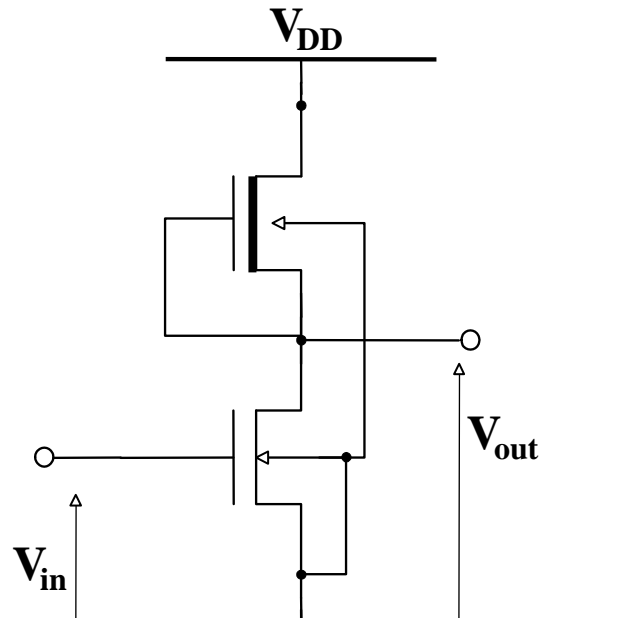

 Good: $V_{OH} = V_{DD}$
 no additional V source
 Bad: addit. fab. process steps




Complementary MOSFET inverter

 

Features:

- Complementary MOS (CMOS) Inverter analysis makes use of both NMOS and PMOS transistors in the same logic gate.
- + All static parameters of CMOS inverters are superior to those of NMOS inverters
- + CMOS is the most widely used digital circuit technology in comparison to other logic families.
 - lowest power dissipation
 - highest packing density
- Increased process complexity (to provide isolated transistors of both polarity types)

Complementary MOSFET (CMOS) inverter

 

Intuitively:

$$\underline{V_{IN} \approx 0}$$

NMOS open ckt. ($V_{GSn} < V_{Tn}$)

PMOS conducting ($V_{GSp} > V_{Tp}$)

$$\rightarrow V_{OUT} = V_{DD}$$

$$V_{OH} = V_{DD} \text{ (Good!)}$$

$$\underline{V_{IN} \approx V_{DD}}$$

NMOS conducting


PMOS open ckt.

$$\rightarrow V_{OUT} = 0$$


$$V_{OL} = 0 \text{ (Great!)}$$

CMOS inverter - VTC

 
1. PMOS linear, NMOS off
2. PMOS linear, NMOS sat
3. PMOS, NMOS both sat
4. PMOS sat, NMOS linear
5. PMOS off, NMOS linear



CMOS inverter – Region 2

 


Region ②

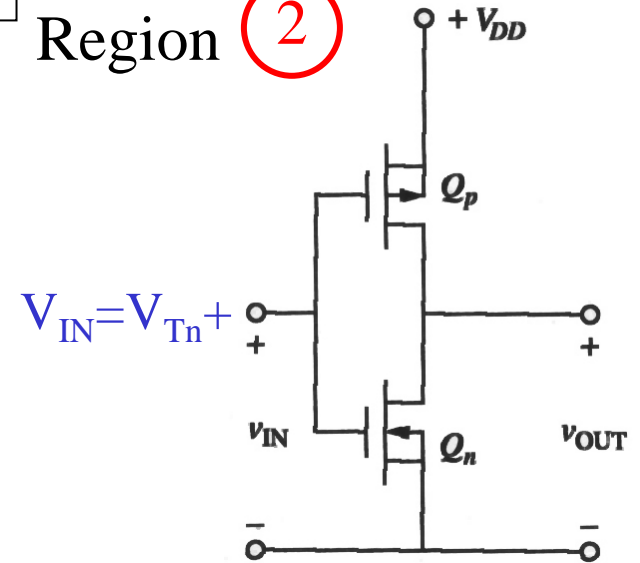

PMOS linear, NMOS saturation

 CMOS inverter – Param. Calculation Example



NMOS linear, PMOS saturation

Calculate V_{IH}

$$I_{Dn} = \frac{k_n}{2} \left[2(V_{IH} - V_{Tn})V_{OUT} - V_{OUT}^2 \right] \quad (1)$$

$$I_{Dp} = \frac{k_p}{2} (|V_{GSp}| - |V_{Tp}|)^2$$


$$\frac{dV_{out}}{dV_{in}} = - \frac{dI_{Dp} - dI_{Dn}}{dV_{in}} \frac{dV_{out}}{dI_{Dp} - dI_{Dn}} = -1$$

$$\frac{dV_{out}}{dV_{in}} = - \frac{k_n V_{OUT} + k_p (V_{DD} - V_{IH} - V_{Tp})}{k_n (V_{IH} - V_{OUT} - V_{Tn})} = -1$$

$$V_{IH} = \frac{2V_{OUT} + V_{Tn} + (k_p / k_n)(V_{DD} - |V_{TP}|)}{1 + (k_p / k_n)}$$

Substitute in (1), then solve for V_{OUT} , finally obtain V_{IH}

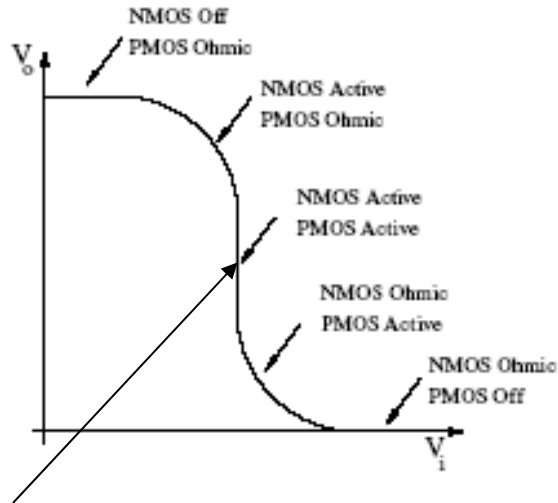CMOS inverter – Param. Calculation Example



NMOS & PMOS saturation

Calculate V_M

$$I_{Dn} = \frac{k_n}{2} (|V_{GSn}| - |V_{Tn}|)^2$$

$$I_{Dp} = \frac{k_p}{2} (|V_{GSp}| - |V_{Tp}|)^2$$

$$\frac{k_n}{2} (|V_M| - |V_{Tn}|)^2 = \frac{k_p}{2} (V_{DD} - V_M - |V_{Tp}|)^2$$

.. Solve for V_M

Summary

- CMOS inverter – most used, smallest, lowest power dissipation, best inverter characteristics.

...base for more complex logic gates


- Calculation of static parameters: V_{IH} ,

V_{IL} , V_{OH} , V_{OL} , V_M .

- Important: Deduce the region of operation of the transistors (verify later)

- V_{IH} , V_{IL} ← slope = -1, use chain rule to simplify calculations

- VTC affected by R , K_R

 

Recordatorio

- Buscar copias de Dr. Jimenez en Reproducciones (\$1-\$2) – “Digital circuits using MOS transistors”