Common Emitter Amplifier

M. Toledo - INEL 4076

## 1. DC Analysis

1. Basic Circuit



Let  $V_{BE} = 0.7V$ .

$$i_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$i_C = \beta i_B = \beta \frac{V_{BB} - V_{BE}}{R_B}$$

$$V_{CE} = V_{CC} - R_C i_C = V_{CC} - R_C \times \beta \times \frac{V_{BB} - V_{BE}}{R_B}$$

Since  $\beta$  is not known precisely, there is considerable uncertainty in the quiescent (operating) point (or Q-point), defined by the (y, x) pair  $(i_C, V_{CE})$ .

### 1.1. Load line

Use

$$i_C = \frac{V_{CC} - V_{CE}}{R_C}$$

to draw load line. Saturation current (y-intercept) is

$$i_{C,sat} = i_C (V_{CE} = 0) = V_{CC} / R_C$$

and x-intercept is

$$V_{CE}(i_C = 0) = V_{CC}$$

The Q-point must be in the load one.

## 2. Four-R Circuit



Use source transformation to transform the circuit as follows:



Observe that

$$R_1 \| R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

Now invoke KVL to write the equation for the base-emitter loop:

$$\begin{array}{rcl} \frac{V_{CC}}{\mathcal{P}_{1}} & \frac{\mathcal{P}_{1}R_{2}}{R_{1}+R_{2}} &=& i_{B}\frac{R_{1}R_{2}}{R_{1}+R_{2}} + V_{BE} + R_{E}i_{E} \\ & i_{B} &=& \frac{i_{E}}{\beta+1} \\ V_{CC}\frac{R_{2}}{R_{1}+R_{2}} &=& \frac{i_{E}}{\beta+1}\frac{R_{1}R_{2}}{R_{1}+R_{2}} + V_{BE} + R_{E}i_{E} \\ V_{CC}\frac{R_{2}}{R_{1}+R_{2}} &=& \left(\frac{1}{\beta+1}\frac{R_{1}R_{2}}{R_{1}+R_{2}} + R_{E}\right)i_{E} + V_{BE} \\ & i_{E} &=& \frac{V_{CC}\frac{R_{2}}{R_{1}+R_{2}} - V_{BE}}{\frac{1}{\beta+1}\frac{R_{1}R_{2}}{R_{1}+R_{2}} + R_{E}} \end{array}$$

Invoking KVL on the collector-emitter loop gives

$$V_{CE} = V_{CC} - i_C \times R_C - i_E \times R_E$$

where  $i_C = \frac{\beta}{\beta+1} i_E$  (often  $\beta >> 1$  and  $i_C \simeq i_E$ ).

### 2.1. Load line

Use

$$i_C = \frac{V_{CC} - V_{CE}}{R_C + R_E}$$

(assuming  $i_C \simeq i_E$ ) to draw load line. Saturation current (y-intercept) is

$$i_{C,sat} = i_C(V_{CE} = 0) = \frac{V_{CC}}{R_C + R_E}$$

and x-intercept is

$$V_{CE}(i_C = 0) = V_{CC}$$

The Q-point must be in the load one.

### Example

Find  $i_C$  if  $V_{CC} = 9V$ ,  $\beta = 100$ ,  $R_1 = 100k\Omega$ ,  $R_2 = 47k\Omega$ ,  $R_E = 3.9k\Omega$  and  $R_C = 6.8k\Omega$ .

$$i_C = \frac{\beta}{\beta+1} i_E = \frac{\beta}{\beta+1} \frac{V_{CC} \frac{R_2}{R_1 + R_2} - V_{BE}}{\frac{1}{\beta+1} \frac{R_1 R_2}{R_1 + R_2} + R_E}$$
$$= \frac{100}{101} \frac{9V \frac{47}{147} - 0.7V}{\frac{1}{101} \frac{100k\Omega \times 47k\Omega}{100k\Omega + 47k\Omega} + 3.9k\Omega} = \boxed{0.51mA}$$

#### **2.2.** Approximation for large $\beta$

If  $i_B \ll i_{R_2}$ , we can neglect  $i_B$  and apply the voltage divider rule to  $R_1$  and  $R_2$  to obtain

$$V_B \simeq V_{CC} \frac{R_2}{R_1 + R_2}$$

so that

$$V_E = V_B - V_{BE} = V_{CC} \frac{R_2}{R_1 + R_2} - V_{BE}$$
$$i_E = \frac{V_E}{R_E} = \frac{V_{CC} \frac{R_2}{R_1 + R_2} - V_{BE}}{R_E}$$

which is equivalent to neglecting the term  $\frac{1}{\beta+1} \frac{R_1 R_2}{R_1 + R_2}$  in our previous result for  $i_E$ .

#### Example

Find  $i_C$  if  $V_{CC} = 9V$ ,  $\beta = \infty$ ,  $R_1 = 100k\Omega$ ,  $R_2 = 47k\Omega$ ,  $R_E = 3.9k\Omega$  and  $R_C = 6.8k\Omega$ .

$$i_C = i_E = \frac{9V\frac{47}{147} - 0.7V}{3.9k\Omega} = \boxed{0.56mA}$$

#### Design example

Problem statement: Design a four resistor biasing network to obtain a Q-point current  $i_{CQ} = 10mA$  with  $V_{CE,Q} = 4V$  using a 12V battery. Assume  $V_{BE} = 0.7V$ . Neglect  $i_B$ .

ANSWER: Since  $V_{CE,Q} = 4V$  and  $V_{CC} = 12V$ , the combined voltage drop in  $R_E$  and  $R_C$  is 8V. Assign voltage drops of 2V and 6V across  $R_E$  and  $R_C$ , respectively. Since  $i_C \simeq i_E$ , this implies that  $R_C \simeq 3R_E$ . Because  $i_{CQ} = 10mA$ , we have

$$8V = 10mA \left( R_C + R_E \right) = 10mA \times 4R_E$$
$$\boxed{R_E = 200\Omega}$$
$$\boxed{R_C = 600\Omega}$$

Since  $V_E = 200\Omega \times 10mA = 2V$ ,

$$V_B = V_E + V_{BE} = 2.7V = 12V \frac{R_1}{R_1 + R_2} = \frac{12V}{1 + R_2/R_1}$$
$$\frac{R_2}{R_1} = \frac{12V}{2.7V} - 1 = 3.444$$

To make sure  $i_{R_1} \gg i_B$  (although we neglected  $i_B$  we know that  $\beta \neq \infty$  but about 100 so  $i_B \simeq 10mA/100 = 0.1mA$ ), select  $R_2 = 10R_E = 2k\Omega$  (other choices are possible, but this gives  $i_{R_2} = 2.7V/2k\Omega = 1.35mA \gg i_B$ ) and  $R_1 = 6890\Omega$ .

Design example



For the following circuit,  $-V_{EE}$  find the values of  $R_E$  and  $R_C$  that will produce a collector current  $i_C = 1mA$  and a collector -to-emitter voltage  $V_{CE} = 5V$ . Assume  $V_{CC} = V_{EE} = 9V$ ,  $V_{BE} = 0.7V$  and  $\beta = 10$ .

$$i_{E} = \frac{\beta + 1}{\beta} i_{C} = 1.1mA = \frac{0V - 0.7V - (-9V)}{R_{E}} = \frac{8.3V}{R_{E}}$$

$$R_{E} = \frac{8.3V}{1.1mA} = \boxed{7546\Omega}$$

$$V_{CE} = V_{CC} - R_{C} \times i_{C} - R_{C} \times i_{E} - (-V_{EE})$$

$$= 18V - 1mA \times R_{C} - 1.1mA \times 7546\Omega = 9.7V - 1mA \times R_{C} = 5V$$

$$R_{C} = \frac{9.7V - 5V}{1mA} = \boxed{4.7k\Omega}$$

## Small-signal analysis

General method:

- 1. Replace DC voltage sources by short circuits.
- 2. Replace DC current sources by open circuits.
- 3. Replace coupling and bypass capacitors with short circuits.
- 4. Redraw diagram to show the AC equivalent circuit.
- 5. Replace transistor by its model.
- 6. Use KVL, KCL and Ohm's law to analyze the circuit and find the desired quantities.

### Transistor model



## CE Amplifier equivalent circuit



(c) AC equivalent circuit with transistor's replaced by its model

# Voltage gain and equivalent resistances removing $R_{sig}$ and $R_L$

To simplify the algebra, remove the non-essential components  $R_1 || R_2$ ,  $R_{sig}$ , and  $R_L$  and calculate the gain from base to collector. The simplified circuit is:



### Gain from collector to base

$$v_{c} = -g_{m}v_{\pi}R_{C}$$

$$v_{b} = v_{\pi} + R_{E}(i_{b} + g_{m}v_{\pi})$$

$$v_{\pi} = i_{b} \times r_{\pi}$$

$$\frac{v_{c}}{v_{b}} = \frac{-g_{m}v_{\pi}R_{C}}{v_{\pi} + R_{E}(i_{b} + g_{m}v_{\pi})}$$

$$= \frac{-g_{m} \times j_{b} \times r_{\pi} \times R_{C}}{j_{b} \times r_{\pi} + R_{E}(j_{b} + g_{m} \times j_{b} \times r_{\pi})}$$

$$= \frac{-g_{m} \times r_{\pi} \times R_{C}}{r_{\pi} + R_{E}(1 + g_{m} \times r_{\pi})}$$

$$g_{m}r_{\pi} = \beta$$

$$\frac{v_{c}}{v_{b}} = \left[ \mu = \frac{-\beta \times R_{C}}{r_{\pi} + R_{E}(1 + \beta)} \right]$$

Input resistance

$$\begin{split} R_{in} &= \frac{v_b}{i_b} \\ v_c &= -g_m v_\pi R_C \\ v_b &= v_\pi + R_E \left( i_b + g_m v_\pi \right) \\ v_\pi &= i_b \times r_\pi \\ v_b &= i_b \times r_\pi + R_E \left( i_b + g_m \times i_b \times r_\pi \right) \\ R_{in} &= \frac{v_b}{i_b} = \frac{\not\!\!\!/ b \times r_\pi + R_E \left( \not\!\!/ b + g_m \times \not\!\!/ b \times r_\pi \right)}{\not\!\!/ b} \\ \hline R_{in} = r_\pi + R_E \left( 1 + \beta \right) \end{split}$$

### **Output resistance**

General procedure to find equivalent resistance:

- 1. Set independent sources to zero
- 2. Apply a test voltage source  $v_t$  across the terminals where the equivalent resistance is to be found.
- 3. Compute current  $i_t$  provided by test source
- 4. Compute equivalent resistance from  $v_t/i_t$

For the amplifier's output resistance, following these steps leads to the following circuit:



The dependent current source will cause  $v_{\pi}$  to reverse polarity. This in turn will reverse the direction of the dependent source's current direction. The only consistent solution is  $v_{\pi} = 0$ , which leads to

$$R_{out} = R_C$$

## Two-port network amplifier model

The amplifier can be represented by its voltage gain  $\mu = v_c/v_b$ ,  $R_{in}$  and  $R_{out}$ 



Two-port network model of the amplifier.



Original circuit, including  $R_{sig}$  and  $R_L$ , using the two-port network model.

To find the gain of the original circuit, include the components previously removed (namely,  $R_1 || R_2$ ,  $R_{sig}$ , and  $R_L$ ) as shown in the second diagram.

Now apply KVL at the two loops to find the voltage gain of the whole circuit.

$$\begin{aligned} A_v &= \frac{v_{out}}{v_{sig}} \\ v_{out} &= \mu v_1 \frac{R_L}{R_{out} + R_L} \\ v_1 &= v_{sig} \frac{R_1 \|R_2\| R_{in}}{R_1 \|R_2\| R_{in} + R_{sig}} \\ v_{out} &= \mu \frac{R_L}{R_{out} + R_L} \frac{R_1 \|R_2\| R_{in}}{R_1 \|R_2\| R_{in} + R_{sig}} v_{sig} \\ \end{aligned}$$

where

$$\mu = \frac{-\beta \times R_C}{r_{\pi} + R_E (1 + \beta)}$$
$$R_{in} = r_{\pi} + R_E (1 + \beta)$$
$$R_{out} = R_C$$

### Example

Find the voltage gain  $A_v = v_{out}/v_{sig}$  for the following amplifier. Assume  $\beta = 100$ . Assume the capacitors are short circuits at the frequency of operation.



The dc analysis was performed in section 2.1 and  $I_{CQ}$  was fount to be 0.51 mA.

$$\begin{split} g_m &= \frac{I_{CQ}}{V_T} = \frac{0.51mA}{0.025V} = 20.4mA \\ r_\pi &= \frac{\beta}{g_m} = \frac{100}{20.4mA} = 4.9k\Omega \\ \mu &= \frac{-\beta \times R_C}{r_\pi + R_E (1+\beta)} \\ &= \frac{-100 \times 6.8k\Omega}{4.9k\Omega + 101 \times 3.9k\Omega} = 1.7 \\ A_v &= \frac{v_{out}}{v_{sig}} = \mu \frac{R_L}{R_{out} + R_L} \times \frac{R_1 ||R_2||R_{in}}{R_1 ||R_2||R_{in} + R_{sig}} \\ R_{in} &= r_\pi + R_E (1+\beta) = 4.9k\Omega + 101 \times 3.9k\Omega = 399k\Omega \\ R_{out} &= R_C = 6.8k\Omega \\ &= -1.7V/V \frac{10k\Omega}{6.8k\Omega + 10k\Omega} \times \frac{32k\Omega ||399k\Omega}{32k\Omega ||399k\Omega + 10k\Omega} \\ &= -1.7V/V \frac{10}{16.8} \frac{29.6}{39.6} = -0.76V/V \end{split}$$

Example

We can increase the gain by including a bypass capacitor across  $R_E$ . The circuit becomes:



The dc analysis is not affected by the presence of the bypass capacitor, but for ac the bypass capacitor is a short circuit and  $R_E$  becomes 0.

$$\begin{split} \mu &= \frac{-\beta \times R_C}{r_{\pi} + R_E \left(1 + \beta\right)} \\ &= \frac{-100 \times 6.8k\Omega}{4.9k\Omega + 101 \times 0} = \frac{-100 \times 6.8k\Omega}{4.9k\Omega} = -139V/V \\ A_v &= \frac{v_{out}}{v_{sig}} = \mu \frac{R_L}{R_{out} + R_L} \times \frac{R_1 \|R_2\| R_{in}}{R_1 \|R_2\| R_{in} + R_{sig}} \\ R_{in} &= r_{\pi} + R_E \left(1 + \beta\right) = 4.9k\Omega + 101 \times 0 = 4.9k\Omega \\ R_{out} &= R_C = 6.8k\Omega \\ A_v &= -139V/V \frac{10k\Omega}{6.8k\Omega + 10k\Omega} \times \frac{32k\Omega \|4.9k\Omega}{32k\Omega \|4.9k\Omega + 10k\Omega} \\ &= -139V/V \frac{10}{16.8} \frac{4.25}{14.25} = -24.7V/V \end{split}$$