### CIRCUIT WITH A DIODE INEL 4076



Diode's law:

$$I_D = I_S \exp\left(v_D / 0.025V\right)$$

Ohms Law:

$$10V = I_D R + v_D \Rightarrow I_D = \frac{10V - v_D}{10k\Omega}$$

Graphical method: Plot both curves. Intercept between curves is solution.



1. Diode's equation, valid for all  $v_D$  and  $i_D$ :

$$I_D = I_S \exp\left(v_D / 0.025V\right)$$

For the given point:

$$1mA = I_S \exp(0.7V/0.025V)$$

Divide second equation into first to get

$$I_D/1mA = \exp\left(\frac{v_D - 0.7V}{0.025V}\right)$$

In logarithmic form

$$v_D = 0.7V + 0.025V \log\left(\frac{I_D}{1mA}\right) \tag{1}$$

2. The Ohms Law:

$$I_D = \frac{10V - v_D}{10k\Omega} \tag{2}$$

- 3. Successive approximation method:
  - (a) Start with a good guess of  $v_D$  (0.7V will do)
  - (b) use (2) to find  $I_D$ ,
  - (c) substitute into equation (1) to find a (better) estimate of  $v_D$ .
  - (d) Repeat steps (b) and (c) until new and old estimates are the same (up to the desired precision)

VD (V)	I <sub>D</sub> (mA)
0.700	0.9300
0.698	0.9302
0.698	0.9302

Very close to 0.7V - diode's voltage is close to constant for a large range of currents

# Successive approx. is a numerical method, like the one use programs like Matlab

#### **Wolfram**Alpha

solve  $(10 - x)/10 = \exp((x - 0.7)/0.025)$ 

Input interpretation:

solve 
$$\frac{10-x}{10} = \exp\left(\frac{x-0.7}{0.025}\right)$$

Result:

$$x = 10 - \frac{W_n(400 \ e^{372})}{40}$$
 and  $n \in \mathbb{Z}$ 

Real solution:

$$x = \frac{1}{40} (400 - W(400 e^{372})) \approx 0.698191$$

### result from <a href="http://m.wolframalpha.com">http://m.wolframalpha.com</a>

## For smaller values of V<sub>SS</sub> the final result will be very different.

Example: find  $I_D$  if (a)  $V_{SS} = 2V$  (b)  $V_{SS} = 1V$  using 1. the graphical method 2. the successive approx. method

Use <u>http://m.wolframalpha.com</u> to confirm your result.