

REPASO EXAMEN 2

INEL 4076 - Marzo 2013


SECCIONES EN LIBRO

- 11-1, 11-2, 11-4
- 13-6 to 13-8 (sect. 13-1 to 13-5 for reference)
- 14-1 to 14-5


TEMAS

- Amplificadores CE con BJT (ganancia, R_{in} , R_{out})
- Modelos de amplificadores
- OPAMPS (análisis ideal, ancho de banda, etc)


COMMON EMITTER AMP

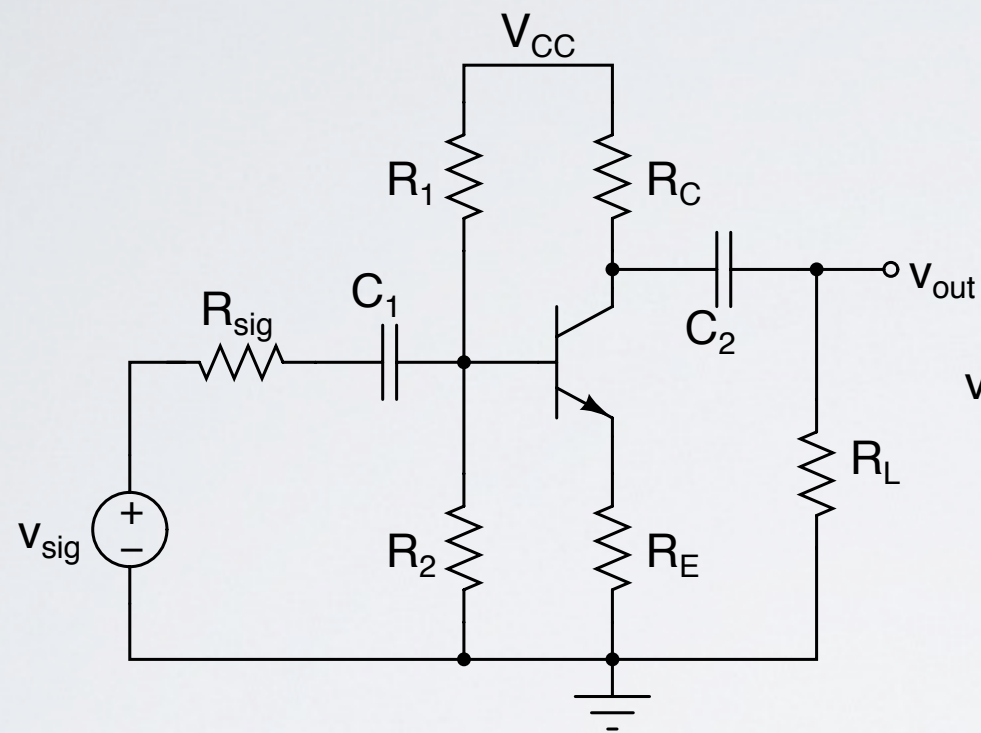


(a) Original circuit

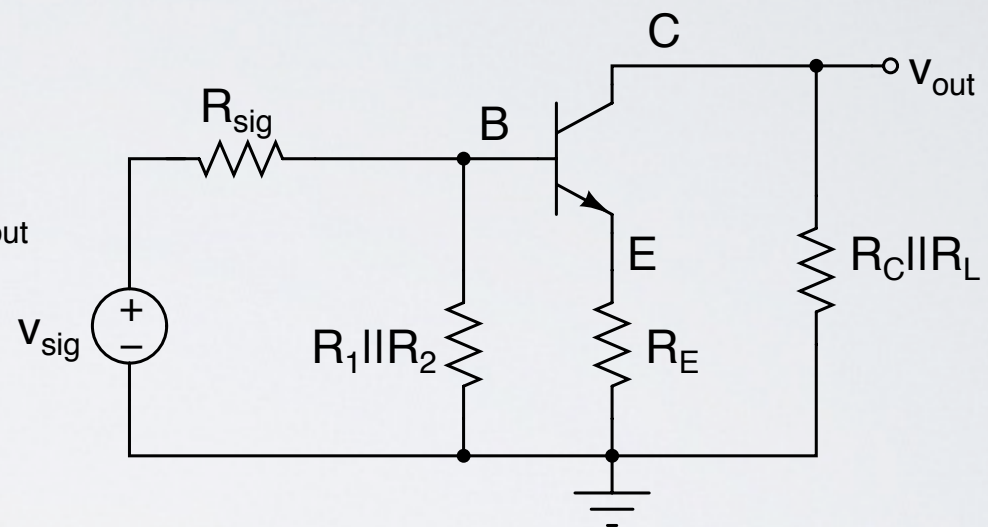

(b) AC equivalent circuit

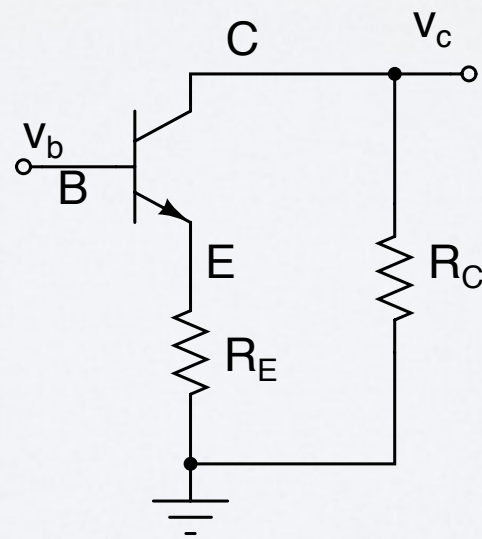


COMMON EMITTER AMP

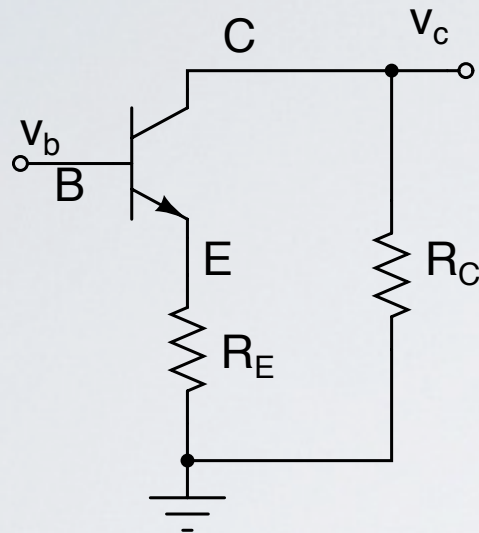


$$\frac{v_c}{v_b} = \frac{-\beta \times R_C}{r_\pi + R_E (1 + \beta)}$$

$$R_{in} = r_\pi + R_E (1 + \beta)$$

$$R_{out} = R_C$$

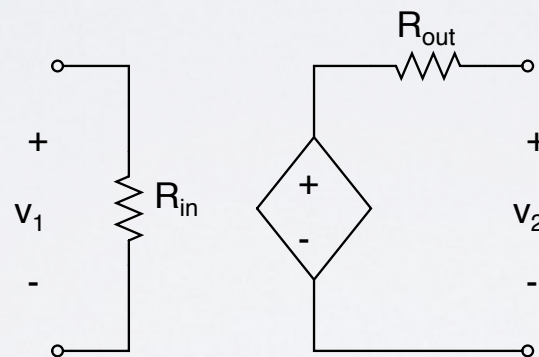


Two-port network model of the amplifier.

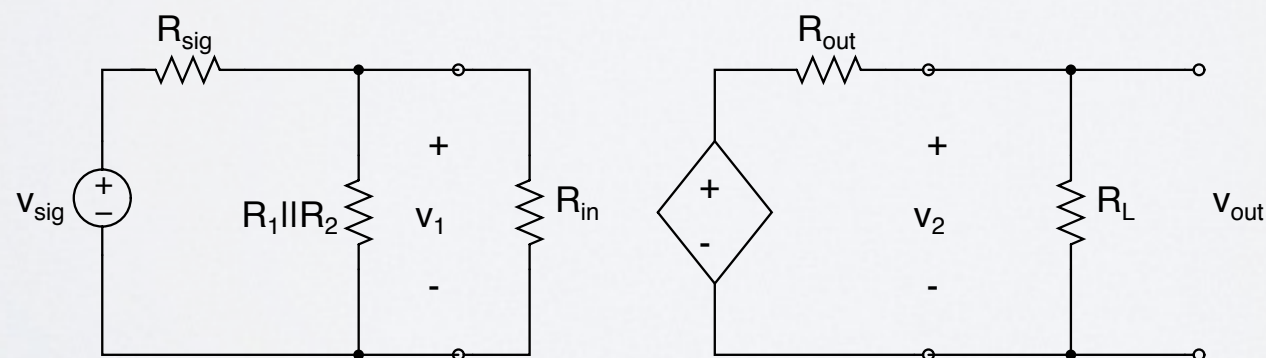


Original circuit, including R_{sig} and R_L , using the two-port network model.

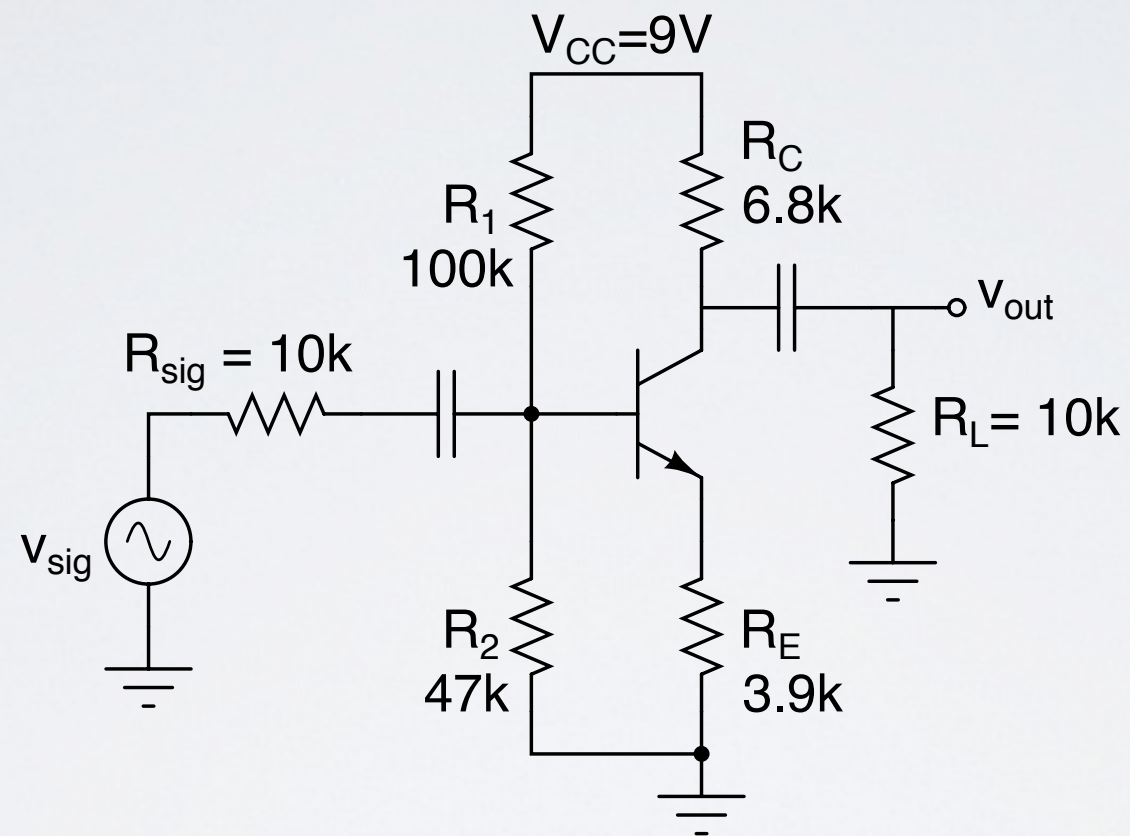Find the voltage gain $A_v = v_{out}/v_{sig}$ for the following amplifier. Assume $\beta = 100$. Assume the capacitors are short circuits at the frequency of operation.



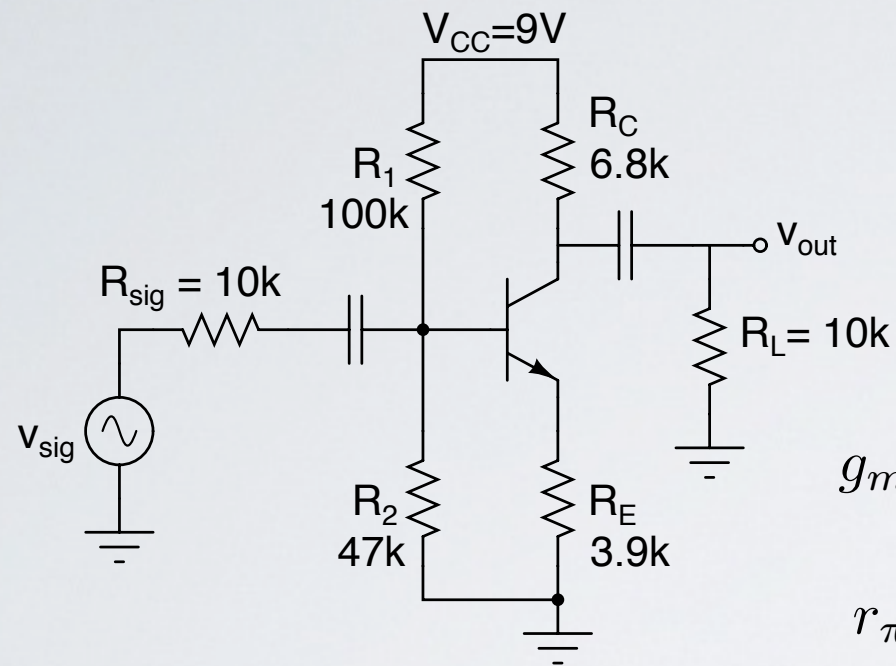Find the voltage gain $A_v = v_{out}/v_{sig}$ for the following amplifier. Assume $\beta = 100$. Assume the capacitors are short circuits at the frequency of operation.



$$i_C = \frac{\beta}{\beta + 1} i_E = \frac{\beta}{\beta + 1} \frac{V_{CC} \frac{R_2}{R_1 + R_2} - V_{BE}}{\frac{1}{\beta + 1} \frac{R_1 R_2}{R_1 + R_2} + R_E}$$

$$= \frac{100}{101} \frac{9V \frac{47}{147} - 0.7V}{\frac{1}{101} \frac{100k\Omega \times 47k\Omega}{100k\Omega + 47k\Omega} + 3.9k\Omega} = \boxed{0.51mA}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.51mA}{0.025V} = 20.4mA$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{20.4mA} = 4.9k\Omega$$

$$\mu = \frac{v_c}{v_b} = \frac{-\beta \times R_C}{r_\pi + R_E (1 + \beta)}$$

$$= \frac{-100 \times 6.8k\Omega}{4.9k\Omega + 101 \times 3.9k\Omega} = 1.7$$

$$A_v = \frac{v_{out}}{v_{sig}} = \mu \frac{R_L}{R_{out} + R_L} \times \frac{R_1 \parallel R_2 \parallel R_{in}}{R_1 \parallel R_2 \parallel R_{in} + R_{sig}}$$


$$R_{in} = r_\pi + R_E (1 + \beta) = 4.9k\Omega + 101 \times 3.9k\Omega = 399k\Omega$$

$$R_{out} = R_C = 6.8k\Omega$$

$$= -1.7V/V \frac{10k\Omega}{6.8k\Omega + 10k\Omega} \times \frac{32k\Omega \parallel 399k\Omega}{32k\Omega \parallel 399k\Omega + 10k\Omega}$$

$$= -1.7V/V \frac{10}{16.8} \frac{29.6}{39.6} = -0.76V/V$$

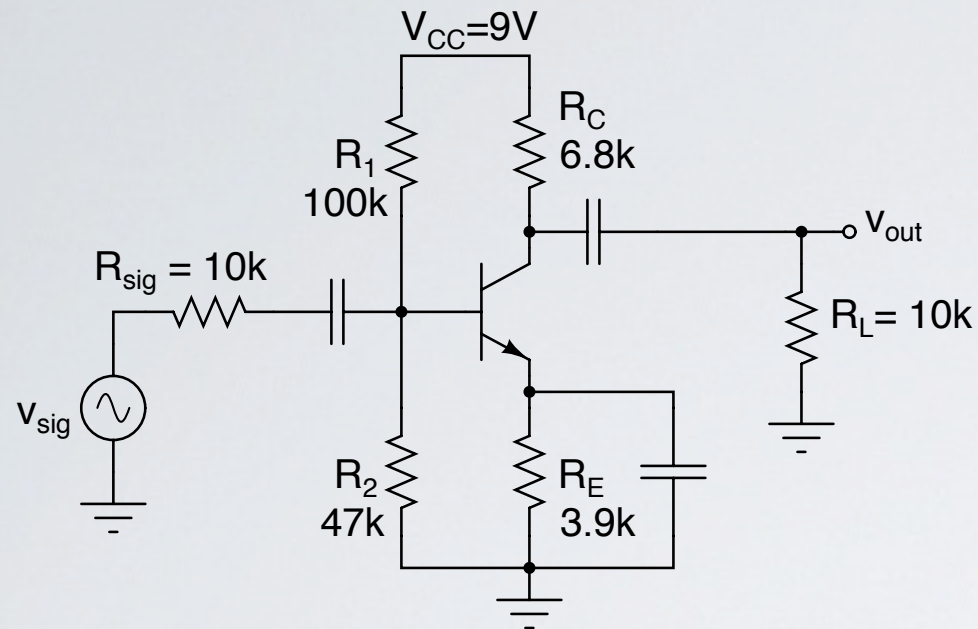We can increase the gain by including a bypass capacitor across R_E . The circuit becomes:



R_E becomes 0.

$$\begin{aligned}\mu &= \frac{-\beta \times R_C}{r_\pi + R_E (1 + \beta)} \\ &= \frac{-100 \times 6.8k\Omega}{4.9k\Omega + 101 \times 0} = \frac{-100 \times 6.8k\Omega}{4.9k\Omega} = -139V/V\end{aligned}$$

$$A_v = \frac{v_{out}}{v_{sig}} = \mu \frac{R_L}{R_{out} + R_L} \times \frac{R_1 \parallel R_2 \parallel R_{in}}{R_1 \parallel R_2 \parallel R_{in} + R_{sig}}$$


$$R_{in} = r_\pi + R_E (1 + \beta) = 4.9k\Omega + 101 \times 0 = 4.9k\Omega$$

$$R_{out} = R_C = 6.8k\Omega$$


$$\begin{aligned}A_v &= -139V/V \frac{10k\Omega}{6.8k\Omega + 10k\Omega} \times \frac{32k\Omega \parallel 4.9k\Omega}{32k\Omega \parallel 4.9k\Omega + 10k\Omega} \\ &= -139V/V \frac{10}{16.8} \frac{4.25}{14.25} = -24.7V/V\end{aligned}$$

- **7.30** Calculate the midband voltage gain of the circuit shown if $\beta = 100$ and $I_E = 2 \text{ mA}$. Calculate the input and output impedances of the circuit.

Figure P7.30

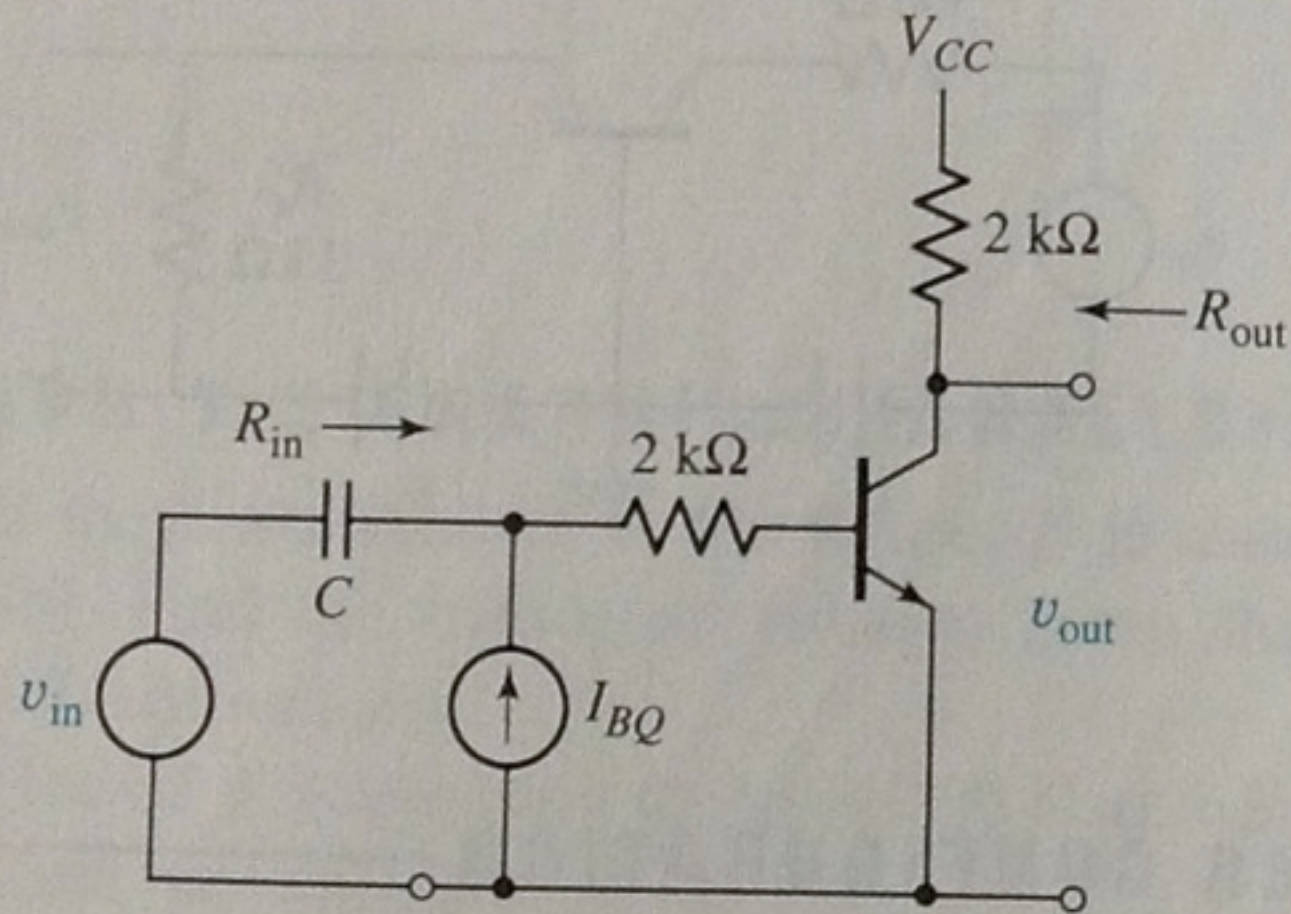


OPAMP IDEAL

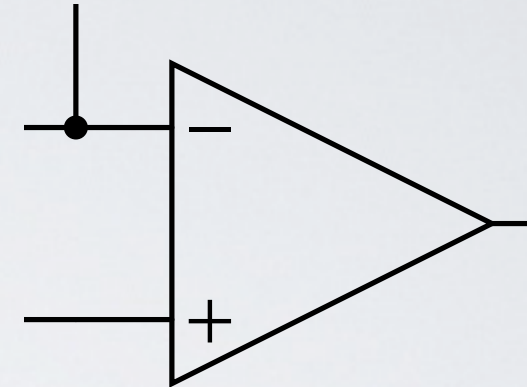


- $A_{MBOA} = \text{infinito}$
- no hay corriente entrando a los terminales - y +
- los voltajes en los terminales - y + son iguales

INVERTING AMPLIFIER

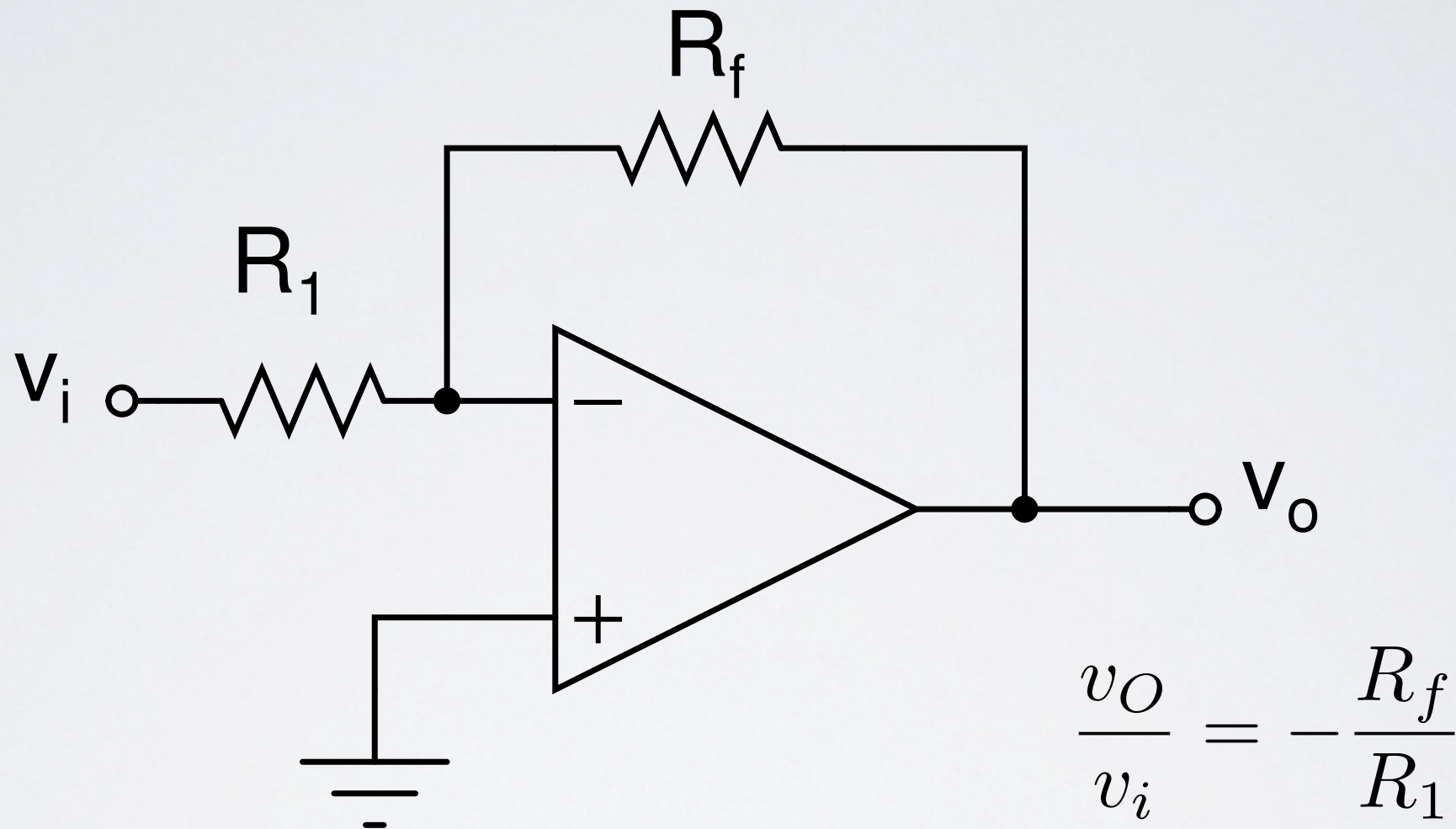


NON-INVERTING AMPLIFIER

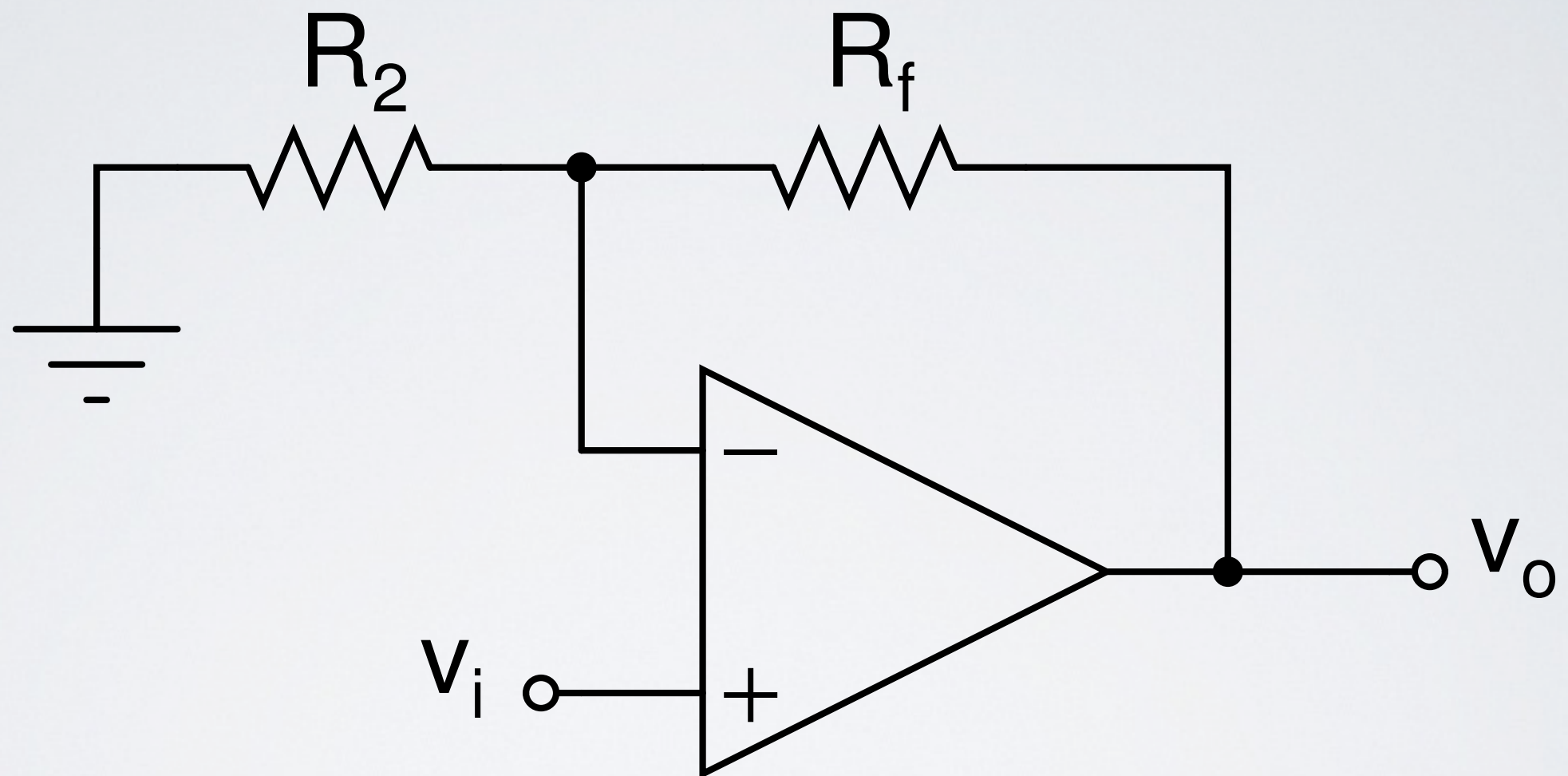

$$\frac{v_o}{v_i} = 1 + \frac{R_f}{R_1}$$

OPAMP NO-IDEAL

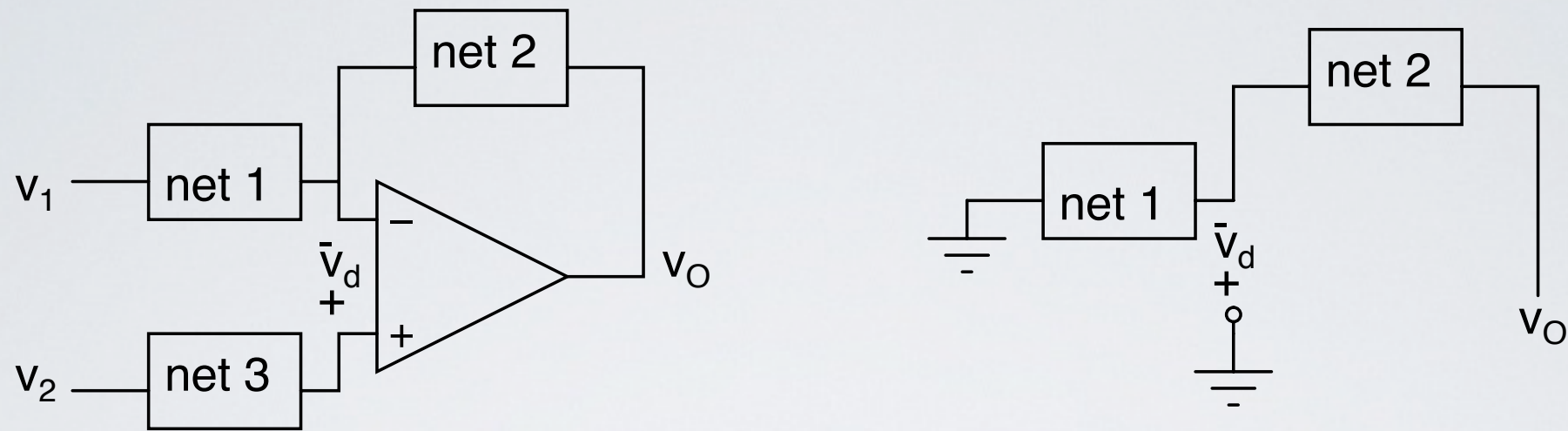

Opamp no-ideal:


- Tiene una ganancia finita A_{MBOA}
- Tiene una frecuencia de ganancia unitaria f_t
- Factor de retro-alimentación: $\beta = -\frac{v_d}{v_O}$
- Ganancia del lazo (loop gain): $L = \beta \times A_{MBOA}$
- Ganancia del amplificador que usa el opamp no ideal:

$$A_f = A_{ideal} \frac{1}{1 + 1/L}$$

- Ancho de banda del amplificador que usa el opamp no ideal: $BW = \beta \times f_t$


- **4.22** The upper corner frequency of the voltage gain for the circuit shown is found to be 150 kHz. What is the GBW of the op amp?

Figure P4.22

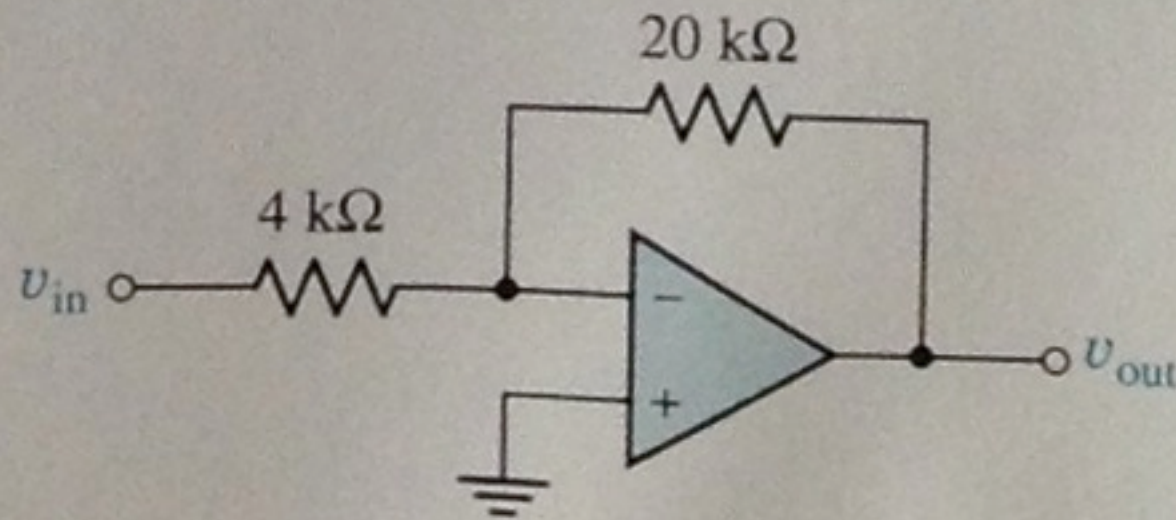

4.21 The upper corner frequency of the voltage gain for the circuit shown is found to be 150 kHz. What is the GBW of the op amp?

Figure P4.21

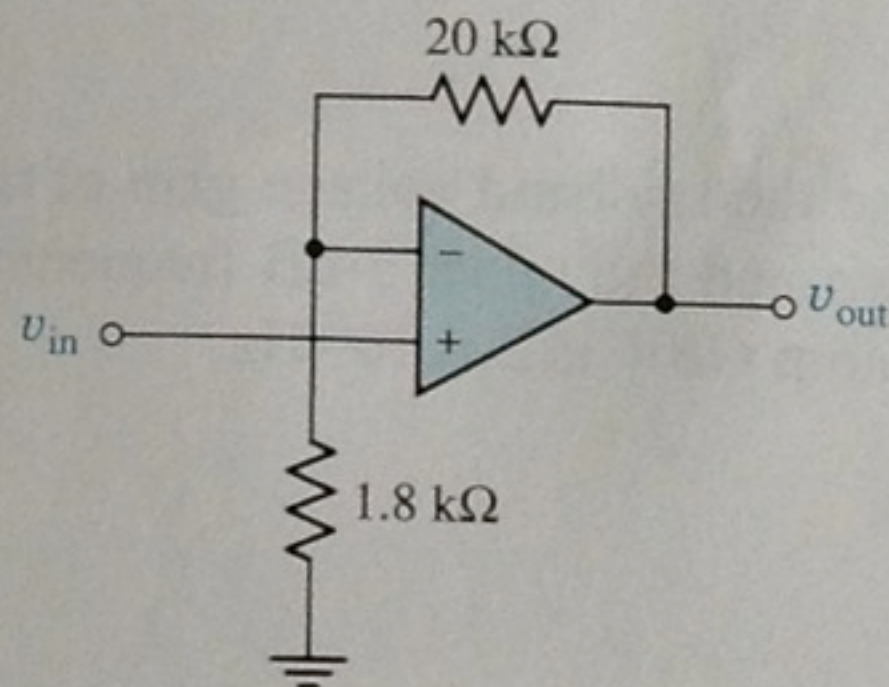

4.25 Calculate the midband voltage gain of the noninverting circuit shown and the upper 3-dB frequency, assuming that the op amp GBW is 2×10^6 Hz.

Figure P4.25

