

SEQUENTIAL LOGIC

INEL 4076 - Spring 2013


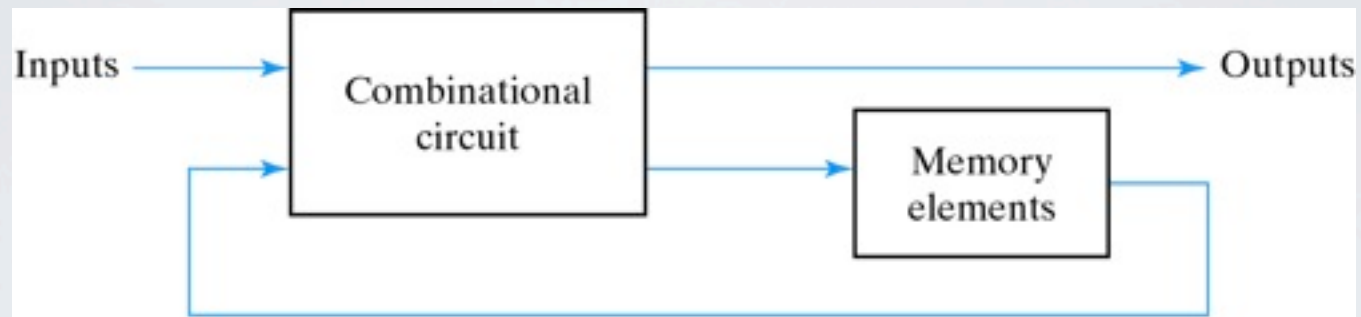


Fig. 5-1 Block Diagram of Sequential Circuit

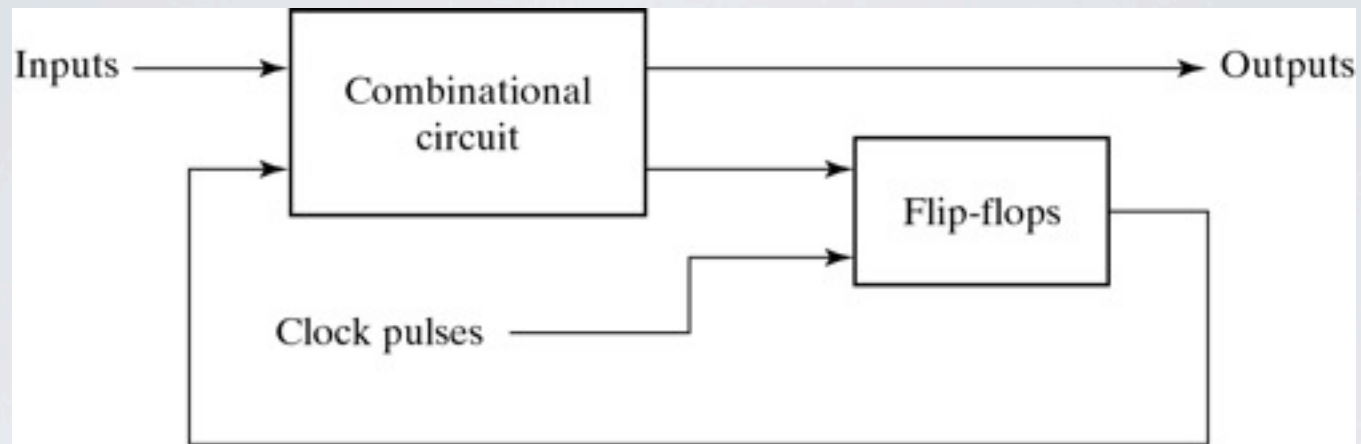

(a) Block diagram



(b) Timing diagram of clock pulses

Fig. 5-2 Synchronous Clocked Sequential Circuit

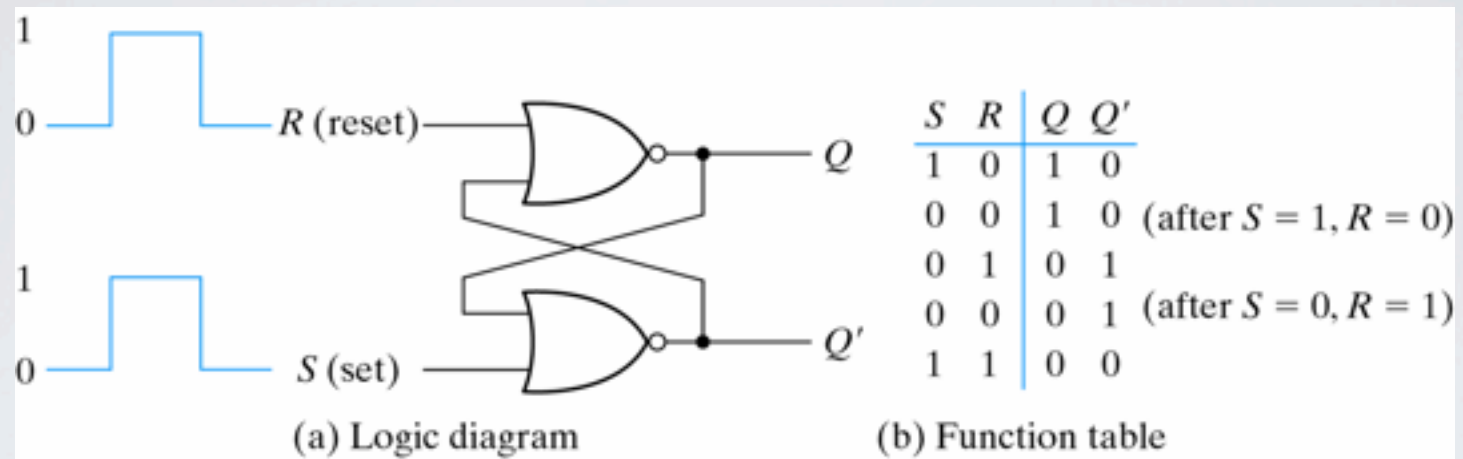


Fig. 5-3 SR Latch with NOR Gates


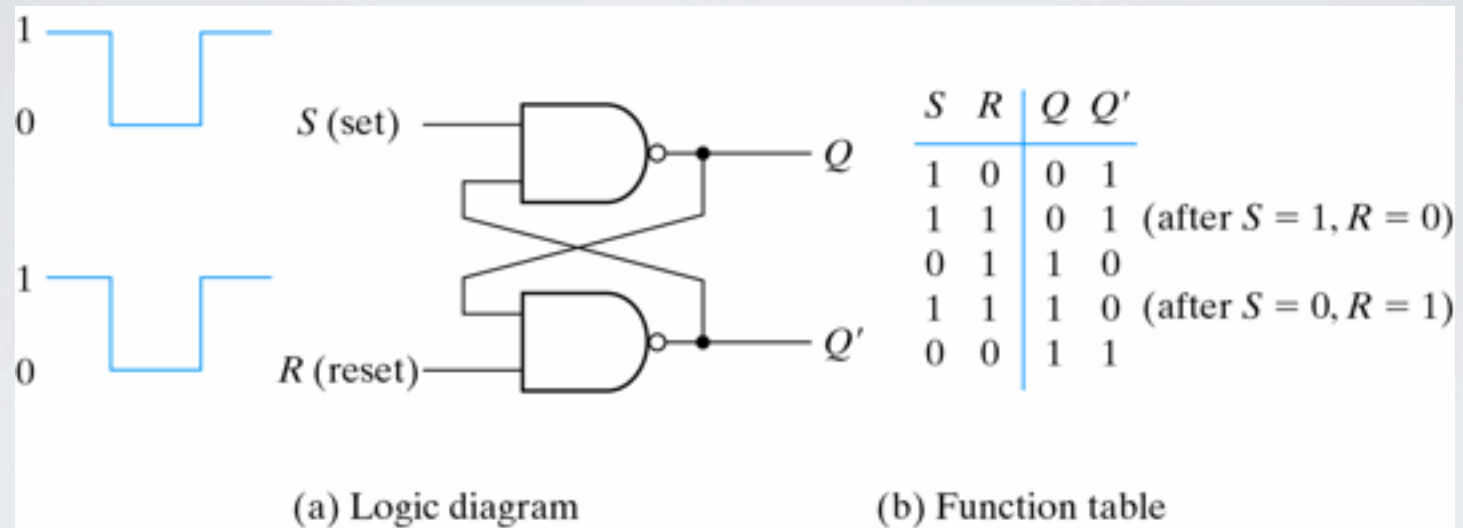


Fig. 5-4 SR Latch with NAND Gates

 


(a) Logic diagram

| C | S | R | Next state of Q |
|-----|-----|-----|-----------------------|
| 0 | X | X | No change |
| 1 | 0 | 0 | No change |
| 1 | 0 | 1 | $Q = 0$; Reset state |
| 1 | 1 | 0 | $Q = 1$; set state |
| 1 | 1 | 1 | Indeterminate |

(b) Function table

Fig. 5-5 SR Latch with Control Input

 

(a) Logic diagram

| C | D | Next state of Q |
|-----|-----|-----------------------|
| 0 | X | No change |
| 1 | 0 | $Q = 0$; Reset state |
| 1 | 1 | $Q = 1$; Set state |

(b) Function table

Fig. 5-6 D Latch

 


Fig. 5-7 Graphic Symbols for Latches

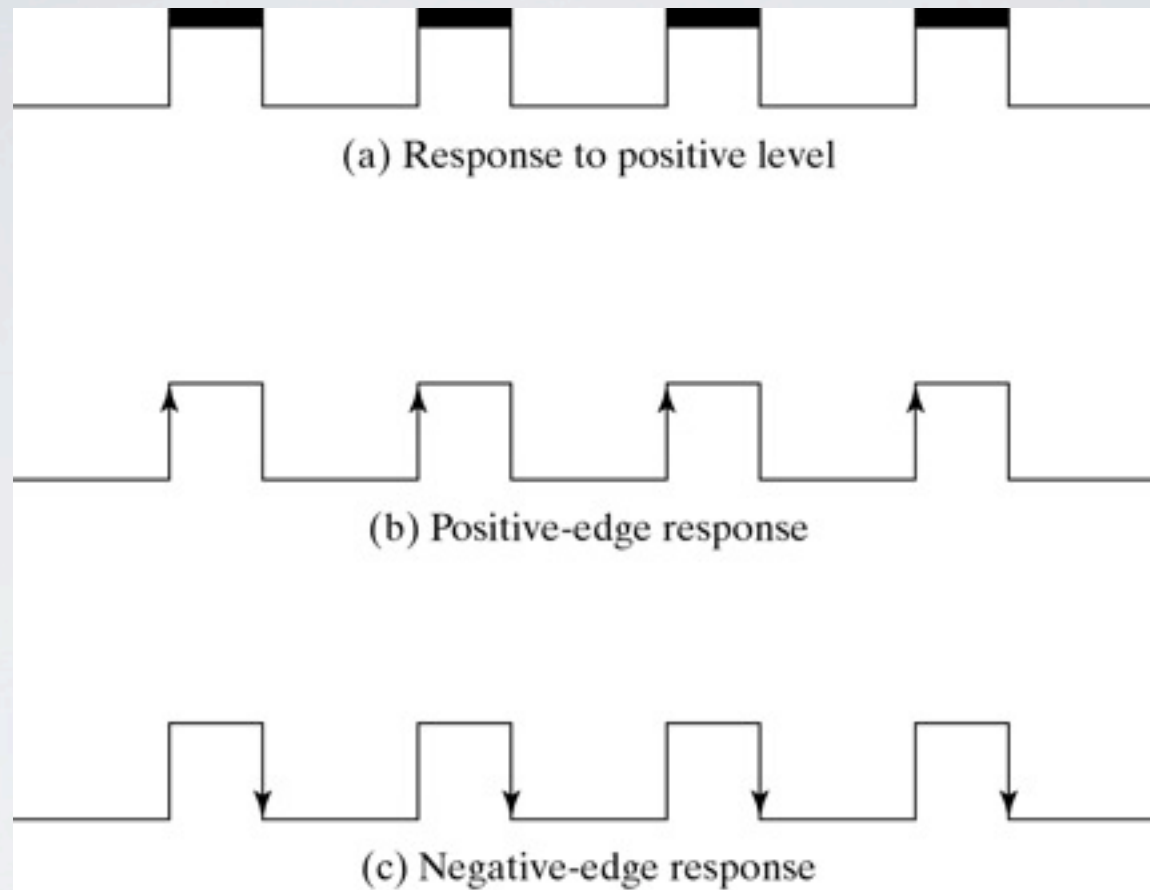


Fig. 5-8 Clock Response in Latch and Flip-Flop

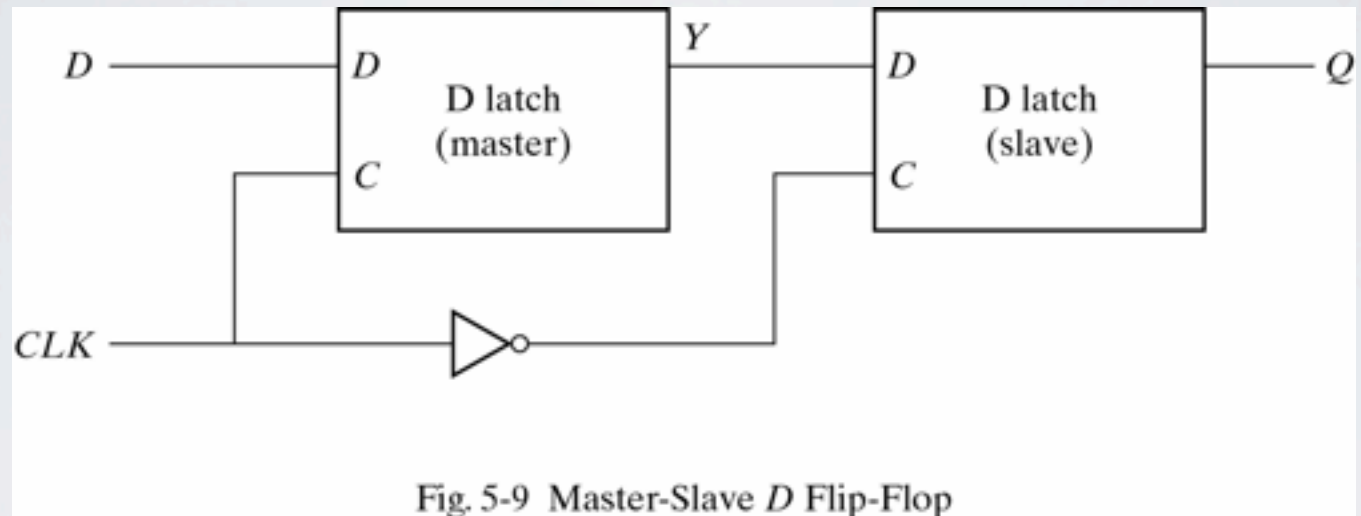


Fig. 5-9 Master-Slave D Flip-Flop

 


Fig. 5-11 Graphic Symbol for Edge-Triggered *D* Flip-Flop

$$A(t + 1) = Ax + Bx$$

$$B(t + 1) = A'x$$

State equations or transition equations

$$y = (A + B)x'$$

Output boolean equation

Table 5-2
State Table for the Circuit of Fig. 5-15

| Present State | | Input | Next State | | Output |
|---------------|---|-------|------------|---|--------|
| A | B | x | A | B | y |
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 | 0 |

Table 5-3
Second Form of the State Table

| Present State | Next State | | Output | |
|---------------|------------|-------|--------|-------|
| | x = 0 | x = 1 | x = 0 | x = 1 |
| AB | AB | AB | y | y |
| 00 | 00 | 01 | 0 | 0 |
| 01 | 00 | 11 | 1 | 0 |
| 10 | 00 | 10 | 1 | 0 |
| 11 | 00 | 10 | 1 | 0 |

/0 represents the output during the present state with the given input


 



Fig. 5-16 State Diagram of the Circuit of Fig. 5-15

Mealy Finite State Machine (FSM) – output is a function of present state and input

Example:

 

 
1. Find the state table
2. Draw the state diagram



(a) Circuit diagram

| Present state | Inputs | | Next state |
|---------------|--------|-----|------------|
| A | x | y | A |
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

(b) State table

 

(c) State diagram

Fig. 5-17 Sequential Circuit with D Flip-Flop

5-6 A sequential circuit with two D flip-flops, A and B ; two inputs, x and y ; and one output, z , is specified by the following next-state and output equations:

$$A(t + 1) = x'y + xA$$

$$B(t + 1) = x'B + xA$$

$$z = B$$

- (a) Draw the logic diagram of the circuit. (b) List the state table for the sequential circuit.
(c) Draw the corresponding state diagram.

Design Procedure

1. From the word description and specifications of the desired operation, derive a state diagram for the circuit.
2. Reduce the number of states if necessary.
3. Assign binary values to the states.
4. Obtain the binary-coded state table.
5. Choose the type of flip-flops to be used.
6. Derive the simplified flip-flop input equations and output equations.
7. Draw the logic diagram.

Sequence detector: circuit that detects 3 consecutive 1's in a string of bits coming through the input line

 


Fig. 5-24 State Diagram for Sequence Detector

 


Fig. 5-25 Maps for Sequence Detector

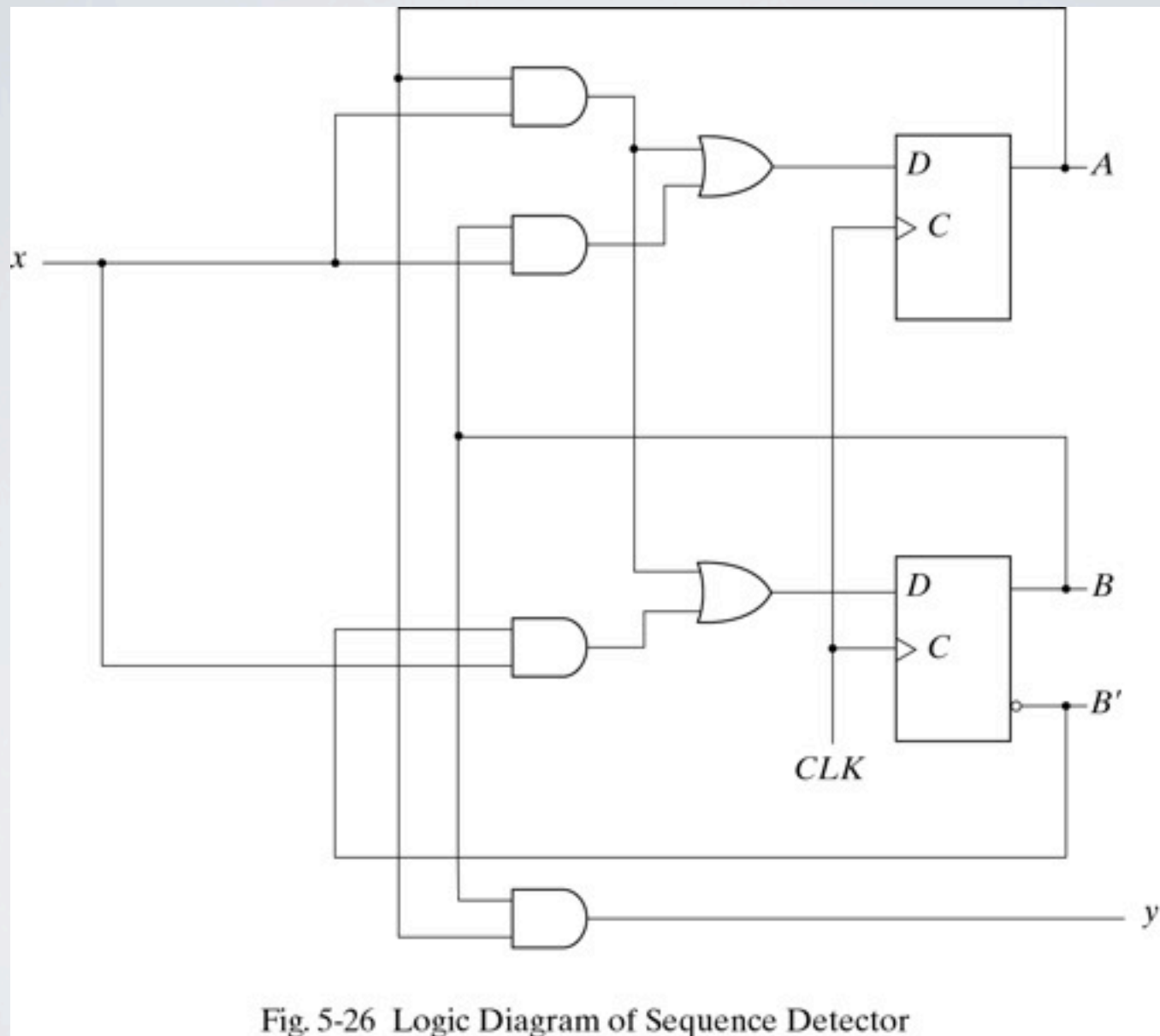


Fig. 5-26 Logic Diagram of Sequence Detector

5-19 A sequential circuit has three flip-flops A, B, C ; one input x ; and one output y . The state diagram is shown in Fig. P5-19. The circuit is to be designed by treating the unused states as don't-care conditions. Analyze the circuit obtained from the design to determine the effect of the unused states.

Use D flip-flops in the design.

 


FIGURE P5-19

5-19 (2)

| Present state | Input | Next state | output |
|---------------|-------|------------|--------|
| ABC | x | ABC | y |
| 000 | 0 | 011 | 0 |
| 000 | 1 | 100 | 1 |
| 001 | 0 | 001 | 0 |
| 001 | 1 | 100 | 1 |
| 010 | 0 | 010 | 0 |
| 010 | 1 | 000 | 1 |
| 011 | 0 | 001 | 0 |
| 011 | 1 | 010 | 1 |
| 100 | 0 | 010 | 0 |
| 100 | 1 | 011 | 0 |

$$d(A, B, C, x) = \sum(10, 11, 12, 13, 14, 15)$$

| AB | Cx | 01 | 11 | 10 |
|----|----|----|----|----|
| 00 | | 1 | 1 | |
| 01 | | | | |
| 11 | x | x | x | x |
| 10 | | | x | x |

$$DA = A'B'x$$

| | | | |
|---|---|---|---|
| 1 | | | 1 |
| | | | 1 |
| x | x | x | x |
| | 1 | x | x |

$$DC = Cx' + Ax + A'B'x'$$

| AB | Cx | 01 | 11 | 10 |
|----|----|----|----|----|
| 00 | 1 | | | |
| 01 | 1 | | 1 | |
| 11 | x | x | x | x |
| 10 | 1 | 1 | x | x |

$$DB = A + C'x' + BCx$$

| | | | |
|---|---|---|---|
| | 1 | 1 | |
| | 1 | 1 | |
| x | x | x | x |
| | | x | x |

$$y = A'x$$

 


Fig. 5-29 State Diagram of 3-Bit Binary Counter

 


Fig. 5-30 Maps for 3-Bit Binary Counter

