
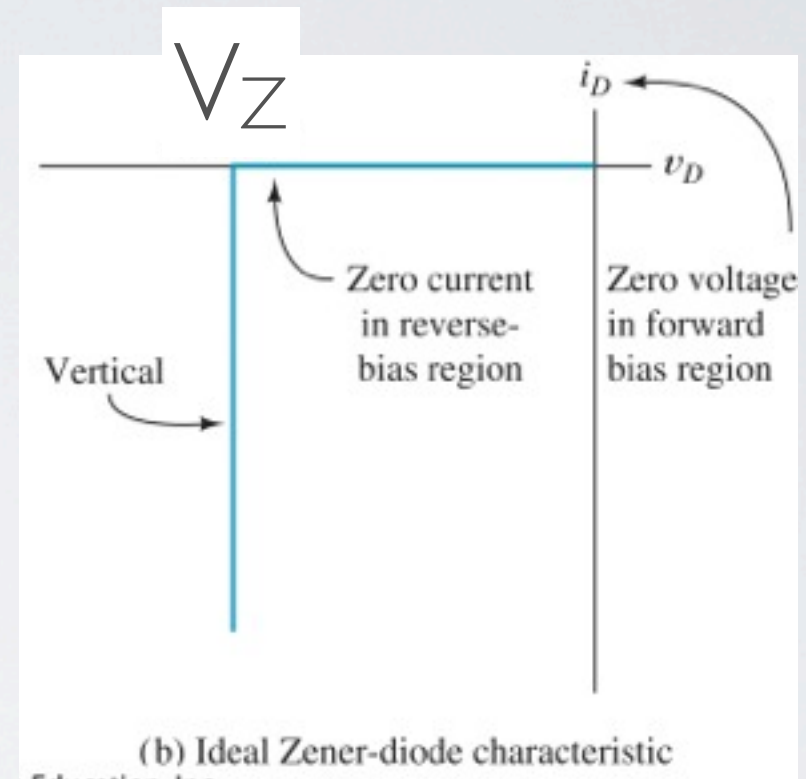


# ZENER REGULATOR


INEL 4076 Fall 2013

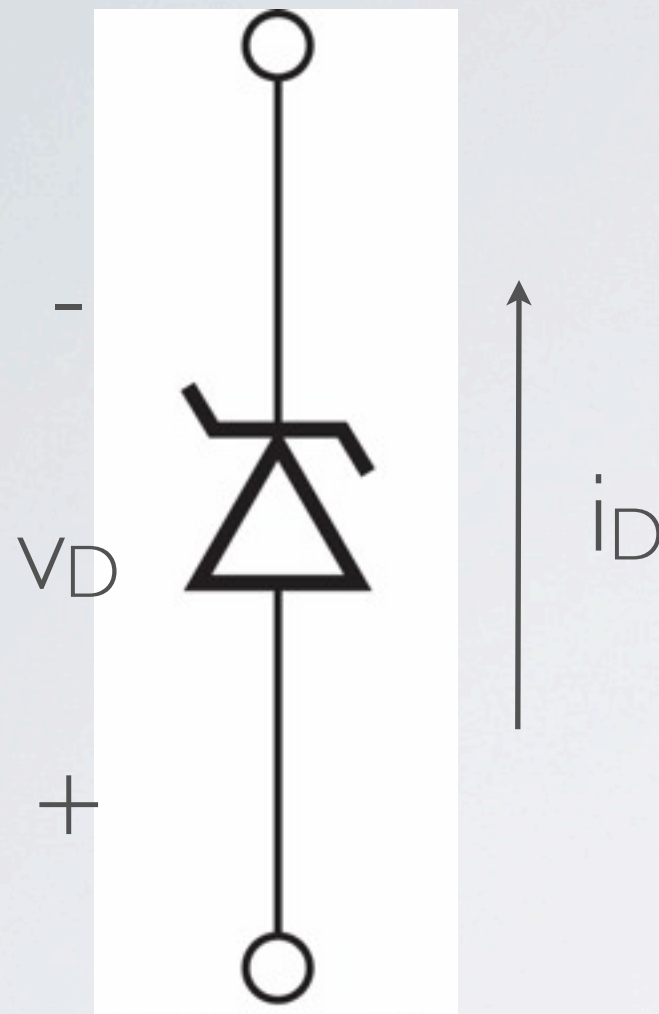

## Zener diodes

- reverse-bias operation
- keeps an approx. constant voltage independent of diode's current

# Voltage regulator

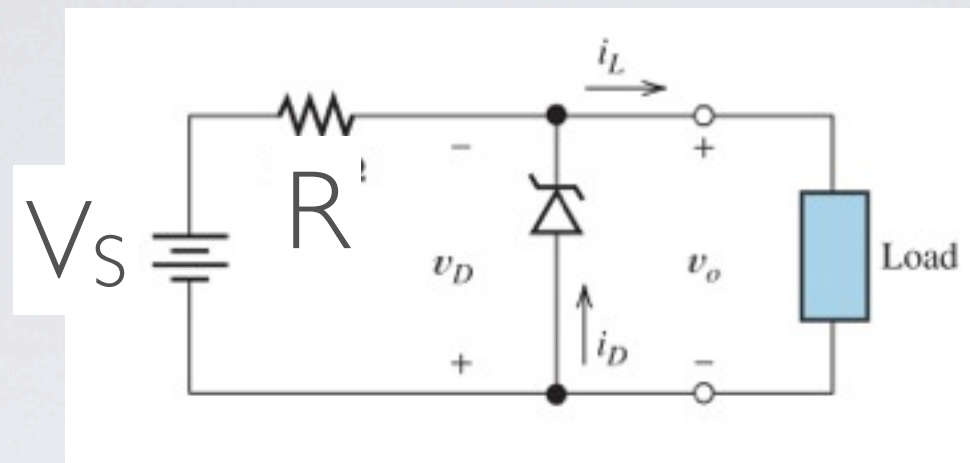

Let:

- $V_Z$  : Zener diode's nominal voltage.
- $i_{Z,min}$  : minimum current through diode required for proper operation.
- $i_{L,max}, i_{L,min}$  : maximum and minimum load's current.
- $V_{S,max}, V_{S,min}$  : maximum and minimum source voltage levels

For proper operation, select  $R$  so that

$$R \leq \frac{V_{S,min} - V_Z}{i_{Z,min} + i_{L,max}}$$

Maximum power dissipated in the resistor:

$$P_{R,max} = \frac{(V_{S,max} - V_Z)^2}{R}$$


Maximum power dissipated in the diode:

$$P_{D,max} = V_Z \times \left( \frac{V_{S,max} - V_Z}{R} - i_{L,min} \right)$$

$D$  and  $R$  must have a power rating greater than  $P_{D,max}$  and  $P_{R,max}$ , respectively.



Piece-wise linear approx.

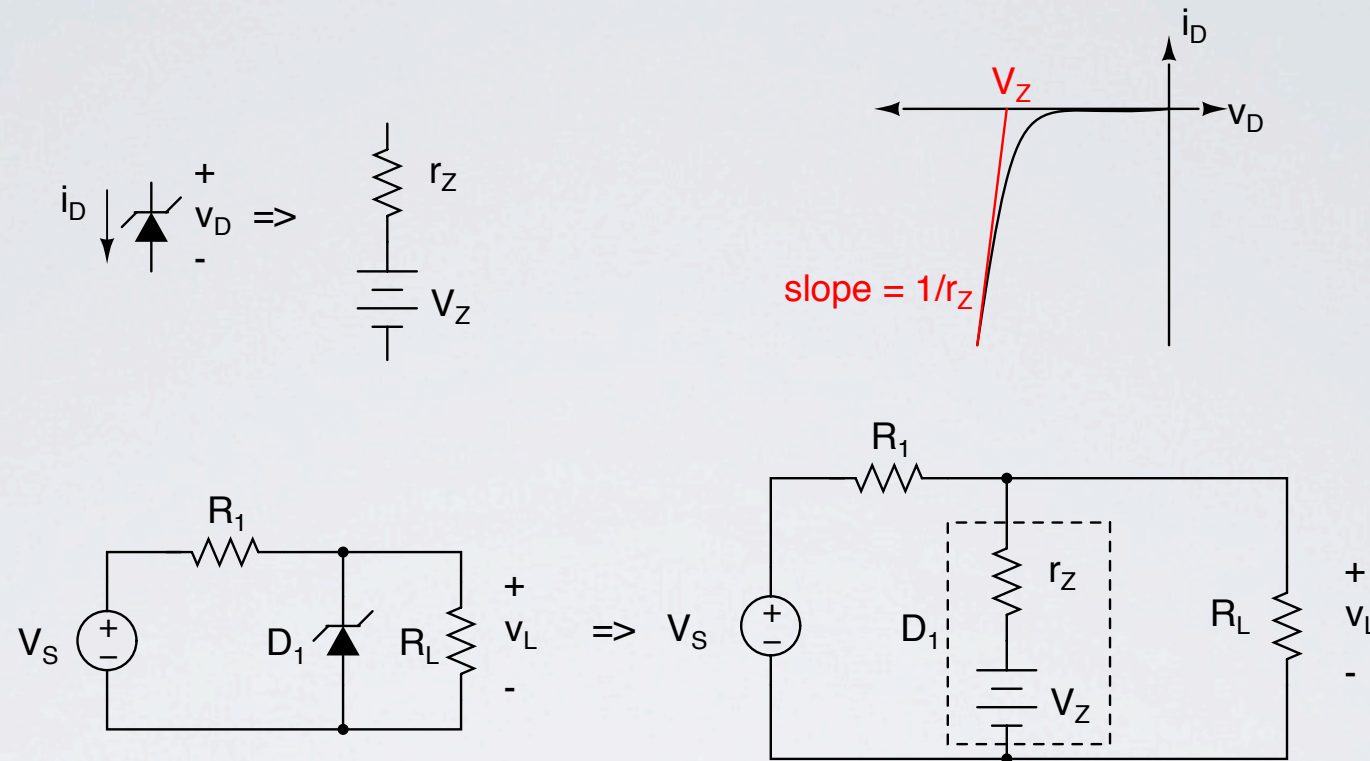

## Analysis of Zener diode circuit using piecewise linear approximation:

1. Transform voltage source to current source then back to voltage source:

$$V'_S = \frac{V_S}{R_1} (R_1 || R_L) = \frac{V_S}{R_1} \frac{R_1 \times R_L}{R_1 + R_L} = \frac{R_L}{R_1 + R_L} V_S$$

in series with a resistance  $R'_1 = R_1 || R_L$ .

2. Find diode's current:

$$i_D = \frac{V'_S - V_Z}{R_1 || R_L + r_Z}$$

3. calculate  $V_L$  by finding voltage across diode:

$$V_L = V_Z + r_Z \times i_D$$