

ARITHMETIC CIRCUITS

INEL 4205 - Ch. 4 - Set I
Spring 2012


 


Fig. 4-1 Block Diagram of Combinational Circuit

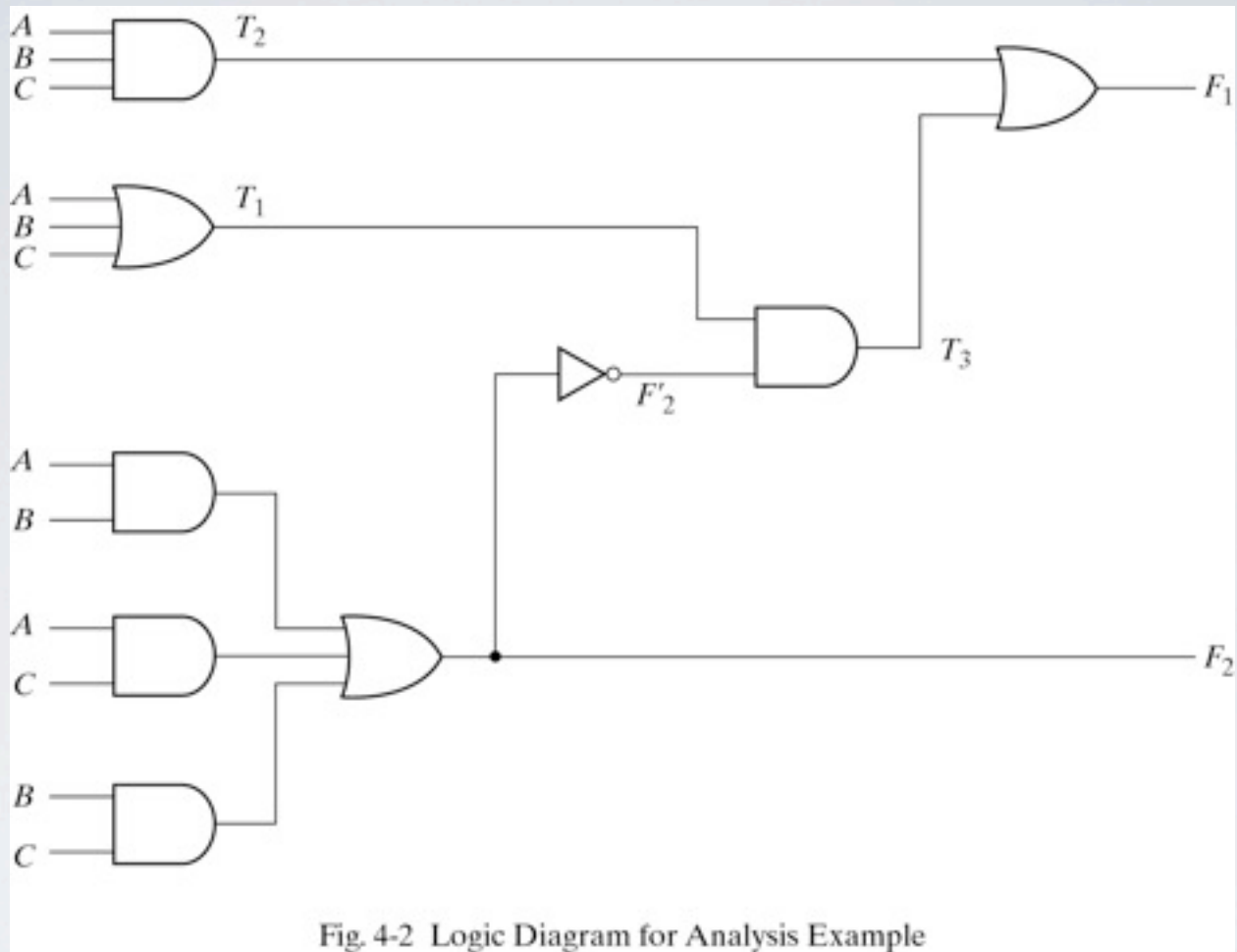

You can use intermediate variables to construct the boolean Functions from a complex logic diagram.

Table 4-2
Truth Table for Code-Conversion Example

Input BCD				Output Excess-3 Code			
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

Table 4-2 BCD to Excess-3 Code

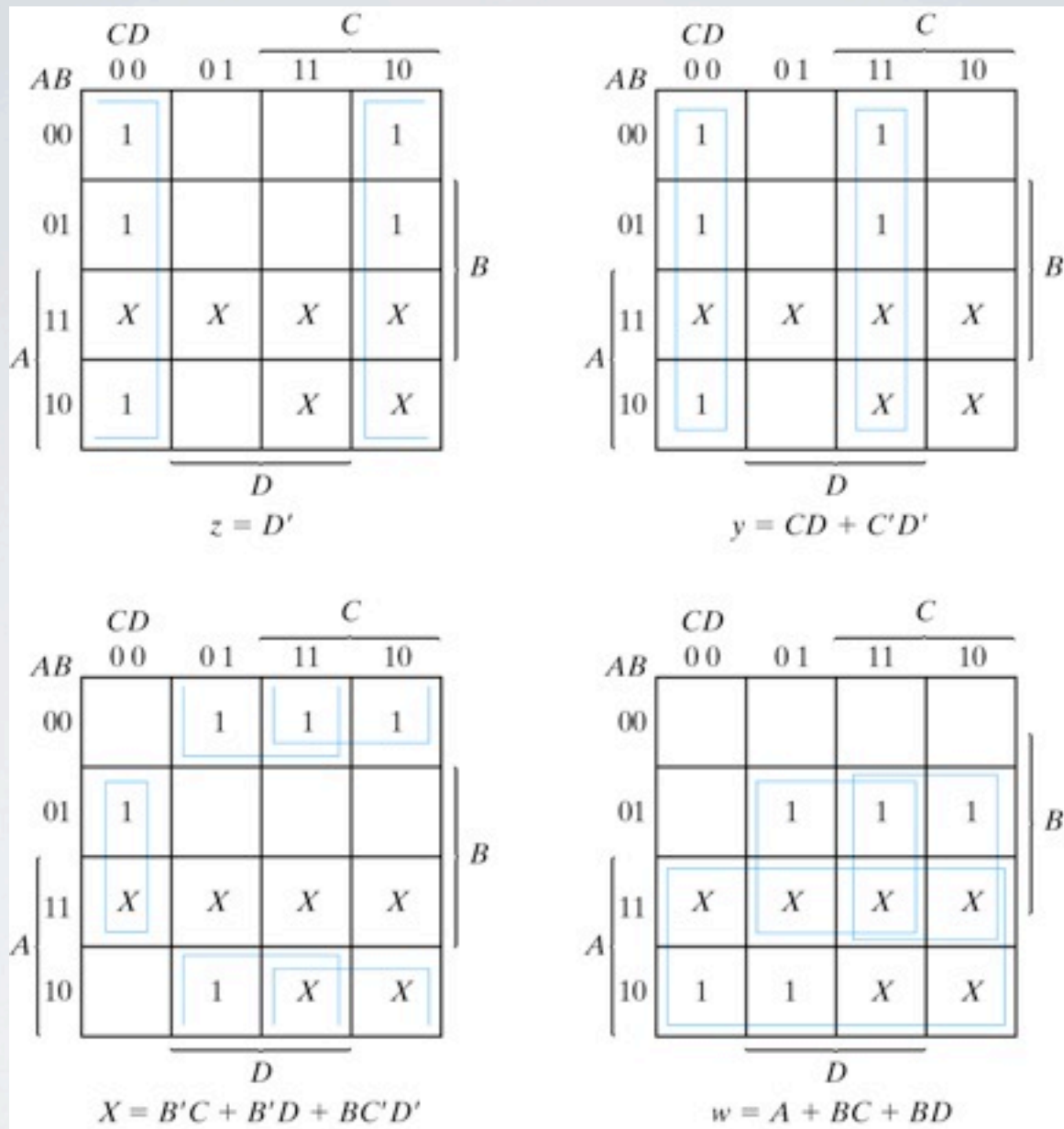


Fig. 4-3 Maps for BCD to Excess-3 Code Converter


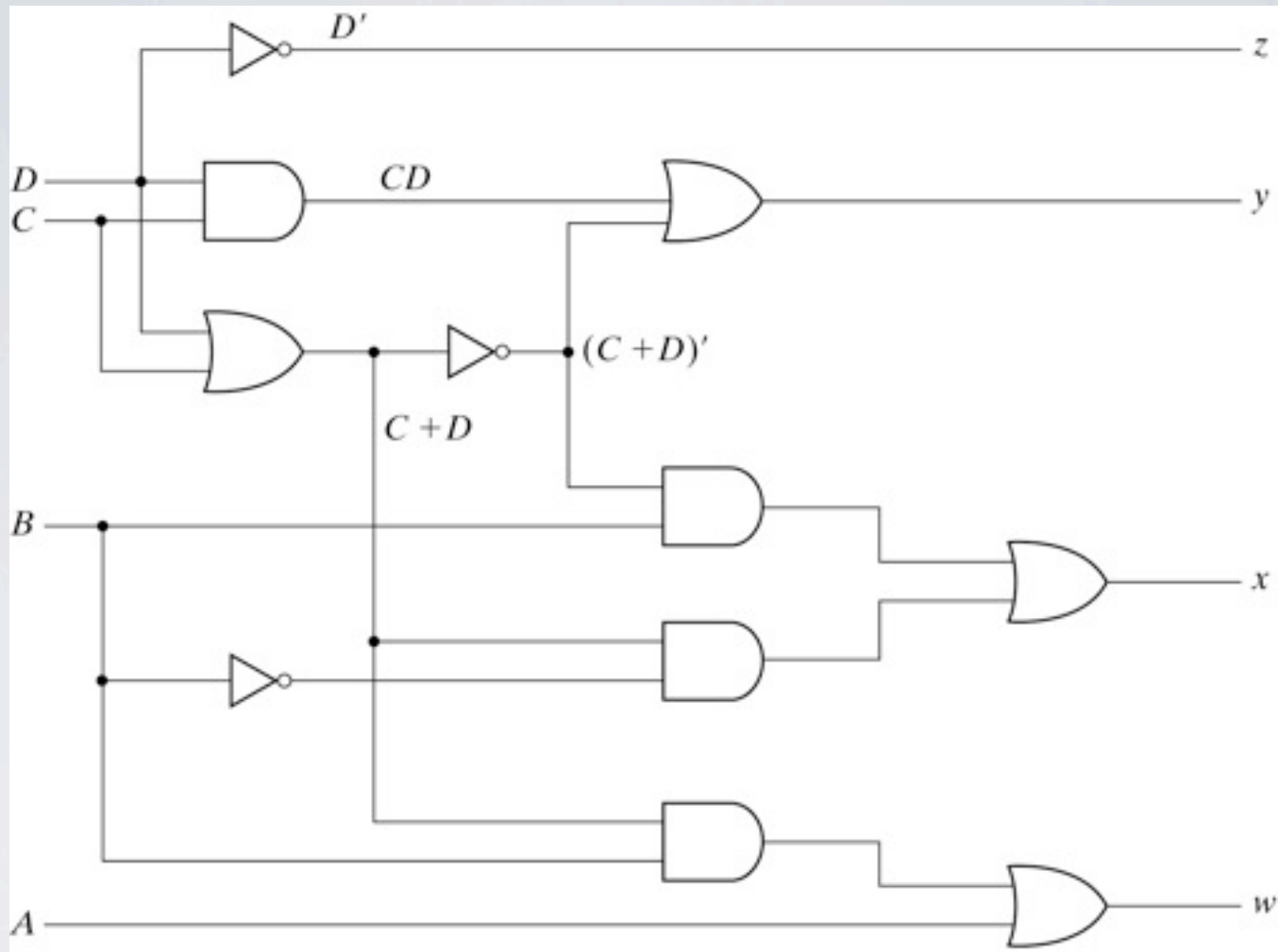



Fig. 4-4 Logic Diagram for BCD to Excess-3 Code Converter

Table 4-3
Half Adder

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

(a) $S = xy' + x'y$
 $C = xy$

 


(b) $S = x \oplus y$
 $C = xy$


Fig. 4-5 Implementation of Half-Adder

Table 4-4
Full Adder

<i>x</i>	<i>y</i>	<i>z</i>	<i>C</i>	<i>S</i>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

$$S = x'y'z + x'yz' + xy'z' + xyz$$

 

$$S = xy + xz + yz$$

$$= xy + xy'z + x'yz$$

Fig. 4-6 Maps for Full Adder

 


Fig. 4-7 Implementation of Full Adder in Sum of Products


 


Fig. 4-8 Implementation of Full Adder with Two Half Adders and an OR Gate

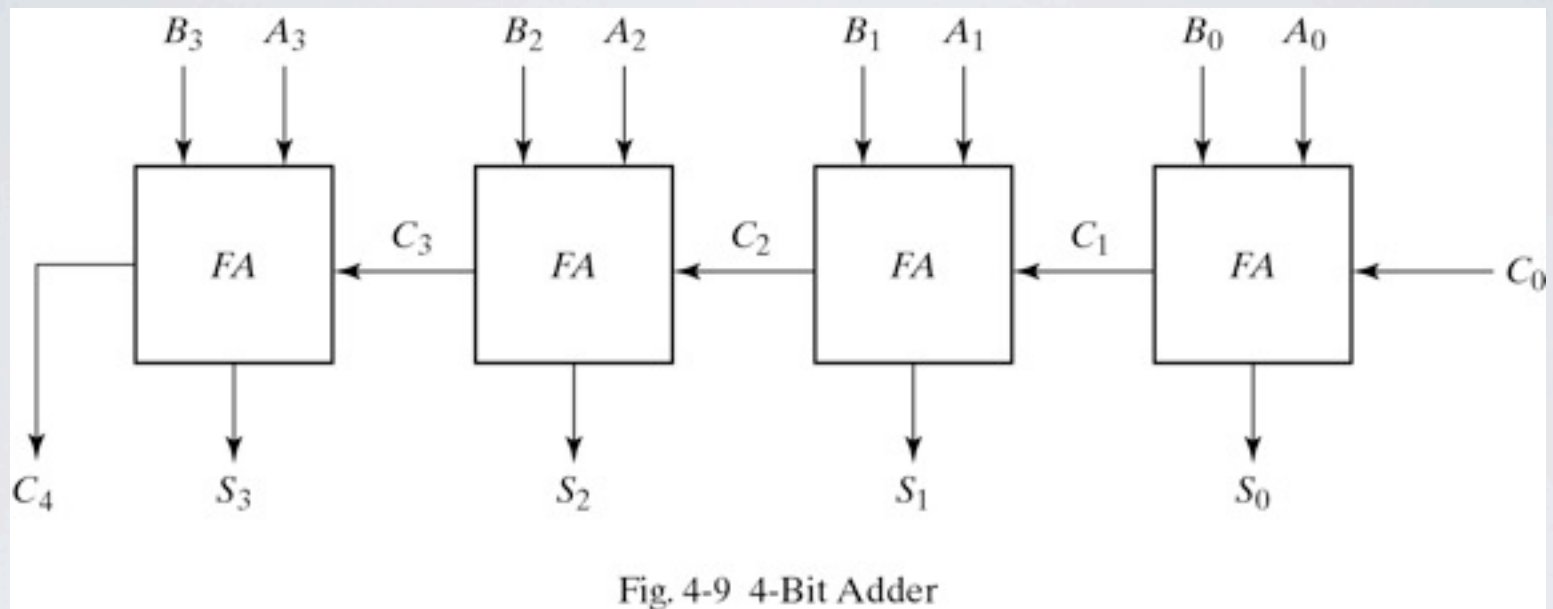

 


Fig. 4-10 Full Adder with P and G Shown

 


Fig. 4-10 Full Adder with P and G Shown

$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

 


Fig. 4-10 Full Adder with P and G Shown

$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

C_0 = input carry

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 (G_0 + P_0 C_0) = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

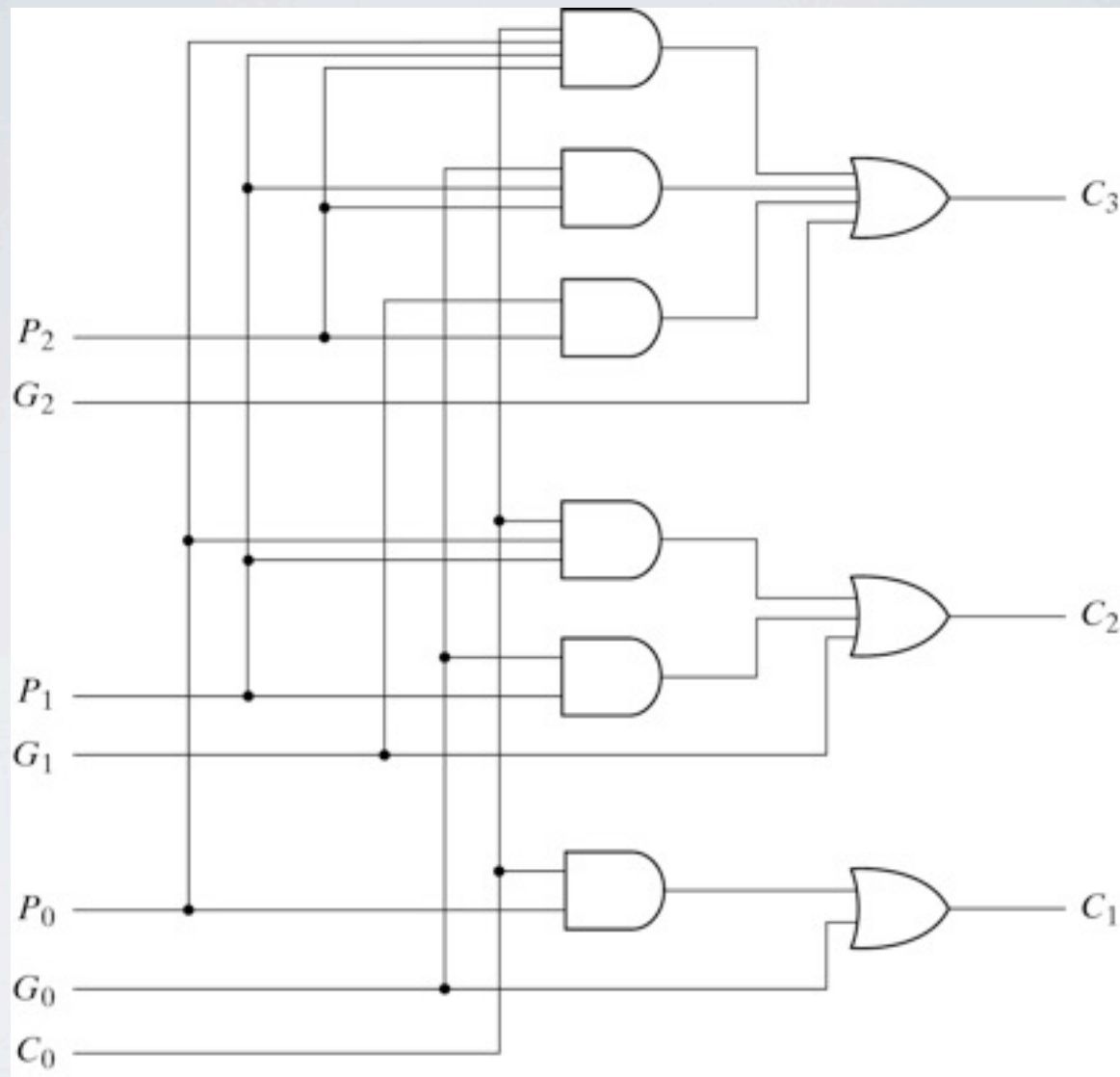


Fig. 4-11 Logic Diagram of Carry Lookahead Generator

 


Fig. 4-12 4-Bit Adder with Carry Lookahead

 


Fig. 4-13 4-Bit Adder Subtractor

$M=1$ complements the B-bits and adds 1, thus forming the 2's complement of B

carries:	0	1		carries:	1	0
+70	0	1000110		-70	1	0111010
+80	0	1010000		-80	1	0110000
<hr/>		<hr/>		<hr/>		<hr/>
+150	1	0010110		-150	0	1101010

overflow occurs if:

For unsigned numbers: carry out of msb

for Signed numbers: if carry into sign bit is different than carry out of sign bit

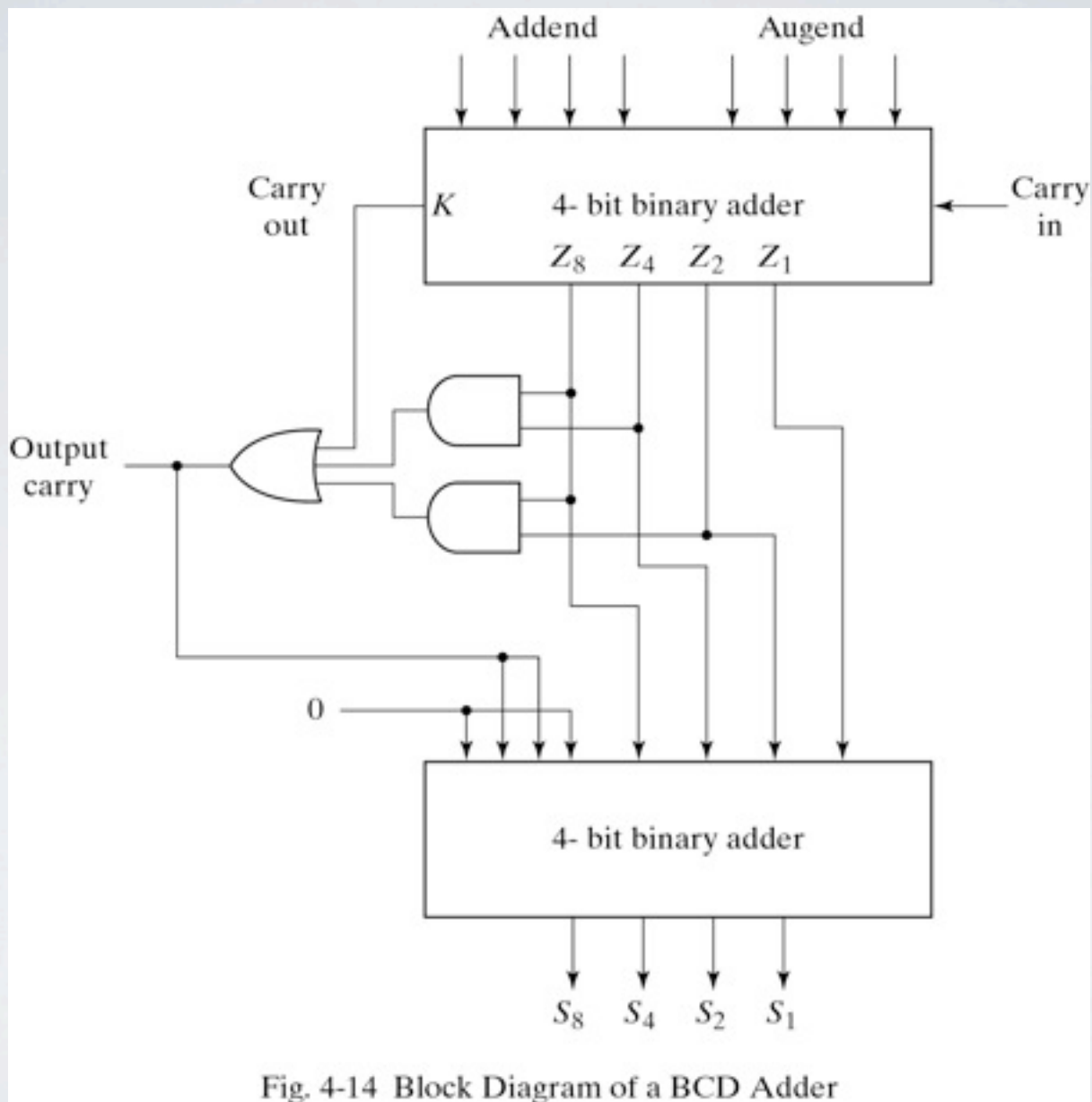


Fig. 4-14 Block Diagram of a BCD Adder

		B_1	B_0
	A_1	A_0B_1	A_0B_0
	A_1B_1	A_1B_0	
C_3	C_2	C_1	C_0

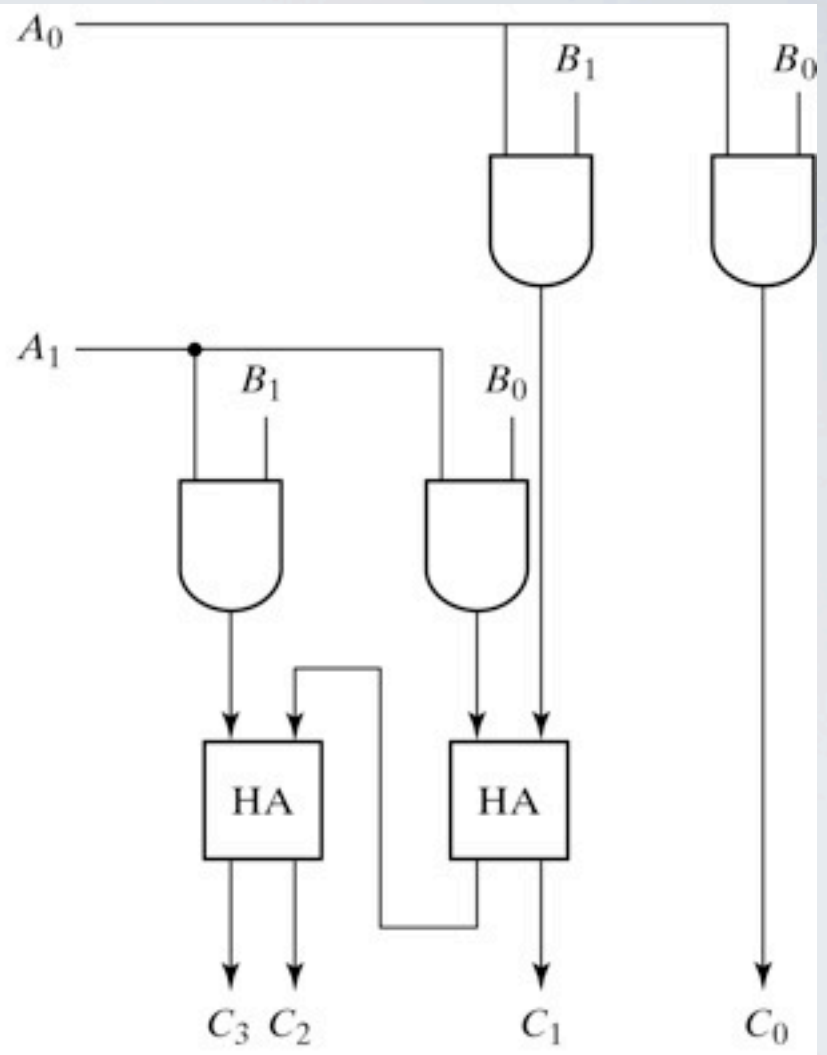


Fig. 4-15 2-Bit by 2-Bit Binary Multiplier

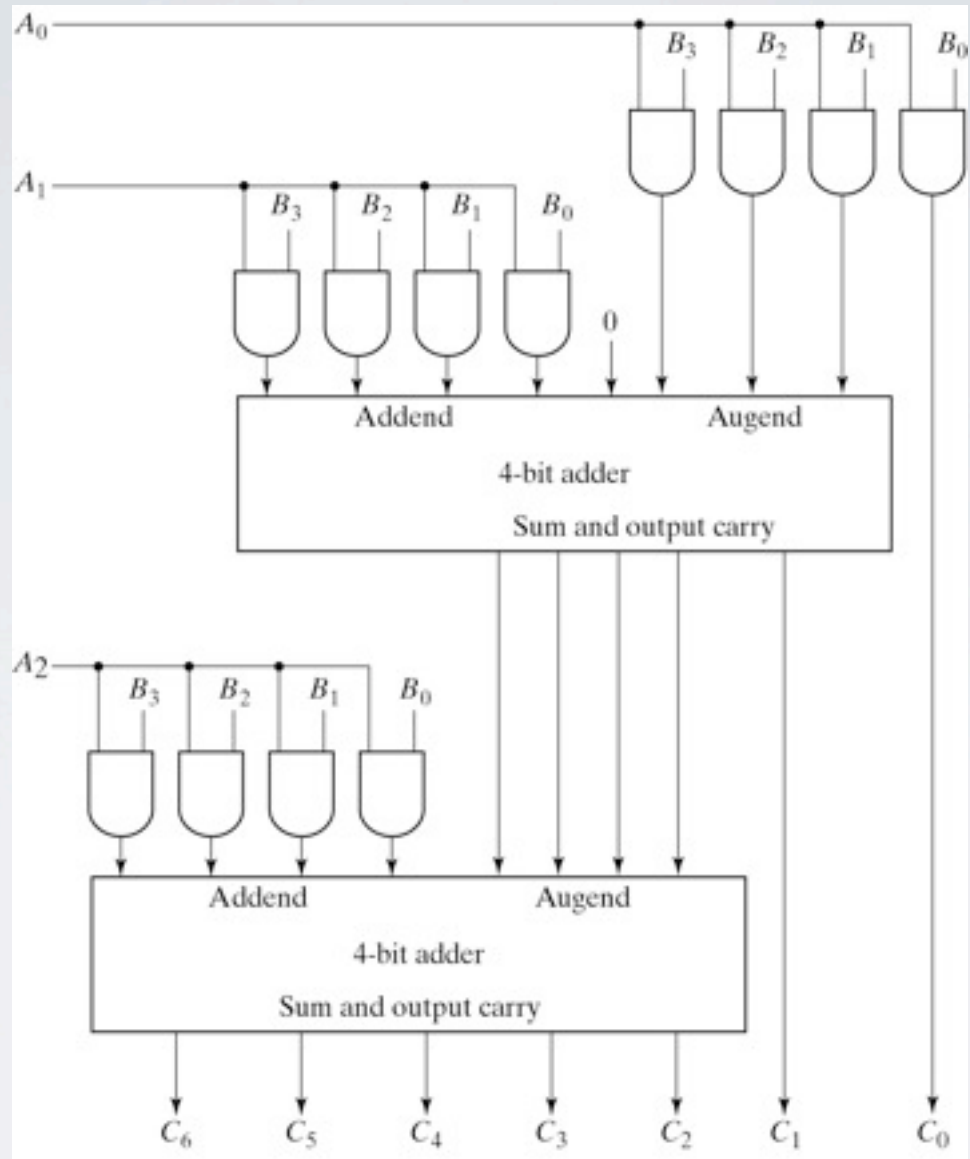


Fig. 4-16 4-Bit by 3-Bit Binary Multiplier

MAGNITUDE COMPARATOR

$$A = A_3A_2A_1A_0$$

$$B = B_3B_2B_1B_0$$

$$x_i = A_iB_i + A'_iB'_i \quad \text{for } i = 0, 1, 2, 3$$

$$(A = B) = x_3x_2x_1x_0$$

$$(A > B) = A_3B'_3 + x_3A_2B'_2 + x_3x_2A_1B'_1 + x_3x_2x_1A_0B'_0$$

$$(A < B) = A'_3B_3 + x_3A'_2B_2 + x_3x_2A'_1B_1 + x_3x_2x_1A'_0B_0$$

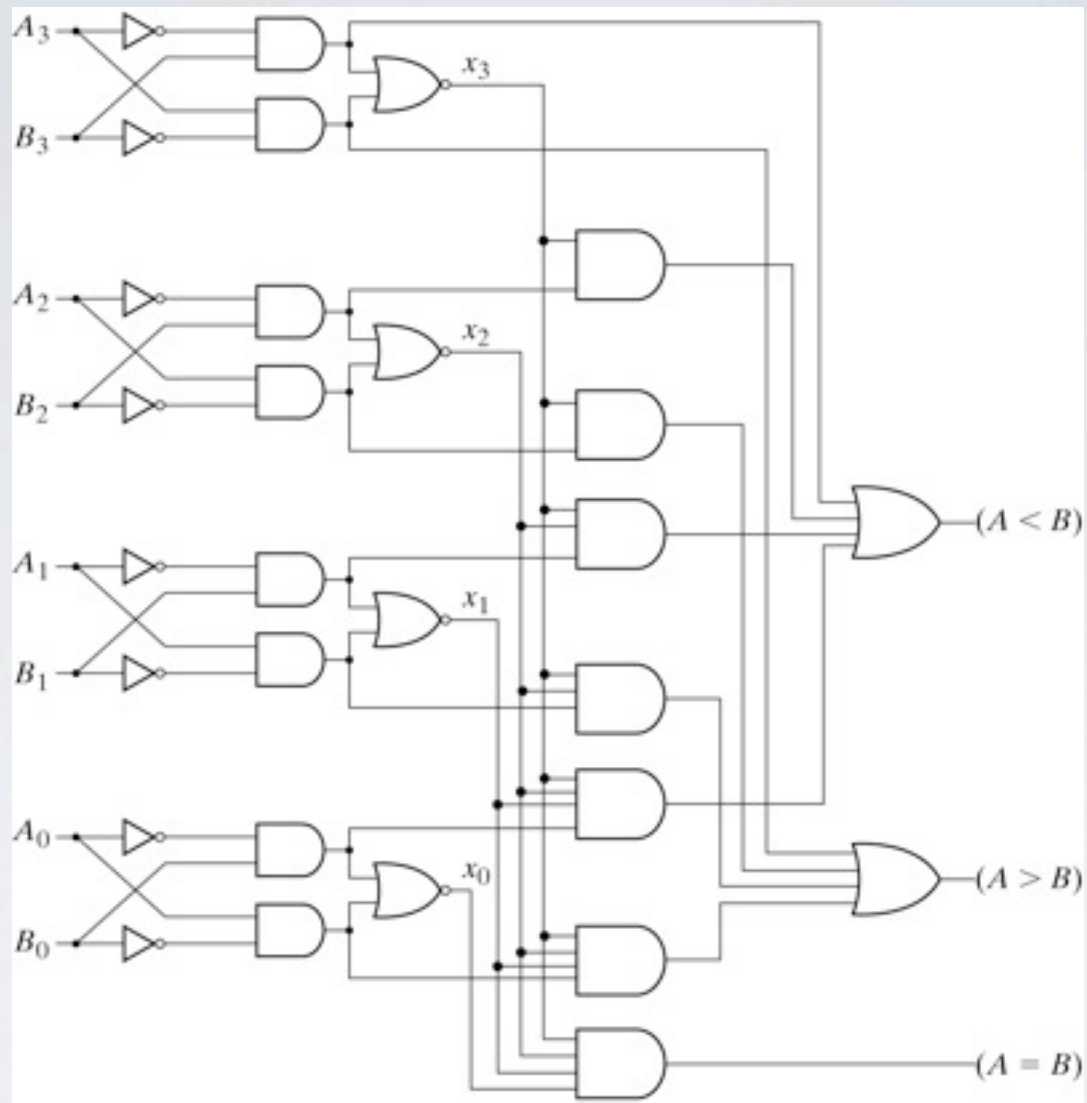


Fig. 4-17 4-Bit Magnitude Comparator