 


# PROGRAMMABLE LOGIC AND MEMORIES

INEL 4205 - Logic Circuits - Spring 2012



(a) Conventional symbol



(b) Array logic symbol

Fig. 7-1 Conventional and Array Logic Diagrams for OR Gate

- Two types of memory

- ROM: read-only memory: EPROM or FLASH / EEPROM

- RAM: read/write memory: SRAM (static) or DRAM (dynamic).

- Memory device address inputs

- select a location on (inside) the memory.

- number from  $A_0$  to  $A_{N-1}$  ( $2^N = \#$  cells)


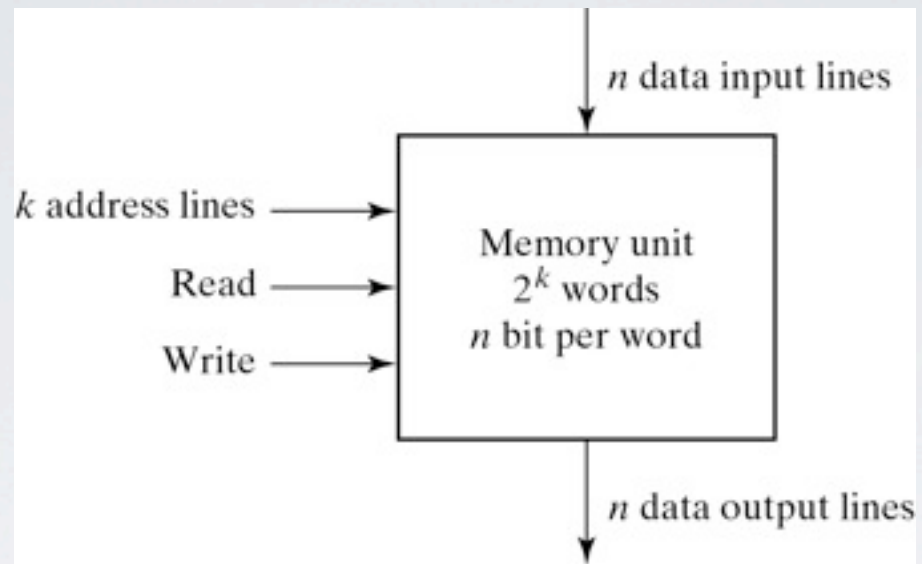


Fig. 7-2 Block Diagram of a Memory Unit

- Data pins
  - 8-bit in width: D0 to D7
  - eight devices form a 64-bit wide memory
  - D0: least significant bit
- Control inputs
  - Output enable ( $\#OE$ ): cause a read
  - Write enable ( $\#WE$ ): causes a write
  - Chip select ( $\#CS$ )

# TMS4016 2K x 8 SRAM Pinout

 

## PIN FUNCTION


A <sub>0</sub> - A <sub>14</sub>	Addresses
IO <sub>0</sub> - IO <sub>7</sub>	Data connections
$\overline{CS}$	Chip select
$\overline{OE}$	Output enable
$\overline{WE}$	Write enable
V <sub>CC</sub>	+5V Supply
GND	Ground

- Location 10000H-17FFFH appear as follows in binary.
- Bits A0-A14 => internally decoded

10000H=	0001	0000	0000	0000	0000
17FFFH=	0001	0111	1111	1111	1111

A19-A15 externally decoded to uniquely select the chip
 
# 168-pin *Dual In-Line Memory Module* (DIMM)





Memory address		
Binary	decimal	Memory content
0000000000	0	1011010101011101
0000000001	1	1010101110001001
0000000010	2	0000110101000110
	⋮	⋮
1111111101	1021	1001110100010100
1111111110	1022	0000110100011110
1111111111	1023	1101111000100101

Fig. 7-3 Content of a  $1024 \times 16$  Memory

# STEPS TO WRITE INTO RAM

- Apply address to address lines
- Apply data to data input lines
- Activate *write* input & enable chip

For reads: do 1 and 3 using *read* input



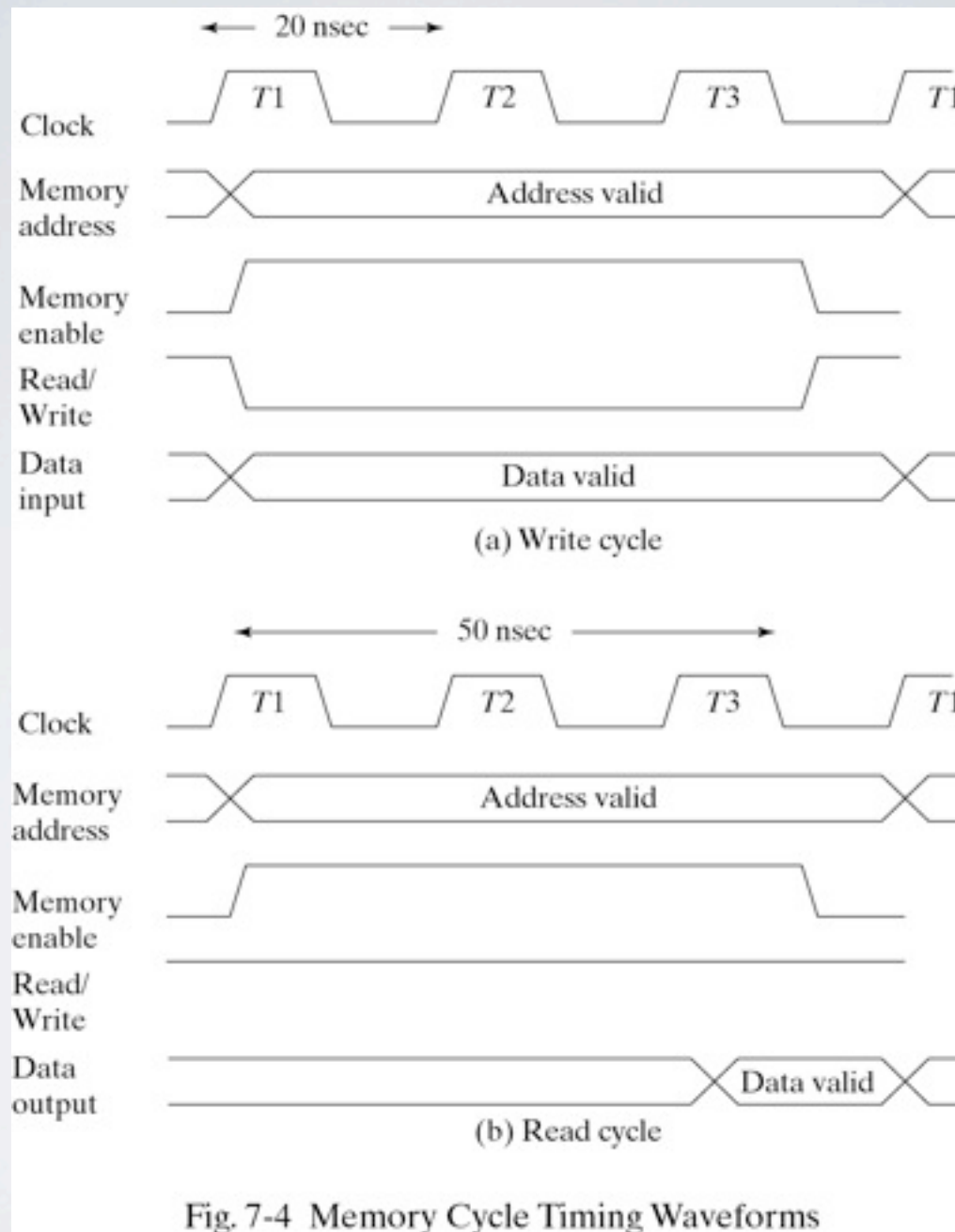


Fig. 7-4 Memory Cycle Timing Waveforms

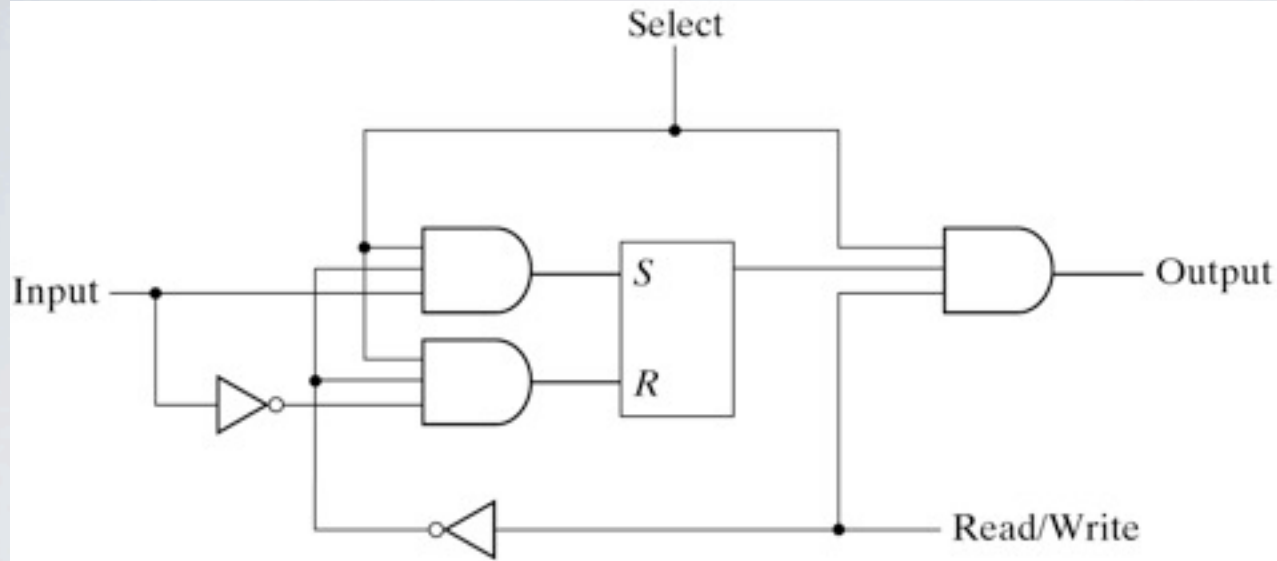

(a) Logic diagram

 

(b) Block diagram

Fig. 7-5 Memory Cell

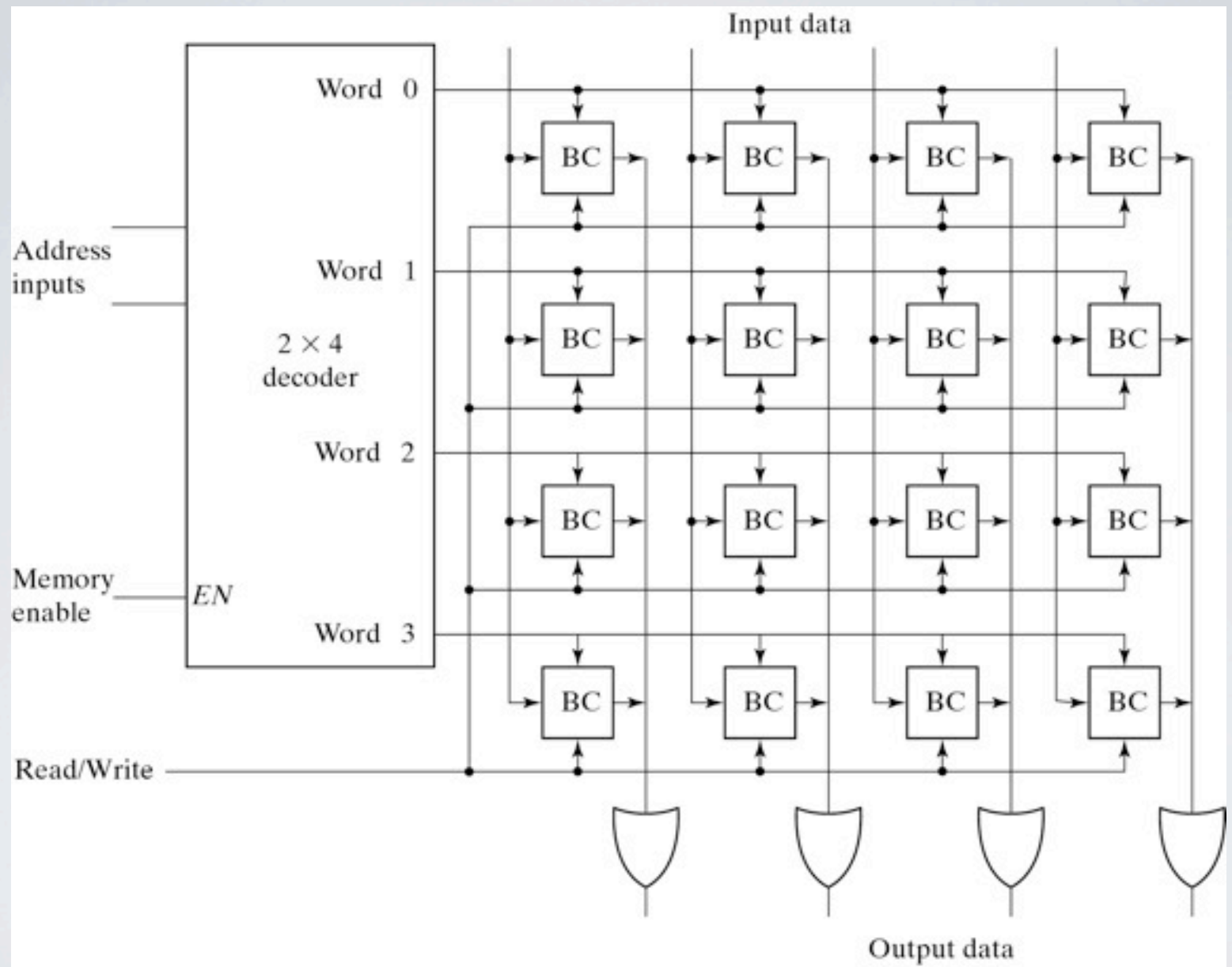


Fig. 7-6 Diagram of a  $4 \times 4$  RAM

# ROW/COLUMN DECODING

- 1K-word memory requires 10 address bits and a  $10 \times 1024$  decoder
- The decoding can also be done with two  $5 \times 32$  decoder, one for the *row* and one for the column. The cell connected to the row-column intersection is selected.

 


Fig. 7-7 Two-Dimensional Decoding Structure for a 1K-Word Memory

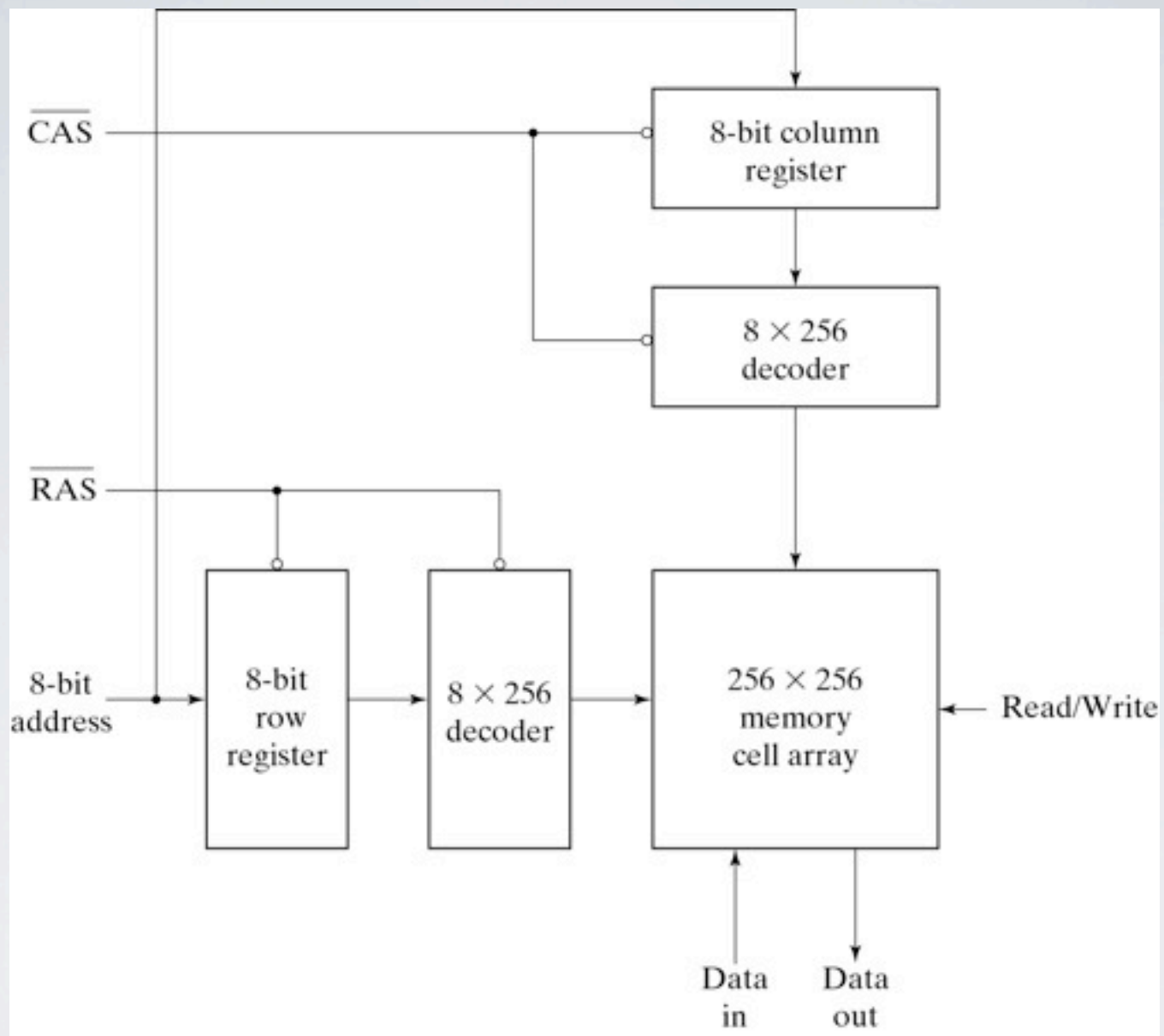


Fig. 7-8 Address Multiplexing for a 64K DRAM




 


Fig. 7-9 ROM Block Diagram

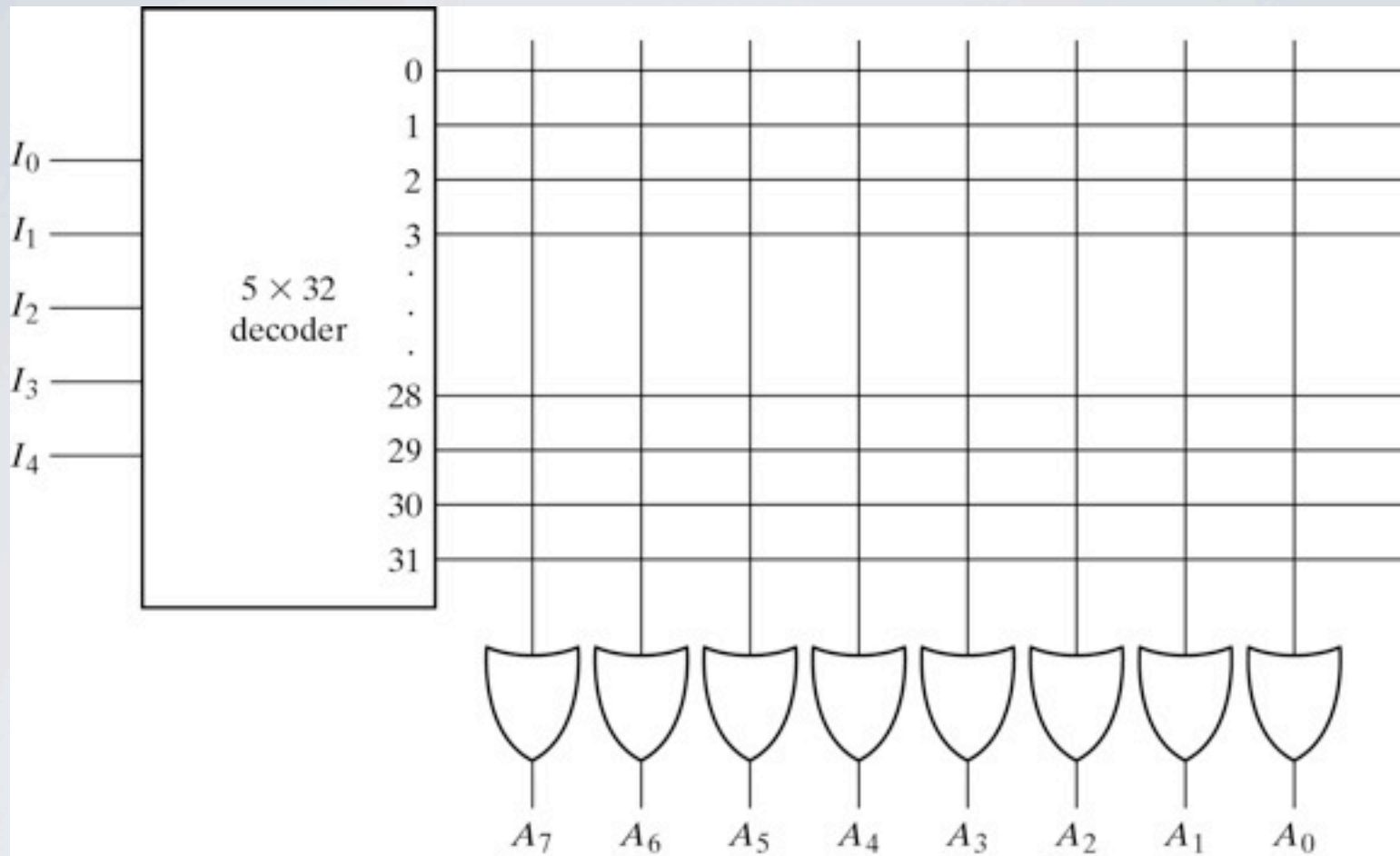

**Fig. 7-10 Internal Logic of a  $32 \times 8$  ROM**

Used as programable logic, a PROM stores the truth table for  $N$  functions of  $M$  inputs.  $N$  = number of bits in each cell.

$M$  = number of address bits; there are  $2^M$  memory locations in the PROM.

“x” indicates a connection, and a “1” in the truth table

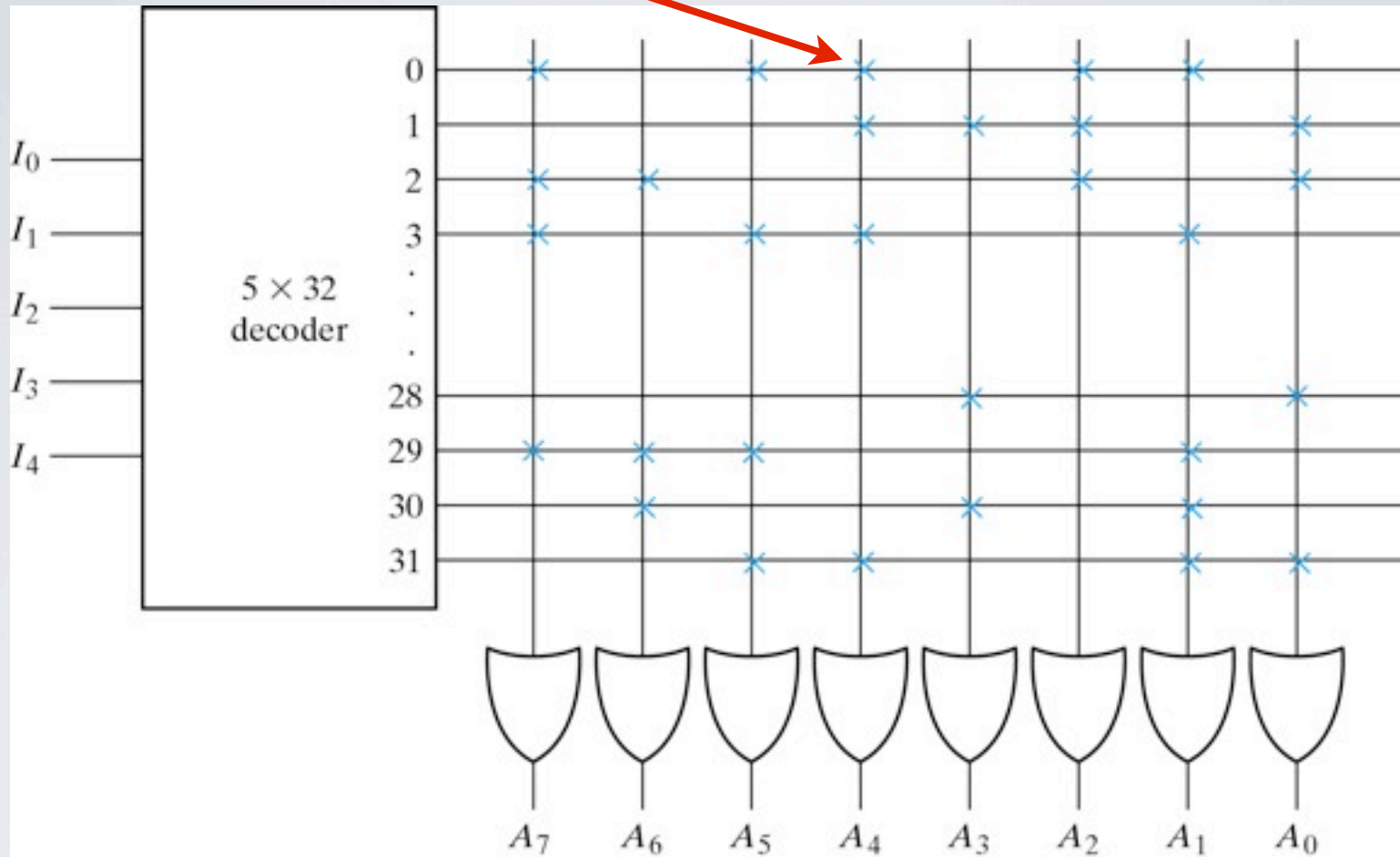



Fig. 7-11 Programming the ROM According to Table 7-3

Address 00000: cell contents is 10110110

Design a combinatorial circuit using a ROM. The circuit accepts a 3-bit input number and outputs a binary number equal to the square of the input.

**Table 7-4**  
*Truth Table for Circuit of Example 7-1*

<b>Inputs</b>			<b>Outputs</b>						<b>Decimal</b>
$A_2$	$A_1$	$A_0$	$B_5$	$B_4$	$B_3$	$B_2$	$B_1$	$B_0$	
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	1	9
1	0	0	0	1	0	0	0	0	16
1	0	1	0	1	1	0	0	1	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	0	0	0	1	49

 

(a) Block diagram

$A_2$	$A_1$	$A_0$	$B_5$	$B_4$	$B_3$	$B_2$
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0

(b) ROM truth table

Fig. 7-12 ROM Implementation of Example 7-1

 
 
 


Fig. 7-13 Basic Configuration of Three PLDs

PLA

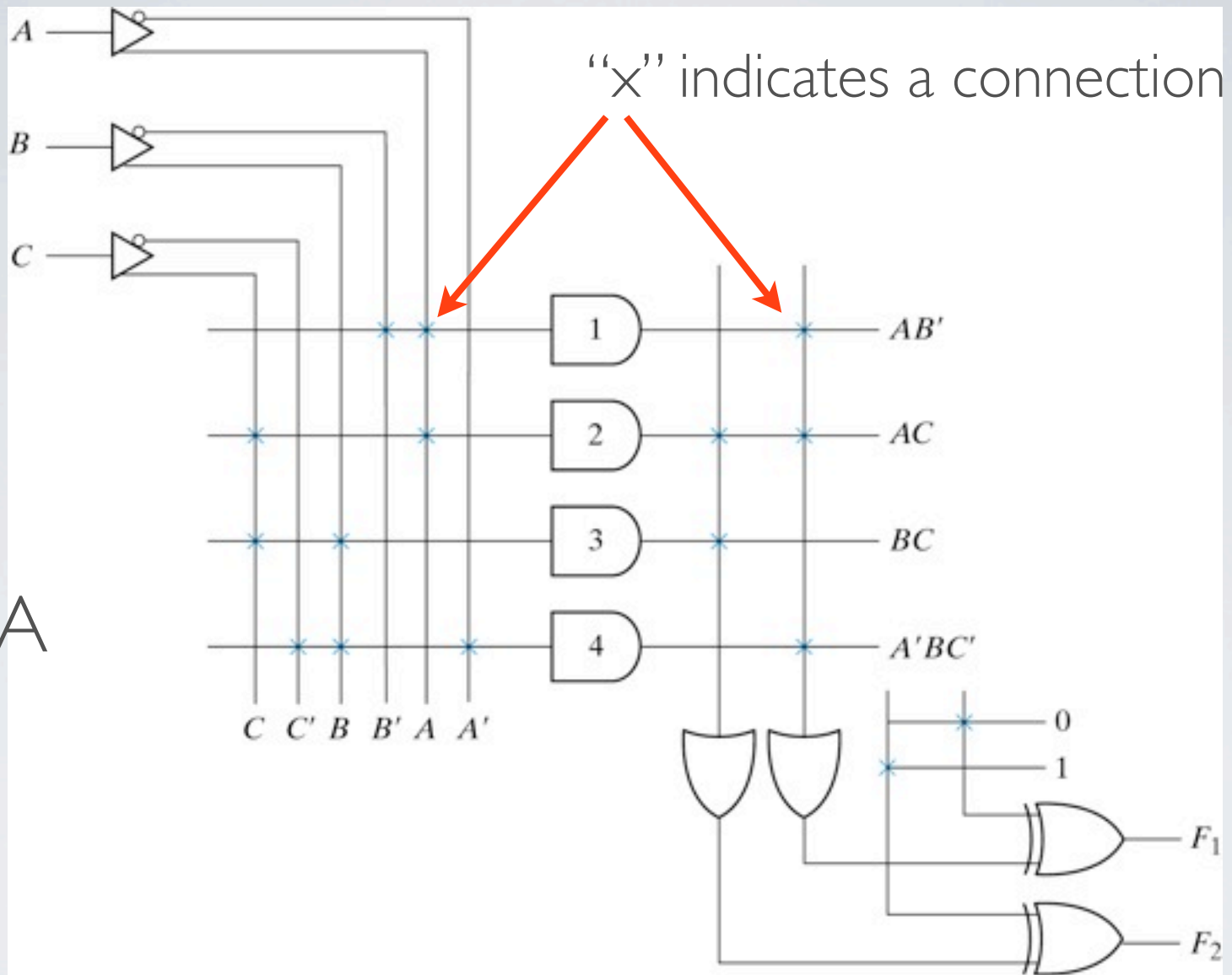


Fig. 7-14 PLA with 3 Inputs, 4 Product Terms, and 2 Outputs


PLA has limited # of ANDs: designer can implement  $F'$  (instead of  $F$ ) to minimize the # of distinct product terms, then complement  $F'$  with the XOR to produce  $F$

Example: Implement the following boolean functions in a PLA:

$$F_1(A,B,C) = \sum(0,1,2,4)$$

$$F_2(A,B,C) = \sum(0,5,6,7)$$



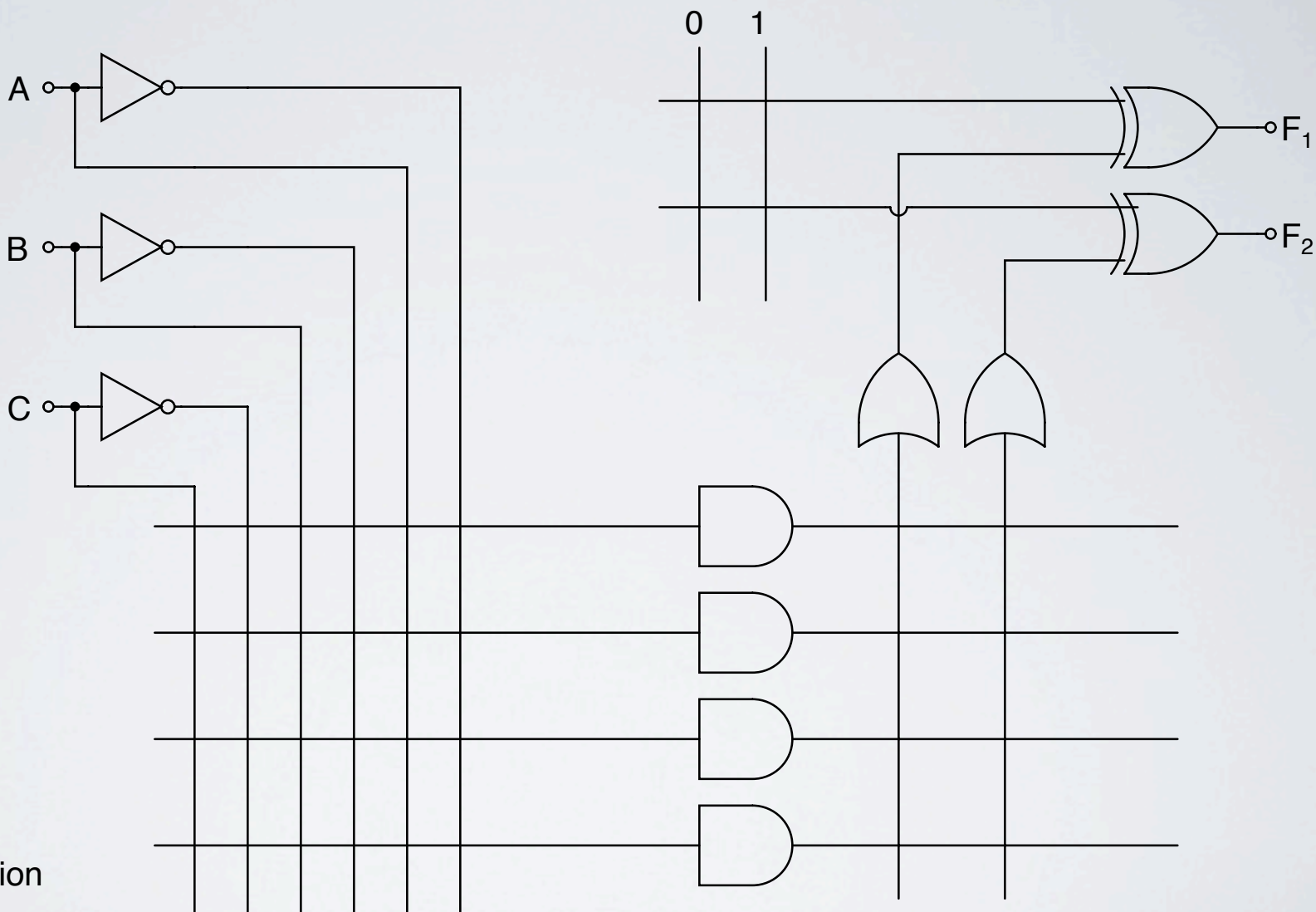

$\times$  = connection  
 $+$  = no connection

		<i>BC</i>		<i>B</i>	
		00	01	11	10
<i>A</i>	0	1	1	0	1
<i>A</i>	1	1	0	0	0
		<i>C</i>			

$$F_1 = A'B' + A'C' + B'C'$$

$$F_1 = (AB + AC + BC)'$$

		<i>BC</i>		<i>B</i>	
		00	01	11	10
<i>A</i>	0	1	0	0	0
<i>A</i>	1	0	1	1	1
		<i>C</i>			

$$F_2 = AB + AC + A'B'C'$$

$$F_2 = (A'C + A'B + AB'C')'$$

PLA programming table

	Product term	Inputs			Outputs	
		<i>A</i>	<i>B</i>	<i>C</i>	( <i>C</i> ) <i>F</i> <sub>1</sub>	( <i>T</i> ) <i>F</i> <sub>2</sub>
<i>AB</i>	1	1	1	-	1	1
<i>AC</i>	2	1	-	1	1	1
<i>BC</i>	3	-	1	1	1	-
<i>A'B'C'</i>	4	0	0	0	-	1

Fig. 7-15 Solution to Example 7-2

**7-21** Derive the PLA programming table for the combinational circuit that squares a 3-bit number. Minimize the number of product terms. (See Fig. 7-12 for the equivalent ROM implementation.)


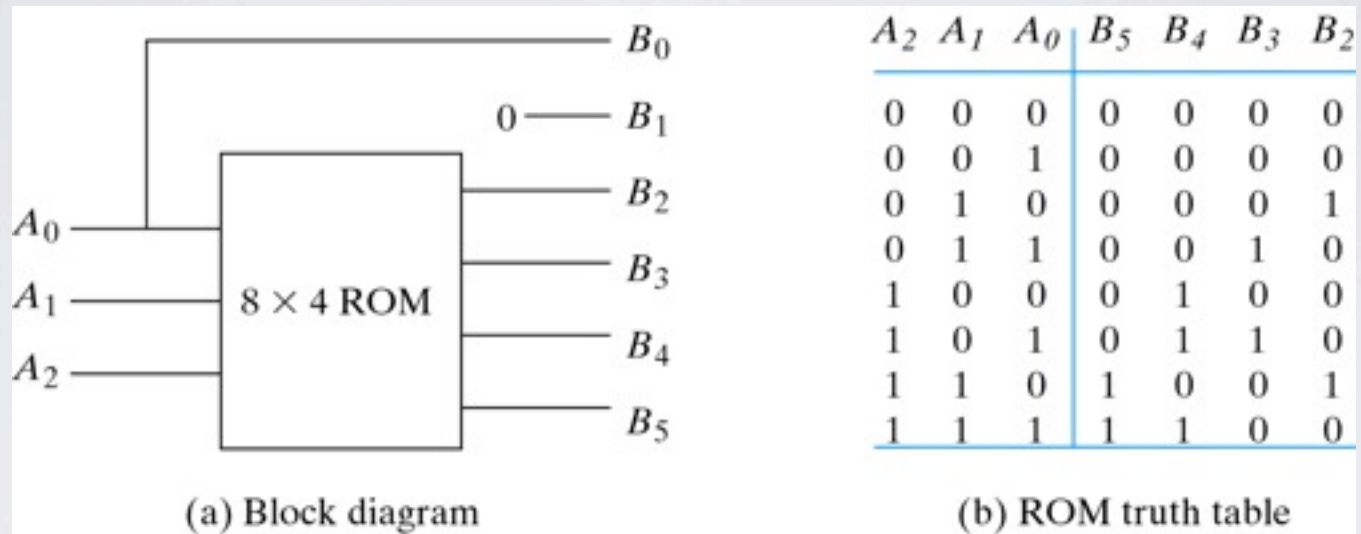


Fig. 7-12 ROM Implementation of Example 7-1

 

$\times$  = connection  
 $+$  = no connection

3. (25 pts) Determine the PLA programming table needed to implement the following two boolean functions. Minimize the number of product terms. Show all your work, including the Karnaugh maps used in the minimization.

$$F_1(A,B,C,D) = \sum(1, 3, 4, 5, 7, 13, 15)$$

$$F_2(A,B,C,D) = \sum(0, 2, 3, 6, 7, 8, 10, 11, 12, 14)$$

Write your result in the following table.

Product terms	Inputs				Outputs	
	A	B	C	D	( ) F <sub>1</sub>	( ) F <sub>2</sub>

Note: not all rows need to be used

# PAL

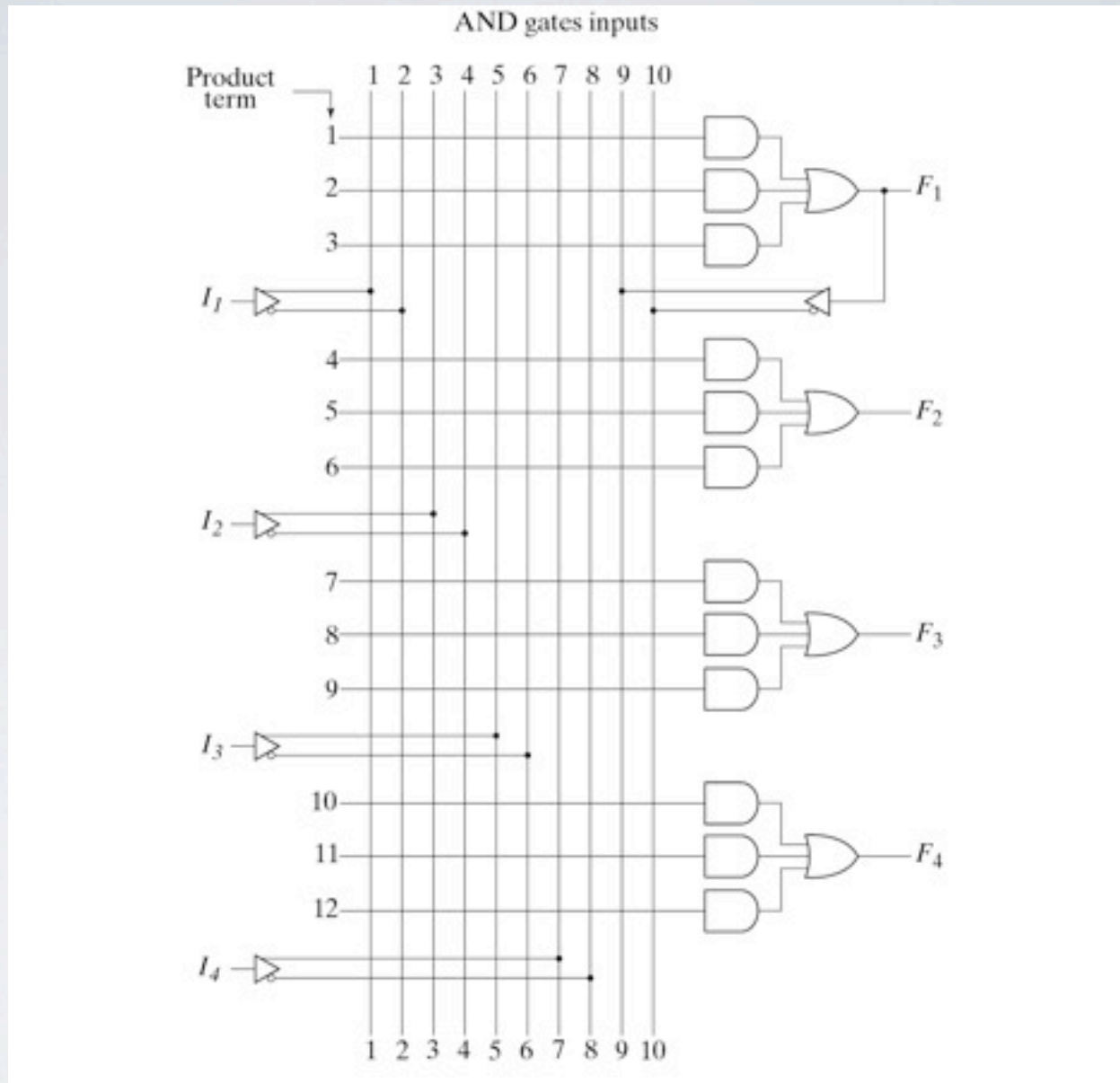


Fig. 7-16 PAL with Four Inputs, Four Outputs, and Three-Wide AND-OR Structure

PAL: Only inputs to AND gates can be programmed but one term ( $F_1$ ) can be re-used in other functions

$$w(A, B, C, D) = \Sigma(2, 12, 13)$$

$$x(A, B, C, D) = \Sigma(7, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$y(A, B, C, D) = \Sigma(0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$$

$$z(A, B, C, D) = \Sigma(1, 2, 8, 12, 13)$$

Manipulate expressions so that a common term is identified.

Assign common term to  $F_1$ .

$$w = ABC' + A'B'CD'$$

$$x = A + BCD$$

$$y = A'B + CD + B'D'$$

$$z = ABC' + A'B'CD' + AC'D' + A'B'C'D$$

$$= w + AC'D' + A'B'C'D$$

**Table 7-6**  
*PAL Programming Table*

Product Term	AND Inputs					Outputs
	A	B	C	D	W	
1	1	1	0	-	-	$w = ABC'$ $+ A'B'CD'$
2	0	0	1	0	-	
3	-	-	-	-	-	
4	1	-	-	-	-	$x = A$ $+ BCD$
5	-	1	1	1	-	
6	-	-	-	-	-	
7	0	1	-	-	-	$y = A'B$ $+ CD$ $+ B'D'$
8	-	-	1	1	-	
9	-	0	-	0	-	
10	-	-	-	-	1	$z = w$ $+ AC'D'$ $+ A'B'C'D$
11	1	-	0	0	-	
12	0	0	0	1	-	



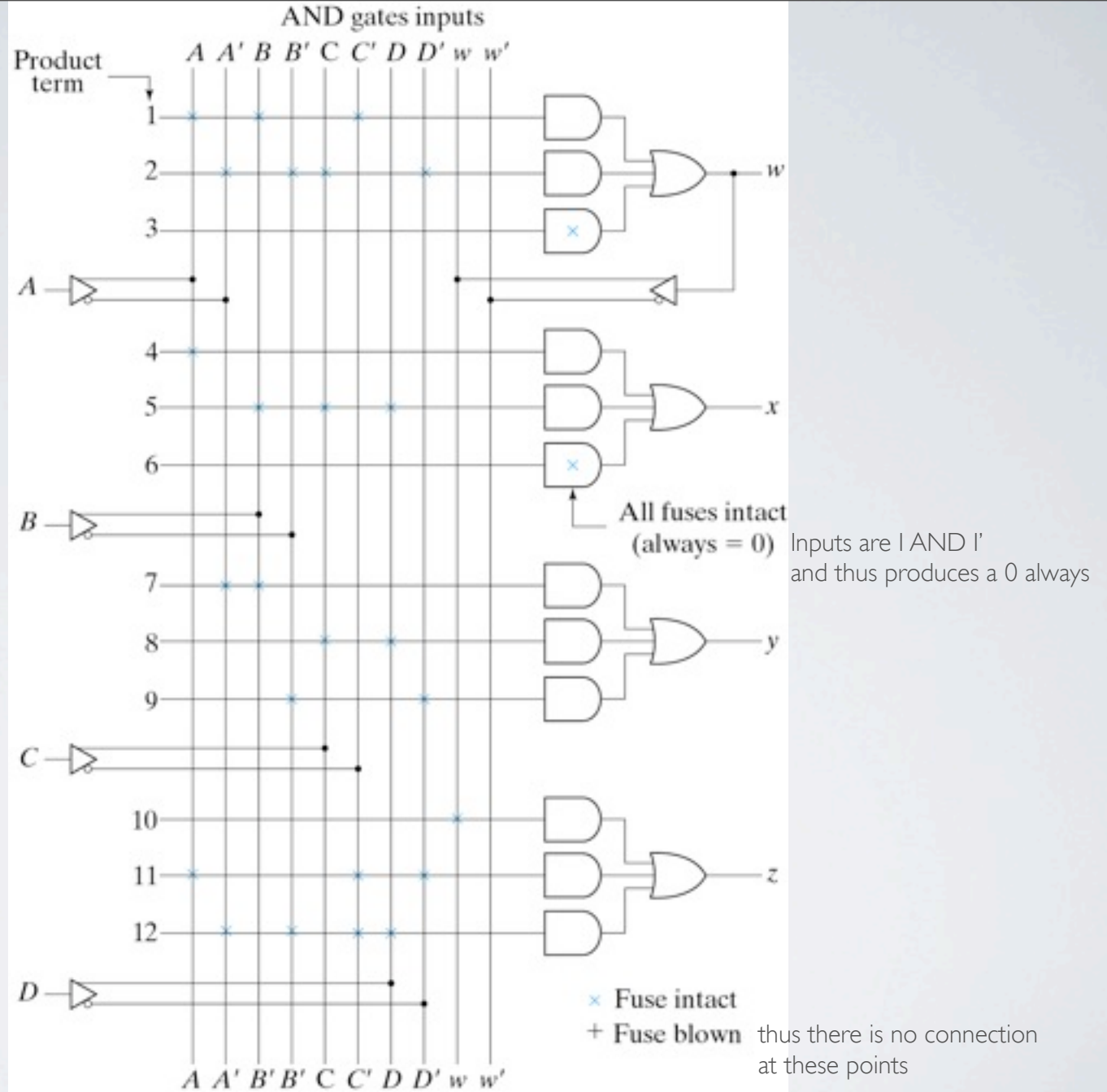


Fig. 7-17 Fuse Map for PAL as Specified in Table 7-6

- PAL practice: problem 7-24

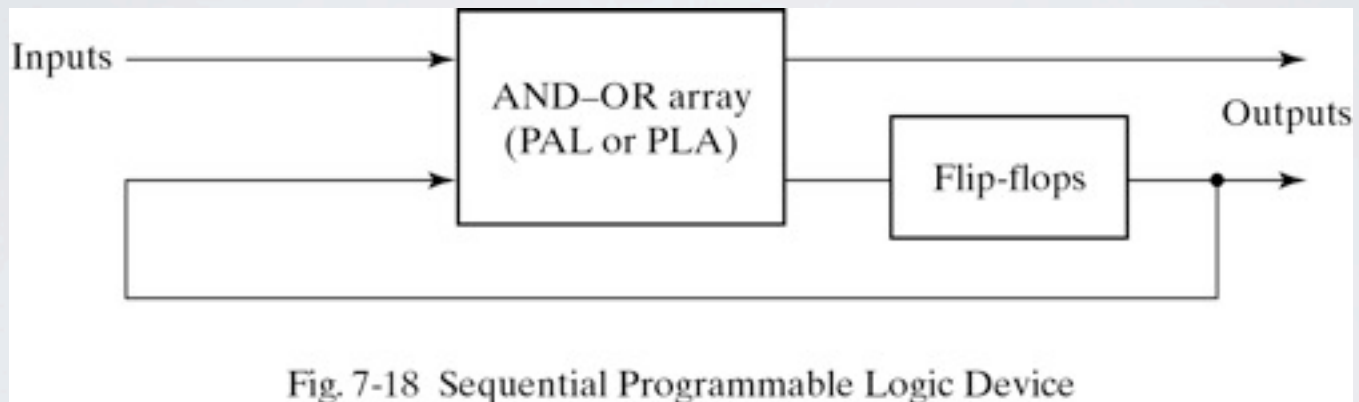


Fig. 7-18 Sequential Programmable Logic Device

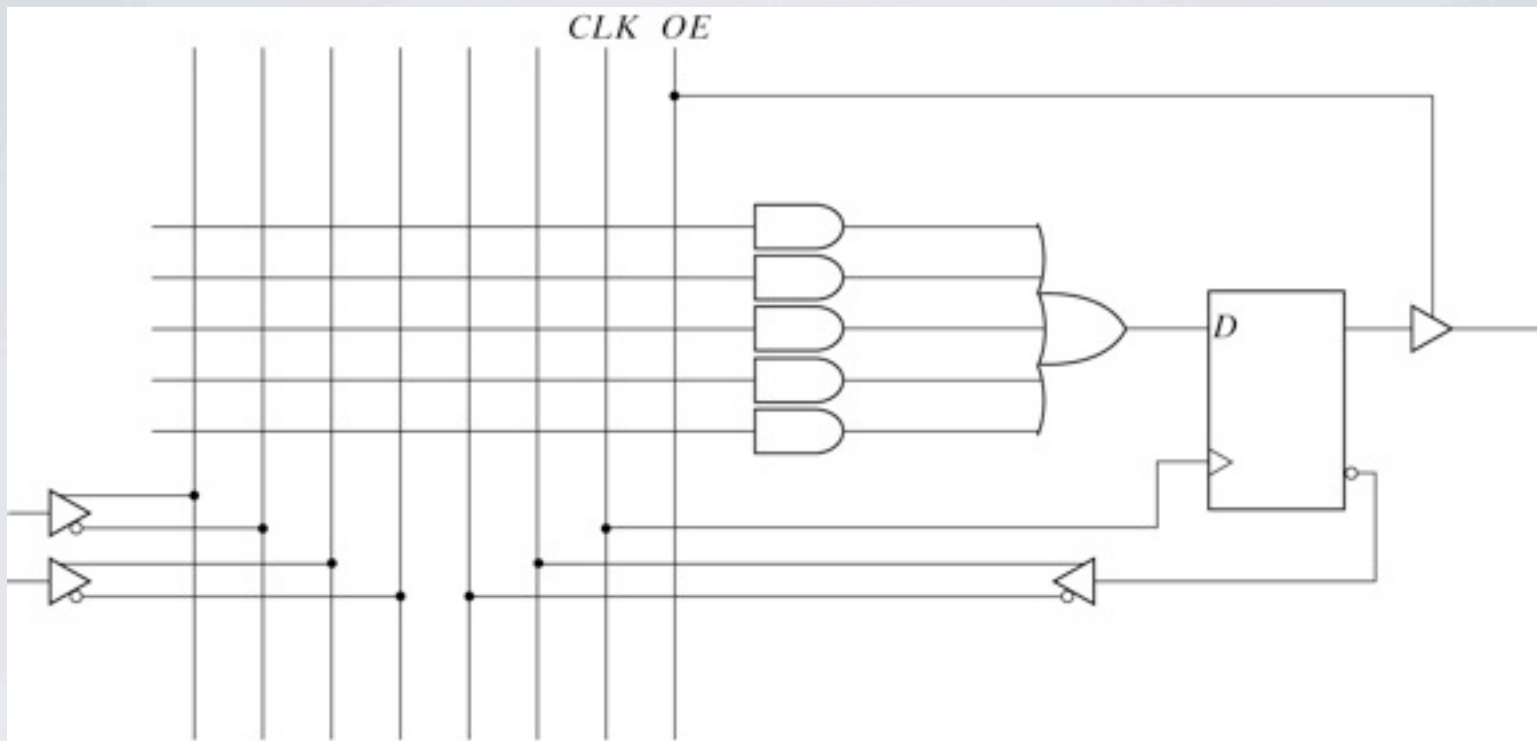


Fig. 7-19 Basic Macrocell Logic


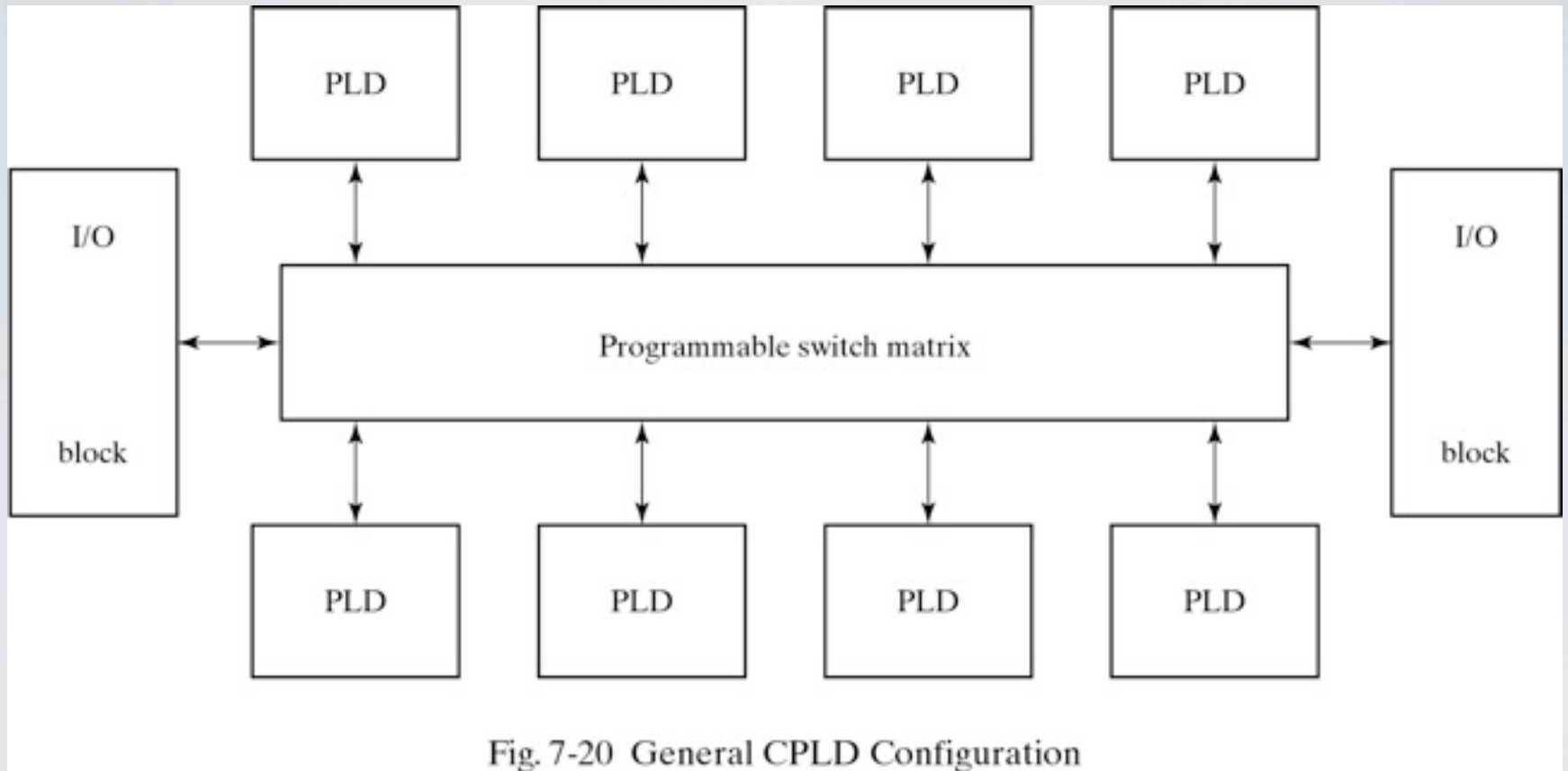


Fig. 7-20 General CPLD Configuration

# Xilinx FPGAs are based on Configurable Logic Blocks (CLBs)


More generally called logic cells

Programmable

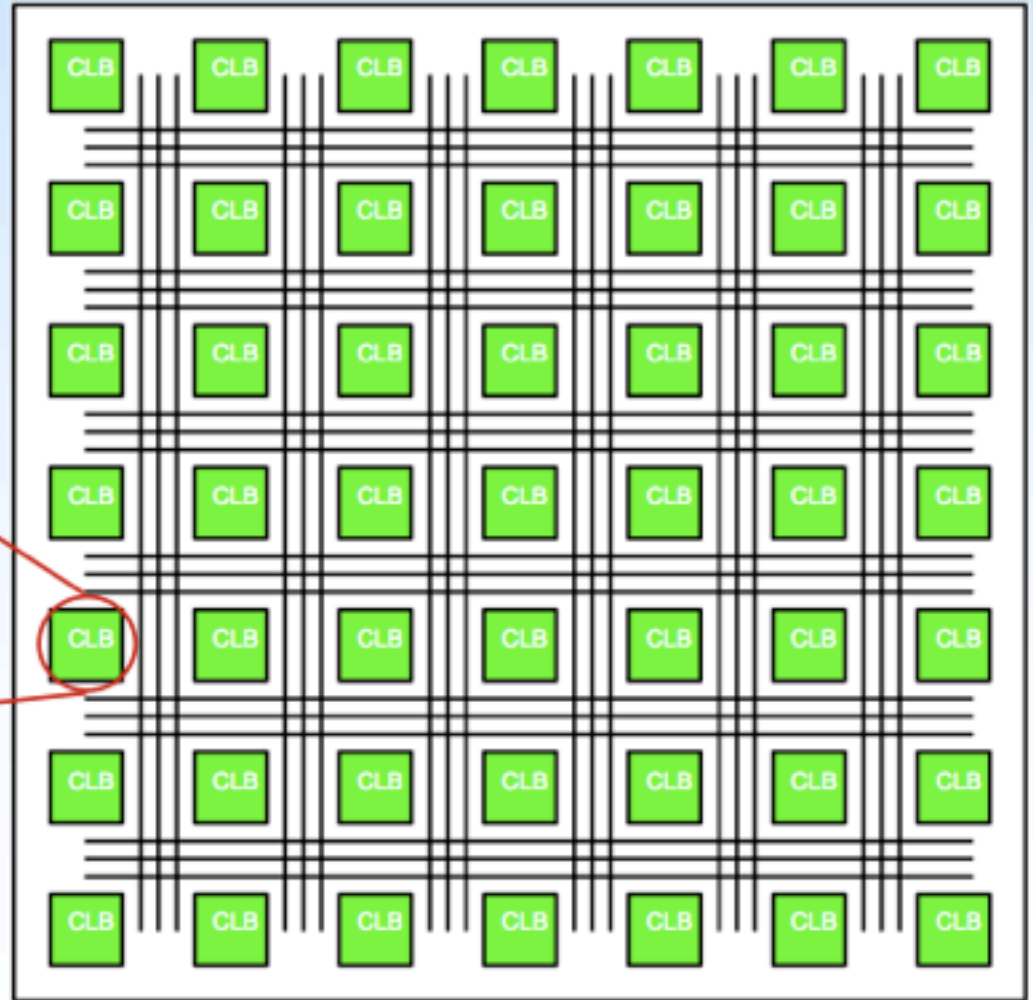

I/O blocks  
not shown



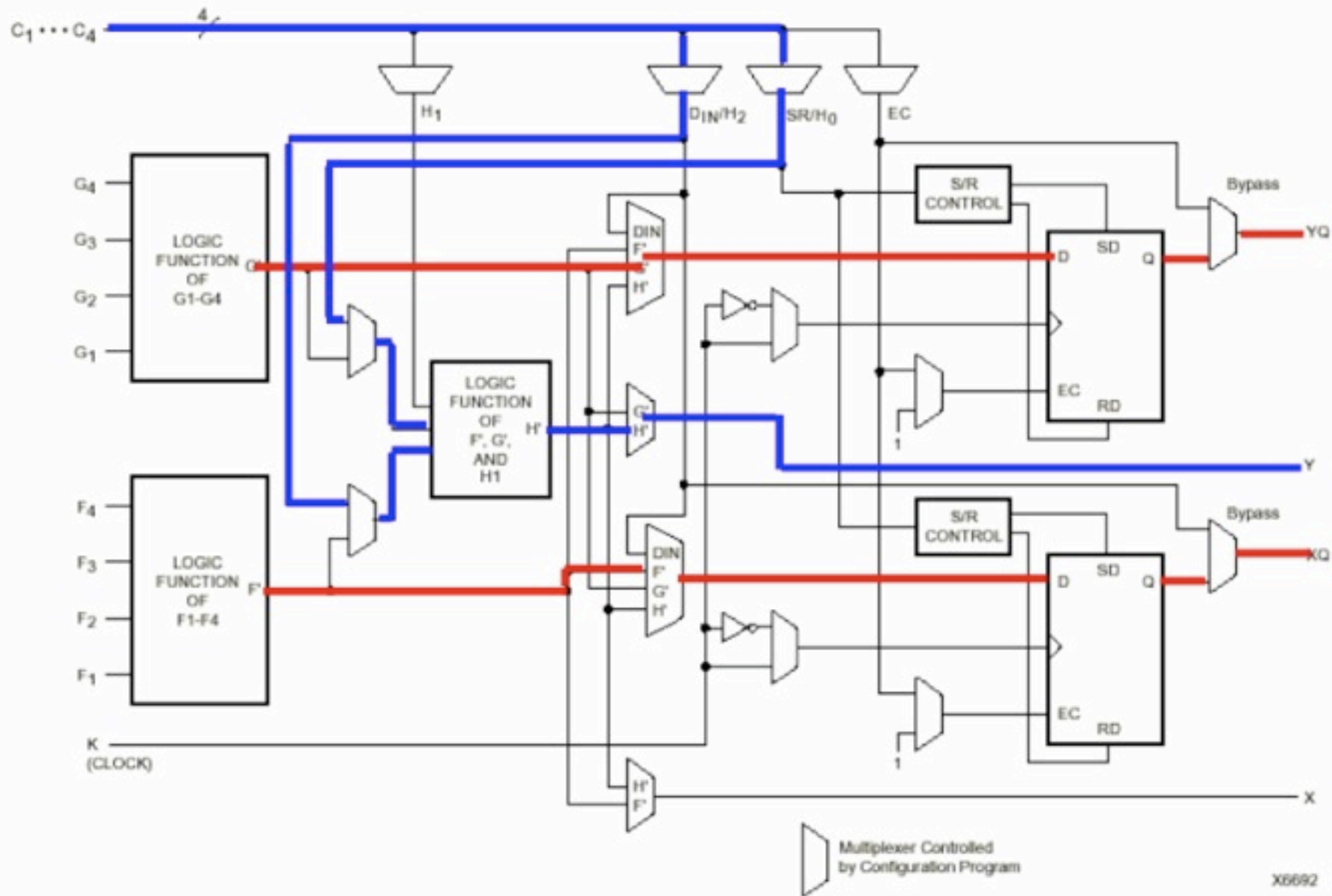

X6692

Figure 1: Simplified Block Diagram of XC4000 Series CLB (RAM and Carry Logic functions not shown)

# HAMMING CODE: ERROR DETECTION AND CORRECTION

Bit position:	1	2	3	4	5	6	7	8	9	10	11	12
	$P_1$	$P_2$	1	$P_4$	1	0	0	$P_8$	0	1	0	0

$$P_1 = \text{XOR of bits (3, 5, 7, 9, 11)} = 1 \oplus 1 \oplus 0 \oplus 0 \oplus 0 = 0$$

$$P_2 = \text{XOR of bits (3, 6, 7, 10, 11)} = 1 \oplus 0 \oplus 0 \oplus 1 \oplus 0 = 0$$

$$P_4 = \text{XOR of bits (5, 6, 7, 12)} = 1 \oplus 0 \oplus 0 \oplus 0 = 1$$

$$P_8 = \text{XOR of bits (9, 10, 11, 12)} = 0 \oplus 1 \oplus 0 \oplus 0 = 1$$

	0	0	1	1	1	0	0	1	0	1	0	0
Bit position:	1	2	3	4	5	6	7	8	9	10	11	12

- Compute correction bits

$$C_1 = \text{XOR of bits (1, 3, 5, 7, 9, 11)}$$

$$C_2 = \text{XOR of bits (2, 3, 6, 7, 10, 11)}$$

$$C_4 = \text{XOR of bits (4, 5, 6, 7, 12)}$$

$$C_8 = \text{XOR of bits (8, 9, 10, 11, 12)}$$



	$C_8$	$C_4$	$C_2$	$C_1$
For no error:	0	0	0	0
With error in bit 1:	0	0	0	1
With error in bit 5:	0	1	0	1

**Table 7-2**

*Range of Data Bits for  $k$  Check Bits*

<b>Number of Check Bits, <math>k</math></b>	<b>Range of Data Bits, <math>n</math></b>
3	2-4
4	5-11
5	12-26
6	27-57
7	58-120

$$2^k - 1 - k \geq n$$

# SINGLE-ERROR CORRECTION,

- To detect a double-error, add an additional parity bit  $P = \text{XOR}(\text{all other bits})$
- 12-bit example:  $P_{13} = \text{XOR}(1 \dots 12)$
- If
  - $C=0$  &  $P=0$ : no error
  - $C \neq 0$  &  $P=1$ : single error at bit indicated by  $C$
  - $C \neq 0$  &  $P=0$ : double error detected
  - $C=0$  &  $P=1$ : error in  $P_{13}$



 


Fig. P7-17