

# GATE-LEVEL MINIMIZATION

INEL 4205 - Spring 2012

 


Fig. 3-1 Two-variable Map


 


Fig. 3-2 Representation of Functions in the Map

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$

(a)

 

(b)

Fig. 3-3 Three-variable Map

 


Fig. 3-4 Map for Example 3-1;  $F(x, y, z) = \Sigma(2, 3, 4, 5) = x'y + xy'$

 


Fig. 3-5 Map for Example 3-2;  $F(x, y, z) = \Sigma(3, 4, 6, 7) = yz + xz'$

 


Fig. 3-6 Map for Example 3-3;  $F(x, y, z) = \Sigma(0, 2, 4, 5, 6) = z' + xy'$


 


Fig. 3-7 Map for Example 3-4;  $A'C + A'B + AB'C + BC = C + A'B$

$m_0$	$m_1$	$m_3$	$m_2$
$m_4$	$m_5$	$m_7$	$m_6$
$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
$m_8$	$m_9$	$m_{11}$	$m_{10}$

(a)

 

(b)

Fig. 3-8 Four-variable Map

$$\text{Example: } f(w,x,y,z) = \sum (0,1,2,4,5,6,8,9,12,13,14)$$

 


Fig. 3-9 Map for Example 3-5;  $F(w, x, y, z)$   
 $= \Sigma (0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14) = y' + w'z' + xz'$


 



Fig.3-10 Map for Example 3-6;  $A'B'C + B'CD' + A'BCD'$   
 $+ AB'C' = B'D' + B'C' + A'CD'$
 
# PRIME IMPLICANTS

- In choosing adjacent squares in a map, we must ensure that
  - all the minterm of the function are covered when we combine the squares
  - the number of terms in the expression is minimized
  - there are no redundant terms (i.e. minterms covered by other terms)
- Prime implicant (PI): product term obtained by combining the maximum possible number of adjacent squares.
- If a minterm in a square is covered by only one PI then the PI is essential.
- To avoid redundant terms, do (1) essential prime implicants, (2) prime implicants, (3) other terms



 
(a) Essential prime implicants  
BD and B'D'




(b) Prime implicants CD, B'C  
AD, and AB'

Fig. 3-11 Simplification Using Prime Implicants

 
Map in (b): do the 1's in (a) first, then CD and AB'



$$\text{Example: } F(A,B,C,D,E) = A'B'E' + BD'E + ACE$$

 

**FIGURE 3.13**  
Map for Example 3.7,  $F = A'B'E' + BD'E + ACE$

 

$$F(A,B,C,D) = \sum(0,1,2,5,8,9,10)$$

- Example 3-8: Simplify to a minimal expression using the:
  - 1's to produce a sum of products (AND-OR)
  - 0's to produce a complemented sum of products (AND-NOR)
  - 0's to produce a product of sums (OR-AND)
  - 1' to produce a complemented product of sums (OR-NAND)



 


Fig. 3-14 Map for Example 3-8;  $F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 9, 10)$   
 $= B'D' + B'C' + A'C'D = (A' + B')(C' + D')(B' + D)$

 

$$(a) F = B'D' + B'C' + A'C'D$$

 

$$(b) F = (A' + B') (C' + D') (B' + D)$$

Fig. 3-15 Gate Implementation of the Function of Example 3-8

**Table 3.2**  
*Truth Table of Function F*

<b>x</b>	<b>y</b>	<b>z</b>	<b>F</b>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

 


Fig. 3-16 Map for the Function of Table 3-2

yz		0 1		y	
wx		1 1		1 0	
w	x	0 0	1	1	X
0	0	X	1	1	X
0	1	0	X	1	0
1	1	0	0	1	0
1	0	0	0	1	0

z

(a)  $F = yz + w'x'$

yz		0 1		y	
wx		1 1		1 0	
w	x	0 0	1	1	X
0	0	X	1	1	X
0	1	0	X	1	0
1	1	0	0	1	0
1	0	0	0	1	0

z

(a)  $F = yz + w'z$

Fig. 3-17 Example with don't-care Conditions



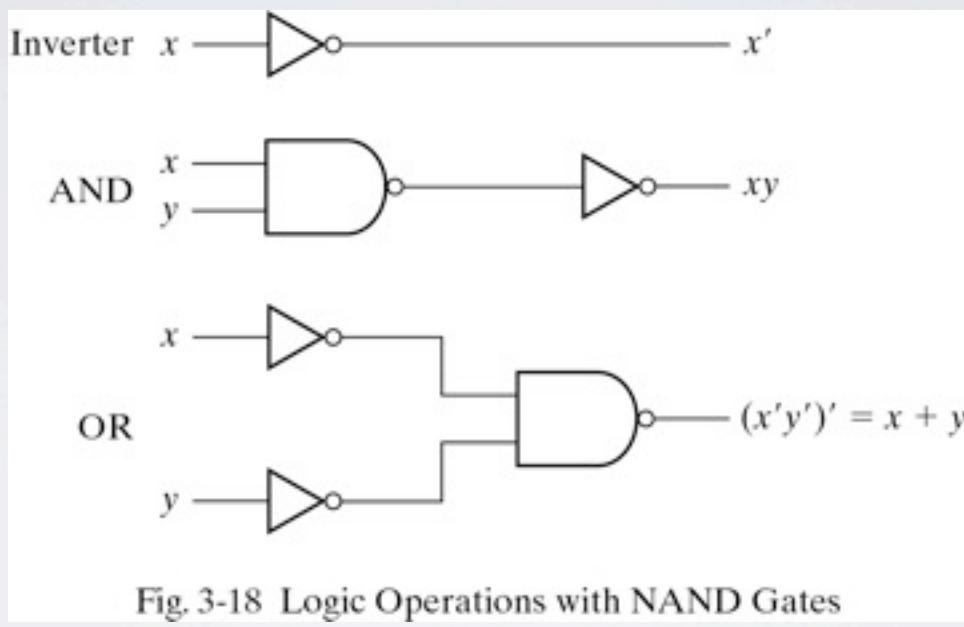


Fig. 3-18 Logic Operations with NAND Gates

 


(a) AND-invert

 


(b) Invert-OR


Fig. 3-19 Two Graphic Symbols for NAND Gate

 

(a)

 

(b)

 

(c)

Fig. 3-20 Three Ways to Implement  $F = AB + CD$



 
 
 


Fig. 3-21 Solution to Example 3-10

 


(a) AND-OR gates

 


(a) NAND gates

Fig. 3-22 Implementing  $F = A(CD + B) + BC$

 

(a) AND-OR gates

 

(b) NAND gates

Fig. 3-23 Implementing  $F = (AB' + A'B)(C + D')$



 


Fig. 3-24 Logic Operations with NOR Gates

 

(a) OR-invert

 

(a) Invert-AND

Fig. 3-25 Two Graphic Symbols for NOR Gate

 


Fig. 3-26 Implementing  $F = (A + B)(C + D)E'$



 


Fig. 3-27 Implementing  $F = (AB' + A'B)(C + D')$  with NOR Gates

 

(a) Wired-AND in open-collector  
TTL NAND gates.


(AND-OR-INVERT)

 


(b) Wired-OR in ECL gates

(OR-AND-INVERT)


Fig. 3-28 Wired Logic

 

(a) AND-NOR

 


(b) AND-NOR

 


(c) NAND-AND


Fig. 3-29 AND-OR-INVERT Circuits;  $F = (AB + CD + E)'$

 

(a) OR-NAND

 

(b) OR-NAND

 

(c) NOR-OR

Fig. 3-30 OR-AND-INVERT Circuits;  $F = [(A + B)(C + D)E]'$


	$yz$	00	01	$\overline{11}$	$y$ 10
$x$	0	1	0	0	0
$x$	1	0	0	0	1

$\underline{z}$


$$F = x'y'z' + xyz'$$

$$F' = x'y + xy' + z$$

 (a) Map simplification in sum of products.




AND-NOR

 


NAND-AND

$$(b) F = (x'y + xy' + z)'$$

 


OR-NAND

 


NOR-OR

$$(c) F = [(x + y + z)(x' + y' + z)]'$$

Fig. 3-31 Other Two-level Implementations

 

(a) With AND-OR-NOT gates

 

(b) With NAND gates

Fig. 3-32 Exclusive-OR Implementations


BC		B	
0 0		0 1	1 1
A		1 0	
0	1	1	1
	1		1
<hr/> C			

(a) Odd function  
 $F = A \oplus B \oplus C$


BC		B	
0 0		0 1	1 1
A		1 0	
0	1		1
	1	1	
<hr/> C			

(a) Even function  
 $F = (A \oplus B \oplus C)'$

Fig. 3-33 Map for a Three-variable Exclusive-OR Function

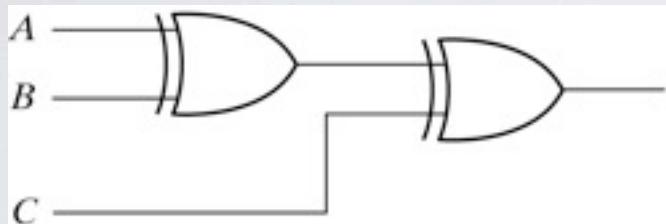


(a) 3-input odd function

 


(b) 3-input even function

Fig. 3-34 Logic Diagram of Odd and Even Functions

 

(a) Odd function


$$F = A \oplus B \oplus C \oplus D$$

 


(b) Even function

$$F = (A \oplus B \oplus C \oplus D)'$$

Fig. 3-35 Map for a Four-variable Exclusive-OR Function

 

(a) 3-bit even parity generator

 

(a) 4-bit even parity checker

Fig. 3-36 Logic Diagram of a Parity Generator and Checker

 


Fig. 3-37 Circuit to Demonstrate HDL

 


Fig. 3-38 Simulation Output of HDL Example 3-3