

COMBINATIONAL LOGIC

INEL 4205 - CHAPTER 4

 


Fig. 4-1 Block Diagram of Combinational Circuit

 


Fig. 4-2 Logic Diagram for Analysis Example

YOU CAN USE INTERMEDIATE VARIABLES TO CONSTRUCT THE BOOLEAN FUNCTIONS FROM A COMPLEX LOGIC DIAGRAM.

Table 4-2
Truth Table for Code-Conversion Example

Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

TABLE 4-2 BCD TO EXCESS-3 CODE

 
 
 
 


Fig. 4-3 Maps for BCD to Excess-3 Code Converter


 



Fig. 4-4 Logic Diagram for BCD to Excess-3 Code Converter

Table 4-3
Half Adder

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

$$(a) S = xy' + x'y \\ C = xy$$

 


$$(b) S = x \oplus y \\ C = xy$$


Fig. 4-5 Implementation of Half-Adder

Table 4-4
Full Adder

x	y	z	c	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

$$S = x'y'z + x'yz' + xy'z' + xyz$$

 

$$\begin{aligned} S &= xy + xz + yz \\ &= xy + xy'z + x'yz \end{aligned}$$

Fig. 4-6 Maps for Full Adder

 
 


Fig. 4-7 Implementation of Full Adder in Sum of Products


 


Fig. 4-8 Implementation of Full Adder with Two Half Adders and an OR Gate

 

 


Fig. 4-10 Full Adder with P and G Shown

 


Fig. 4-10 Full Adder with P and G Shown

$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

 


Fig. 4-10 Full Adder with P and G Shown

$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

C_0 = input carry

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1(G_0 + P_0 C_0) = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

 


Fig. 4-11 Logic Diagram of Carry Lookahead Generator

 


Fig. 4-12 4-Bit Adder with Carry Lookahead

 


Fig. 4-13 4-Bit Adder Subtractor

$M=1$ COMPLEMENTS THE B -BITS AND ADDS 1,
THUS FORMING THE 2'S COMPLEMENT OF B

carries: 0 1

$$\begin{array}{r} +70 \\ +80 \\ \hline +150 \end{array} \qquad \begin{array}{r} 0 \ 1000110 \\ 0 \ 1010000 \\ \hline 1 \ 0010110 \end{array}$$

carries: 1 0

$$\begin{array}{r} -70 \\ -80 \\ \hline -150 \end{array} \qquad \begin{array}{r} 1 \ 0111010 \\ 1 \ 0110000 \\ \hline 0 \ 1101010 \end{array}$$

 


Fig. 4-14 Block Diagram of a BCD Adder

$$\begin{array}{r}
 \begin{array}{c} B_1 \\ A_1 \end{array} \quad \begin{array}{c} B_0 \\ A_0 \end{array} \\
 \hline
 \begin{array}{c} A_0B_1 \\ A_1B_0 \end{array} \quad \begin{array}{c} A_0B_0 \end{array} \\
 \hline
 \begin{array}{cc} A_1B_1 & A_1B_0 \\ \hline C_3 & C_2 & C_1 & C_0 \end{array}
 \end{array}$$

 


Fig. 4-15 2-Bit by 2-Bit Binary Multiplier

 


Fig. 4-16 4-Bit by 3-Bit Binary Multiplier

MAGNITUDE COMPARATOR

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

$$x_i = A_i B_i + A'_i B'_i \quad \text{for } i = 0, 1, 2, 3$$

$$(A = B) = x_3 x_2 x_1 x_0$$

$$(A > B) = A_3 B'_3 + x_3 A_2 B'_2 + x_3 x_2 A_1 B'_1 + x_3 x_2 x_1 A_0 B'_0$$

$$(A < B) = A'_3 B_3 + x_3 A'_2 B_2 + x_3 x_2 A'_1 B_1 + x_3 x_2 x_1 A'_0 B_0$$

 


Fig. 4-17 4-Bit Magnitude Comparator

Table 4-6
Truth Table of a 3-to-8-Line Decoder


 


Fig. 4-18 3-to-8-Line Decoder

 

(a) Logic diagram

E	A	B	D ₀	D ₁	D ₂	D ₃
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

(b) Truth table

Fig. 4-19 2-to-4-Line Decoder with Enable Input

 


Fig. 4-20 4×16 Decoder Constructed with Two 3×8 Decoders


 



Fig. 4-21 Implementation of a Full Adder with a Decoder

Table 4-7
Truth Table of Octal-to-Binary Encoder

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

 

$$x = D_2 + D_3$$

 

$$y = D_3 + D_1D'_2$$

Fig. 4-22 Maps for a Priority Encoder



 


Fig. 4-23 4-Input Priority Encoder

 


(a) Logic diagram

 

(b) Block diagram

Fig. 4-24 2-to-1-Line Multiplexer

 

(a) Logic diagram

s_1	s_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

(b) Function table

Fig. 4-25 4-to-1-Line Multiplexer


 


Fig. 4-26 Quadruple 2-to-1-Line Multiplexer

x	y	z	F
0	0	0	0
0	0	1	1 $F = z$
0	1	0	1
0	1	1	0 $F = z'$
1	0	0	0 $F = 0$
1	0	1	0
1	1	0	1
1	1	1	1 $F = 1$

(a) Truth table

 

(b) Multiplexer implementation

Fig. 4-27 Implementing a Boolean Function with a Multiplexer

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1 $F = D$
0	0	1	0	0
0	0	1	1	1 $F = D$
0	1	0	0	1
0	1	0	1	0 $F = D'$
0	1	1	0	0
0	1	1	1	0 $F = 0$
1	0	0	0	0
1	0	0	1	0 $F = 0$
1	0	1	0	0
1	0	1	1	1 $F = D$
1	1	0	0	1
1	1	0	1	1 $F = 1$
1	1	1	0	1
1	1	1	1	1 $F = 1$

 


Fig. 4-28 Implementing a 4-Input Function with a Multiplexer



 


Fig. 4-29 Graphic Symbol for a Three-State Buffer

 


(a) 2-to-1- line mux

 


(b) 4 - to - 1 line mux


Fig. 4-30 Multiplexers with Three-State Gates

 


bufif1

 

bufif0

 

notifl

 

notif0

Fig. 4-31 Three-State Gates


 


Fig. 4-32 2-to-1-Line Multiplexer with Three-State Buffers

Stimulus module

 

Design module

 


Fig. 4-33 Stimulus and Design Modules Interaction

 


Fig. P4-1


 


Fig. P4-2

 

(a) Segment designation



(b) Numerical designation for display

Fig. P4-9

 


Fig. P4-17 First Stage of a Parallel Adder