
 


Programmable Logic and Memories

INEL 4205 - Logic Circuits - Spring 2008

 

(a) Conventional symbol



(b) Array logic symbol

Fig. 7-1 Conventional and Array Logic Diagrams for OR Gate

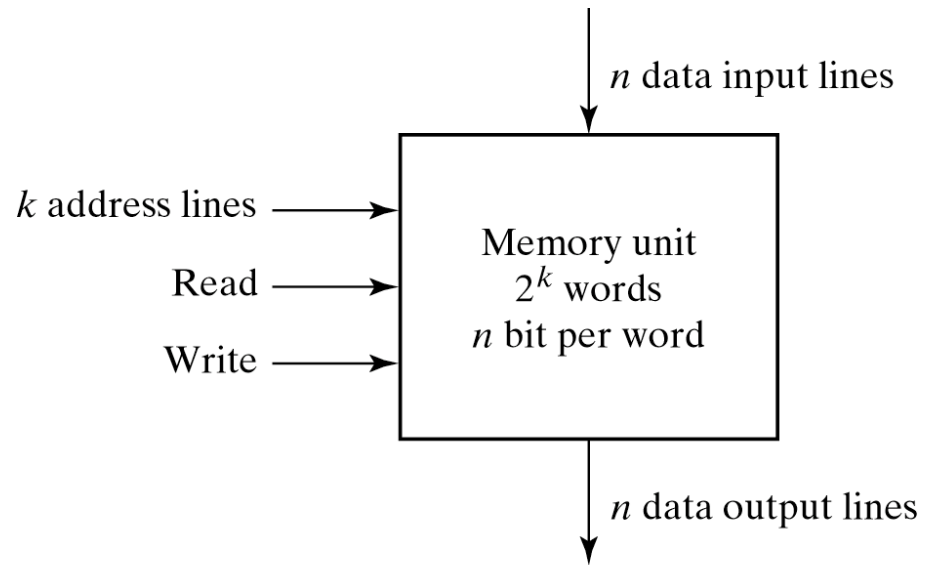


Fig. 7-2 Block Diagram of a Memory Unit


Memory address		
Binary	decimal	Memory content
0000000000	0	1011010101011101
0000000001	1	1010101110001001
0000000010	2	0000110101000110
	⋮	⋮
1111111101	1021	1001110100010100
1111111110	1022	0000110100011110
1111111111	1023	1101111000100101

Fig. 7-3 Content of a 1024×16 Memory


Steps to Write into RAM

- Apply address to address lines
- Apply data to data input lines
- Activate *write* input & enable chip

For reads: do 1 and 3 using *read* input

 


(a) Write cycle

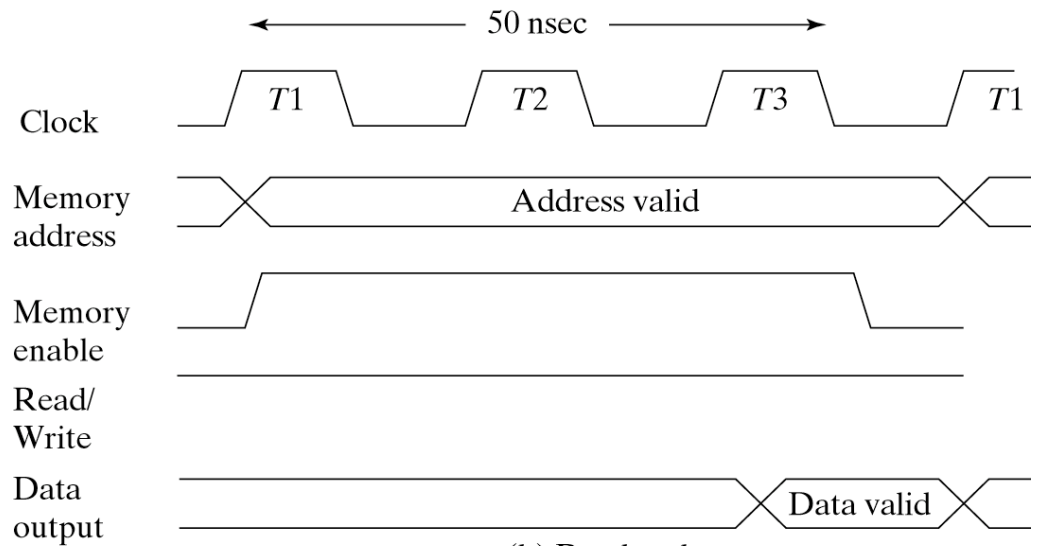


(b) Read cycle

Fig. 7-4 Memory Cycle Timing Waveforms

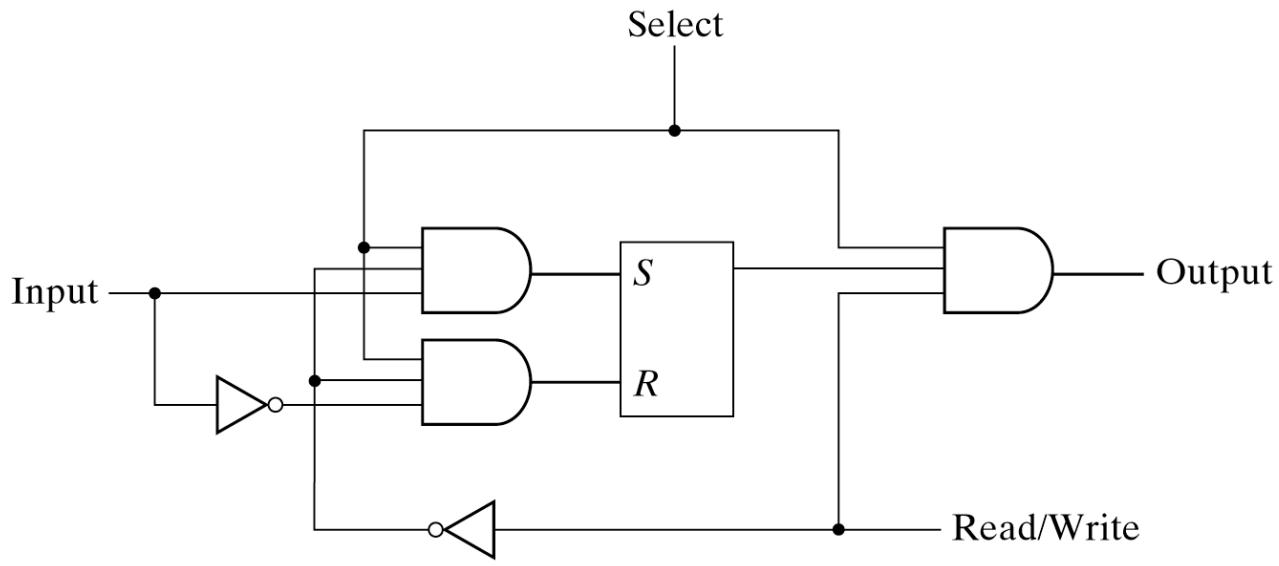

(a) Logic diagram

 

(b) Block diagram

Fig. 7-5 Memory Cell


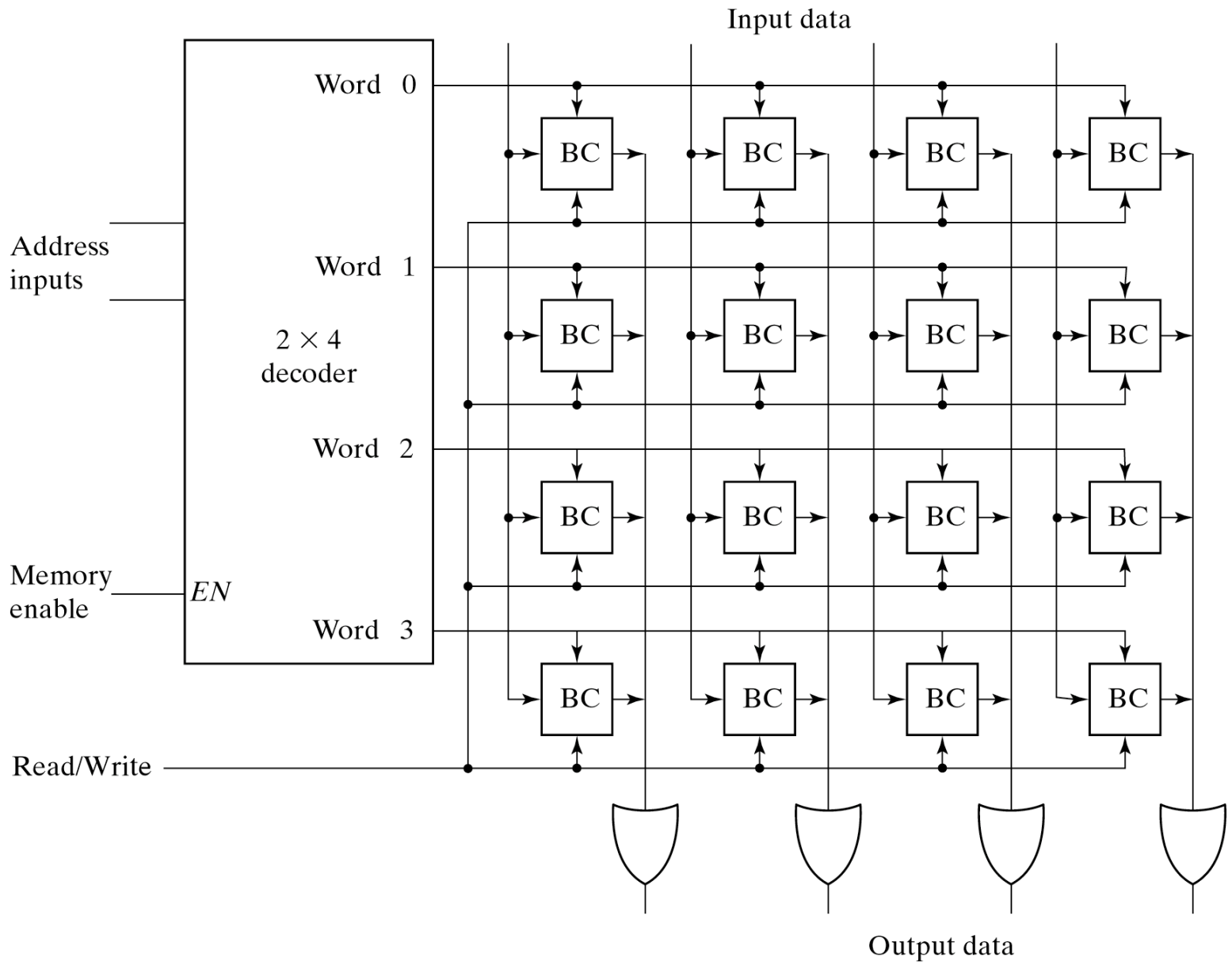


Fig. 7-6 Diagram of a 4×4 RAM

Row/Column decoding

 - 1K-word memory requires 10 address bits and a 10×1024 decoder
- The decoding can also be done with two 5×32 decoder, one for the *row* and one for the column. The cell connected to the row-column intersection is selected.



binary address

01100	10100
\underline{X}	\underline{Y}

Fig. 7-7 Two-Dimensional Decoding Structure for a 1K-Word Memory

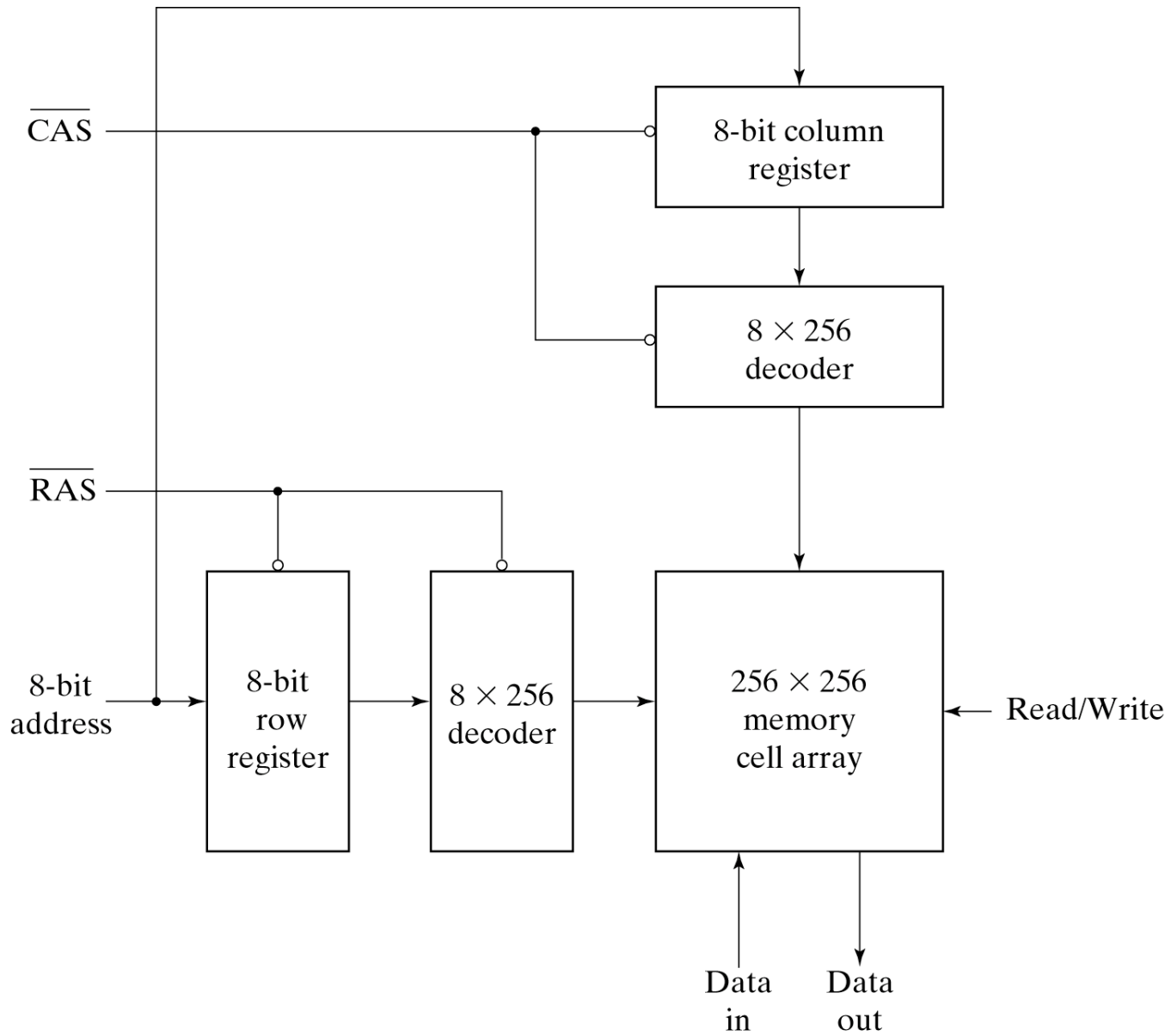


Fig. 7-8 Address Multiplexing for a 64K DRAM

 


Fig. 7-9 ROM Block Diagram

 


Fig. 7-10 Internal Logic of a 32×8 ROM

Used as programmable logic, a **PROM** stores the truth table for N functions of M inputs.

N = number of bits in each cell.

M = number of address bits; there are 2^M memory locations in the PROM.

“x” indicates a connection, and a “1” in the truth table

 



Fig. 7-11 Programming the ROM According to Table 7-3

Address 00000: cell contents is 10110110

Design a combinatorial circuit using a ROM. The circuit accepts a 3-bit input number and outputs a binary number equal to the square of the input.

Table 7-4
Truth Table for Circuit of Example 7-1

Inputs			Outputs						Decimal
A_2	A_1	A_0	B_5	B_4	B_3	B_2	B_1	B_0	
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	1	9
1	0	0	0	1	0	0	0	0	16
1	0	1	0	1	1	0	0	1	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	0	0	0	1	49

 

(a) Block diagram

A_2	A_1	A_0	B_5	B_4	B_3	B_2
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0

(b) ROM truth table

Fig. 7-12 ROM Implementation of Example 7-1

 
 
 


Fig. 7-13 Basic Configuration of Three PLDs

PLA

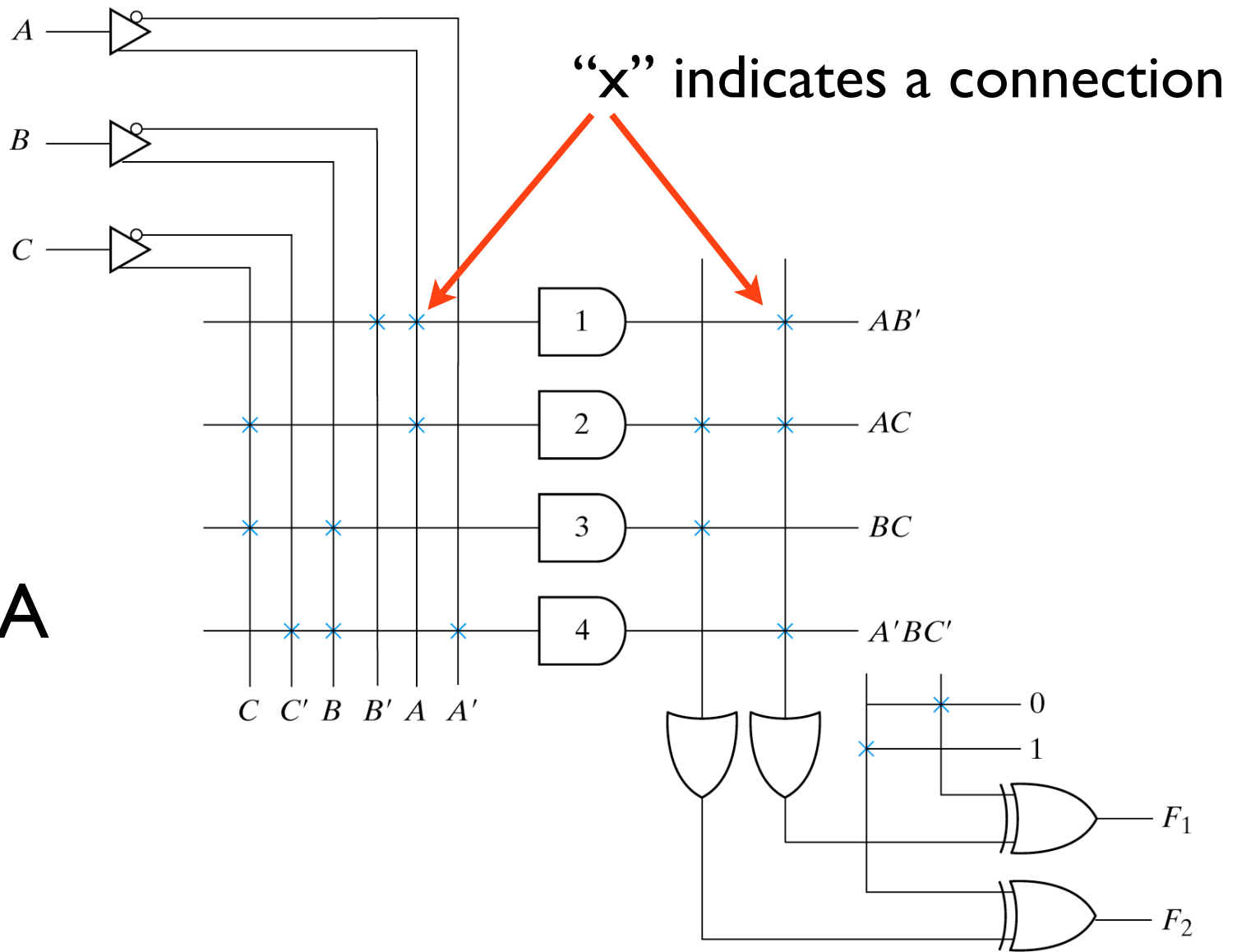



Fig. 7-14 PLA with 3 Inputs, 4 Product Terms, and 2 Outputs

PLA has limited # of ANDs: designer can use F or F' to minimize the # of distinct product terms, the complement F' if necessary.

Example: Implement the following boolean functions in a PLA:

$$F_1(A,B,C) = \sum(0,1,2,4)$$

$$F_2(A,B,C) = \sum(0,5,6,7)$$

 

		<i>BC</i>		<i>B</i>	
		00	01	11	10
<i>A</i>	0	1	1	0	1
<i>A</i>	1	1	0	0	0
		<i>C</i>			

$$F_1 = A'B' + A'C' + B'C'$$

$$F_1 = (AB + AC + BC)'$$

		<i>BC</i>		<i>B</i>	
		00	01	11	10
<i>A</i>	0	1	0	0	0
<i>A</i>	1	0	1	1	1
		<i>C</i>			

$$F_2 = AB + AC + A'B'C'$$


$$F_2 = (A'C + A'B + AB'C)'$$

PLA programming table

	Product term	Inputs			Outputs	
		<i>A</i>	<i>B</i>	<i>C</i>	(C)	(T)
					<i>F</i> ₁	<i>F</i> ₂
<i>AB</i>	1	1	1	-	1	1
<i>AC</i>	2	1	-	1	1	1
<i>BC</i>	3	-	1	1	1	-
<i>A'B'C'</i>	4	0	0	0	-	1

Fig. 7-15 Solution to Example 7-2

 7-21 Derive the PLA programming table for the combinational circuit that squares a 3-bit number. Minimize the number of product terms. (See Fig. 7-12 for the equivalent ROM implementation.)




(a) Block diagram

A_2	A_1	A_0	B_5	B_4	B_3	B_2
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0

(b) ROM truth table

Fig. 7-12 ROM Implementation of Example 7-1

 

X = connection
 + = no connection

3. (25 pts) Determine the PLA programming table needed to implement the following two boolean functions. Minimize the number of product terms. Show all your work, including the Karnaugh maps used in the minimization.

$$F_1(A,B,C,D) = \sum(1, 3, 4, 5, 7, 13, 15)$$

$$F_2(A,B,C,D) = \sum(0, 2, 3, 6, 7, 8, 10, 11, 12, 14)$$

Write your result in the following table.

Product terms	Inputs				Outputs	
	A	B	C	D	() F ₁	() F ₂

Note: not all rows need to be used

PAL

 


Fig. 7-16 PAL with Four Inputs, Four Outputs, and Three-Wide AND-OR Structure

PAL: Only inputs to AND gates can be programmed but one term (F_1) can be re-used in other functions

$$w(A, B, C, D) = \Sigma(2, 12, 13)$$

$$x(A, B, C, D) = \Sigma(7, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$y(A, B, C, D) = \Sigma(0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$$

$$z(A, B, C, D) = \Sigma(1, 2, 8, 12, 13)$$

Manipulate expressions so that a common term is identified.

Assign common term to F_1 .

$$w = ABC' + A'B'CD'$$

$$x = A + BCD$$

$$y = A'B + CD + B'D'$$

$$z = ABC' + A'B'CD' + AC'D' + A'B'C'D$$

$$= w + AC'D' + A'B'C'D$$

Table 7-6
PAL Programming Table

Product Term	AND Inputs					Outputs
	A	B	C	D	W	
1	1	1	0	-	-	$w = ABC'$ $+ A'B'CD'$
2	0	0	1	0	-	
3	-	-	-	-	-	
4	1	-	-	-	-	$x = A$ $+ BCD$
5	-	1	1	1	-	
6	-	-	-	-	-	
7	0	1	-	-	-	$y = A'B$ $+ CD$ $+ B'D'$
8	-	-	1	1	-	
9	-	0	-	0	-	
10	-	-	-	-	1	$z = w$ $+ AC'D'$ $+ A'B'C'D$
11	1	-	0	0	-	
12	0	0	0	1	-	

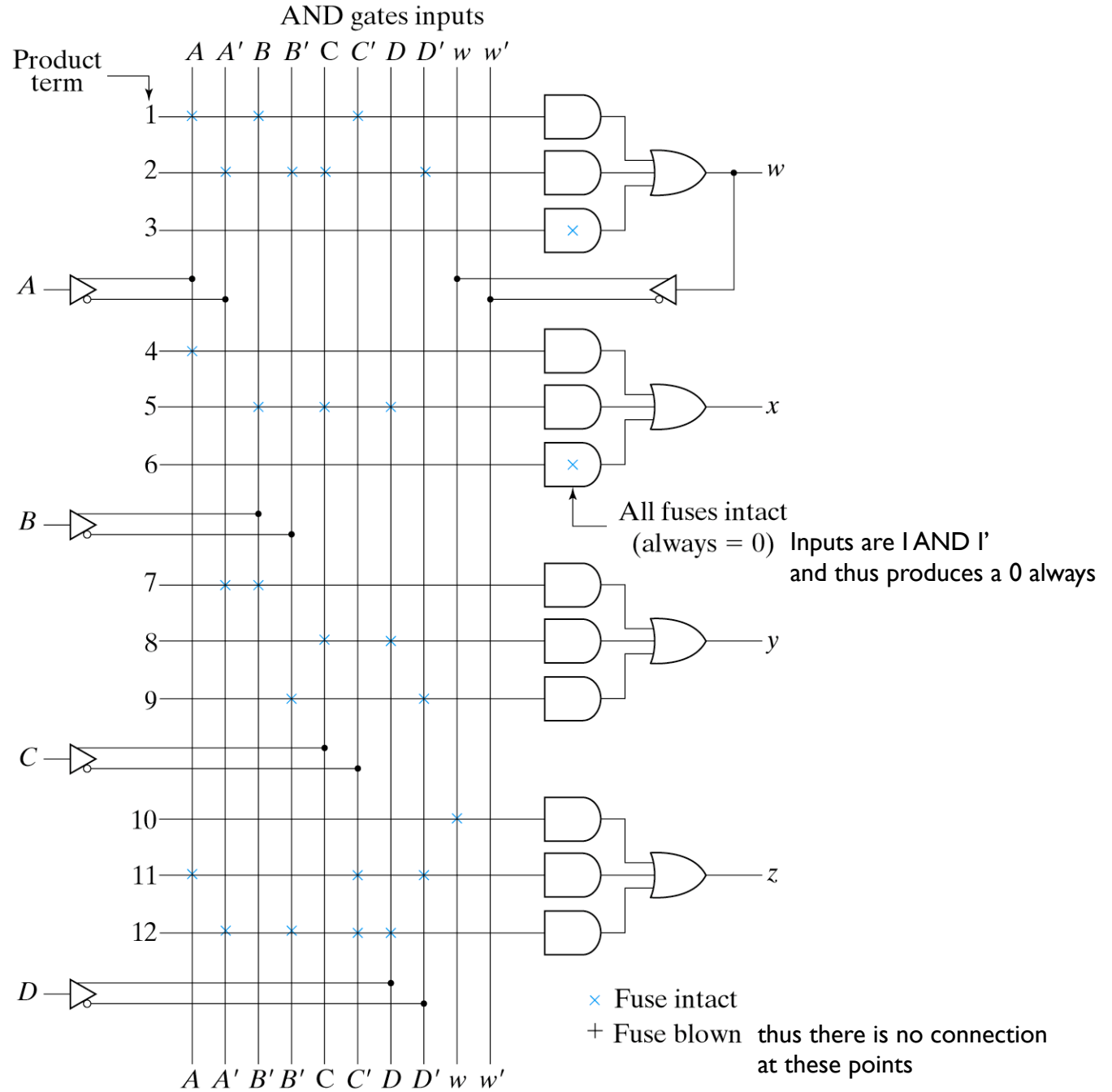


Fig. 7-17 Fuse Map for PAL as Specified in Table 7-6

- PAL practice: problem 7-24

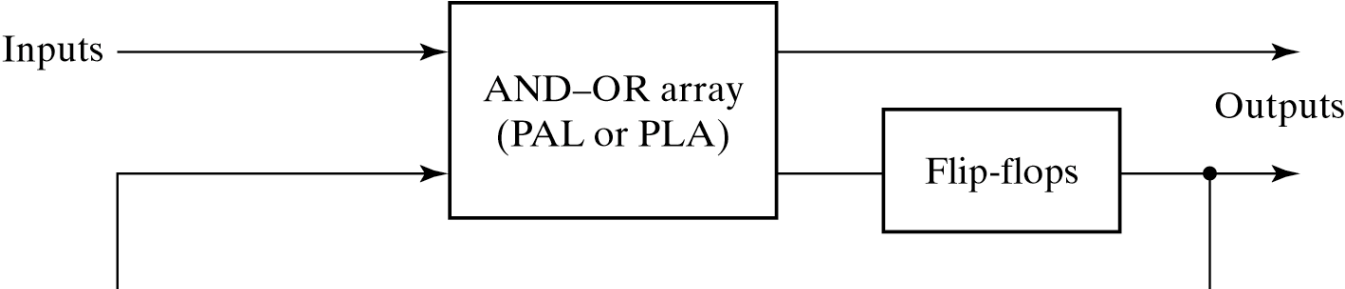


Fig. 7-18 Sequential Programmable Logic Device

 


Fig. 7-19 Basic Macrocell Logic


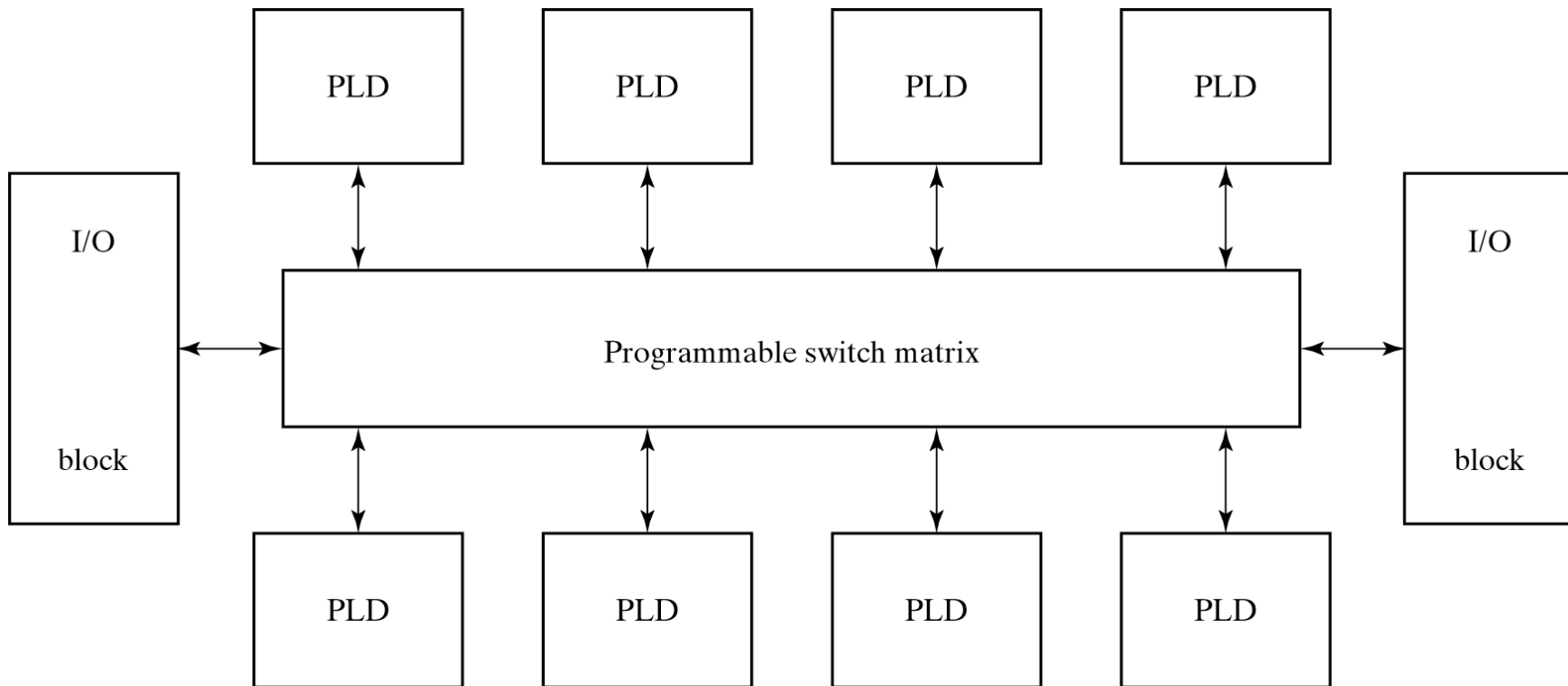
 


Fig. 7-20 General CPLD Configuration

Xilinx FPGAs are based on Configurable Logic Blocks (CLBs)

More generally called logic cells

Programmable

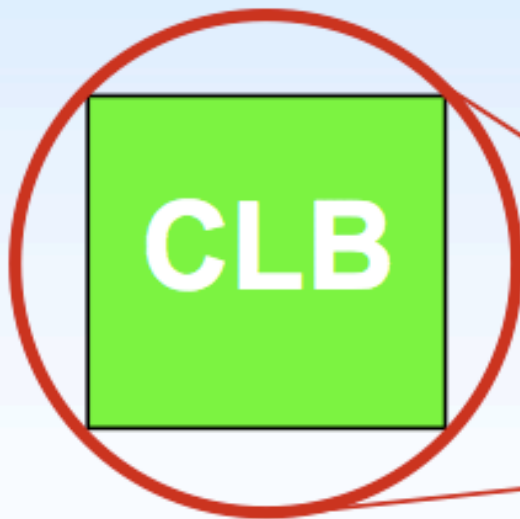

I/O blocks
not shown

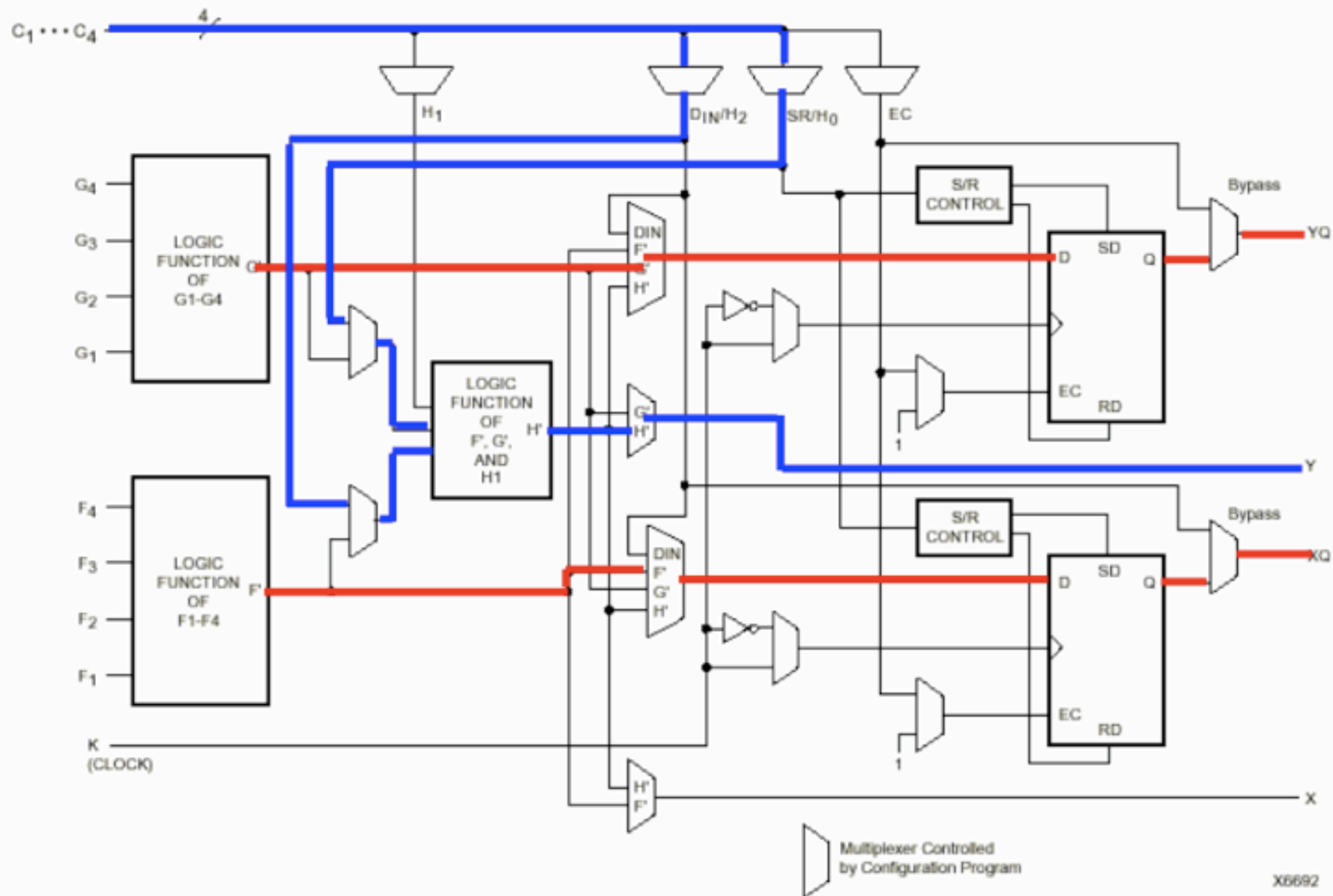


Figure 1: Simplified Block Diagram of XC4000 Series CLB (RAM and Carry Logic functions not shown)

Hamming code: Error Detection and Correction

Bit position:	1	2	3	4	5	6	7	8	9	10	11	12
	P_1	P_2	1	P_4	1	0	0	P_8	0	1	0	0

$$P_1 = \text{XOR of bits (3, 5, 7, 9, 11)} = 1 \oplus 1 \oplus 0 \oplus 0 \oplus 0 = 0$$

$$P_2 = \text{XOR of bits (3, 6, 7, 10, 11)} = 1 \oplus 0 \oplus 0 \oplus 1 \oplus 0 = 0$$

$$P_4 = \text{XOR of bits (5, 6, 7, 12)} = 1 \oplus 0 \oplus 0 \oplus 0 = 1$$

$$P_8 = \text{XOR of bits (9, 10, 11, 12)} = 0 \oplus 1 \oplus 0 \oplus 0 = 1$$

	0	0	1	1	1	0	0	1	0	1	0	0
Bit position:	1	2	3	4	5	6	7	8	9	10	11	12

- Compute correction bits

$$C_1 = \text{XOR of bits (1, 3, 5, 7, 9, 11)}$$

$$C_2 = \text{XOR of bits (2, 3, 6, 7, 10, 11)}$$

$$C_4 = \text{XOR of bits (4, 5, 6, 7, 12)}$$

$$C_8 = \text{XOR of bits (8, 9, 10, 11, 12)}$$

	C_8	C_4	C_2	C_1
For no error:	0	0	0	0
With error in bit 1:	0	0	0	1
With error in bit 5:	0	1	0	1

Table 7-2
Range of Data Bits for k Check Bits

Number of Check Bits, k	Range of Data Bits, n
3	2-4
4	5-11
5	12-26
6	27-57
7	58-120

$$2^k - 1 - k \geq n$$

Single-error correction, double-error

- To detect a double-error, add an additional parity bit $P = \text{XOR}(\text{all other bits})$
- 12-bit example: $P_{13} = \text{XOR}(1 \dots 12)$
- If
 - $C=0$ & $P=0$: no error
 - $C \neq 0$ & $P=1$: single error at bit indicated by C
 - $C \neq 0$ & $P=0$: double error detected
 - $C=0$ & $P=1$: error in P_{13}

 


Fig. P7-17