

Verilog

INEL 4205 - November 2009

```
module counter(out, clk, reset);  
  parameter WIDTH = 4;  
  
  output [WIDTH-1 : 0] out;  
  reg [WIDTH-1 : 0] out;  
  input clk, reset;  
  wire clk, reset;  
  
  always @(posedge clk)  
    if (~reset)  
      out = out + 1;  
  
  always @(reset)  
    if (reset) out = 0;  
  
endmodule // counter
```

```

module test;

  reg reset, clk;
  wire [3:0] value;
  initial
    begin
      // system command to create a file for gtkview
      $dumpfile("icounter.vcd");
      $dumpvars ;

      // Monitor variables "reset" or "value"
      $monitor("Time = %g reset = %b count = %b",$time, reset, value);

      // Do the simulation
      reset = 0;
      clk = 0;
      # 17 reset = 1;
      # 11 reset = 0;
      # 29 reset = 1;
      # 11 reset = 0;
      # 300 $finish;
    end

    /* Make a regular pulsing clock. */
    always #5 clk = !clk;

    counter c1 (value, clk, reset); // instantiate module counter

endmodule // test

```

Table 4-10
Verilog HDL Operators

Symbol	Operation
+	binary addition
-	binary subtraction
&	bit-wise AND
	bit-wise OR
^	bit-wise XOR
~	bit-wise NOT
==	equality
>	greater than
<	less than
{ }	concatenation
?:	conditional

Signals

- Nets - represent structural connections
 - “wire” is the most common net type
- reg - represent variables used to store data
 - store the last value assigned to them until another assignment statement changes their value
- Constants:
 - `3' b010; // 3 bits, equal to binary 010`
 - `3' d2; // 3 bits, equal to decimal 2`
 - `8' hAB; // 8 bits, equal to hex AB = 101010112`

Continuous Assignment Statement:

- used to assign a value to a net type (i.e. a wire) outside of an *always* block
- taken as concurrent (happening at the same time)
- assign statement is implied if done when declaring the variable

HDL Example 3-4

```
//Circuit specified with Boolean expressions
module circuit_bln (x,y,A,B,C,D);
    input A,B,C,D;
    output x,y;
    assign x = A | (B & C) | (~B & D);
    assign y = (~B & C) | (B & ~C & ~D);
endmodule
```

HDL Example 4-4

```
//Dataflow description of 4-bit adder
module binary_adder (A,B,Cin,SUM,Cout);
    input [3:0] A,B;
    input Cin;
    output [3:0] SUM;
    output Cout;
    assign {Cout,SUM} = A + B + Cin;
endmodule
```

HDL Example 4-5

```
//Dataflow description of a 4-bit comparator.  
module magcomp (A,B,ALSB,AGTB,AEQB) ;  
    input [3:0] A,B;  
    output ALTB,AGTB,AEQB;  
    assign ALTB=(A < B) ,  
           AGTB = (A > B) ,  
           AEQB = (A == B) ;  
endmodule
```

HDL Example 4-6

```
//Dataflow description of 2-to-1-line multiplexer
module mux2x1_df (A,B,select,OUT);
    input A,B,select;
    output OUT;
    assign OUT = select ? A : B;
endmodule
```

Behavioral constructs

initial blocks - provide initial values for simulations

always block - use to contain the procedural constructs.

```
Always @(sensitivity_list)  
[begin]  
[procedural statements  
consisting of assignment, if,  
case, while, and for loops. May  
also include task and function  
calls. ]  
[end]
```

```
//HDL Example 5-1  
//Description of D latch (See Fig.5-6)  
module D_latch (Q,D,control);  
    output Q;  
    input D,control;  
    reg Q;  
    always @ (control or D)  
    if (control) Q = D;  
        //Same as: if (control = 1)  
endmodule
```

```

module ccounter(clock, control, count);
  input clock ;
  input control ;
  output count ;
  reg [2:0] count ;

initial
  count=3'h0 ;

always @ (posedge clock)
  if (control)
    case (count)
      3'h0: count = 3'h1;
      3'h1: count = 3'h4;
      3'h4: count = 3'h5;
      3'h5: count = 3'h7;
      3'h7: count = 3'h0;
      default:
        count = 3'h5;
    endcase // case (count)
  else // counting down
    case (count)
      3'h1: count = 3'h6;
      3'h2: count = 3'h1;
      3'h3: count = 3'h2;
      3'h5: count = 3'h3;
      3'h6: count = 3'h5;
      default:
        count = 3'h5;
    endcase // case (count)
endmodule // ccounter

```

```

module testb ; // stimulus or testbench

reg control, clk;
wire [2:0] value;

initial
  begin
    // create a dump of all variables to use gtkwave
    // to view
    $dumpfile("ccounter.vcd");
    $dumpvars ;

    // print a message on the screen each time a
    // variable changes
    $monitor("Time = %g control = %b count = %b",
      $time, control, value);

    // now describe the simulation
    control = 1'b0 ;
    clk = 1'b0 ;
    #60 control = 1'b1;
    #60 control = 1'b0;
    #60 $finish;
  end // initial begin

// create clock
always
  #5 clk = ~clk;

// instantiate module under test
ccounter mycount(clk, control, value);
endmodule // testb

```

 


Fig. 5-16 State Diagram of the Circuit of Fig. 5-15

//HDL Example 5-5: Mealy state diagram (Fig 5-16)

module Mealy_md1 (x,y,CLK,RST);

input x,CLK,RST;

output y;

reg y;

reg [1:0] Prstate, Nxtstate;

parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;

always @ (posedge CLK or negedge RST)

if (~RST) Prstate = S0; //Initialize to state S0

else Prstate = Nxtstate; //Clock operations

always @ (Prstate or x) //Find next state

case (Prstate)

S0: if (x) Nxtstate = S1;

S1: if (x) Nxtstate = S3;

else Nxtstate = S0;

S2: if (~x)Nxtstate = S0;

S3: if (x) Nxtstate = S2;

else Nxtstate = S0;

endcase

always @ (Prstate or x) //Evaluate output

case (Prstate)

S0: y = 0;

S1: if (x) y = 1'b0; else y = 1'b1;

S2: if (x) y = 1'b0; else y = 1'b1;

S3: if (x) y = 1'b0; else y = 1'b1;

endcase

endmodule