

Introduction to Verilog



INEL 4205 - Logic Circuits
M. Toledo - Spring 2008

Hardware description languages (HDL)

- High-level program-like description of logic circuit
- Developed for circuit simulation, now also used to synthesize circuits for ASIC's and FPGA's
- Two main hdl's used today
 - VHDL - ADA-like synTax;
 - Verilog - C-like syntax;

Verilog

- Basic units: *module*
 - normally describe a single piece of hardware
 - has *declarations* that describe names & types of module's inputs & outputs

```
module fourbitadder( X, Y, S, C) ; // c++ style remarks
  input [3:0] X, Y; // four-bit input vectors
  output reg [3:0] S; // 4-bit sum vector
  output reg C ; // & one-bit carry
```

Gate-level modeling

- Textual description of schematic diagram
- Uses keywords like **and**, **nand**, **or**, **nor**, **xor**, **xnor**, **not**, **buf**
- Four-level logic: 0, 1, high-impedance (z), unknown (x)
- Use ``timescale <reference_time_unit>/<time_precision>` to change the reference time scale and precision of a simulation. Example:
``timescale 1ns/1p`

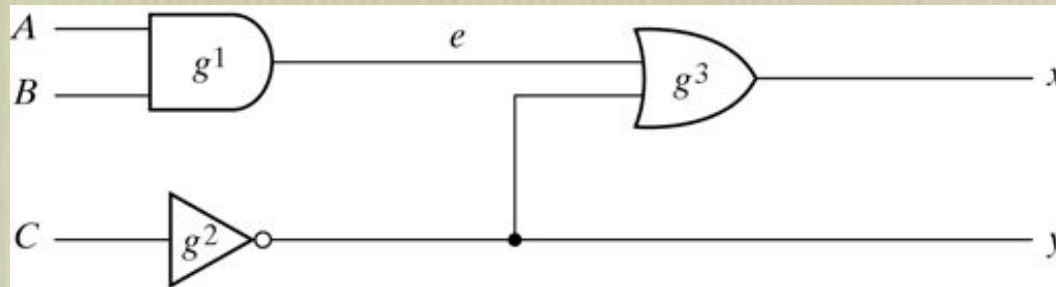


Fig. 3-37 Circuit to Demonstrate HDL

HDL Example 3-2

```

//Description of circuit with delay
module circuit_with_delay (A,B,C,x,y);
    input A,B,C;
    output x,y;
    wire e;
    and #(30) g1(e,A,B);
    or #(20) g3(x,e,y);
    not #(10) g2(y,C);
endmodule
  
```

Modules and testing

- Gate primitives: or, nor, and, nand, xor, xnor
 - 1 output (1st terminal) and any no. of inputs
- Transmission gate primitives: buf, not (inverter); with active-high control input: bufif1, notif1; with active-low control input: bufifo, notifo
- Also switch primitives
- User-defined primitives are declared with the keyword *primitive* - not used frequently

Simulations are specified in a *testbench* which is a module

```
//Stimulus for simple circuit
module stimcrct;
reg A,B,C;
wire x,y;
circuit_with_delay cwd(A,B,C,x,y);
initial
    begin
        A = 1'b0; B = 1'b0; C = 1'b0;
        #100
        A = 1'b1; B = 1'b1; C = 1'b1;
        #100    $finish;
    end
endmodule
```

Data Types

- Nets - represent structural connections
 - “wire” is the most common net type
- reg - represent variables used to store data
 - store the last value assigned to them until another assignment statement changes their value

Port Connection Rules

- **Inputs** : internally must always be type net, externally the inputs can be connected to variable reg or net (wire) type.
- **Outputs** : internally can be type net or reg, externally the outputs must be connected to a variable net type.
- **Inouts** : internally or externally must always be type net, can only be connected to a variable net type.
- **implicit type** (not explicitly declared) is one-bit wire

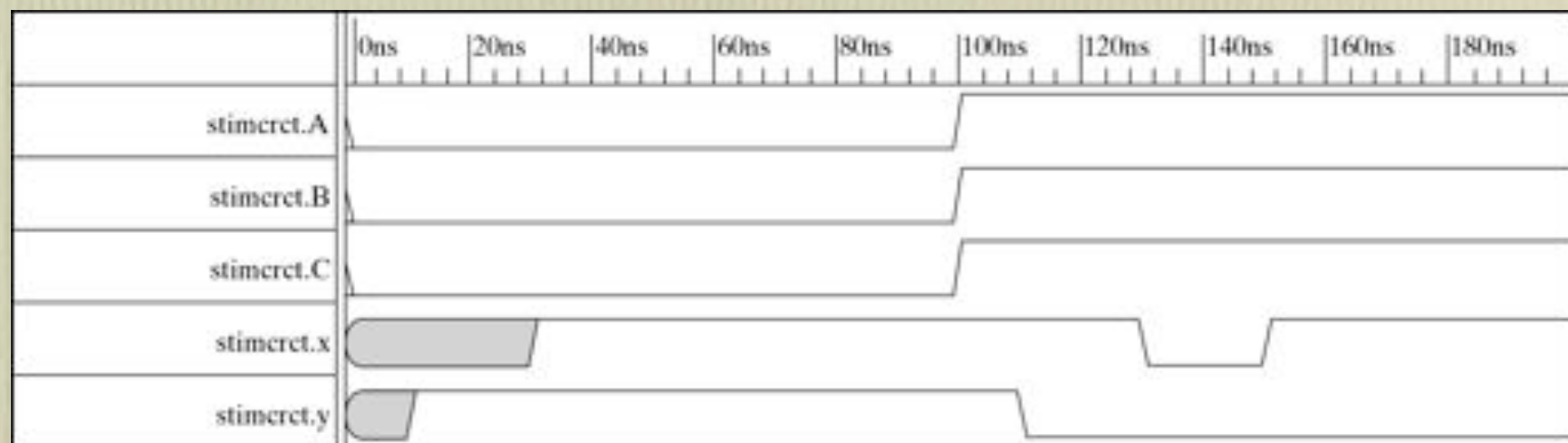


Fig. 3-38 Simulation Output of HDL Example 3-3

Table 4-9*Truth Table for Predefined Primitive Gates*

and	0	1	x	z
0	0	0	0	0
1	0	1	x	x
x	0	x	x	x
z	0	x	x	x

or	0	1	x	z
0	0	1	x	x
1	1	1	1	1
x	x	1	x	x
z	x	1	x	x

xor	0	1	x	z
0	0	1	x	x
1	1	0	x	x
x	x	x	x	x
z	x	x	x	x

not	input	output
	0	1
	1	0
	x	x
	z	x

HDL Example 4-1

```
//Gate-level description of a 2-to-4-line decoder
//Figure 4-19
module decoder_g1 (A,B,E,D);
    input A,B,E;
    output [0:3]D;
    wire Anot,Bnot,Enot;
    not
        n1 (Anot,A),
        n2 (Bnot,B),
        n3 (Enot,E);
    nand
        n4 (D[0],Anot,Bnot,Enot),
        n5 (D[1],Anot,B,Enot),
        n6 (D[2],A,Bnot,Enot),
        n7 (D[3],A,B,Enot);
endmodule
```

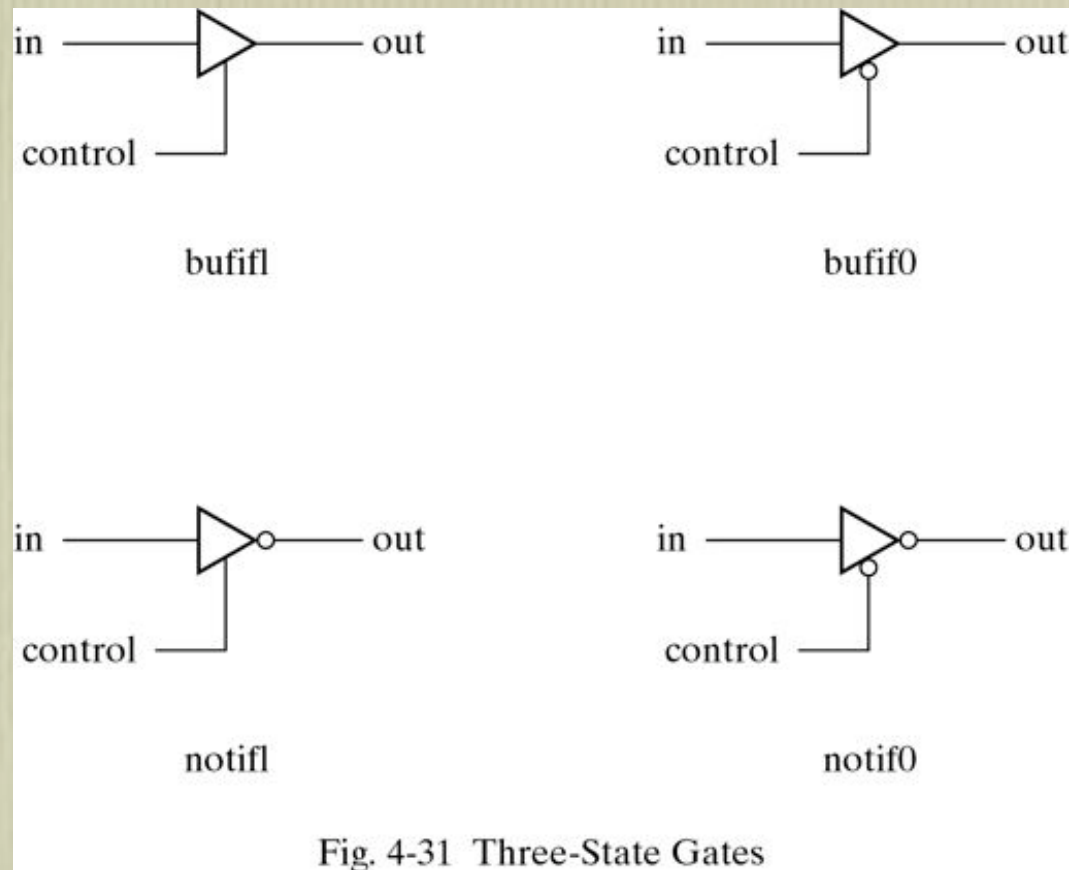


Fig. 4-31 Three-State Gates

```
bufif1 (OUT,A,control);
notif0 (Y,B,enable);
```

In the first example, input A is transferred to OUT when $\text{control} = 1$. OUT goes to z when $\text{control} = 0$. In the second example, output $Y = z$ when $\text{enable} = 1$ and output $Y = B'$ when $\text{enable} = 0$.

```

module muxtri (A,B,select,OUT);
  input A,B,select;
  output OUT;
  tri OUT;
  bufif1 (OUT,A,select);
  bufif0 (OUT,B,select);
endmodule

```

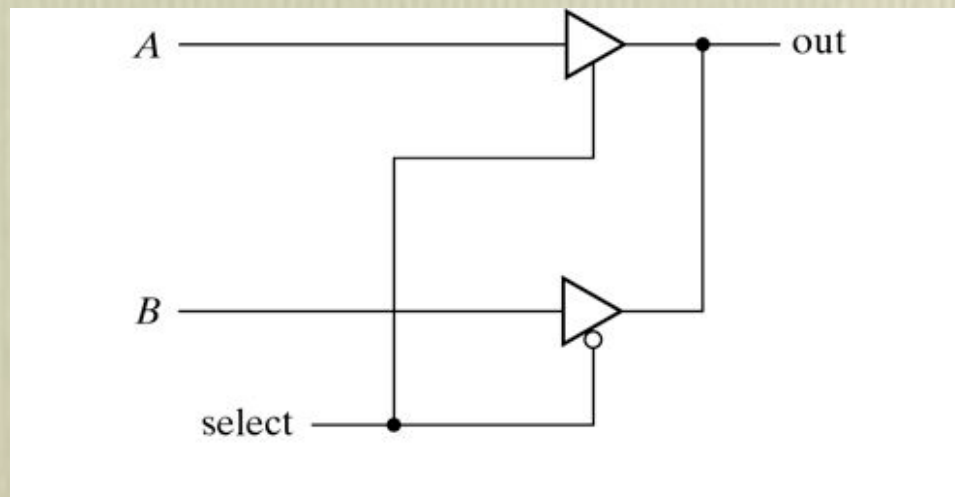


Fig. 4-32 2-to-1-Line Multiplexer with Three-State Buffers

Dataflow modelling

- Uses operators instead of gates
- Keyword **assign**
- Represent structural connections
- Drives wire data type; left-hand side must be wire
- Continuous assignments
- Used outside procedural blocks (**always** and **initial**)
- Syntax: **assign** **#(delay)** **net** = **expression**

Table 4-10
Verilog HDL Operators

Symbol	Operation
+	binary addition
-	binary subtraction
&	bit-wise AND
	bit-wise OR
^	bit-wise XOR
~	bit-wise NOT
==	equality
>	greater than
<	less than
{ }	concatenation
? :	conditional

HDL Example 3-4

```
//Circuit specified with Boolean expressions
module circuit_bln (x,y,A,B,C,D);
    input A,B,C,D;
    output x,y;
    assign x = A | (B & C) | (~B & D);
    assign y = (~B & C) | (B & ~C & ~D);
endmodule
```

HDL Example 4-3

```
//Dataflow description of a 2-to-4-line decoder
//See Fig. 4-19
module decoder_df (A,B,E,D);
    input A,B,E;
    output [0:3] D;
    assign D[0] = ~(~A & ~B & ~E),
           D[1] = ~(~A & B & ~E),
           D[2] = ~(A & ~B & ~E),
           D[3] = ~(A & B & ~E);
endmodule
```

HDL Example 4-4

```
//Dataflow description of 4-bit adder
module binary_adder (A,B,Cin,SUM,Cout);
    input [3:0] A,B;
    input Cin;
    output [3:0] SUM;
    output Cout;
    assign {Cout,SUM} = A + B + Cin;
endmodule
```

HDL Example 4-5

```
//Dataflow description of a 4-bit comparator.  
module magcomp (A,B,ALSB,AGTB,AEQB);  
    input [3:0] A,B;  
    output ALTB,AGTB,AEQB;  
    assign ALTB=(A < B),  
           AGTB = (A > B),  
           AEQB = (A == B);  
endmodule
```

HDL Example 4-6

```
//Dataflow description of 2-to-1-line multiplexer
module mux2x1_df (A,B,select,OUT);
    input A,B,select;
    output OUT;
    assign OUT = select ? A : B;
endmodule
```

32-bit adder

```
module adder(a, b, y);  
  input [31:0] a, b;  
  output [31:0] y;  
  
  assign y = a + b;  
  
endmodule
```

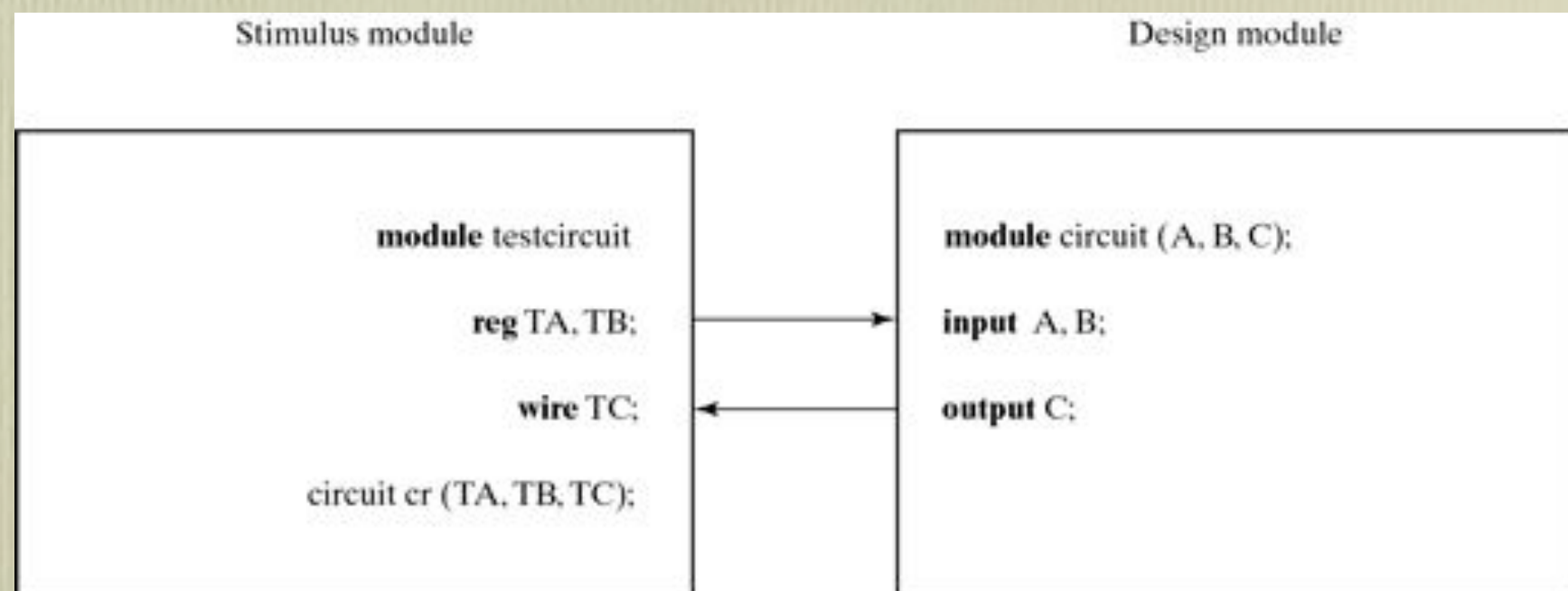


Fig. 4-33 Stimulus and Design Modules Interaction

Behavioral Model

- Declared using keywords
 - **initial** : Executes following block once
 - **always**: Executes repeatedly. Block is reevaluated only when signals in the header change
- Executes following statement, or block of statements within begin and end

Example: 15 clock cycles

```
initial
begin
    clock = 1'b0 ;
    repeat (30)
    #10 clock = ~ clock;
end
```

```
initial
begin
    clock = 1'b0;
    #300 $finish;
end
always
    #10 clock = ~clock;
```

Example: use of **always** with event control expressions

```
always @ (A or B or Reset)
```

```
always @ (posedge clock or negedge reset)
```

Following block or statement executes only if the expression is True.

- procedural assignment: occur within a **begin** or **always** block
- target output must be of **reg** type
- Blocking: use symbol =
 - are executed sequentially in the order they appear
- Non-blocking: use symbol <=
 - first evaluate all right-hand side, then assign to the left-hand side

Blocking

```
B = A ; // A copied into B  
C = B+1 ; // A+1 copied into B
```

Non-blocking

```
B<= A ; // A <- B  
C<=B+1; // C is Orig B + 1
```

//HDL Example 5-1

//Description of D latch (See Fig.5-6)

module D_latch (Q,D,control);

output Q;

input D,control;

reg Q;

always @ (control or D)

if (control) Q = D;

//Same as: if (control = 1)

endmodule

//HDL Example 5-2

//D flip-flop

```
module D_FF (Q,D,CLK);  
    output Q;  
    input D,CLK;  
    reg Q;  
    always @ (posedge CLK)  
        Q = D;  
endmodule
```

//D flip-flop with asynchronous reset.

```
module DFF (Q,D,CLK,RST);  
    output Q;  
    input D,CLK,RST;  
    reg Q;  
    always @(posedge CLK or negedge  
        RST)  
        if (~RST) Q = 1'b0; // Same as: if  
        (RST = 0)  
        else Q = D;  
endmodule
```

//HDL Example 5-3: T flip-flop from D flip-flop and gates

module TFF (Q,T,CLK,RST);

output Q;

input T,CLK,RST;

wire DT;

assign DT = Q ^ T ;

DFF TF1 (Q,DT,CLK,RST); //Instantiate the D flip-flop

endmodule

//HDL Example 5-3: Continuation

//JK flip-flop from D flip-flop and gates

module JKFF (Q,J,K,CLK,RST);

output Q;

input J,K,CLK,RST;

wire JK;

assign JK = (J & ~Q) | (~K & Q);

DFF JK1 (Q,JK,CLK,RST); //Instantiate D FF (prev slide)

endmodule

//HDL Example 5-4

**// Functional description
of JK flip-flop**

**module JK_FF
 (J,K,CLK,Q,Qnot);**

output Q,Qnot;

input J,K,CLK;

reg Q;

assign Qnot = ~ Q ;

//HDL Example 5-4 (cont)

**always @ (posedge
 CLK)**

case ({J,K})

2'b00: Q = Q;

2'b01: Q = 1'b0;

2'b10: Q = 1'b1;

2'b11: Q = ~ Q;

endcase

endmodule

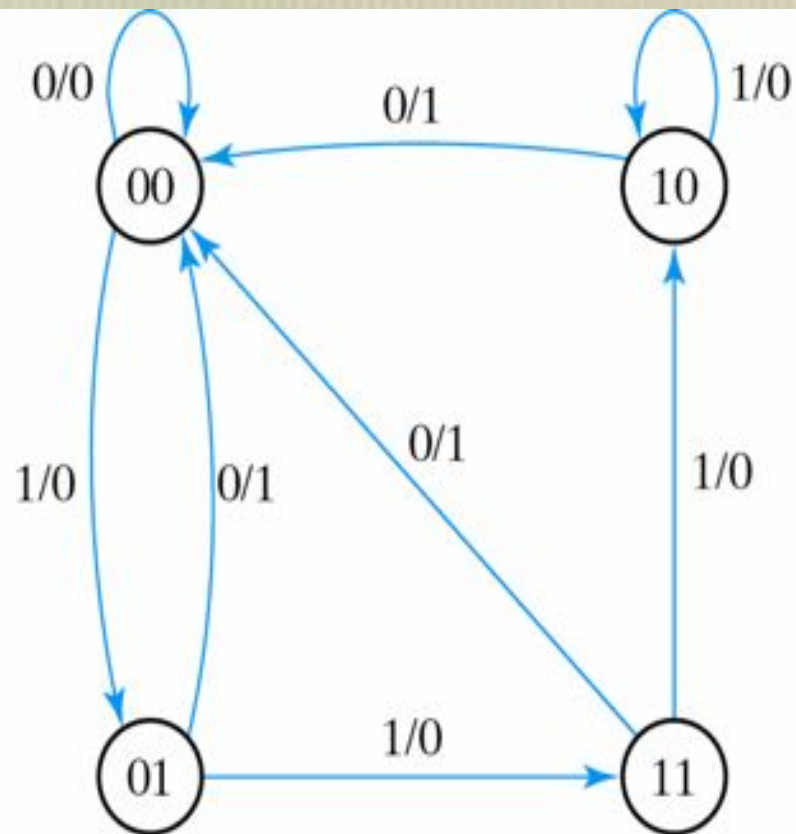


Fig. 5-16 State Diagram of the Circuit of Fig. 5-15

//HDL Example 5-5: Mealy state diagram (Fig 5-16)

module Mealy_mdl (x,y,CLK,RST);

input x,CLK,RST;

output y;

reg y;

reg [1:0] Prstate, Nxtstate;

parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;

always @ (posedge CLK or negedge RST)

if (~RST) Prstate = S0; //Initialize to state S0

else Prstate = Nxtstate; //Clock operations



always @ (Prstate or x) //Find next state

case (Prstate)

S0: if (x) Nxtstate = S1;

S1: if (x) Nxtstate = S3;

else Nxtstate = S0;

S2: if (~x)Nxtstate = S0;

S3: if (x) Nxtstate = S2;

else Nxtstate = S0;

endcase

always @ (Prstate or x) //Evaluate output

case (Prstate)

S0: y = 0;

S1: if (x) y = 1'b0; else y = 1'b1;

S2: if (x) y = 1'b0; else y = 1'b1;

S3: if (x) y = 1'b0; else y = 1'b1;

endcase

endmodule

Verilog Problem

- Write Verilog gate-level, dataflow and behavioral descriptions for the following circuits. Test the circuit by writing a testbench module and running a simulation.
 - a priority encoder such as the one shown in figure 4.23,
 - a four-bit adder-subtractor such as the one shown in figure 4.13, and
 - a sequence detector such as the one shown in figure 5.29