

## Chapter 2 Circuit elements

### Exercises

Ex. 2.3-1

$$\text{If } v_1 = \frac{di_1}{dt} \text{ and } v_2 = \frac{di_2}{dt} \text{ then } v_1 + v_2 = \frac{di_1}{dt} + \frac{di_2}{dt} = \frac{d}{dt}(i_1 + i_2)$$

thus satisfying the property of superposition.

$$\text{Since } v_1 = \frac{di_1}{dt} \text{ and for } ki_1 \text{ we get } \frac{d}{dt}(ki_1) = k \frac{di_1}{dt}, \text{ thus the property of homogeneity}$$

is also satisfied. Thus the element is linear.

Ex. 2.3-2

Consider homogeneity only.

For  $i < 0$  an excitation,  $i$ , yields  $v = 0$  and an excitation,  $Ki$ , yields  $v = 0$  as well.

Since the response,  $v$ , does not scale in the manner of the excitation,  $i$ , the property of homogeneity is not satisfied.

Ex. 2.3-3 a)  $v = \left(\frac{2.5}{1}\right)i$  for  $-1 < i < 1$

b)  $v = \left(\frac{-2}{1.5}\right)i = \frac{-4}{3}i = \underline{-1.333i}$  for  $-1.5 < i < 1.5$

$$P = \frac{v^2}{R} = \frac{(10v)^2}{100\Omega} = \underline{1 \text{ W}}$$

Ex. 2.5-1


Ex. 2.5-2  $P = \frac{v^2}{R} = \frac{(10 \cos t)^2}{10} = \underline{10 \cos^2 t \text{ W}}$

Ex. 2.8-1  $i_c = -1.2\text{A}$ ,  $v_d = 24\text{V}$   
 $i_d = 4(-1.2) = -4.8\text{A}$   
 $P = vi = (24)(-4.8\text{A}) = \underline{-115.2 \text{ W absorbed}}$

Ex. 2.8-2  $v_c = 2\text{V}$ ,  $i_d = 1.5 \text{ A}$   
 $v_d = 2(2) = 4\text{V}$   
 $P = vi = (4\text{V})(1.5\text{A}) = \underline{6 \text{ W absorbed}}$

Ex. 2.8-3  $i_c = 1.25\text{A}$ ,  $i_d = 1.75\text{A}$   
 $v_d = 2(1.25) = 2.5 \text{ V}$   
 $P = vi = (2.5\text{V})(1.75\text{A}) = \underline{4.375 \text{ W absorbed}}$

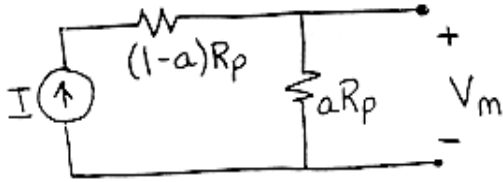Ex. 2.9-1  $\theta = 45^\circ$ ,  $I = 2\text{mA}$ ,  $R_p = 20\text{k}\Omega$



$$\text{where } a = \frac{\theta}{360} \Rightarrow aR_p = \frac{45}{360}(20\text{k}\Omega) = 2.5\text{k}\Omega$$

$$v = iR$$

$$v_m = (2\text{mA})(2.5\text{k}\Omega) = \underline{5\text{V}}$$

Ex. 2.9-2  $v = 10\text{V}$ ,  $i = 280\mu\text{A}$ ,  $k = 1 \frac{\mu\text{A}}{^\circ\text{K}}$  for AD590

$$i = kT$$

$$T = \frac{i}{k} = (280\mu\text{A}) \left( 1 \frac{^\circ\text{K}}{\mu\text{A}} \right) = \underline{280^\circ\text{K}}$$

Ex. 2.10-1  $t = 1\text{s}$  (switch closed)

$$i = \frac{v}{R} = \frac{12\text{V}}{3\text{k}\Omega} = \underline{4\text{mA}}$$

$$t = 5 \text{ (switch open) } \underline{i = 0\text{A}}$$

Ex. 2.10-2  $t = 4\text{s}$  (both switches open)

$$\underline{i = 0}$$

Ex. 2.10-3  $t = 4\text{s}$  (switch up)

$$v = iR = (2\text{mA})(3\text{k}\Omega) = \underline{6\text{V}}$$

$t = 6\text{s}$  (switch down)

$$\underline{v = 0}$$

Ex. 2.10-4  $t = 1\text{s}$  (switch up)

$$i = \frac{v}{R} = \frac{(6\text{V})}{(3\text{k}\Omega)} = \underline{2\text{mA}}$$

$t = 3\text{s}$  (switch up)

$$i = \frac{v}{R} = \frac{(12\text{V})}{(3\text{k}\Omega)} = \underline{4\text{mA}}$$

## Problems

### Section 2-3 Engineering and Linear Models

**P 2.3-1** The element is not linear. For example, doubling the current from 2 A to 4 A does not double the voltage. Hence, the property of homogeneity is not satisfied.

**P 2.3-2** Plotting  $v$  versus  $i$  using the given data produces a straight line with a slope equal to 16 V/A. This straight line passes through the origin. The equation of the line is  $v = 16i$ . Such a relationship was shown to be linear in Example 2.3-1.

**P 2.3-3** (a) The data points do indeed lie on a straight line. The slope of the line is 120 V/A and the line passes through the origin so the equation of the line is  $v = 120i$ . The element is indeed linear.

(b) When  $i = 40$  mA,  $v = (120 \text{ V/A}) \times (40 \text{ mA}) = (120 \text{ V/A}) \times (0.04 \text{ A}) = 4.8 \text{ V}$

(c) When  $v = 4$  V,  $i = \frac{4}{120} = 0.033 \text{ A} = 33 \text{ mA}$ .

**P 2.3-4** (a) The data points do indeed lie on a straight line. The slope of the line is 256.5 V/A and the line passes through the origin so the equation of the line is  $v = 256.5i$ . The element is indeed linear.

(b) When  $i = 4$  mA,  $v = (256.5 \text{ V/A}) \times (4 \text{ mA}) = (256.5 \text{ V/A}) \times (0.004 \text{ A}) = 1.026 \text{ V}$

(c) When  $v = 12$  V,  $i = \frac{12}{256.5} = 0.04678 \text{ A} = 46.78 \text{ mA}$ .

**P2.3-5**

$$v = \sqrt{i}$$


$$v^2 = i$$

Element is not linear

**P 2.3-6** Let  $i = 1$  A, then  $v = 3i + 5 = 8$  V. Next  $2i = 2$  A but  $16 = 2v \neq 3(2i) + 5 = 11$ . Hence, the property of homogeneity is not satisfied. The element is not linear.

**P2.3-7**

a)

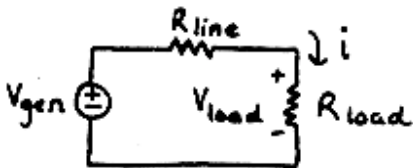

b)

$$\text{efficiency} = \frac{P_{\text{load}}}{P_{\text{gen}}}$$

$$\text{now } P_{\text{load}} = \frac{v_{\text{load}}^2}{R_{\text{load}}} \Rightarrow R_{\text{load}} = \frac{(9 \times 10^5)^2}{1.2 \times 10^9 \text{ W}} = 675 \Omega$$

$$\therefore i = \frac{v_{\text{load}}}{R_{\text{load}}} = \frac{9 \times 10^5}{675} = 1.33 \times 10^3 \text{ A}$$

$$\therefore P_{\text{gen}} = v_{\text{gen}} i = (9.5 \times 10^5)(1.33 \times 10^3) = 1.27 \times 10^9 \text{ W}$$

$$\therefore \text{efficiency} = \frac{P_{\text{load}}}{P_{\text{gen}}} = \frac{1.2 \text{ GW}}{1.27 \text{ GW}} = \underline{0.945}$$

c) lost power goes to the resistance in power lines

d)  $W = P\Delta t = (1.2 \times 10^9 \text{ W})(24 \text{ hr})(3600 \text{ s/hr}) = \underline{1.04 \times 10^{14} \text{ J}}$

**P2.3-8**

Charging power to battery:  $P = 12(2.8\text{A}) = \underline{33.6\text{ W}}$

total power to charging source:  $P_c = (14.52) \times 2.8 = \underline{40.66\text{ W}}$

total power to battery:  $P_b = (12.0 + 1.68) \times 2.8 = \underline{38.3\text{ W}}$

total power lost in charger:  $P_l = .84 (2.8) = \underline{2.352\text{ W}}$

now  $2.8(12+1.68+.84) = 2.8(14.52)$

so power from source = total power absorbed by 3 elements


need 3360 C of charge

$$i = \frac{\Delta q}{\Delta t} \text{ or } \Delta t = \frac{\Delta q}{i} = \frac{3360}{2.8} = 1200\text{s} = \underline{20\text{ minutes}}$$

Section 2-4 Active and Passive Circuit Elements

P2.4-1

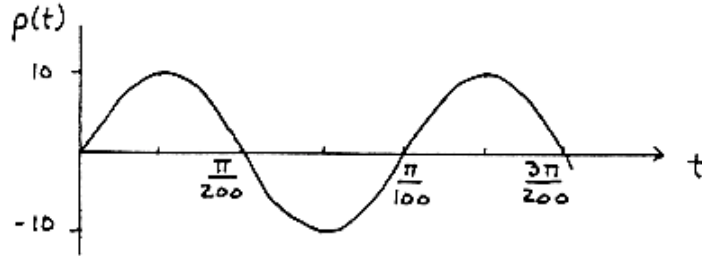a)  $P(t) = v i = (10 \sin 100 t)(2 \cos 100 t \text{ mA})$   
 $= 20 \sin 100 t \cos 100 t = \underline{10 \sin 200 t \text{ mW}}$



b) power absorbed for  $\frac{2n\pi}{200} < t < \frac{(2n+1)\pi}{200}$   $n = 0, 1, 2, \dots$   
 power delivered for  $\frac{(2n-1)\pi}{200} < t < \frac{2n\pi}{200}$   $n = 1, 2, 3, \dots$

P2.4-2

$$P = v i = \left( 2 \frac{d}{dt} (2 \sin t) \right) (2 \sin t)$$

$$= (4 \cos t)(2 \sin t) = 8 \cos t \sin t \quad t > 0$$


$$W = \int_0^t P dt = 8 \int_0^t \cos t \sin t dt$$

$$= \frac{8}{2} \sin^2 t \Big|_0^t = 4 \sin^2 t > 0$$

$\therefore$  element is passive

## Section 2-5 Resistors

P2.5-1

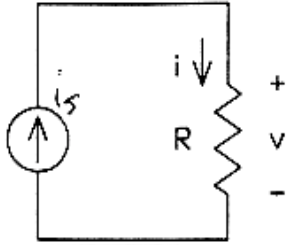


$$i = i_s = 3\text{A} \text{ and } v = Ri = 7 \times 3 = \underline{21\text{V}}$$

$v$  and  $i$  adhere to the passive convention

$$\therefore P = vi = 21 \times 3 = \underline{63\text{ W}}$$
 is the power absorbed by the resistor.

P2.5-2

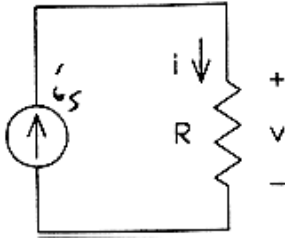


$$i = i_s = 3\text{mA} \text{ and } v = 24\text{ V}$$

$$R = \frac{v}{i} = \frac{24}{.003} = 8000 = \underline{8\text{ K}\Omega}$$

$$P = (3 \times 10^{-3}) \times 24 = 72 \times 10^{-3} = \underline{72\text{ mW}}$$

P2.5-3

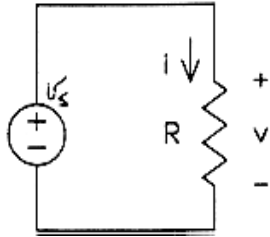

$$v = v_s = 10\text{V} \text{ and } R = 5\Omega$$


$$i = \frac{v}{R} = \frac{10\text{V}}{5\Omega} = \underline{2\text{A}}$$

$v$  and  $i$  adhere to the passive convention

$$\therefore p = vi = 2\text{A} \cdot 10\text{V} = \underline{20\text{ W}}$$

is the power absorbed by the resistor

P2.5-4

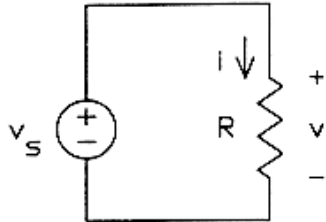


$$v = v_s = 24\text{V} \text{ and } i = 2\text{A}$$

$$R = \frac{v}{i} = \frac{24\text{V}}{2\text{A}} = \underline{12\Omega}$$

$$p = vi = 24 \cdot 2 = \underline{48\text{ W}}$$

**P2.5-5**

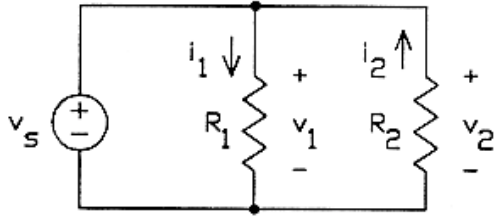

$$v_1 = v_2 = v_s = 150\text{V}; R_1 = 50\Omega; R_2 = 25\Omega$$


$$v_1 \text{ and } i_1 \text{ adhere to the passive convention so } i_1 = \frac{v_1}{R_1} = \frac{150}{50} = \underline{3\text{A}}$$

$$v_2 \text{ and } i_2 \text{ do not adhere to the passive convention so } i_2 = -\frac{v_2}{R_2} = -\frac{150}{25} = \underline{-6\text{A}}$$

$$\text{The power absorbed by } R_1 \text{ is } P_1 = v_1 i_1 = 150 \cdot 3 = \underline{450\text{W}}$$

$$\text{The power absorbed by } R_2 \text{ is } P_2 = -v_2 i_2 = -150(-6) = \underline{900\text{W}}$$

**P2.5-6**

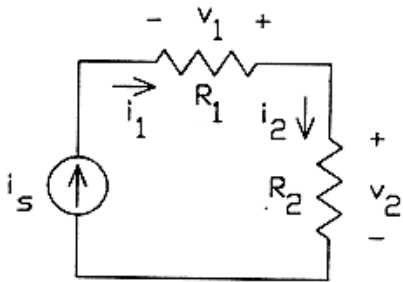

$$i_1 = i_2 = i_s = 2\text{A}; R_1 = 4\Omega \text{ and } R_2 = 8\Omega$$

$$v_1 \text{ and } i_1 \text{ do not adhere to the passive convention so } v_1 = -R_1 i_1 = -4 \cdot 2 = \underline{-8\text{V}}$$

$$\text{The power absorbed by } R_1 \text{ is } P_1 = -v_1 i_1 = -(-8)(2) = \underline{16\text{W}}$$

$$v_2 \text{ and } i_2 \text{ do adhere to the passive convention so } v_2 = R_2 i_2 = 8 \cdot 2 = \underline{12\text{V}}$$

$$\text{The power absorbed by } R_2 \text{ is } P_2 = v_2 i_2 = 12 \cdot 2 = \underline{24\text{W}}$$

**P2.5-7**

$$\text{Model the heater as a resistor, then from } P = \frac{v^2}{R} \Rightarrow R = \frac{v^2}{P} = \frac{(250)^2}{1000} = \underline{62.5\Omega}$$

$$\text{with a } 210\text{ V source} \quad P = \frac{v^2}{R} = \frac{(210)^2}{62.5} = \underline{705.6\text{ W}}$$

**P2.5-8**

$$\text{The current required by the mine lights is: } i = \frac{P}{v} = \frac{5000}{120} = \underline{125/3\text{ A}}$$

$$\text{Power loss in the wire is: } i^2 R$$

Thus the resistance of the copper wire is

$$R = \frac{0.05P}{i^2} = \frac{0.05 \times 5000}{(125/3)^2} = \underline{0.144\ \Omega}$$

now since the length of the wire is

$$L = 2 \times 100 = 200\text{m}$$

thus  $R = PL/A$  with  $P = 1.7 \times 10^{-6} \Omega \cdot \text{cm}$  from table 2-1

$$\Rightarrow A = \frac{PL}{R} = \frac{1.7 \times 10^{-6} \times 20,000}{0.144} = \underline{0.236\text{cm}^2}$$

## Section 2-6 Independent Sources

**P2.6-1** (a)  $i = \frac{v_s}{R} = \frac{15}{5} = \underline{3A}$   
 $P = Ri^2 = 5(3^2) = \underline{45 W}$


- (b)  $i$  and  $P$  do not depend on  $i_s$ . The values of  $i$  and  $P$  are  $3A$  and  $45W$  both when  $i_s = 3A$  and when  $i_s = 5A$ .

**P2.6-2** (a)  $v = Ri_s = 5 \cdot 2 = \underline{10V}$   
 $P = \frac{v^2}{R} = \frac{10^2}{5} = \underline{20 W}$


- (b)  $v$  and  $P$  do not depend on  $V_s$ . The values of  $v$  and  $P$  are  $10V$  and  $20 W$  both when  $v_s = 10V$  and when  $v_s = 5V$
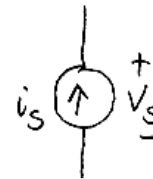
### P2.6-3

Consider the current source.  $i_s$  and  $v_s$  do not adhere to the passive convention, so  $P_{cs} = i_s v_s = 3 \cdot 12 = \underline{36 W}$  is the power supplied by the current source.




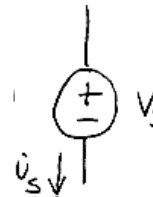Consider the voltage source.  $i_s$  and  $v_s$  do adhere to the passive convention, so  $P_{vs} = i_s v_s = 3 \cdot 12 = \underline{36 W}$  is the power absorbed by the voltage source.  
 $\therefore$  The voltage source supplies  $-36 W$ .



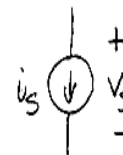
### P2.6-4

Consider the current source.  $i_s$  and  $v_s$  adhere to the passive convention so  $P_{cs} = i_s v_s = 3 \cdot 12 = \underline{36 W}$  is the power absorbed by the current source.  
 Current source supplies  $-36W$ .



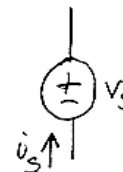Consider the voltage source.  $i_s$  and  $v_s$  do not adhere to the passive convention so  $P_{vs} = i_s v_s = 3 \cdot 12 = \underline{36 W}$  is the power supplied by the voltage source.




**P2.6-5** a)  $P = vi = (2 \cos t)(10 \cos t) = \underline{20 \cos^2 t \text{ mW}}$

b)  $W = \int_0^1 P dt = \int_0^1 20 \cos^2 t dt$   
 $= 20 \left( \frac{1}{2}t + \frac{1}{4} \sin 2t \right) \Big|_0^1 = \underline{10 + 5 \sin 2 \text{ mJ}}$



Section 2-7 Voltmeters and Ammeters


P2.7-1

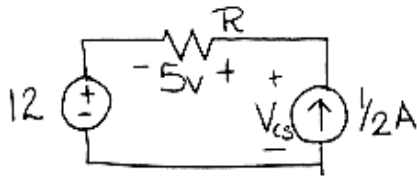

(a)  $R = \frac{v}{i} = \frac{5V}{.5A} = \underline{10 \Omega}$

(b) The voltage, 12V, and current, 0.5 A, of the voltage source adhere to the passive convention. So  $P = 12(0.5) = 6 \text{ W}$  is the power absorbed by the voltage source. The voltage source delivers -6 W.

P2.7-2

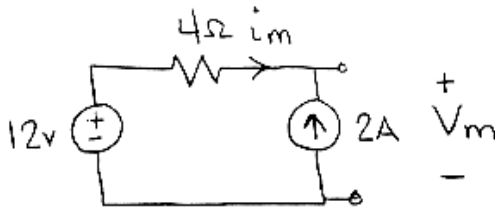


$i_m = -2A$

$i_m$  and  $v_m$  adhere to the passive convention so

$i_m \cdot v_m = -40 \text{ W} \Rightarrow \underline{v_m = 20V}$

Section 2-8 Dependent Sources

P2.8-1

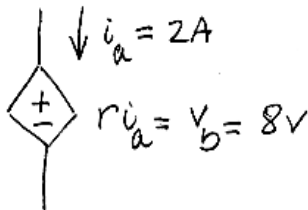

$r = \frac{v_b}{i_a} = \frac{8V}{2A} = \underline{4\Omega}$


P2.8-2  $v_b = 8V$ ;  $g v_b = i_a = 2A$ ;  $g = \frac{i_a}{v_b} = \frac{2A}{8V} = \underline{0.25 \frac{A}{V}}$

P2.8-3  $i_b = 8A$ ;  $d i_b = i_a = 32A$ ;  $d = \frac{i_a}{i_b} = \frac{32A}{8A} = \underline{4 \frac{A}{A}}$

P2.8-4  $v_a = 2V$ ;  $b v_a = v_b = 8V$ ;  $b = \frac{v_b}{v_a} = \frac{8V}{2V} = \underline{4 \frac{V}{V}}$

Section 2-9 Transducers

P2.9-1

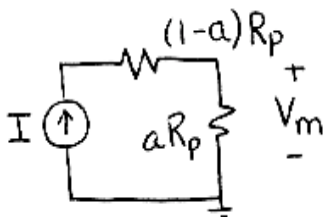

$a = \frac{\theta}{360}$ ,  $\theta = \frac{360 v_m}{R_p i}$

$\theta = \frac{(360)(23V)}{(100k\Omega)(1.1mA)} = \underline{75.27^\circ}$

**P2.9-2**

AD590 :  $K = 1 \frac{\mu\text{A}}{^\circ\text{K}}$  ,  $V = 20\text{V}$  (voltage condition satisfied)

$4 \mu\text{A} < i < 13\mu\text{A}$


$T = i/k$

$4^\circ\text{K} < T < 13^\circ\text{K}$

Section 2-10 Switches

**P2.10-1**

$t = 1\text{s}$

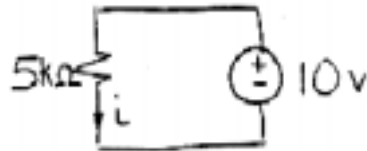

$i = v/R = \frac{10\text{V}}{5\text{k}\Omega} = \underline{2\text{mA}}$


$t = 4\text{s}$



$i = v/R = \frac{15\text{V}}{5\text{k}\Omega} = \underline{3\text{mA}}$


**P2.10-2**

$t = 1\text{s}$

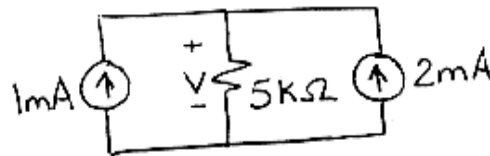

$v = iR = (3\text{mA})(5\text{k}\Omega)$   
 $v = 15\text{V}$

$t = 4\text{s}$

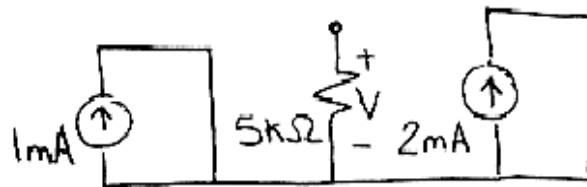

$V = 0$

## Verification Problems

**VP 2-1**  $v_0=40$  and  $i_s = -(-2) = 2$ . (Notice that the ammeter measures  $-i_s$  rather than  $i_s$ .) So

$$\frac{v_0}{i_s} = \frac{40V}{2A} = 20 \frac{V}{A}$$

Your lab partner is wrong.

**VP 2-2** We expect the resistor current to be  $i = \frac{v_s}{R} = \frac{12V}{25\Omega} = 0.48A$ . The Power absorbed by

this resistor will be  $P = iv_s = (0.48A)(12V) = 5.76W$  A half watt resistor can't absorb this much power.

You should not try another resistor.

## Design Problems

**DP 2-1:**

$$1.) \frac{10}{R} > 0.04 \Rightarrow R < \frac{10}{0.04} = 250 \Omega$$

$$2.) \frac{10^2}{R} < \frac{1}{2} \Rightarrow R > 200 \Omega$$

Therefore  $200 < R < 250 \Omega$ . For example,  $R = 225 \Omega$ .

**DP 2-2:**

$$1.) 2R > 40 \Rightarrow R > 20 \Omega$$

$$2.) 2^2 R < 15 \Rightarrow R < \frac{15}{4} = 3.75 \Omega$$

Therefore  $20 < R < 3.75 \Omega$ . These conditions cannot be satisfied simultaneously.

**DP 2-3:**

$$P_1 = (10 \text{ mA})^2 \cdot (1000 \Omega) = (.01)^2 (1000) = 0.1 \text{ W} < \frac{1}{8} \text{ W}$$

$$P_2 = (10 \text{ mA})^2 \cdot (2000 \Omega) = (.01)^2 (2000) = 0.2 \text{ W} < \frac{1}{4} \text{ W}$$

$$P_3 = (10 \text{ mA})^2 \cdot (4000 \Omega) = (.01)^2 (4000) = 0.4 \text{ W} < \frac{1}{2} \text{ W}$$